
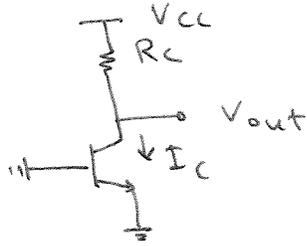


(1)

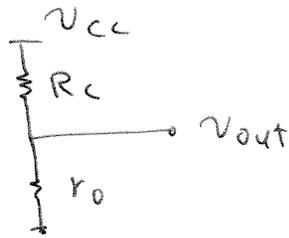


the small signal model is as follows:




$$\frac{v_{out}}{v_{CC}} = \frac{r_o}{r_o + R_C} = \frac{\frac{V_A}{I_C}}{\frac{V_A}{I_C} + R_C} = \frac{V_A}{V_A + R_C I_C}$$

(2)

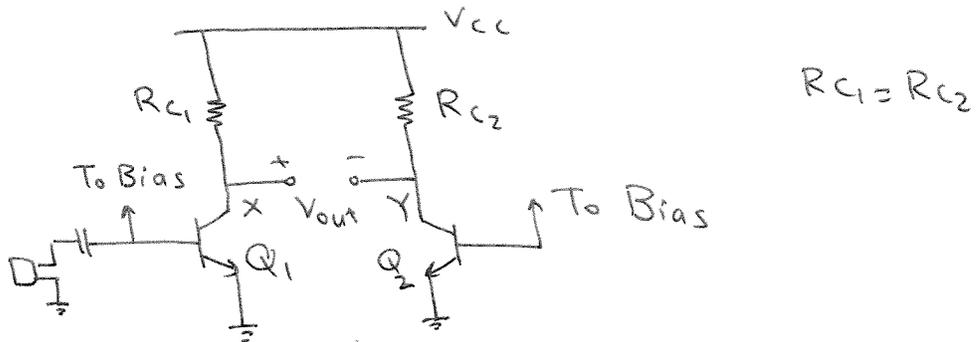


The small signal model is:

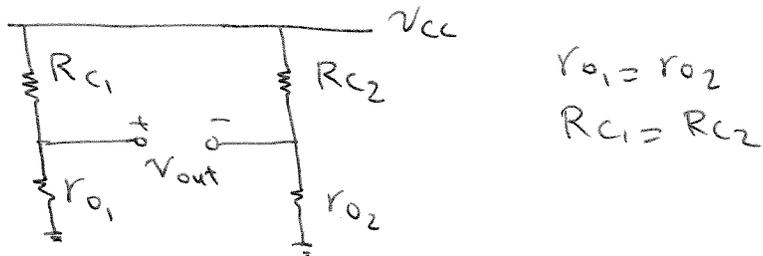


$$\frac{V_{out}}{V_{cc}} = \frac{1}{V_{cc}} \left( \frac{r_{o1}}{R_{C1} + r_{o1}} - \frac{r_{o2}}{R_{C2} + r_{o2}} \right) V_{cc} = 0$$

(3)

(a)


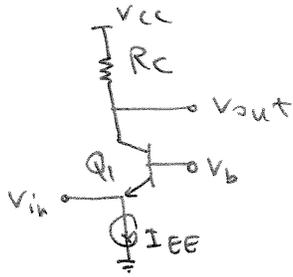


The small signal model is:

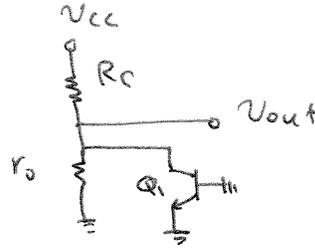




$$\frac{V_{out}}{V_{CC}} = \frac{r_o}{r_o + R_C} = \frac{V_A}{V_A + R_C I_{EE}}$$

(b)

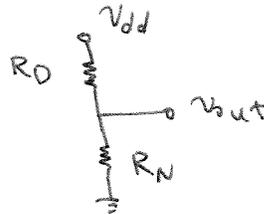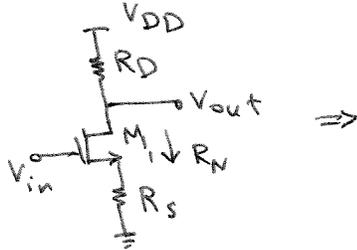

$$R_N = g_{m1} r_{o1} R_S + r_{o1} + R_S, \quad \frac{V_{out}}{V_{DD}} = \frac{R_N}{R_N + R_D}$$



(c)

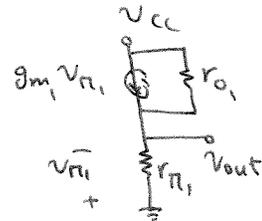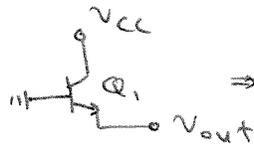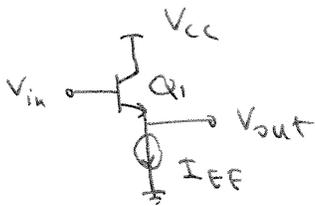

$$\frac{V_{out}}{r_{\pi 1}} + \frac{V_{out} - V_{CC}}{r_{o1}} + g_{m1} V_{out} = 0 \rightarrow (r_{\pi 1} + r_{o1} + g_{m1} r_{o1} r_{\pi 1}) V_{out} = \frac{r_{\pi 1}}{r_{\pi 1}} V_{CC}$$

$$\Rightarrow \frac{V_{out}}{V_{CC}} = \frac{r_{\pi 1}}{\beta r_{o1} + r_{o1} + r_{\pi 1}}$$

(3) (d)

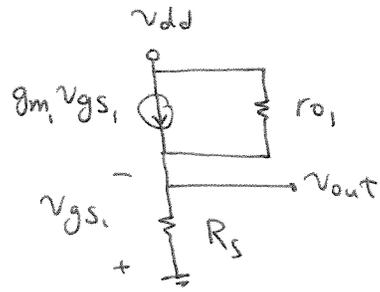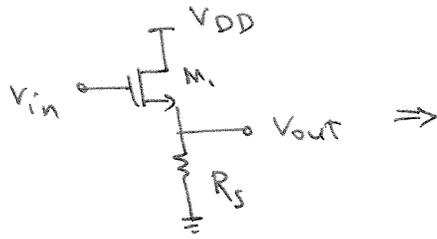


$$\frac{v_{out}}{R_S} + \frac{v_{out} - v_{dd}}{r_{o_1}} + g_m v_{out} = 0$$

$$\Rightarrow (r_{o_1} + R_S + g_m r_{o_1} R_S) v_{out} = R_S v_{dd}$$


$$\Rightarrow \frac{v_{out}}{v_{dd}} = \frac{R_S}{g_m r_{o_1} R_S + R_S + r_{o_1}}$$

④

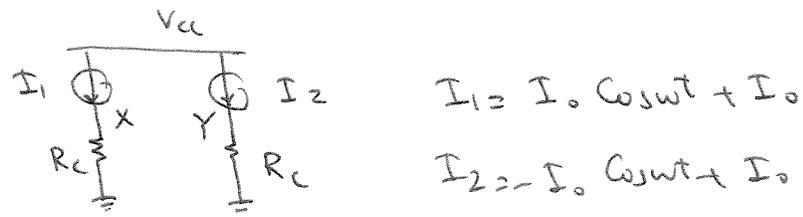

$$V_X = R_C I_1 = R_C I_0 (1 + \cos \omega t)$$

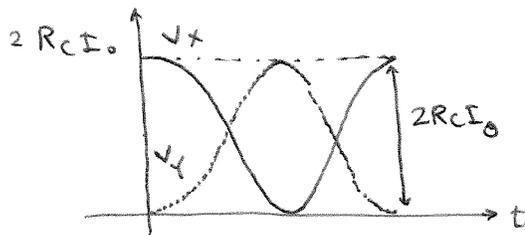
$$V_Y = R_C I_2 = R_C I_0 (1 - \cos \omega t)$$



$$V_{X,P-P} = V_{Y,P-P} = 2R_C I_0$$

$$V_{X,CM} = V_{Y,CM} = R_C I_0$$

⑤

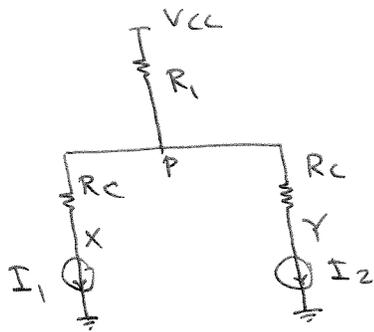

$$I_1 = I_0 \cos \omega t + I_0$$


$$I_2 = -I_0 \cos \omega t + I_0$$

$$V_P = V_{CC} - R_1 (I_1 + I_2) = V_{CC} - 2R_1 I_0$$

$$V_X = V_P - R_C I_1 = V_{CC} - 2R_1 I_0 - R_C I_0 - R_C I_0 \cos \omega t$$

$$\Rightarrow V_X = V_{CC} - (2R_1 + R_C) I_0 - R_C I_0 \cos \omega t$$

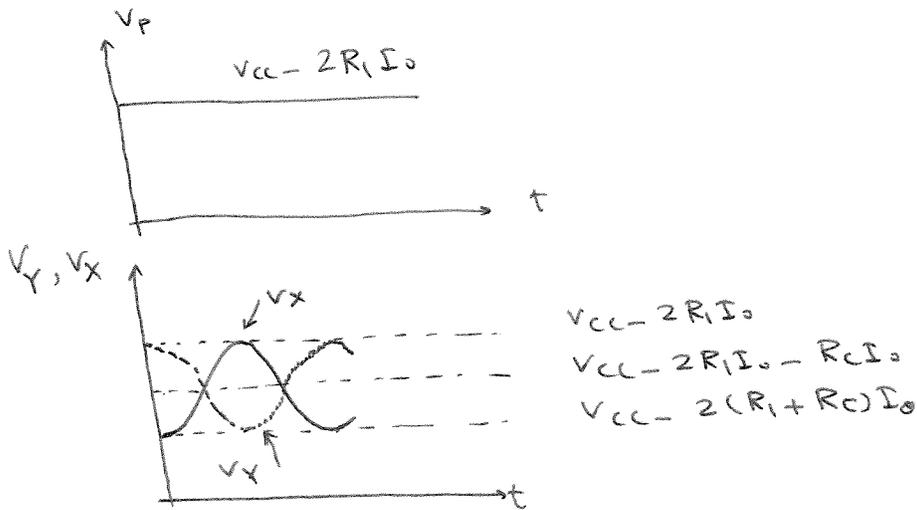
$$V_Y = V_P - R_C I_2 = V_{CC} - (2R_1 + R_C) I_0 + R_C I_0 \cos \omega t$$



$$V_{X,CM} = V_{Y,CM} = V_{CC} - (2R_1 + R_C) I_0$$

$$V_{X,P-P} = V_{Y,P-P} = 2R_C I_0$$

6

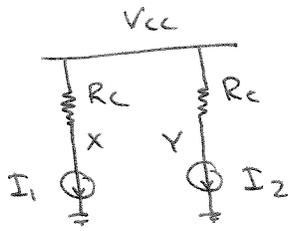


$$I_1 = I_0 \cos \omega t + I_0$$

$$I_2 = -I_0 \cos \omega t + I_0$$

$$V_X = V_{CC} - R_C I_1 = V_{CC} - R_C I_0 (1 + \cos \omega t)$$

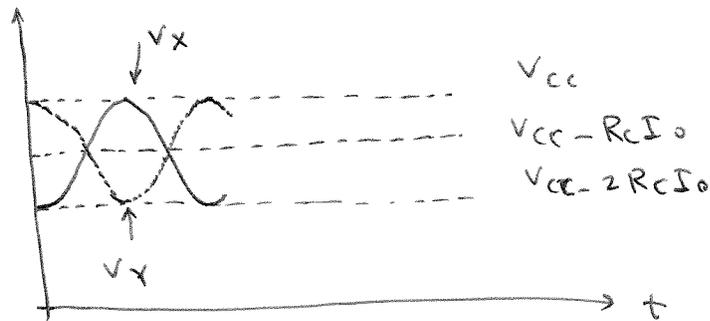
$$V_Y = V_{CC} - R_C I_2 = V_{CC} - R_C I_0 (1 - \cos \omega t)$$



$$V_{X,CM} = V_{Y,CM} = V_{CC} - R_C I_0$$

$$V_{X,P-P} = V_{Y,P-P} = 2 R_C I_0$$

⑦

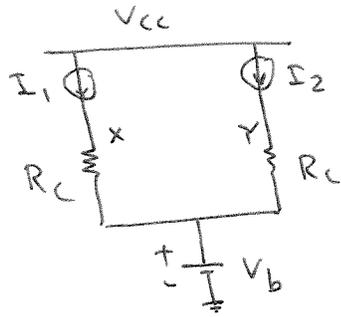


$$I_1 = I_0 \cos \omega t + I_0$$

$$I_2 = -I_0 \cos \omega t + I_0$$

$$V_X = R_C I_1 + V_b = R_C I_0 (1 + \cos \omega t) + V_b$$

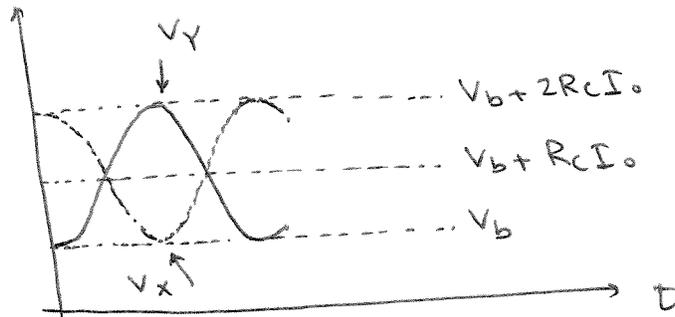
$$V_Y = R_C I_2 + V_b = R_C I_0 (1 - \cos \omega t) + V_b$$



$$V_{X,CM} = V_{Y,CM} = V_b + R_C I_0$$

$$V_{X,P-P} = V_{Y,P-P} = 2R_C I_0$$

(8)

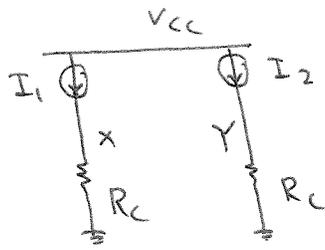


$$I_1 = I_0 \cos \omega t + I_0$$

$$I_2 = -I_0 \cos \omega t + 0.8 I_0$$

$$V_x = R_c I_1 = R_c I_0 (1 + \cos \omega t)$$
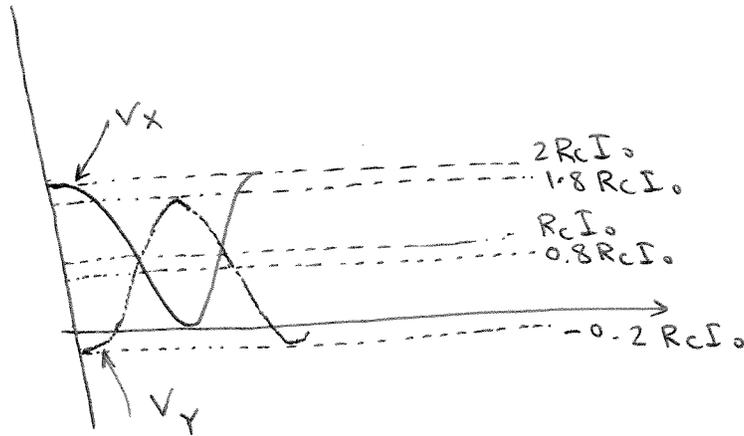
$$V_y = R_c I_2 = R_c I_0 (0.8 - \cos \omega t)$$



$$V_{x,CM} = R_c I_0 \quad V_{y,CM} = 0.8 R_c I_0$$

$$V_{x,P-P} = 2 R_c I_0 \quad V_{y,P-P} = 2 R_c I_0$$


X and Y are true differential signals.

9)

$$I_1 = I_0 \cos \omega t + I_0$$

$$I_2 = -I_0 \cos \omega t + I_0$$



(a)

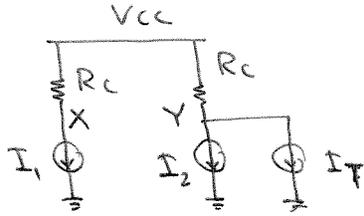


$$V_x = R_c I_1 = R_c I_0 (1 + \cos \omega t)$$

$$V_y = R_c (I_2 + I_T) =$$
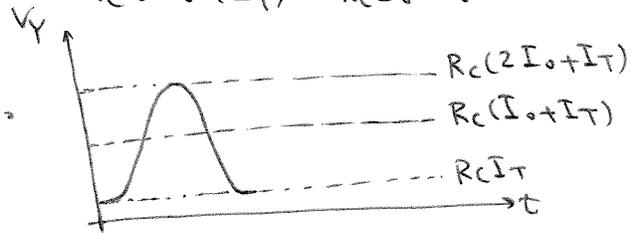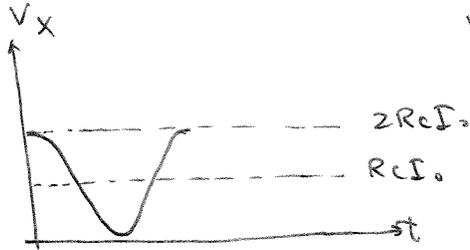
$$R_c (I_0 + I_T) - R_c I_0 \cos \omega t$$





(b)

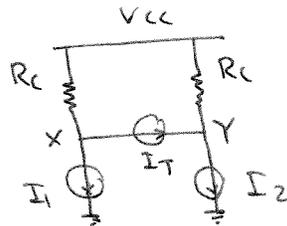


$$V_x = V_{cc} - R_c (I_1 + I_T) = V_{cc} - R_c (I_0 + I_T) - R_c I_0 \cos \omega t$$
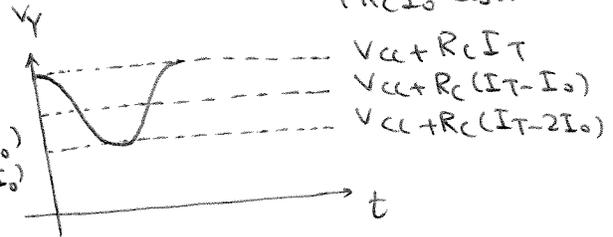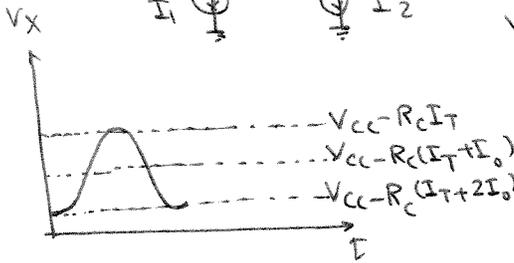
$$V_y = V_{cc} - R_c (I_2 - I_T) = V_{cc} - R_c (I_0 - I_T) + R_c I_0 \cos \omega t$$




(c)

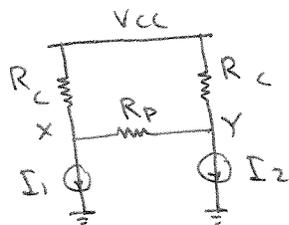


$$\begin{cases} \frac{V_x - V_{cc}}{R_c} + \frac{V_x - V_y}{R_p} + I_1 = 0 \\ \frac{V_y - V_{cc}}{R_c} + \frac{V_y - V_x}{R_p} + I_2 = 0 \end{cases} \Rightarrow$$

$$V_x = V_{cc} - R_c I_0 - \frac{R_c R_p}{2 R_c + R_p} I_0 \cos \omega t$$
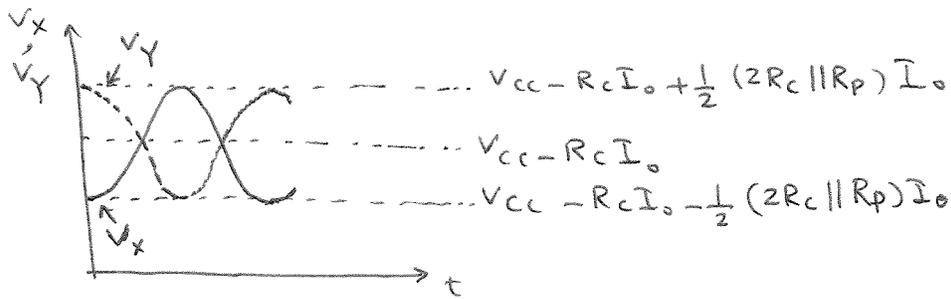
$$V_y = V_{cc} - R_c I_0 + \frac{R_c R_p}{2 R_c + R_p} I_0 \cos \omega t$$





(d)

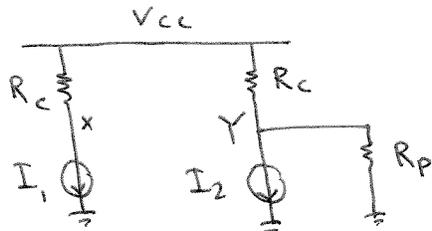

$$V_x = V_{CC} - R_c I_1 = V_{CC} - R_c I_0 (1 + \cos \omega t)$$

$$V_Y = \frac{R_p}{R_p + R_c} V_{CC} - (R_c || R_p) I_2 =$$

$$\frac{R_p}{R_p + R_c} V_{CC} - (R_c || R_p) I_0 (1 - \cos \omega t)$$

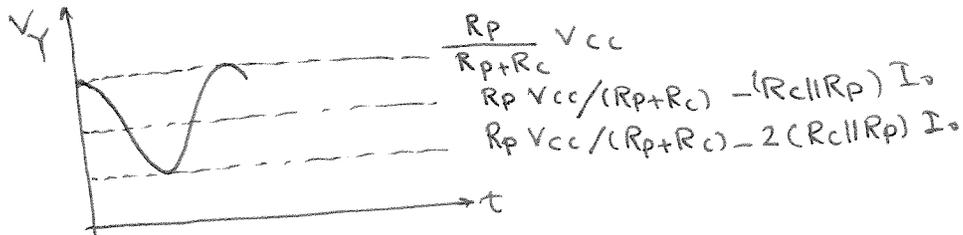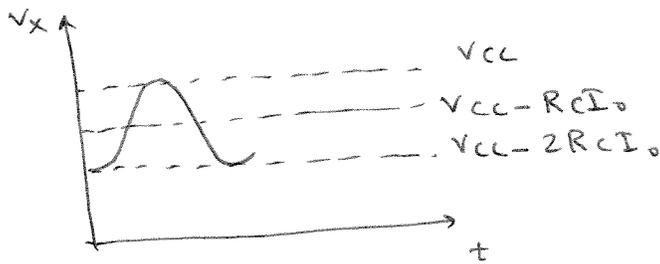


(10)

$$V_1 = V_0 \cos \omega t + V_0$$

$$V_2 = -V_0 \cos \omega t + V_0$$


(a)

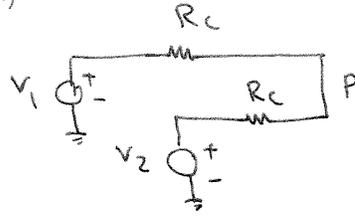

$$V_P = \frac{V_1 + V_2}{2} = V_0$$




(b)

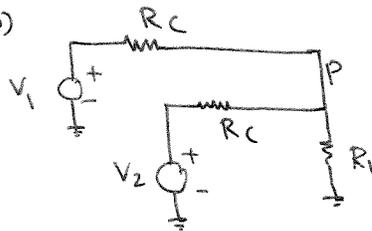


$$\frac{2V_P - V_1 - V_2}{R_c} + \frac{V_P}{R_i} = 0 \Rightarrow$$

$$\frac{2V_P - 2V_0}{R_c} + \frac{V_P}{R_i} = 0 \Rightarrow (2R_i + R_c)V_P = 2V_0 R_i$$
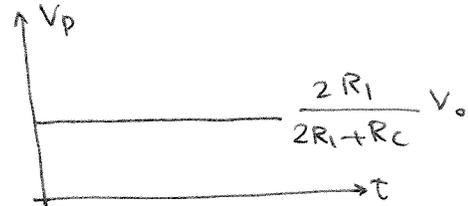
$$\rightarrow V_P = \frac{2R_i}{2R_i + R_c} V_0$$




(c)

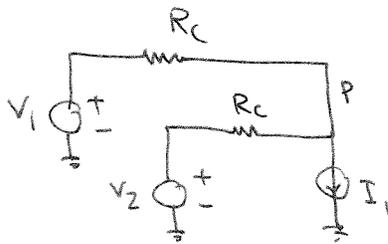


$$\frac{2V_P - V_1 - V_2}{R_c} + I_1 = 0 \Rightarrow$$

$$\frac{2V_P - 2V_0}{R_c} = -I_1 \Rightarrow$$

$$V_P = V_0 - \frac{R_c I_1}{2}$$

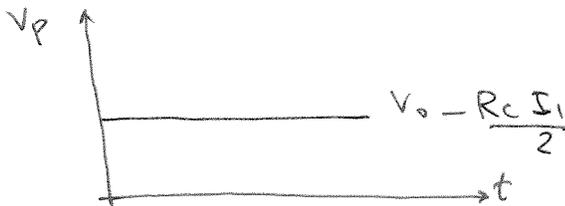

(11)

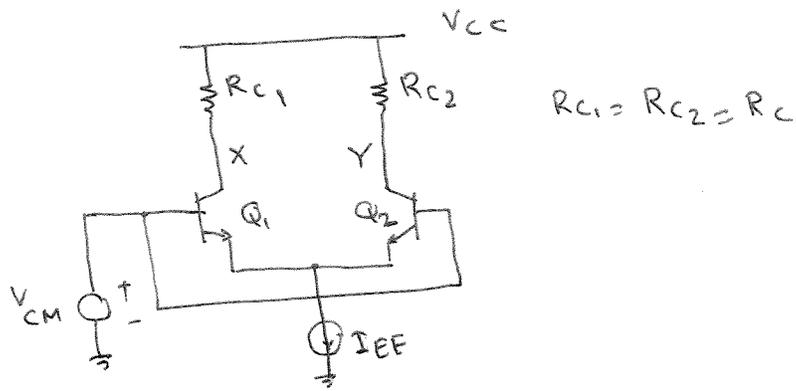


if  $V_{CC}$  changes by  $\Delta V$  then:

$$\Delta V_X = \Delta V, \quad \Delta V_Y = \Delta V \Rightarrow$$

$$\Delta (V_X - V_Y) = 0$$

Since both  $V_X$  and  $V_Y$  response to the supply changes similarly, the circuit rejects supply noise.

12

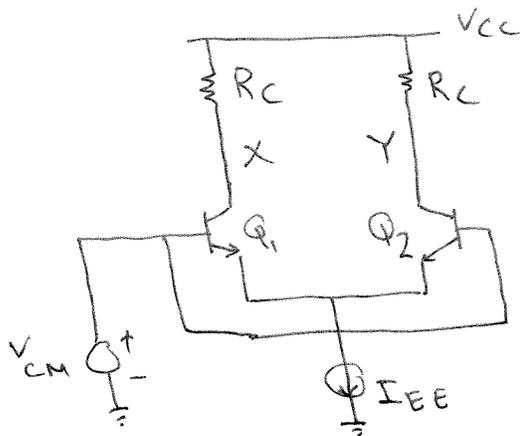


$$\Delta V_X = - \frac{R_C \Delta I_{EE}}{2} = - \frac{R_C \Delta I}{2}$$

$$\Delta V_Y = - \frac{R_C \Delta I_{EE}}{2} = - \frac{R_C \Delta I}{2}$$

$$\Rightarrow \Delta(V_X - V_Y) = 0$$

(13)

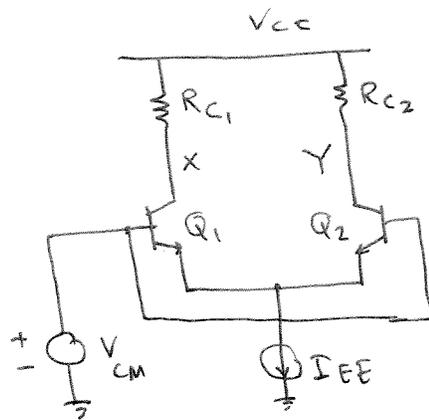


$$R_{C1} = R_{C2} + \Delta R$$

$$\Delta V_X = - \frac{R_{C1} \Delta I}{2} = - \frac{(R_{C2} + \Delta R) \Delta I}{2}$$

$$\Delta V_Y = - \frac{R_{C2} \Delta I}{2} \Rightarrow$$

$$\Delta(V_X - V_Y) = - \frac{\Delta R \Delta I}{2}$$


14

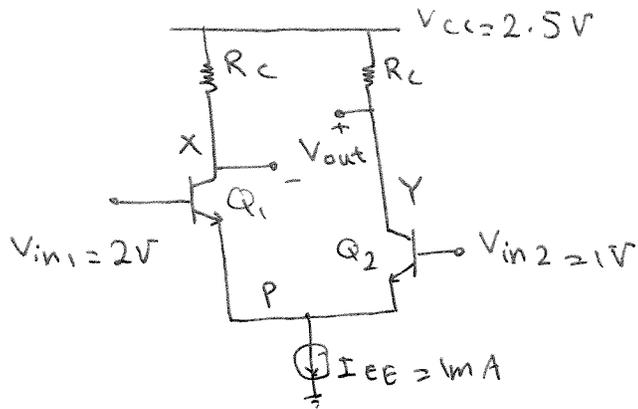

$$V_X \geq V_{in1} \Rightarrow V_X \geq 2 \Rightarrow V_{CC} - R_C I_{EE} \geq 2$$

$$\Rightarrow 2.5 - R_C^{(k\Omega)} \geq 2 \Rightarrow R_C \leq 0.5 \text{ k}\Omega$$


15

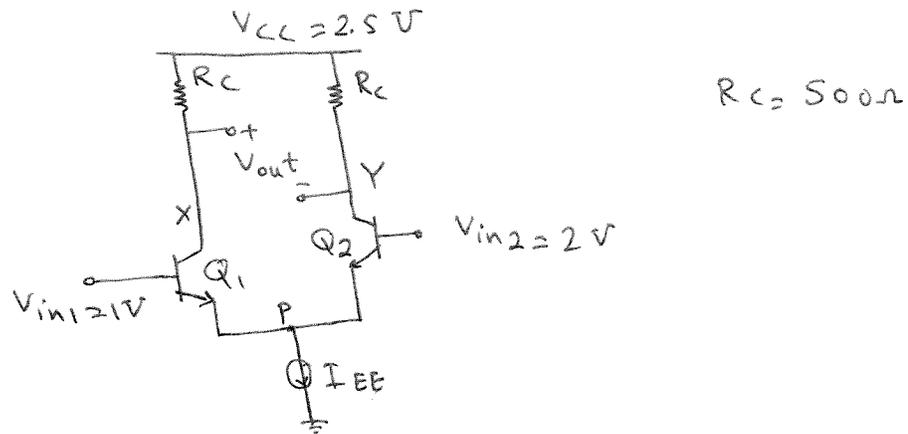

$$V_Y \geq V_{in2} \Rightarrow V_{CC} - R_c I_{EE} \geq 2 \Rightarrow$$

$$2.5 - 500 I_{EE} \geq 2 \Rightarrow I_{EE} \leq 1\text{ mA}$$

16

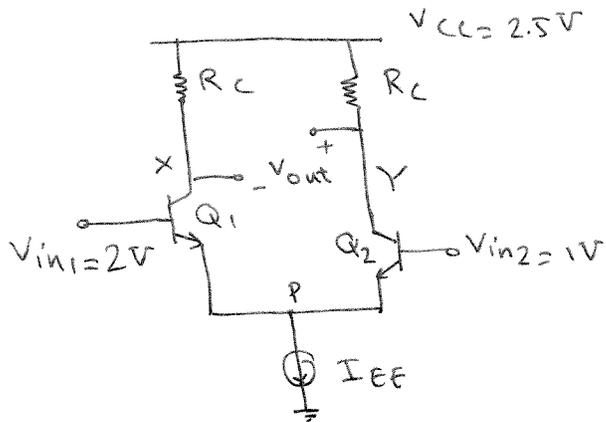

$$I_{EE} = 1mA$$



$$R_C = 800\Omega$$

$$V_X = V_{CC} - R_C \bar{I}_{EE} = 2.5 - 0.8 = 1.7V$$



$\Rightarrow V_X < V_{in1} \Rightarrow Q_1$  is in saturation region.

(17)



(a)

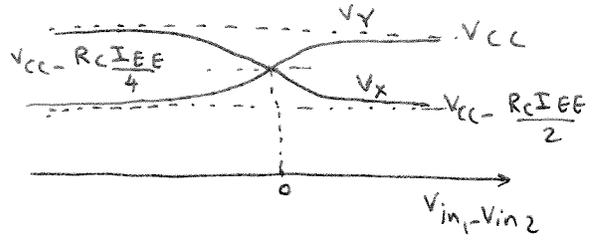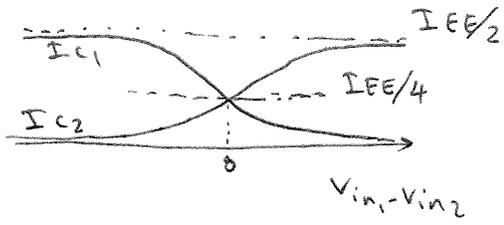


(b)

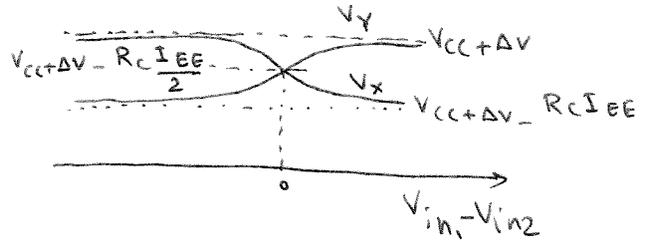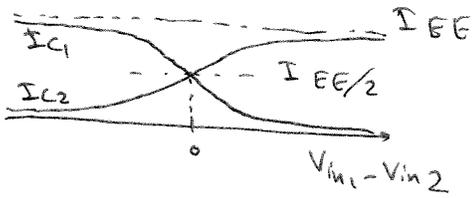

(c)

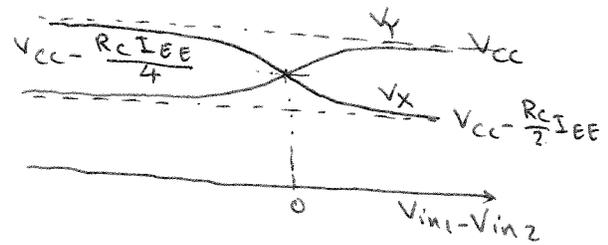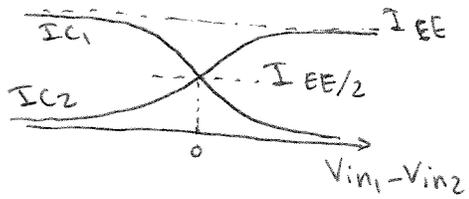

18

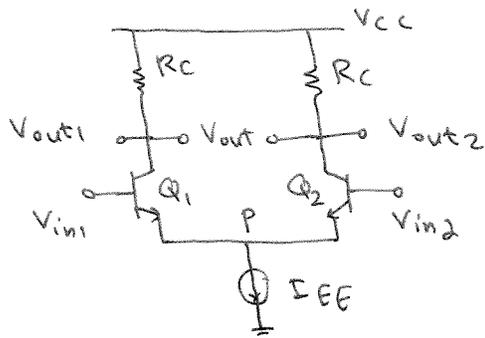

$$\frac{I_{C1}}{I_{C2}} = 5$$

$$V_{in1} - V_{in2} = V_T \ln \frac{I_{C1}}{I_{C2}} = 0.026 \ln 5 = 41.845 \text{ mV}$$

at  $27^\circ$ ,  $V_T = 26 \text{ mV} \Rightarrow$  at  $100^\circ$ ,

$$V_T = \frac{(273 + 100)}{273 + 27} 26^{\text{mV}} = 32.33 \text{ mV}$$

$$\Rightarrow \frac{41.845 \text{ mV}}{\text{mV}} = \frac{32.33 \text{ mV}}{\text{mV}} \ln \frac{I_{C1}}{I_{C2}} \Rightarrow \frac{I_{C1}}{I_{C2}} = 3.65$$

(19)

$$I_{C2} = I_{C1} = \frac{I_{EE}}{2}$$

if  $I_{C2}$  changes by 10% then


$$1.1 \times I_{C2 \text{ bias}} = \frac{I_{EE}}{1 + \exp \frac{V_{in1} - V_{in2}}{V_T}} \Rightarrow$$

$$1.1 \times \frac{I_{EE}}{2} = \frac{I_{EE}}{1 + \exp \frac{V_{in1} - V_{in2}}{V_T}} \Rightarrow$$

$$V_{in1} - V_{in2} = V_T \ln \frac{0.9}{1.1} = -0.2 V_T = -5.217 \text{ mV}$$

So the input differential voltage should change by no more than 5.2 mV.

(20)

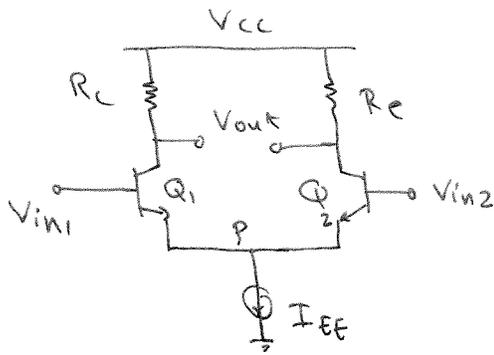

$$I_{C2} = \frac{I_{EE}}{1 + \exp\left(\frac{V_{in1} - V_{in2}}{V_T}\right)}$$

$$I_{C2 \text{ bias}} = \frac{I_{EE}}{2}$$

if the transconductance of  $Q_2$  drops by a factor of 2, then  $I_{C2} = \frac{I_{EE}}{4}$

$$\Rightarrow \frac{I_{EE}}{4} = \frac{I_{EE}}{1 + \exp\left(\frac{V_{in1} - V_{in2}}{V_T}\right)} \Rightarrow$$


$$V_{in1} - V_{in2} = V_T \ln 3 = 1.0986 V_T = 28.564 \text{ mV}$$

$$(21) \quad v_{in1} - v_{in2} = \Delta v_{in}$$

$$I_{C1} - I_{C2} = \frac{I_{EE} \exp \frac{\Delta v_{in}}{V_T}}{1 + \exp \frac{\Delta v_{in}}{V_T}} - \frac{I_{EE}}{1 + \exp \frac{\Delta v_{in}}{V_T}}$$

$$\Rightarrow \frac{\partial (I_{C1} - I_{C2})}{\partial (\Delta v_{in})} = I_{EE} \left[ \frac{\frac{1}{V_T} \exp \left( \frac{\Delta v_{in}}{V_T} \right) (1 + \exp \frac{\Delta v_{in}}{V_T}) - \frac{(\exp \frac{\Delta v_{in}}{V_T})^2}{V_T}}{(1 + \exp \frac{\Delta v_{in}}{V_T})^2} + \frac{\frac{1}{V_T} \exp \frac{\Delta v_{in}}{V_T}}{(1 + \exp \frac{\Delta v_{in}}{V_T})^2} \right]$$
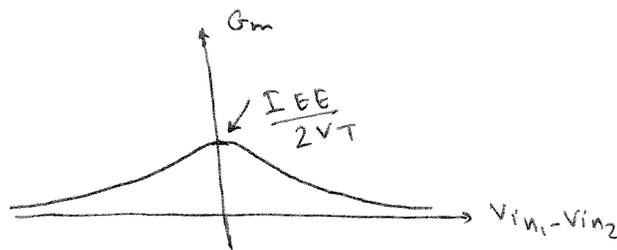
$$= \frac{2 I_{EE}}{V_T} \frac{\exp \left( \frac{v_{in1} - v_{in2}}{V_T} \right)}{\left( 1 + \exp \left( \frac{v_{in1} - v_{in2}}{V_T} \right) \right)^2}$$



$$\begin{cases} \max G_m = \frac{I_{EE}}{2V_T} \\ \text{At } v_{in1} - v_{in2} = 0 \end{cases}$$

$$\text{if } G_m = \frac{1}{2} G_{m_{\max}} = \frac{I_{EE}}{4V_T} \Rightarrow$$

$$\frac{\exp \left( \frac{v_{in1} - v_{in2}}{V_T} \right)}{\left( 1 + \exp \left( \frac{v_{in1} - v_{in2}}{V_T} \right) \right)^2} = \frac{1}{8} \Rightarrow v_{in1} - v_{in2} = \pm 1.763 V_T = \pm 45.838 \text{ mV}$$

Q2)

$$V_{out1} - V_{out2} = -R_C I_{EE} \tanh \frac{V_{in1} - V_{in2}}{2V_T}$$

$$A_V = \frac{\partial (V_{out1} - V_{out2})}{\partial (V_{in1} - V_{in2})} = -\frac{2R_C I_{EE}}{V_T} \frac{\exp\left(\frac{V_{in1} - V_{in2}}{V_T}\right)}{\left[1 + \exp\left(\frac{V_{in1} - V_{in2}}{V_T}\right)\right]^2}$$


if  $V_{in1} - V_{in2} = 30 \text{ mV} \Rightarrow$

$$A_V = -14.02 R_C I_{EE}$$

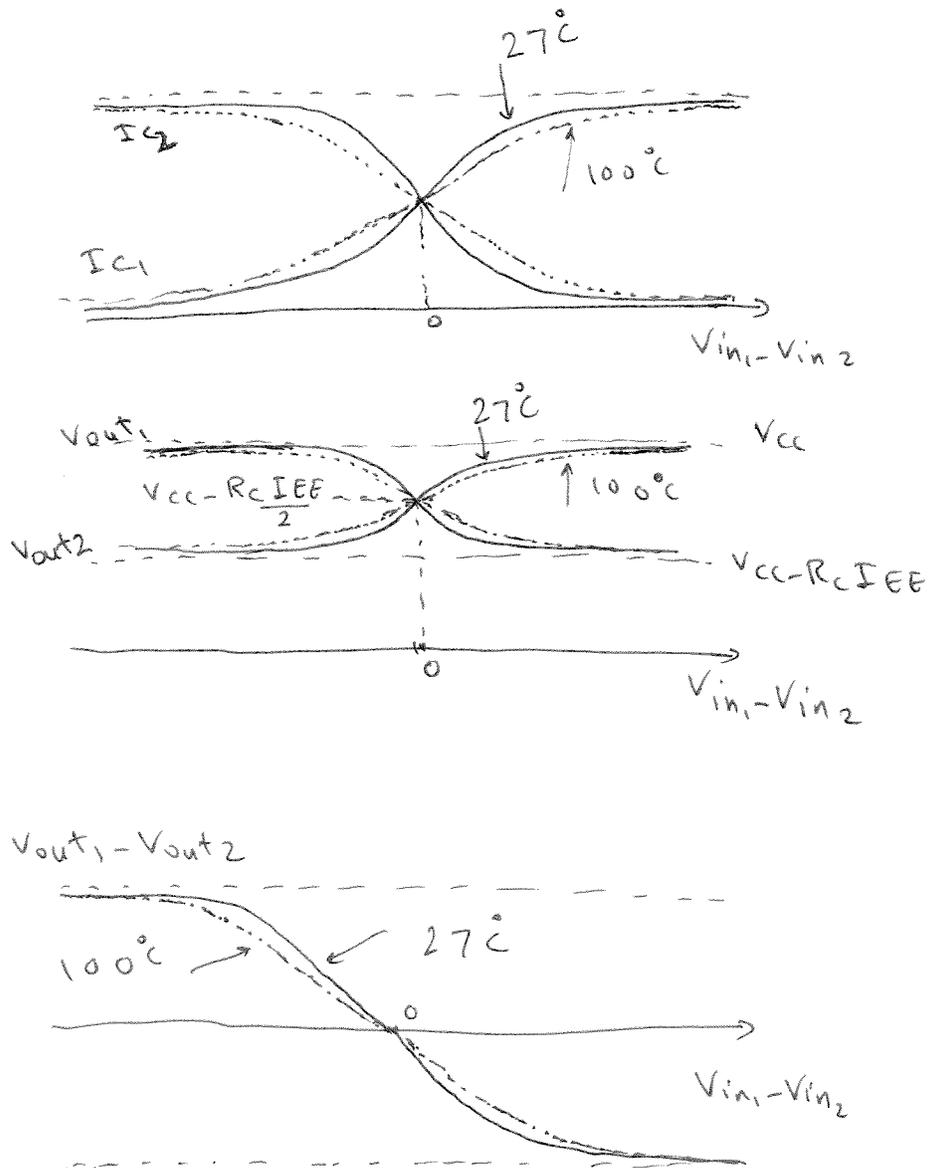
(23)

if the ambient temperature goes from  $27^{\circ}\text{C}$  to  $100^{\circ}\text{C}$ ,  $V_T$  will change from  $26\text{mV}$  to  $32.33\text{mV}$ .

Therefore the curves stretch out as shown below to the sides:



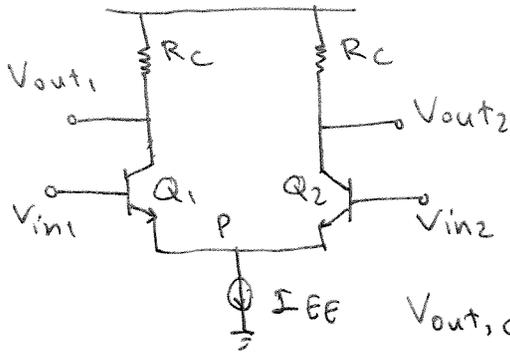(24)  $R_C = 500 \Omega$ ,  $I_{EE} = 1 \text{ mA}$ ,  $V_{CC} = 2.5 \text{ V}$   
 $V_{in1} = V_0 \sin \omega t + V_{CM}$   $V_{in2} = -V_0 \sin \omega t + V_{CM}$ ,  $V_{CM} = 1 \text{ V}$   
 $V_{CC}$




$$A_v = -g_m R_C = -\frac{I_{EE}}{2V_T} R_C =$$

$$= -\frac{10^{-3} \times 500}{2 \times 0.026} = -9.615$$

$$V_{out, CM} = V_{CC} - R_C \frac{I_{EE}}{2} = 2.5 - 0.5 \times 0.5 \Rightarrow$$

$$V_{out, CM} = 2.25$$

(a)  $|V_{out}| = |A_v V_{in}| = 9.615 \times 2 \text{ m} = 19.23 \text{ mV}$

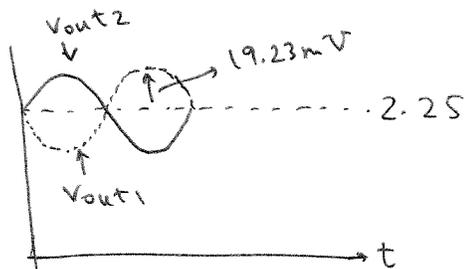


(b)  $I_{C1} = 0.95 I_{EE}$ ,  $I_{C2} = 0.05 I_{EE}$ ,  $\frac{I_{C1}}{I_{C2}} = 19$


$$V_{in1} - V_{in2} = V_T \ln \frac{I_{C1}}{I_{C2}} = 76.555 \text{ mV}$$

$$\frac{V_{in1} - V_{in2}}{2} = \frac{50 \text{ mV}}{2} \sin \omega t_1 \Rightarrow 38.278 = \frac{50 \text{ mV}}{2} \sin \omega t_1 \Rightarrow$$

$$t_1 = \frac{0.872}{\omega}$$

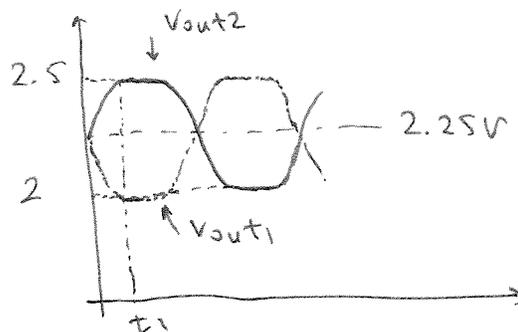

(25)

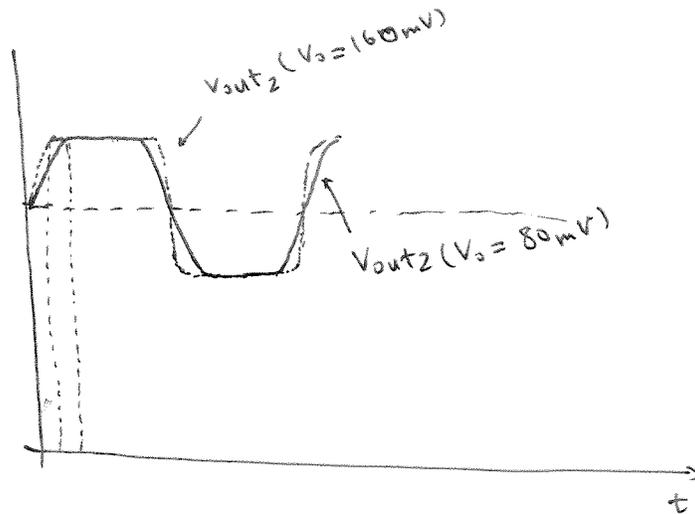

The time at which one transistor takes 95% of the tail current source is achievable through:

$$\frac{I_{C1}}{I_{C2}} = 19 \Rightarrow V_{in1} - V_{in2} = V_T \ln \frac{I_{C1}}{I_{C2}} = 76.555 \text{ mV}$$

$$\frac{V_{in1} - V_{in2}}{2} = V_o \sin \omega t_1 \Rightarrow t_1 = \frac{\text{Arc Sin } \frac{38.278}{V_o}}{\omega}$$

evidently as  $V_o$  increases,  $t_1$  decreases and the output waveform becomes sharper.

$$t_1 (V_o = 80 \text{ mV}) = \frac{0.499}{\omega}$$

$$t_1 (V_o = 160 \text{ mV}) = \frac{0.242}{\omega}$$


$$(26) \quad \omega = 2\pi \times (100 \text{ MHz})$$

$$\text{Slope} \approx \frac{V_{CC} - V_{CM}}{t_1} = \frac{0.25 \text{ V}}{\text{Arc Sin}\left(\frac{38.278}{V_o \text{ (mV)}}\right)}$$


$$\Rightarrow \text{if } V_o = 80 \text{ mV} \Rightarrow \text{slope} = 3.148 \times 10^8 \text{ V/s}$$

$$\text{if } V_o = 160 \text{ mV} \Rightarrow \text{slope} = 6.491 \times 10^8 \text{ V/s}$$

(27)

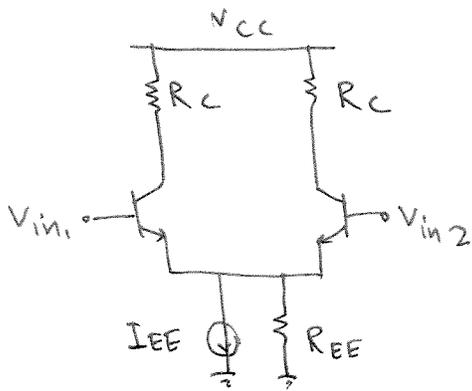

The small signal model is,

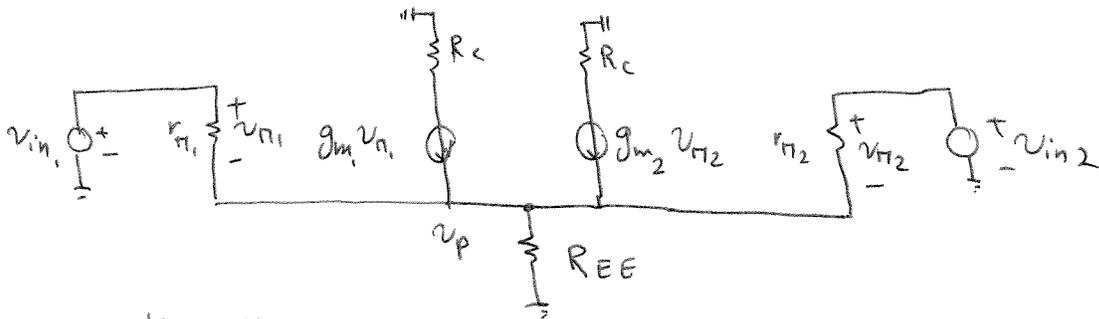


writing the node equation at P we have:

$$\frac{v_p}{R_{EE}} + \frac{v_p - v_{in1}}{r_{\pi 1}} + g_{m1}(v_p - v_{in1}) + \frac{v_p - v_{in2}}{r_{\pi 2}} + g_{m2}(v_p - v_{in2}) = 0$$


Since  $v_{in1} = -v_{in2}$  and  $\begin{cases} r_{\pi 1} = r_{\pi 2} \\ g_{m1} = g_{m2} \end{cases}$ , the above equation simplifies to:
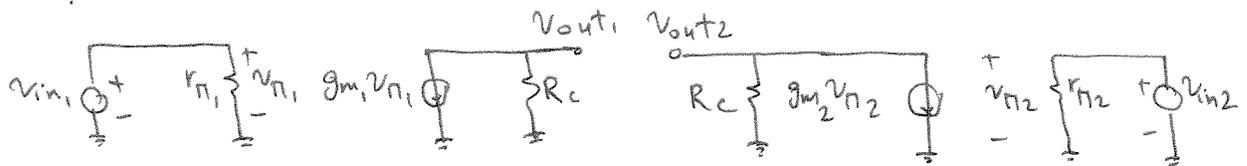
$$\frac{v_p}{R_{EE}} + \frac{2v_p}{r_{\pi 1}} + 2g_{m1}v_p = 0 \Rightarrow v_p = 0 \Rightarrow \text{the small signal model is:}$$



$$A_v = \frac{v_{out1} - v_{out2}}{v_{in1} - v_{in2}} = \frac{-g_{m1}v_{in1}R_C + g_{m2}v_{in2}R_C}{v_{in1} - v_{in2}} = -g_{m1}R_C$$

(28)

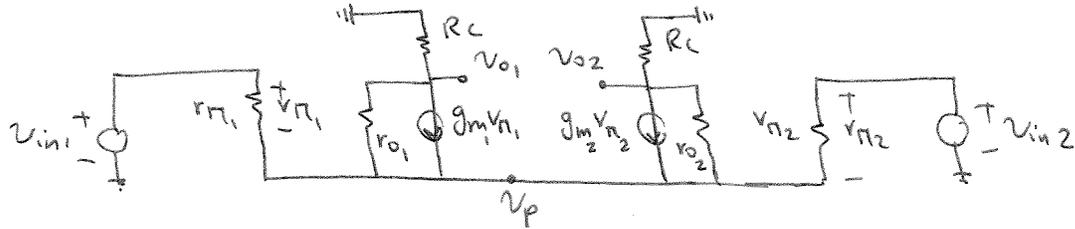

$$v_{in1} = -v_{in2} \rightarrow v_{in1} + v_{in2} = 0$$
$$g_{m1} = g_{m2}, r_{\pi_1} = r_{\pi_2}, r_{o1} = r_{o2}$$

Writing the node equation at  $v_p$ :

$$\frac{v_p - v_{in1}}{r_{\pi_1}} + \frac{v_p - v_{o1}}{r_{o1}} + g_{m1}(v_p - v_{in1}) + g_{m2}(v_p - v_{in2}) +$$
$$\frac{v_p - v_{in2}}{r_{\pi_2}} + \frac{v_p - v_{o2}}{r_{o2}} = 0 \Rightarrow 2g_{m1} v_p + \frac{2v_p - v_{o1} - v_{o2}}{r_{o1}} + \frac{2v_p \times 2}{r_{\pi_1}} = 0 \quad (1)$$

Now the node equations at nodes  $v_{o1}$  and  $v_{o2}$  leads to:


$$\begin{cases} \frac{v_{o1}}{R_c} + \frac{v_{o1} - v_p}{r_{o1}} + g_{m1}(v_{in1} - v_p) = 0 & (2) \\ \frac{v_{o2}}{R_c} + \frac{v_{o2} - v_p}{r_{o2}} + g_{m2}(v_{in2} - v_p) = 0 & (3) \end{cases} \Rightarrow (2) + (3) =$$

$$(v_{o1} + v_{o2}) \left( \frac{1}{R_c} + \frac{1}{r_{o1}} \right) = \frac{2v_p}{r_{o1}} + 2g_{m1} v_p \quad (4)$$

placing 4 in (1)  $\Rightarrow$

$$2g_{m1} v_p + \frac{1}{r_{o1}} \left( 2v_p - \frac{1}{\frac{1}{R_c} + \frac{1}{r_{o1}}} \left( \frac{2v_p}{r_{o1}} + 2g_{m1} v_p \right) \right) + \frac{2v_p \times 2}{r_{\pi_1}} = 0$$
$$\Rightarrow \underline{v_p = 0}$$

(29)

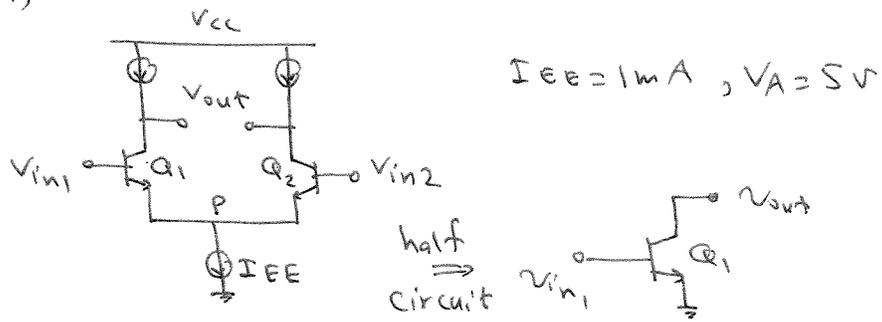


$$I_{EE} = 1 \text{ mA}, V_A = 5 \text{ V}$$


$$A_v = -g_{m1} \cdot r_{o1} = -\frac{I_{EE}}{2V_T} \cdot \frac{V_A}{\frac{I_{EE}}{2}} = -\frac{V_A}{V_T} = \frac{-5}{0.026}$$

$$\rightarrow A_v = -192.31$$

(30)

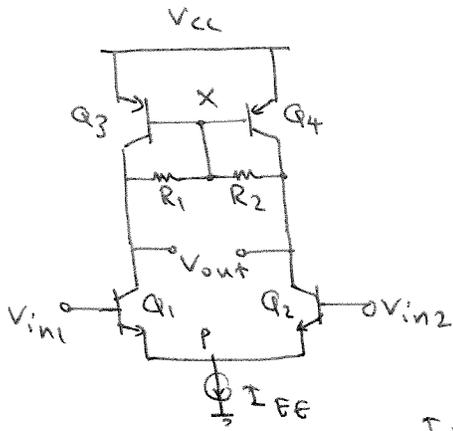

half  
⇒  
circuit

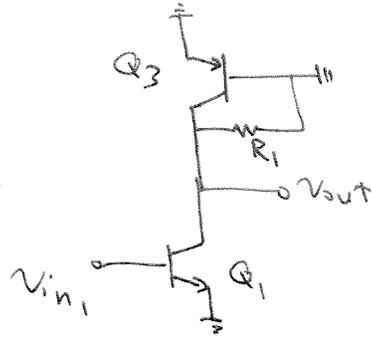

$$I_{EE} = 2\text{mA}, V_{A,n} = 5\text{V}, V_{A,p} = 4\text{V}$$

$$A_v = -g_{m1} (r_{o1} \parallel r_{o3} \parallel R_1)$$

$$\Rightarrow 50 = \frac{I_{EE}}{2V_T} \left( \frac{V_{A,n}}{\frac{I_{EE}}{2}} \parallel \frac{V_{A,p}}{\frac{I_{EE}}{2}} \parallel R_1 \right) \Rightarrow$$

$$50 = \frac{2}{2 \times 26} \left( \frac{5}{10^{-3}} \parallel \frac{4}{10^{-3}} \parallel R_1 \right) \rightarrow$$

$$R_1 = 3132.53 \Omega$$

(31)

The half circuit is:

$$A_v = -g_{m1} (r_{o1} \parallel r_{o3} \parallel R_1)$$


$\Rightarrow$

$$S_0 = \frac{I_{EE}}{2 \times 0.026} \left( \frac{5}{\frac{I_{EE}}{2}} \parallel \frac{4}{\frac{I_{EE}}{2}} \parallel 5K \right) \Rightarrow$$

$$S_0 = \frac{1}{0.052} \left( 10 \parallel 8 \parallel 5I_{EE} \right) \Rightarrow$$


$\downarrow$        $\downarrow$   
10K    8MA

$$I_{EE} = 1.253 \text{ mA}$$

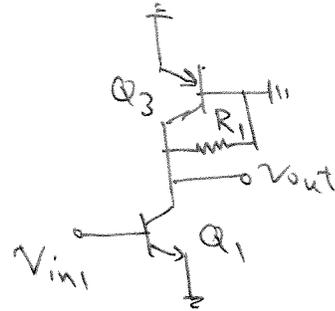


32


(a)

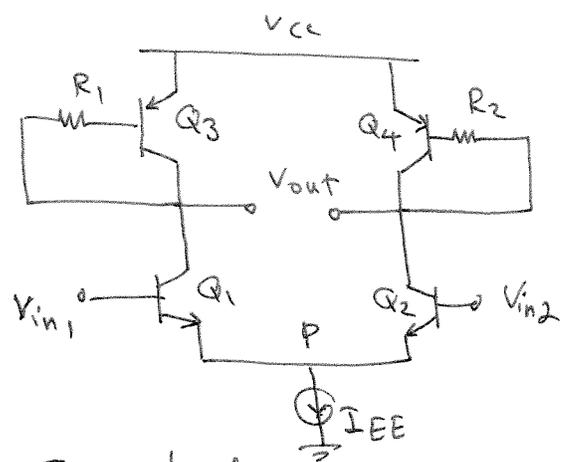

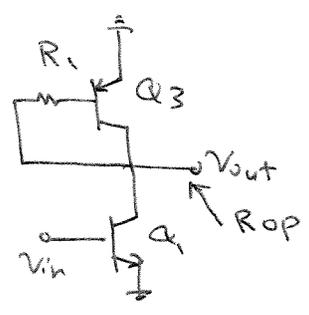From half circuit concept we have:  $A_v = -g_{m1}(r_{o1} \parallel R_{op})$



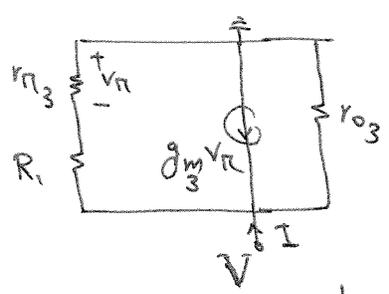To calculate  $R_{op}$ , from small signal model we have:




$$I = \frac{V}{r_{o3}} - g_{m3}V_{\pi} + \frac{V}{R_1 + r_{\pi 3}} = V \left[ \frac{1}{r_{o3}} + \frac{1}{R_1 + r_{\pi 3}} \right] + g_{m3} \frac{r_{\pi 3}}{R_1 + r_{\pi 3}} V$$

$$\rightarrow R_{op} = \frac{V}{I} = r_{o3} \parallel (R_1 + r_{\pi 3}) \parallel \left( \left( 1 + \frac{R_1}{r_{\pi 3}} \right) \frac{1}{g_{m3}} \right)$$


$$\rightarrow A_v = -g_{m1} \left[ r_{o1} \parallel r_{o3} \parallel (R_1 + r_{\pi 3}) \parallel \left( \left( 1 + \frac{R_1}{r_{\pi 3}} \right) \frac{1}{g_{m3}} \right) \right]$$

32


b)

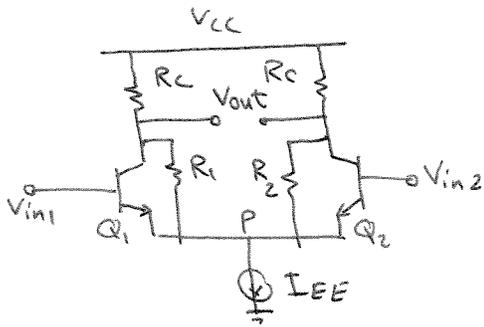


From half circuit concept:

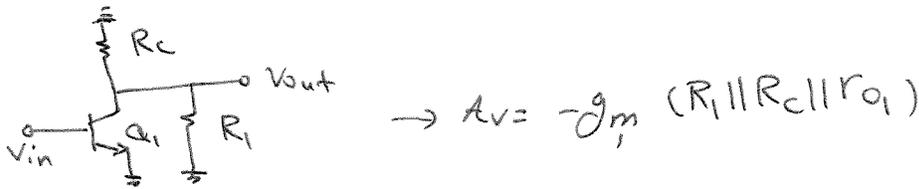

(c)

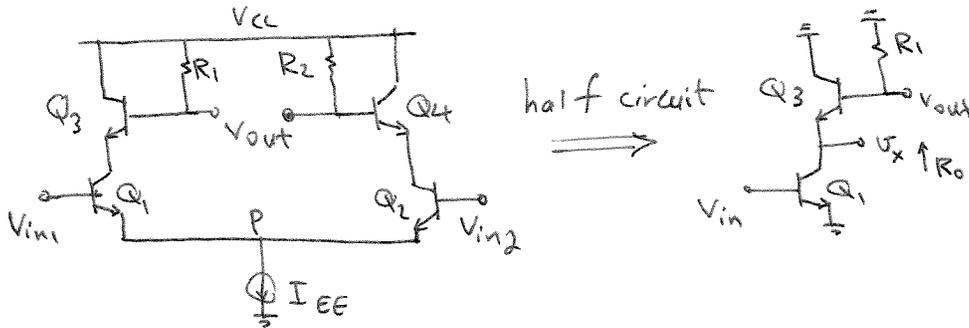

To calculate  $R_o$  we have:

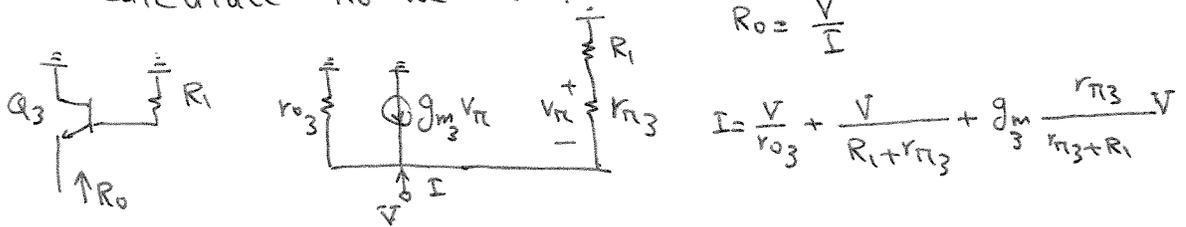

$$R_o = \frac{V}{I}$$


$$I = \frac{V}{r_{o3}} + \frac{V}{R_1 + r_{\pi 3}} + g_{m3} \frac{r_{\pi 3}}{r_{\pi 3} + R_1} V$$

$$\Rightarrow R_o = r_{o3} \parallel (R_1 + r_{\pi 3}) \parallel \left(1 + \frac{R_1}{r_{\pi 3}}\right) \frac{1}{g_{m3}}$$


$$A_v = \frac{v_{out}}{v_{in}} = \frac{v_x}{v_{in}} \frac{v_{out}}{v_x} = -g_{m1} (r_{o1} \parallel R_o) \frac{R_1}{R_1 + r_{\pi 3}}$$

32

(d)

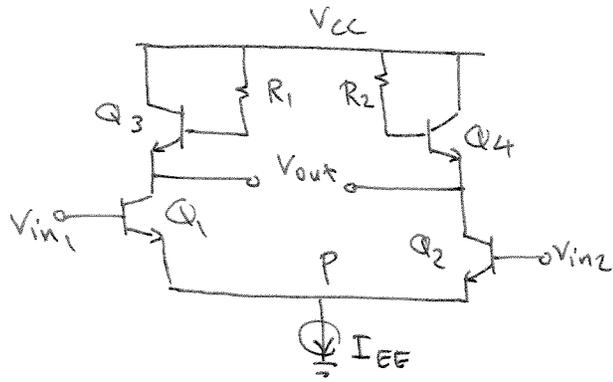

From half circuit concept :

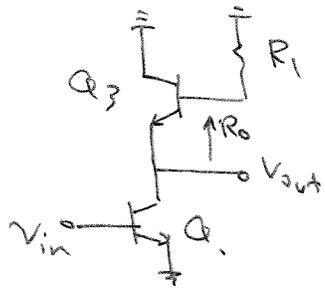


we already proved in part (c) that

$$R_o = r_{o3} \parallel (R_1 + r_{\pi 3}) \parallel \left(1 + \frac{R_1}{r_{\pi 3}}\right) \frac{1}{g_{m3}}$$


$$\rightarrow A_v = \frac{v_{out}}{v_{in}} = -g_{m1} (r_{o1} \parallel R_o)$$

(33)

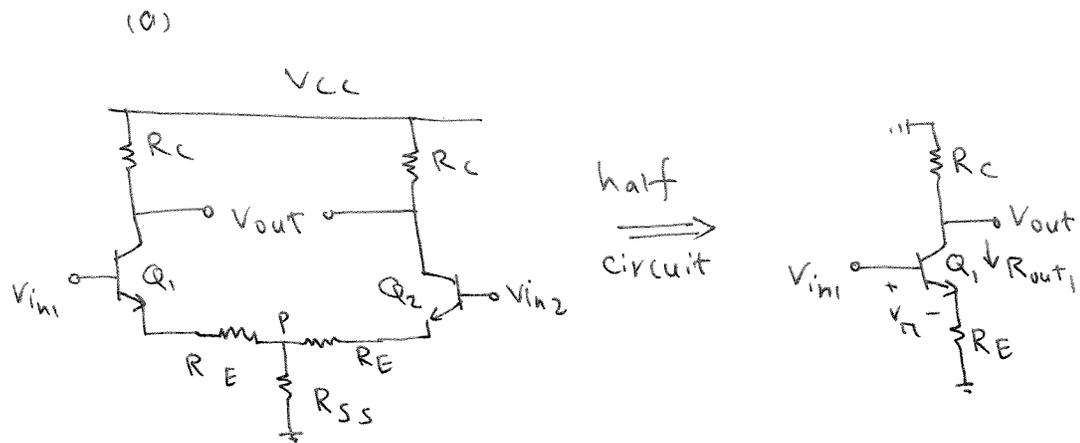

$$R_{out} = R_C \parallel R_{out1} = R_C \parallel (g_{m1} r_{o1} (R_E \parallel r_{\pi1}) + r_{o1} + (R_E \parallel r_{\pi1}))$$

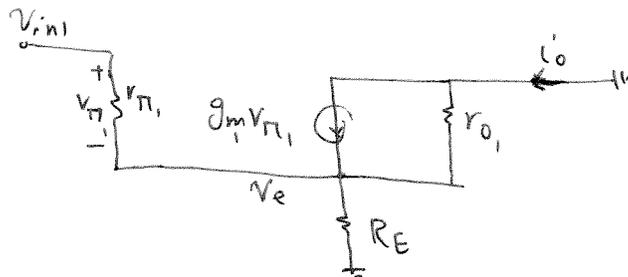To calculate  $G_m$ , the small signal model is:



writing node equation at node  $v_e$ :

$$\frac{v_e}{R_E \parallel r_{o1}} = (g_{m1} + \frac{1}{r_{\pi1}}) v_{\pi1} = \underbrace{(g_{m1} + \frac{1}{r_{\pi1}})}_{g_{m1}} (v_{in1} - v_e)$$


$$\Rightarrow v_e = \frac{g_{m1}}{g_{m1} + \frac{1}{R_E \parallel r_{o1}}} v_{in1} \Rightarrow i_o = \frac{v_e}{r_{o1}} - g_{m1} v_{\pi1}$$

$$= \frac{v_e}{r_{o1}} + g_{m1} (v_e - v_{in1}) \Rightarrow G_m = \frac{i_o}{v_{in1}} = + \frac{g_{m1} r_{o1}}{g_{m1} r_{o1} R_E + r_{o1} + R_E}$$

$$\Rightarrow A_v = -G_m R_{out}$$

(33)

(b)

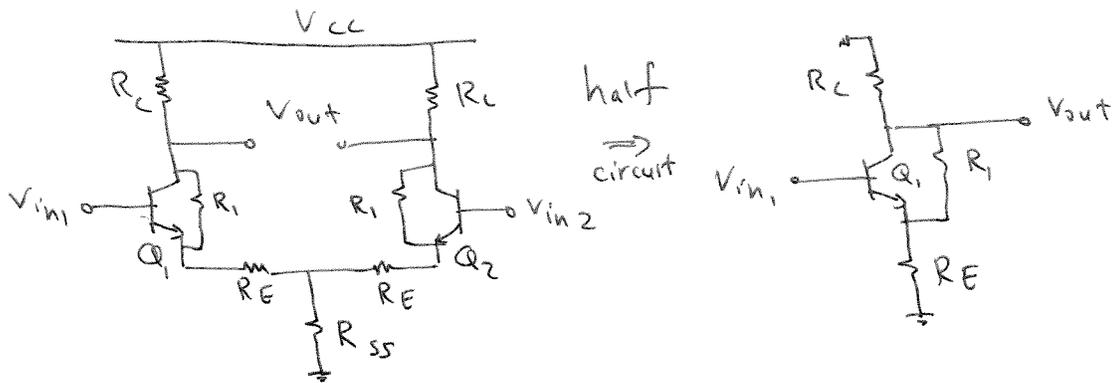


$$R_{out} = R_C \parallel \left( g_{m_1} (r_{o_1} \parallel R_1) (R_E \parallel r_{\pi_1}) + (r_{o_1} \parallel R_1) + (R_E \parallel r_{\pi_1}) \right)$$

Similar to the approach in part (a)


$$G_m = + \frac{g_{m_1} (r_{o_1} \parallel R_1)}{g_{m_1} (r_{o_1} \parallel R_1) R_E + (r_{o_1} \parallel R_1) + R_E}$$

$$\Rightarrow A_v = -G_m R_{out}$$

34

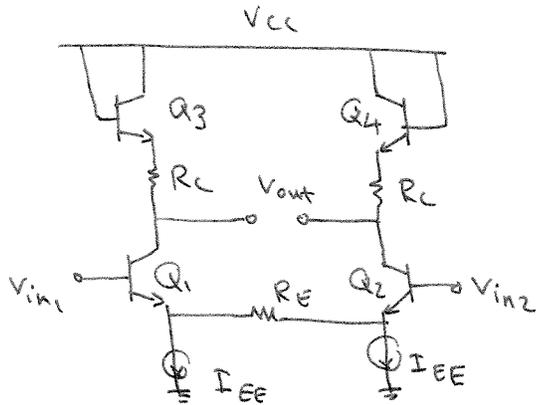


The half circuit is shown as:

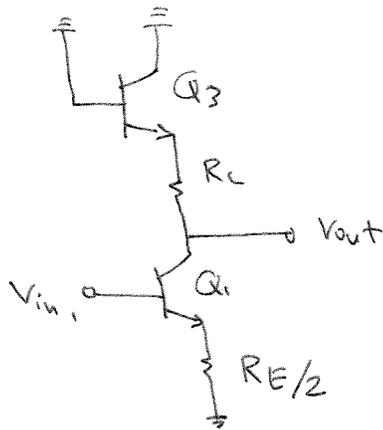

$$a) A_v = \frac{v_{out}}{v_{in1}} = - \frac{R_c + 1/g_{m3}}{R_{E/2} + 1/g_{m1}}$$

b) if  $\frac{R_c}{R_{E/2}} = A$ , then if  $\frac{1/g_{m3}}{1/g_{m1}} = A$   
we conclude  $A_v = -A$ . So the circuit  
is very linear.

35

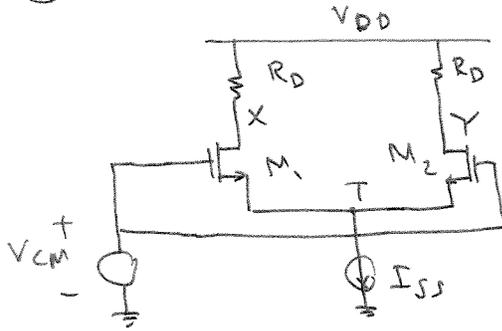

$$V_T = V_{CM} - V_{GS1} = V_{CM} - V_{TH} - \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

(a)  $V_T = V_{CM} - V_{TH} - \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{2W}{L}}}$

The tail voltage increases


(b)  $V_T = V_{CM} - V_{TH} - \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$

The tail voltage decreases

(c)  $V_T = V_{CM} - V_{TH} - \sqrt{\frac{I_{SS}}{\mu_n \frac{C_{ox}}{2} \frac{W}{L}}}$

The tail voltage decreases

36

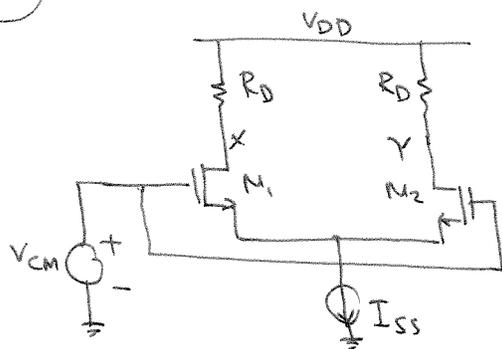

$$\begin{aligned}V_{CM} &= 1V \\ I_{SS} &= 1mA \\ R_D &= 1k\Omega\end{aligned}$$


$$V_x = V_{DD} - R_D \frac{I_{SS}}{2} = V_{DD} - 0.5$$

To ensure that the devices work in saturation

$$V_{CM} \leq V_x - V_{TH} \rightarrow V_{DD} - 0.5 - V_{TH} \geq 1$$

$$\text{if } V_{TH} = 0.5 \rightarrow V_{DD} > 2$$

37

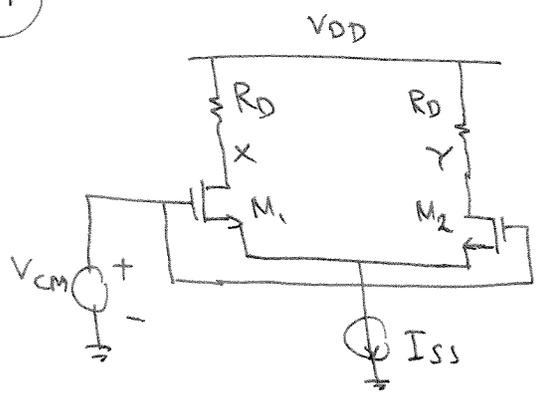


$$V_{GS} - V_{TH} = 200 \text{ mV}$$
$$\mu_n C_{ox} = 100 \text{ } \mu\text{A/V}^2$$
$$\frac{W}{L} = 20/0.18$$

$$(V_{GS} - V_{TH})_{\text{equil}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \rightarrow$$

$$0.2 = \sqrt{\frac{I_{SS}}{10^{-4} \times \frac{20}{0.18}}} \rightarrow I_{SS} = 0.44 \text{ mA}$$

38

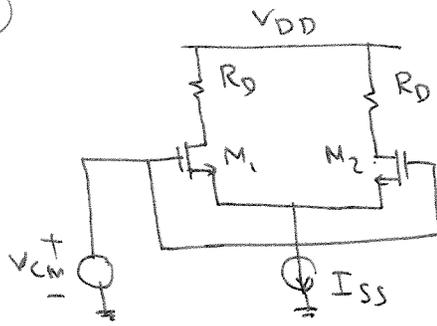


$$\frac{I_{D1}}{W} = \frac{I_{SS}}{2W} = J$$

current density


$$(V_{GS} - V_{TH})_{\text{equil}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} =$$

$$\sqrt{\frac{2J}{\mu_n C_{ox} \frac{1}{L}}}$$

(39)

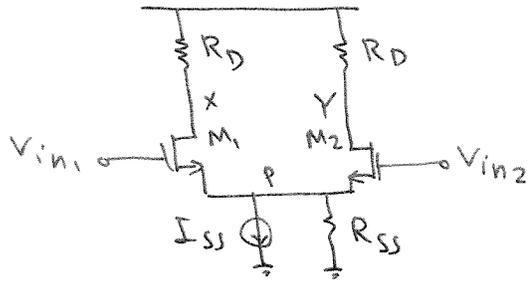

$$g_{m1} = g_{m2} = g_m$$

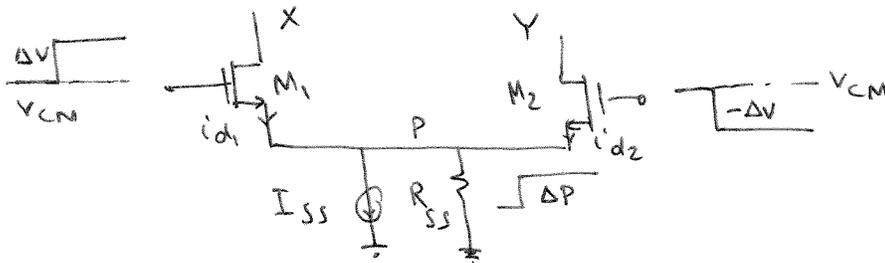


if  $V_{in1}$  and  $V_{in2}$  change by  $\Delta V$  and  $-\Delta V$  we have:

node equation at P:  $i_{d1} + i_{d2} + \frac{\Delta P}{R_{SS}} = 0 \Rightarrow$

$$g_m (\Delta V - \Delta P) + g_m (-\Delta V - \Delta P) + \frac{\Delta P}{R_{SS}} = 0 \Rightarrow$$

$$-g_m \Delta P - g_m \Delta P + \frac{\Delta P}{R_{SS}} = 0 \Rightarrow \Delta P = 0$$

40

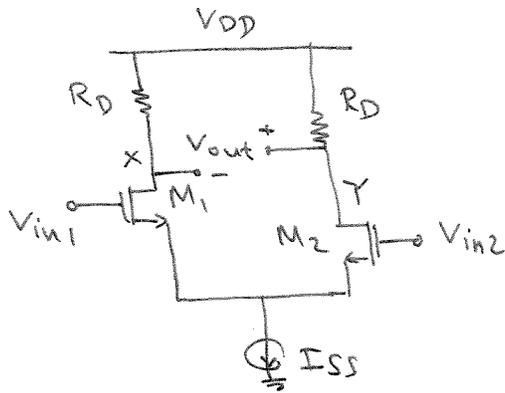

$$V_{in1} = 1.5$$
$$V_{in2} = 0.3$$

$$V_x - V_{TH} > V_{in1} \rightarrow V_{DD} - R_D I_{SS} - V_{TH} > 1.5$$

41

$$P = 2 \text{ mW}$$

$$V_{DD} = 2 \text{ V} \rightarrow I_{SS} = 1 \text{ mA}$$

$$V_{CM, out} = V_{DD} - R_D \frac{I_{SS}}{2} = 2 - 0.5 R_D \rightarrow$$

$$R_D = \frac{2 - V_{CM, out}}{0.5} \text{ (k}\Omega\text{)}$$

$$g_m R_D = 5 \rightarrow \sqrt{2 \mu_n C_{ox} \frac{W}{L} \frac{I_{SS}}{2}} \cdot \frac{2 - V_{CM, out}}{0.5} = 5 \quad \downarrow \text{k}\Omega$$

$$\rightarrow \sqrt{2 \times 10^{-4} \frac{W}{L} \frac{10^{-3}}{2}} \cdot 2 \times 10^3 (2 - V_{CM, out}) = 5$$

$$\text{if } V_{CM, out} = 1.6 \rightarrow \frac{W}{L} = 390.625$$


To formulate the trade off we have:

$$I_{SS} = \frac{2}{V_{DD}} \text{ mA} \Rightarrow R_D = \frac{V_{DD} - V_{CM, out}}{1} \times V_{DD} \text{ (k}\Omega\text{)}$$

$$\Rightarrow |g_m R_D| = 5 \Rightarrow$$

$$\sqrt{2 \times 10^{-4} \left(\frac{W}{L}\right) \frac{1}{V_{DD}} \times 10^{-3}} (V_{DD} - V_{CM, out}) V_{DD} = 5$$

(42)

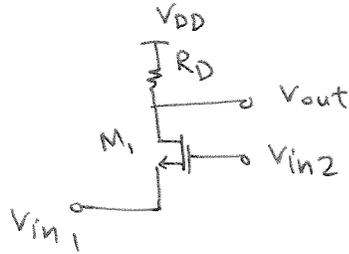

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{in2} - V_{in1} - V_{TH})^2$$

- (1) The current is not an odd function of  $(V_{in2} - V_{in1})$ . Therefore it is not symmetric around  $V_{in1} = V_{in2} [(V_{in1} - V_{in2}) = 0]$ .
- (2) The input impedance seen at  $V_{in1}$  and  $V_{in2}$  are different
- (3) The circuit cannot suppress the supply noise, because there is no differential output available.

(43)

$$(V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} (I_{SS} - 2\sqrt{I_{D1} I_{D2}})$$

(a)

$$I_{D1} = 0 \Rightarrow$$

$$(V_{in1} - V_{in2})^2 = \frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}} \rightarrow V_{in1} - V_{in2} = \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

This is the minimum differential input voltage to turn  $M_1$  off.

$$(b) \quad I_{D1} = \frac{I_{SS}}{2} \Rightarrow I_{D2} = \frac{I_{SS}}{2}$$

$$(V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} (I_{SS} - I_{SS}) = 0 \rightarrow V_{in1} - V_{in2} = 0$$

This is the equilibrium input case.

$$(c) \quad I_{D1} = I_{SS} \rightarrow I_{D2} = 0$$

$$(V_{in1} - V_{in2})^2 = \frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}} \rightarrow V_{in1} - V_{in2} = \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

This is the minimum input differential

voltage to turn  $M_2$  off.

(44)

$$I_{D1} = \frac{I_{SS}}{2} - \frac{1}{4} \sqrt{4I_{SS}^2 - \left[ \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 - 2I_{SS} \right]}$$

The analyses which led to the above equation assume that the transistors work in saturation region.

So,

$$-(V_{in1} - V_{in2})_{\max} \leq V_{in1} - V_{in2} \leq (V_{in1} - V_{in2})_{\max}$$

$$(V_{in1} - V_{in2})_{\max} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow$$

$$\mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 \leq 2I_{SS} \Rightarrow$$


$$- \left[ \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 - 2I_{SS} \right] \geq 0 \Rightarrow$$

$$\frac{1}{4} \sqrt{4I_{SS}^2 - \left[ \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 - 2I_{SS} \right]} \geq \frac{1}{2} I_{SS}$$

$$\Rightarrow I_{D1} < 0$$

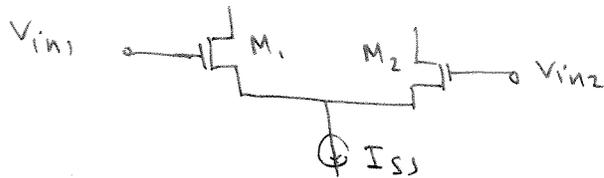(45)

$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$



The equilibrium overdrive voltage is:

$$(V_{GS1} - V_{TH})_{\text{equil}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} = V_{OV} \Rightarrow$$

$$\mu_n C_{ox} \frac{W}{L} = \frac{I_{SS}}{V_{OV}^2} \quad \text{therefore}$$

$$I_{D1} - I_{D2} = \frac{I_{SS}}{2} \frac{(V_{in1} - V_{in2})}{V_{OV}^2} \sqrt{\frac{4I_{SS}}{\frac{I_{SS}}{V_{OV}^2}} - (V_{in1} - V_{in2})^2} \Rightarrow$$

$$I_{D1} - I_{D2} = I_{SS} \Rightarrow$$

$$I_{SS} = \frac{I_{SS}}{2} \frac{(V_{in1} - V_{in2})}{V_{OV}^2} \sqrt{4V_{OV}^2 - (V_{in1} - V_{in2})^2}$$

$$\Rightarrow (V_{in1} - V_{in2})^4 - 4V_{OV}^2 (V_{in1} - V_{in2})^2 + 4V_{OV}^4 = 0$$

$$\Rightarrow ((V_{in1} - V_{in2})^2 - 2V_{OV}^2)^2 = 0 \Rightarrow$$

$$V_{in1} - V_{in2} = \sqrt{2} V_{OV} = \sqrt{2} \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

(46)

$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$

$$V_{ov} = (V_{GS} - V_{TH})_{\text{equil}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow \mu_n C_{ox} \frac{W}{L} = \frac{I_{SS}}{V_{ov}^2}$$

$$\Rightarrow I_{D1} - I_{D2} = \frac{I_{SS}}{2} \frac{(V_{in1} - V_{in2})}{V_{ov}^2} \sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}$$

$$\Rightarrow G_m = \frac{\partial(I_{D1} - I_{D2})}{\partial(V_{in1} - V_{in2})} =$$


$$\frac{I_{SS}}{2V_{ov}^2} \left[ \frac{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}}{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}} - \frac{(V_{in1} - V_{in2})^2}{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}} \right] =$$

$$\frac{I_{SS}}{2V_{ov}^2} \frac{4V_{ov}^2 - 2(V_{in1} - V_{in2})^2}{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}} =$$

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} \frac{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - 2(V_{in1} - V_{in2})^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}}$$

$$V_{in1} - V_{in2} = 0 \Rightarrow$$
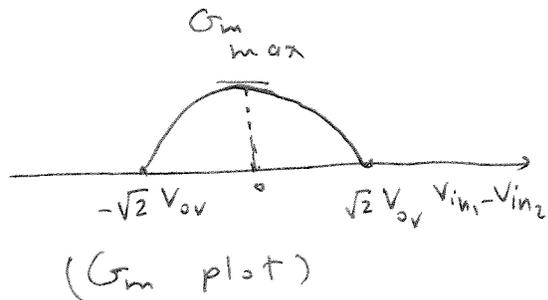
$$G_{m \max} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}}$$



47

From problem 46:

$$G_{m \max} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} = \sqrt{\frac{I_{SS}}{V_{ov}^2} I_{SS}} = \frac{I_{SS}}{V_{ov}}$$

$$\Rightarrow \text{if } G_m = \frac{1}{2} \frac{I_{SS}}{V_{ov}} \text{ we have}$$

$$\frac{1}{2} \frac{I_{SS}}{V_{ov}} = \frac{I_{SS}}{2 V_{ov}^2} \frac{4V_{ov}^2 - 2(V_{in1} - V_{in2})^2}{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}} \Rightarrow$$

$$V_{ov} = \frac{4V_{ov}^2 - 2(V_{in1} - V_{in2})^2}{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}} \Rightarrow$$

$$(4V_{ov}^2 - (V_{in1} - V_{in2})^2) V_{ov}^2 = 16V_{ov}^4 + 4(V_{in1} - V_{in2})^4 - 16V_{ov}^2 (V_{in1} - V_{in2})^2$$

$$\Rightarrow 4(V_{in1} - V_{in2})^4 - 15V_{ov}^2 (V_{in1} - V_{in2})^2 + 12V_{ov}^4 = 0$$

$$\Rightarrow (V_{in1} - V_{in2})^2 = \frac{15V_{ov}^2 \pm \sqrt{225V_{ov}^4 - 192V_{ov}^4}}{8} =$$

$$\frac{15V_{ov}^2 \pm \sqrt{33} V_{ov}^2}{8}$$


positive sign is not accepted

$$\text{because } (V_{in1} - V_{in2})^2 \leq 2V_{ov}^2 \Rightarrow$$


$$V_{in1} - V_{in2} = \pm \sqrt{\frac{15 - \sqrt{33}}{8}} V_{ov} = \pm 1.0756 V_{ov}$$

48-

$$I_D = \gamma (V_{GS} - V_{TH})^3$$

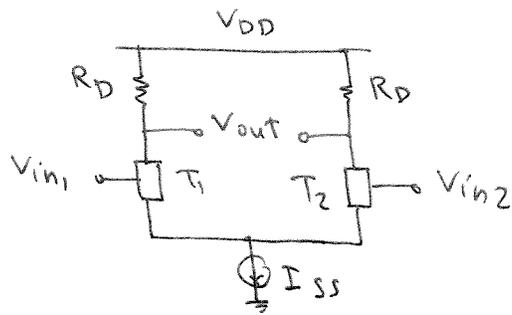

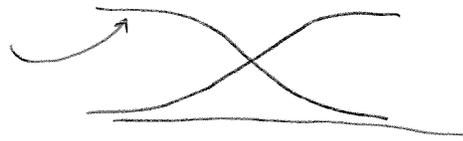(a) The characteristic of  $I_{D1} - I_{D2}$  vs.  $V_{in1} - V_{in2}$  is similar to the standard CMOS differential pair, because it has saturation part.



(b)  $I_D = \frac{I_{SS}}{2} = \gamma (V_{GS} - V_{TH})^3 \Rightarrow$

$$(V_{GS} - V_{TH})_{\text{equil}} = \sqrt[3]{\frac{I_{SS}}{2\gamma}}$$

(c)  $I_{D1} = I_{SS} = \gamma (V_{GS1} - V_{TH})^3 \Rightarrow V_{GS1} - V_{TH} = \sqrt[3]{\frac{I_{SS}}{\gamma}}$

$I_{D2} = 0 = \gamma (V_{GS2} - V_{TH})^3 \Rightarrow V_{GS2} - V_{TH} = 0$

$\Rightarrow V_{GS1} - V_{GS2} = V_{in1} - V_{in2} = \sqrt[3]{\frac{I_{SS}}{\gamma}} =$


$$\sqrt[3]{2} (V_{GS} - V_{TH})_{\text{equil}}$$

(49)

(a)

gate oxide thickness is doubled  $\Rightarrow C_{ox}$  is halved  $\Rightarrow$

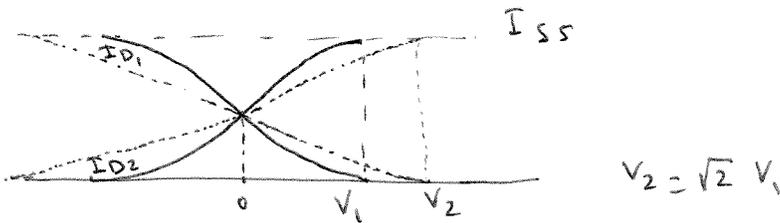$(V_{in1} - V_{in2})_{max}$  scales up by  $\sqrt{2}$ .



so all the curves stretch out to the sides by  $\sqrt{2}$  times.

(b) if threshold voltage is halved, nothing will change in the curves. The reason is that the curves depend on  $V_{in1} - V_{in2}$ .


(c) In this case,  $(V_{in1} - V_{in2})_{max}$  does not change so all the curves scale half downward because  $I_{SS}$  is halved.




(50)

if mobility falls then  $(V_{in1} - V_{in2})_{max}$  will increase because  $(V_{in1} - V_{in2})_{max} = \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$


So the curves stretch out to the sides.

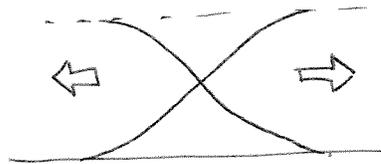

(51)

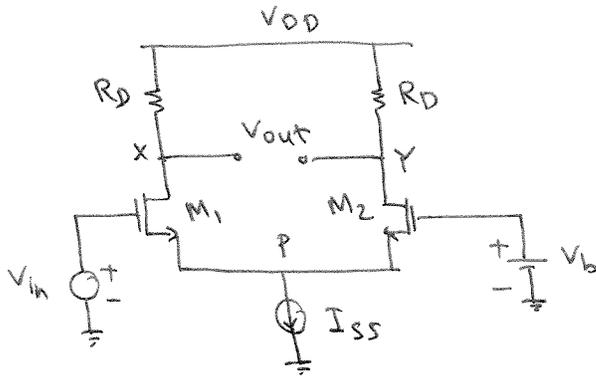


$$g_{m1} = g_{m2} = g_m$$

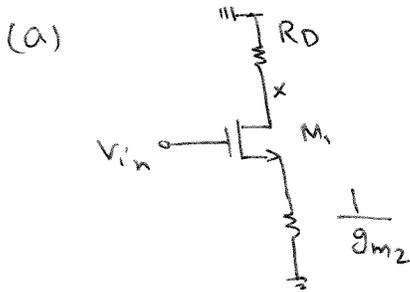

$$v_x = -g_{m1} v_{gs1} R_D =$$

$$-g_{m1} \frac{\frac{1}{g_{m1}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} v_{in} R_D =$$
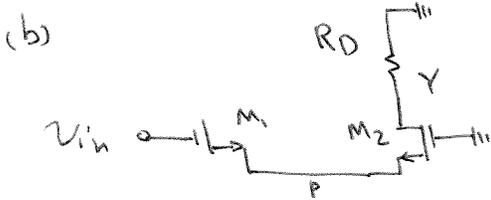
$$-\frac{g_{m1} g_{m2}}{g_{m1} + g_{m2}} R_D v_{in} = -\frac{g_m}{2} R_D v_{in}$$



$$v_p = \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} v_{in}$$

$$\Rightarrow v_p = \frac{g_{m1}}{g_{m1} + g_{m2}} v_{in} \Rightarrow$$

$$v_y = -g_{m2} v_{gs2} R_D = g_{m2} v_p R_D = \frac{g_{m1} g_{m2}}{g_{m1} + g_{m2}} R_D v_{in}$$


$$\rightarrow v_y = \frac{g_m}{2} R_D v_{in}$$

(c)  $\frac{v_x - v_y}{v_{in}} = -g_m R_D$

This value is equal to the gain of the differential amplifier.


(52)

(a)

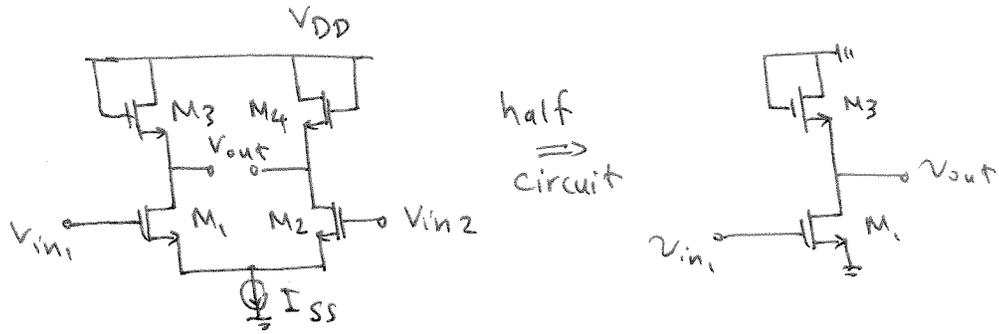


$$A_v = -g_{m1} (r_{o1} \parallel r_{o3} \parallel \frac{1}{g_{m3}})$$

(b)

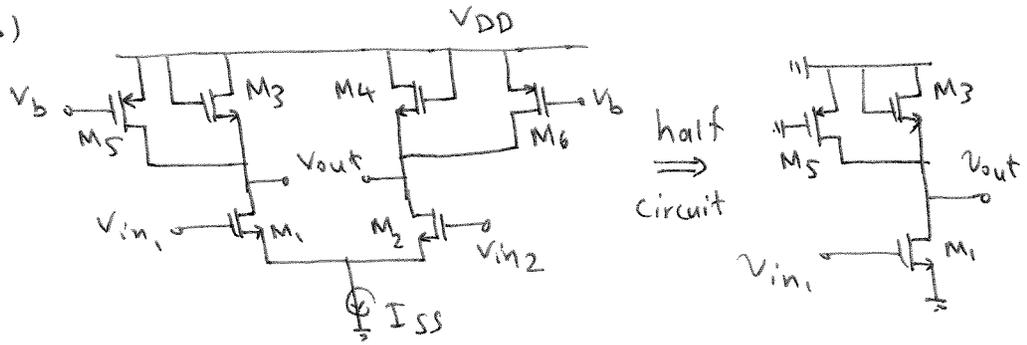


$$A_v = -g_{m1} (r_{o1} \parallel r_{o5} \parallel \frac{1}{g_{m3}} \parallel r_{o3})$$

(c)

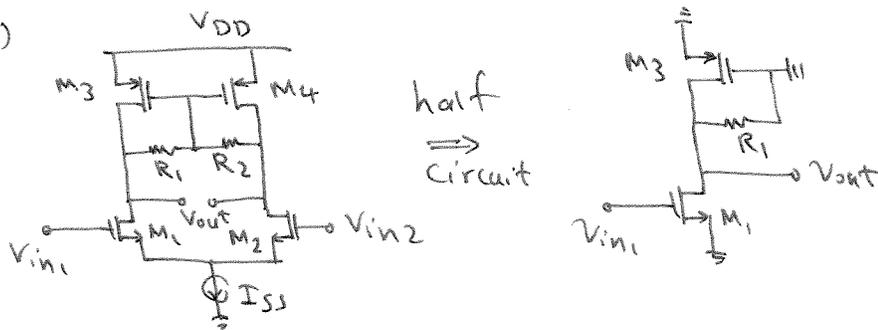


$$A_v = -g_{m1} (r_{o1} \parallel r_{o3} \parallel R_1)$$

(53)

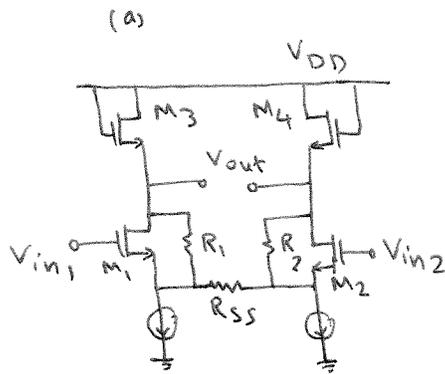


half  
⇒  
circuit

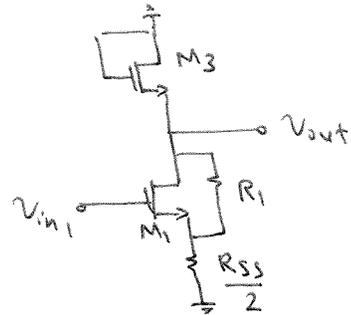

$$R_{out} = (r_{o3} \parallel \frac{1}{g_{m3}}) \parallel (g_{m1} (R_1 \parallel r_{o1}) \frac{R_{SS}}{2} + \frac{R_{SS}}{2} + R_1 \parallel r_{o1})$$

To calculate  $G_m$ :

$$v_{gs1} = v_{in} - v_s$$

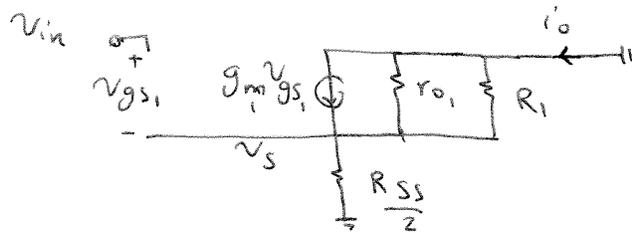

$$\frac{v_s}{\frac{R_{SS}}{2} \parallel R_1 \parallel r_{o1}} + g_{m1} v_s = g_{m1} v_{in} \Rightarrow v_s = \frac{g_{m1} v_{in}}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel R_1 \parallel r_{o1}}}$$


$$i_o = + \frac{v_s}{\frac{R_{SS}}{2}} = + \frac{1}{\frac{R_{SS}}{2}} \frac{g_{m1} v_{in}}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel R_1 \parallel r_{o1}}} \Rightarrow$$

$$G_m = \frac{i_o}{v_{in}} = + \frac{2 g_{m1}}{R_{SS}} \frac{1}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel R_1 \parallel r_{o1}}}$$


$$A_v = -G_m R_{out}$$

53

(b)

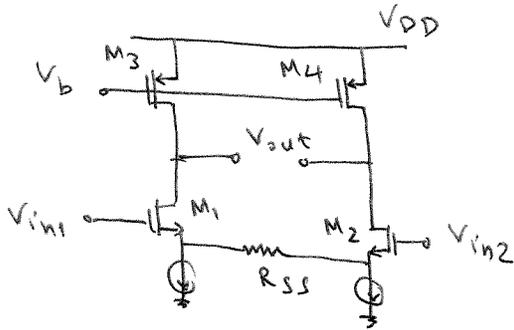


half  
=>  
circuit

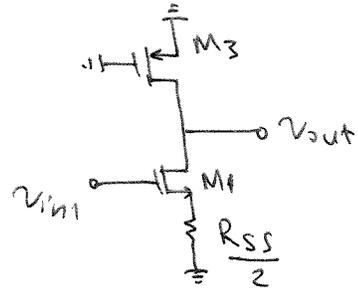

$$R_{out} = r_{o3} \parallel \left( g_{m1} r_{o1} \frac{R_{SS}}{2} + r_{o1} + \frac{R_{SS}}{2} \right)$$


To calculate  $G_m$ :

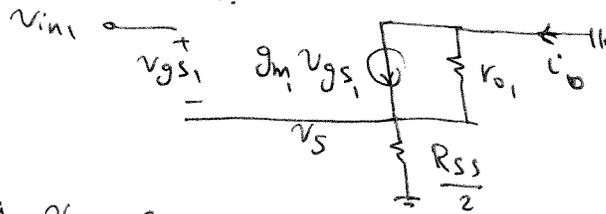


$$\frac{v_s}{r_{o1} \parallel \frac{R_{SS}}{2}} + g_{m1} v_s = g_{m1} v_{in} \Rightarrow v_s = \frac{g_{m1} v_{in}}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel r_{o1}}}$$

$$G_m = \frac{i_o}{v_{in}} = + \frac{v_s}{\frac{R_{SS}}{2}} \frac{1}{v_{in}} = + \frac{2g_{m1}}{R_{SS}} \frac{1}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel r_{o1}}}$$

$\rightarrow A_{v3} = -G_m R_{out}$

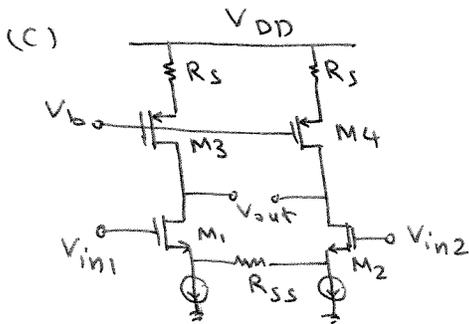

half  
=>  
circuit

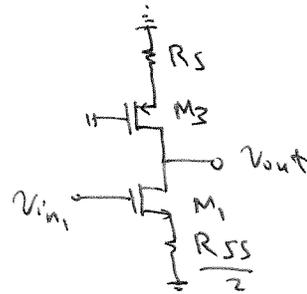


$$R_{out} = (g_{m3} r_{o3} R_s + r_{o3} + R_s) \parallel \left( g_{m1} r_{o1} \frac{R_{SS}}{2} + r_{o1} + \frac{R_{SS}}{2} \right)$$


$G_m$  for this circuit is equal to the one for part (b) so:

$$G_m = + \frac{2g_{m1}}{R_{SS}} \frac{1}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel r_{o1}}} \Rightarrow A_{v2} = -G_m R_{out}$$

(54)

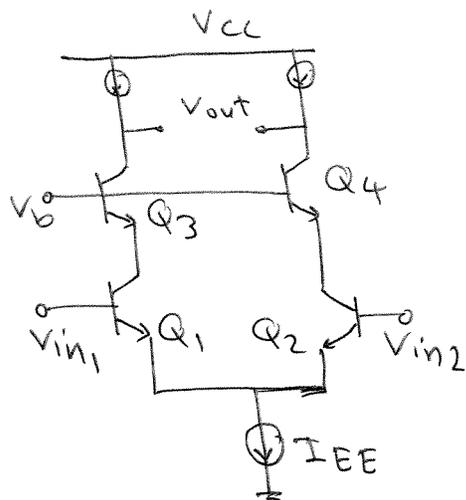

half  
=>  
circuit

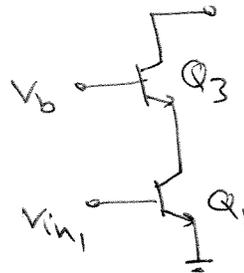

$$A_v = 4000$$
$$\beta = 100$$

$$A_v = -g_{m1} [g_{m3}(r_{o1} \parallel r_{\pi 3})r_{o3} + r_{o3} + r_{o1} \parallel r_{\pi 3}]$$

$$g_{m_{1-4}} = \frac{I_{EE}}{2V_T} \quad r_{o_{1-4}} = \frac{2V_A}{I_{EE}} \quad r_{\pi 3} = \frac{2V_T \beta}{I_{EE}}$$

$$4000 = \frac{I_{EE}}{2V_T} \left[ \frac{I_{EE}}{2V_T} \left( \frac{2V_A}{I_{EE}} \parallel \frac{2V_T \beta}{I_{EE}} \right) \frac{2V_A}{I_{EE}} + \frac{2V_A}{I_{EE}} + \left( \frac{2V_A}{I_{EE}} \parallel \frac{2V_T \beta}{I_{EE}} \right) \right]$$

$$\Rightarrow 4000 = \frac{1}{2V_T} \left[ \frac{V_A}{V_T} (2V_A \parallel 2V_T \beta) + 2V_A + (2V_A \parallel 2V_T \beta) \right] \Rightarrow$$


$$4000 = \frac{1}{V_T} \left[ \frac{V_A}{V_T} (V_A \parallel \beta V_T) + V_A + (V_A \parallel \beta V_T) \right] \Rightarrow$$

$$4000 = \frac{1}{V_T} \left[ \frac{\beta V_A^2}{\beta V_T + V_A} + V_A + \frac{\beta V_A V_T}{\beta V_T + V_A} \right] \Rightarrow$$


$$4000 = \frac{1}{0.026} \left[ \frac{100 V_A^2}{2.6 + V_A} + V_A + \frac{2.6 V_A}{2.6 + V_A} \right] \Rightarrow$$

$$V_A = 2.197$$

(55)

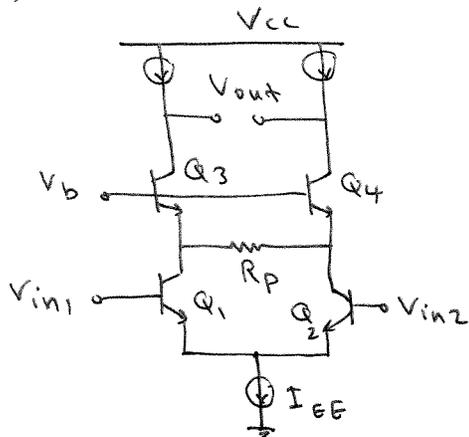

half  
 $\Rightarrow$   
 circuit

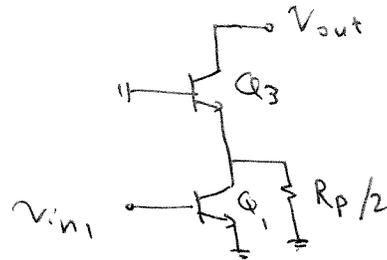


$$R_{out} = g_{m3} r_{o3} \left( \frac{R_p \parallel r_{o1} \parallel r_{o3}}{2} \right) + r_{o3} + \frac{R_p \parallel r_{o1} \parallel r_{o3}}{2}$$

To calculate  $G_m$


$$G_m = \frac{i_o}{v_{in}}$$
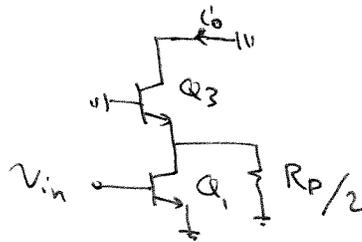
$$\frac{i_o}{v_{in}} = +g_{m1} \frac{g_{m3} \left( \frac{R_p \parallel r_{o1}}{2} \right)}{g_{m3} \left( \frac{R_p \parallel r_{o1}}{2} \right) + 1}$$




$$A_v = -G_m R_{out}$$

(56)

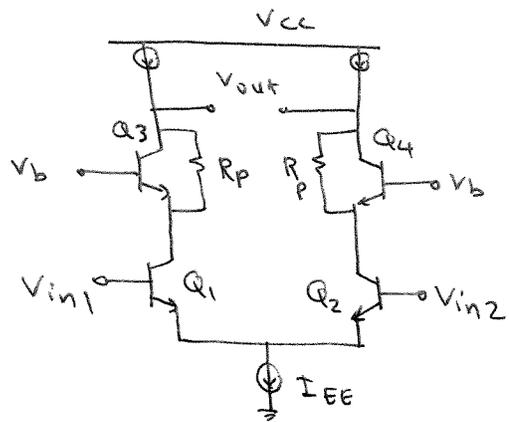


half  
 $\Rightarrow$   
circuit

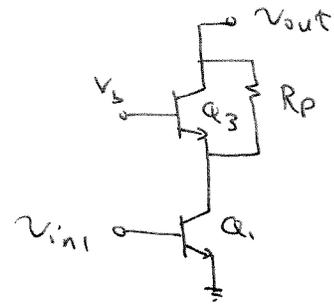


$$A_V = -g_{m1} (g_{m3} (r_{o3} \parallel R_P) (r_{o1} \parallel r_{\pi3}) + (r_{o3} \parallel R_P) + (r_{o1} \parallel r_{\pi3}))$$

(57)

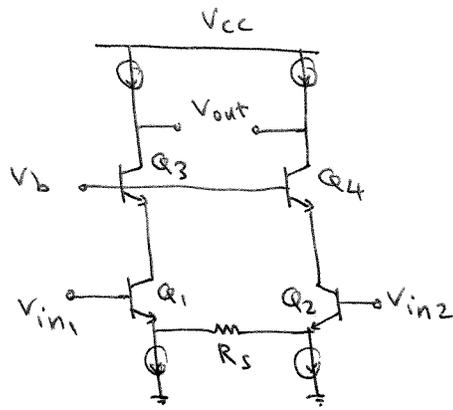

half  
⇒  
circuit

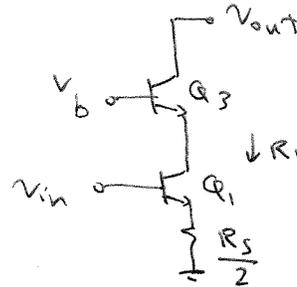


$$R_1 = g_{m1} r_{o1} \left( \frac{R_s}{2} \parallel r_{\pi 1} \right) + r_{o1} + \frac{R_s}{2} \parallel r_{\pi 1}$$

$$R_{out} = g_{m3} r_{o3} (R_1 \parallel r_{\pi 3}) + r_{o3} + (R_1 \parallel r_{\pi 3})$$

To calculate  $G_m$ :

$$v_{\pi 1} \approx \frac{1}{\frac{1}{g_{m1}} + \frac{R_s}{2}} v_{in}$$

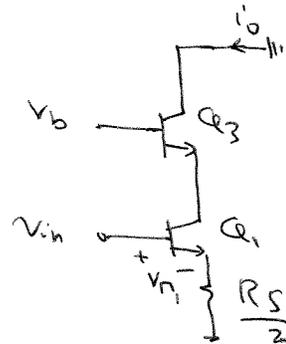
$$= \frac{1}{1 + g_{m1} \frac{R_s}{2}} v_{in}$$




$$G_m = \frac{i_o}{v_{in}} = \frac{+g_{m1} v_{\pi 1}}{v_{in}} = \frac{+g_{m1}}{1 + g_{m1} \frac{R_s}{2}}$$

$$A_v = -G_m R_{out}$$

(58)

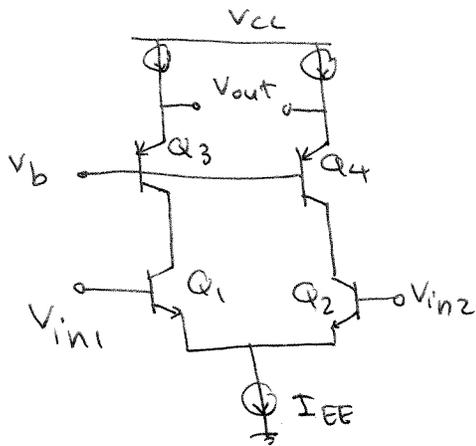


half  
=>  
Circuit

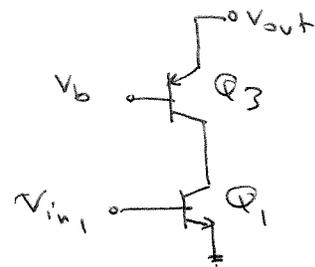

To calculate Rout

$$v_{\pi 3} = v_t$$

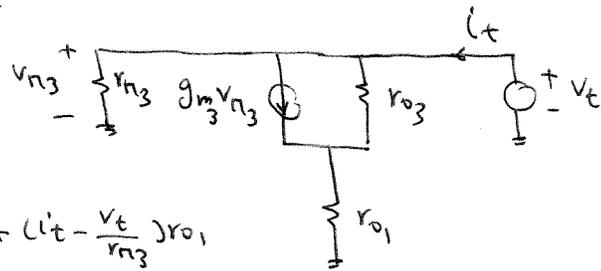

$$v_t = (i_t - g_{m3} v_t - \frac{v_t}{r_{\pi 3}}) r_{o3} + (i_t - \frac{v_t}{r_{\pi 3}}) r_{o1}$$

$$\rightarrow v_t \left( 1 + g_{m3} r_{o3} + \frac{r_{o3}}{r_{\pi 3}} + \frac{r_{o1}}{r_{\pi 3}} \right) = i_t (r_{o1} + r_{o3})$$


$$\rightarrow \frac{v_t}{i_t} = \frac{r_{o1} + r_{o3}}{1 + g_{m3} r_{o3} + \frac{g_{m3} r_{o3}}{\beta_3} + \frac{g_{m3} r_{o1}}{\beta_3}} = R_{out} \rightarrow$$

$$R_{out} \approx \frac{r_{o1} + r_{o3}}{g_{m3} r_{o3}}$$


$$G_m = +g_{m1} \Rightarrow$$

$$A_v \approx -G_m R_{out} \approx -g_{m1} \frac{r_{o1} + r_{o3}}{g_{m3} r_{o3}}$$

(59)

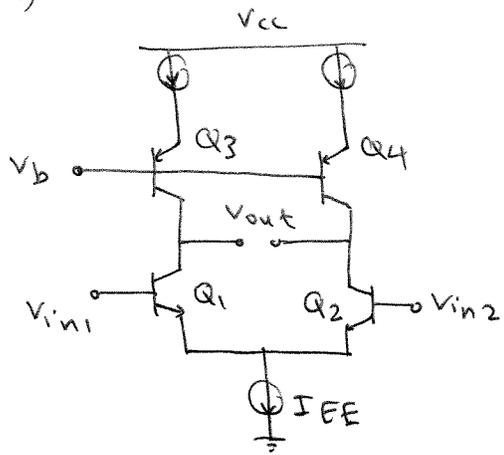


half  
 $\Rightarrow$   
circuit

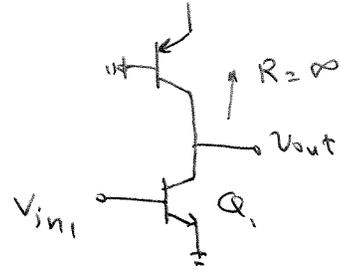


$$A_v = -g_{m1} r_{o1}$$

60

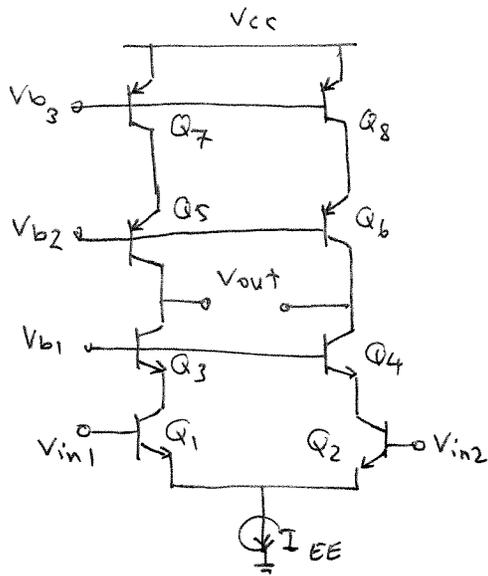

half circuit  
 $\Rightarrow$

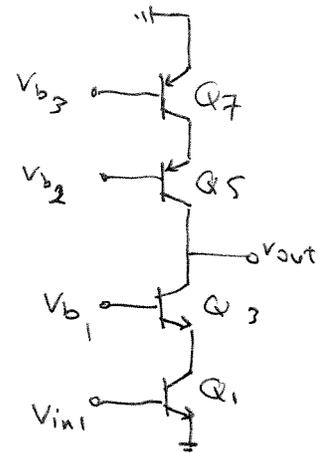

$$A_V = 800, \quad \beta_n = 2\beta_p = 100, \quad V_{A,n} = 2V_{A,p}$$

$$A_V \approx -g_{m1} \left[ g_{m3} r_{o3} (r_{o1} \parallel r_{\pi3}) \right] \parallel \left[ g_{m5} r_{o5} (r_{o7} \parallel r_{\pi5}) \right] =$$

$$- \frac{I_{EE}}{2V_T} \left[ \frac{I_{EE}}{2V_T} \frac{V_{A,n}}{I_{EE}} \left( \frac{V_{A,n}}{I_{EE}} \parallel \frac{\beta_n V_T}{I_{EE}} \right) \right] \parallel \left[ \frac{I_{EE}}{2V_T} \frac{V_{A,p}}{I_{EE}} \left( \frac{V_{A,p}}{I_{EE}} \parallel \frac{\beta_p V_T}{I_{EE}} \right) \right]$$


$$= - \frac{1}{V_T^2} \left[ V_{A,n} (V_{A,n} \parallel \beta_n V_T) \right] \parallel \left[ V_{A,p} (V_{A,p} \parallel \beta_p V_T) \right] =$$

$$- \frac{1}{V_T^2} \left[ V_{A,n} (V_{A,n} \parallel \beta_n V_T) \right] \parallel \left[ \frac{V_{A,n}}{2} \left( \frac{V_{A,n}}{2} \parallel \frac{\beta_n V_T}{2} \right) \right] \Rightarrow$$


$$800 = \frac{1}{5V_T^2} (V_{A,n} (V_{A,n} \parallel 2.6)) \Rightarrow V_{A,n} = 2.245 \text{ V}$$

$$\Rightarrow V_{A,p} = 1.225 \text{ V}$$

61

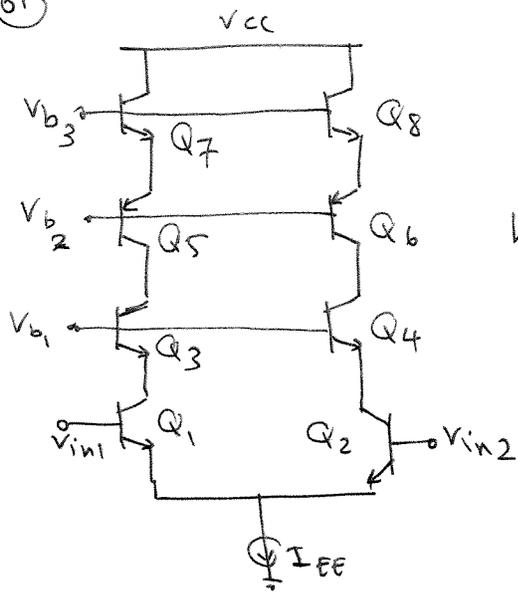

half circuit  
 $\Rightarrow$

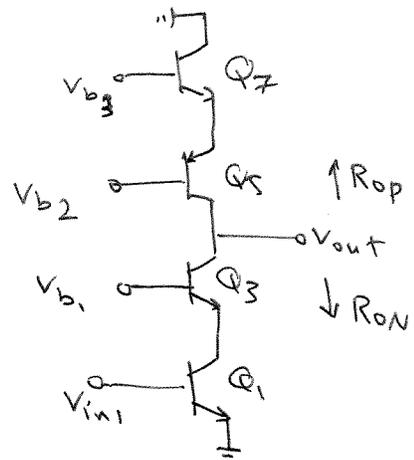



$$R_{ON} = (r_{o1} \parallel r_{\pi 3}) + r_{o3} + g_{m3} r_{o3} (r_{o1} \parallel r_{\pi 3})$$

$$R_{OP} = \frac{1}{g_{m7}} \parallel r_{o7} \parallel r_{\pi 5} + r_{o5} + g_{m5} r_{o5} \left( \frac{1}{g_{m7}} \parallel r_{o7} \parallel r_{\pi 5} \right) \approx$$

$$\frac{1}{g_{m7}} \parallel r_{\pi 5} + r_{o5} + g_{m5} r_{o5} \left( \frac{1}{g_{m7}} \parallel r_{\pi 5} \right)$$

$$A_v = -g_{m1} (R_{ON} \parallel R_{OP})$$

(62)

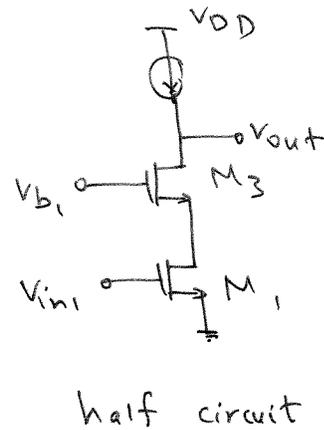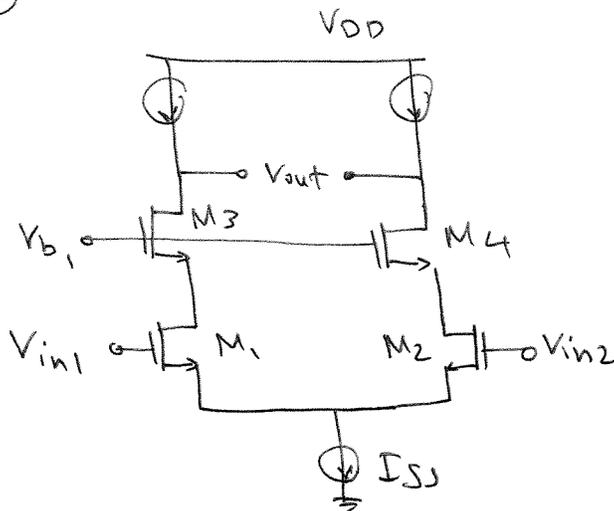

$$A_v = 300, \quad W/L = \frac{20}{0.18}, \quad \mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$$
$$\lambda = 0.1 \text{ V}^{-1}$$

$$A_v \approx -g_{m3} r_{o3} g_{m1} r_{o1}$$

$$g_{m1} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 \frac{I_{SS}}{2}} \quad g_{m3} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_3 \frac{I_{SS}}{2}}$$

$$\rightarrow g_{m1} = g_{m3} = \sqrt{10^{-4} \frac{20}{0.18} I_{SS}}$$



$$r_{o1} = \frac{1}{\lambda \frac{I_{SS}}{2}}, \quad r_{o3} = \frac{1}{\lambda \frac{I_{SS}}{2}} \rightarrow r_{o1} = r_{o3} = \frac{20}{I_{SS}}$$

So:

$$300 = \left(10^{-4} \frac{20}{0.18} I_{SS}\right) \frac{400}{I_{SS}} \Rightarrow$$

$$I_{SS} = 14.815 \text{ mA}$$

63

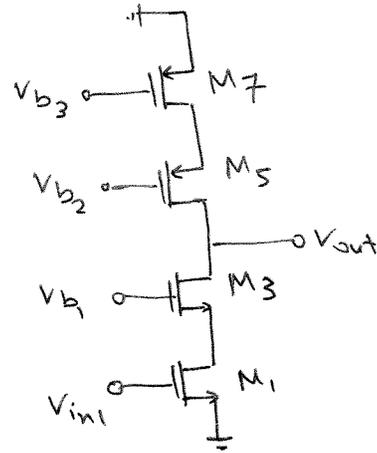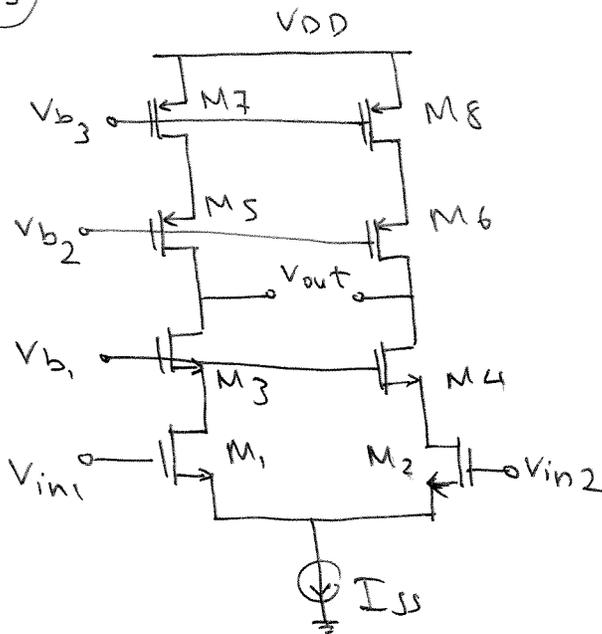

$A_v = 200$ ,  $I_{SS} = 1\text{mA}$ ,  $\mu_n C_{ox} = 100 \mu\text{A/V}^2$   
 $\mu_p C_{ox} = 50 \mu\text{A/V}^2$ ,  $\lambda_n = 0.1\text{V}^{-1}$ ,  $\lambda_p = 0.2\text{V}^{-1}$

$(\frac{W}{L})_1 = \dots = (\frac{W}{L})_8 = ?$



$A_v \approx -g_{m1} \left[ (g_{m3} r_{o3} r_{o1}) \parallel (g_{m5} r_{o5} r_{o7}) \right] \Rightarrow$

$200 = \sqrt{\mu_n C_{ox} (\frac{W}{L})_1 I_{SS}} \left[ \left( \sqrt{\mu_n C_{ox} (\frac{W}{L})_3 I_{SS}} \left( \frac{2}{\lambda_n I_{SS}} \right)^2 \right) \parallel \right.$   
 $\left. \left( \sqrt{\mu_p C_{ox} (\frac{W}{L})_5 I_{SS}} \left( \frac{2}{\lambda_p I_{SS}} \right)^2 \right) \right]$

$\Rightarrow 200 = \sqrt{10^{-4} (\frac{W}{L})_1 10^{-3}} \left[ \left( \sqrt{10^{-4} (\frac{W}{L})_3 10^{-3}} \left( \frac{20}{10^{-3}} \right)^2 \right) \parallel \right.$   
 $\left. \left( \sqrt{0.5 \times 10^{-4} (\frac{W}{L})_5 10^{-3}} \left( \frac{10}{10^{-3}} \right)^2 \right) \right]$


$\Rightarrow \frac{W}{L} = 33.28$

(64)

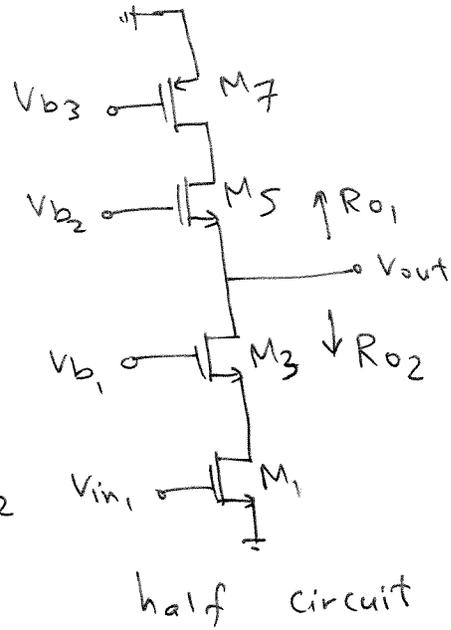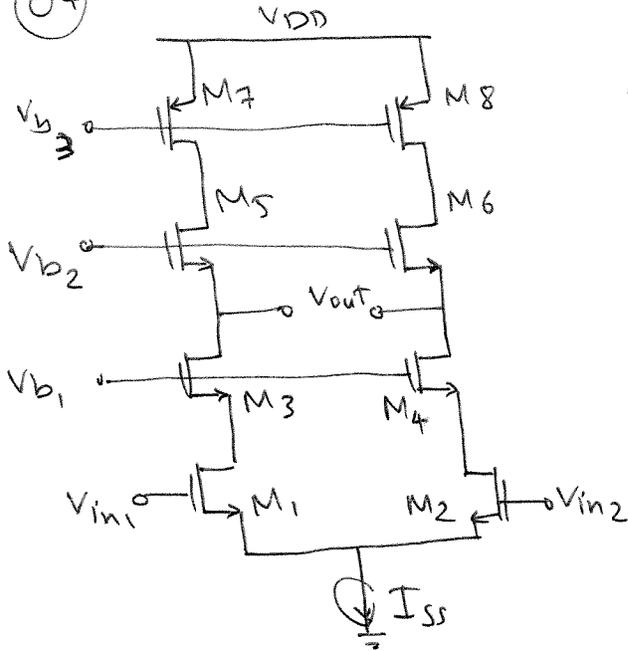

$$R_{o2} = g_{m3} r_{o3} r_{o1} + r_{o1} + r_{o3}$$

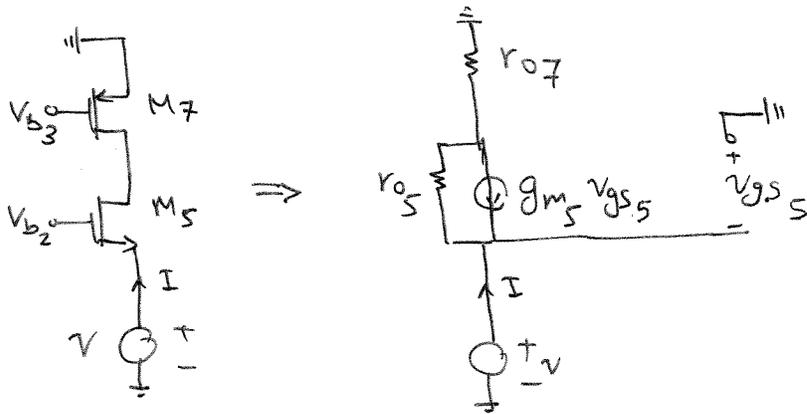To calculate  $R_{o1}$ , using the small signal model we have:






$$v_{gs5} = -v \rightarrow g_{m5} v_{gs5} = -g_{m5} v$$

From KVL: 
$$v = r_{o5} (I - g_{m5} v) + r_{o7} I$$

$$\rightarrow \frac{v}{I} = R_{o1} = \frac{r_{o5} + r_{o7}}{1 + g_{m5} r_{o5}} \Rightarrow A_v = -g_{m1} (R_{o1} \parallel R_{o2})$$


(65)

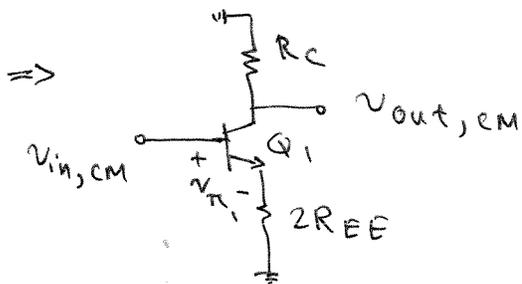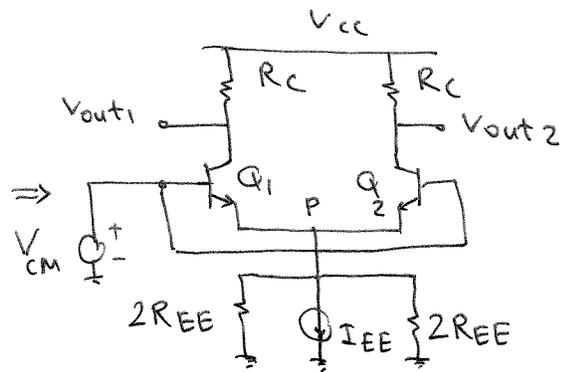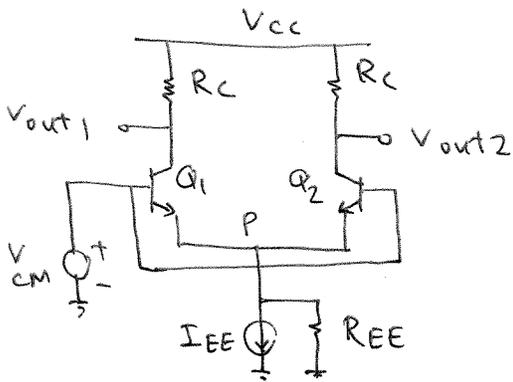

$$v_{out,cm} = -g_{m1} v_{\pi_1} R_c = -g_{m1} R_c \frac{\frac{1}{g_{m1}}}{\frac{1}{g_{m1}} + 2R_{EE}} v_{in,cm}$$

$$\Rightarrow \frac{v_{out,cm}}{v_{in,cm}} = -\frac{g_{m1} R_c}{1 + 2R_{EE} g_{m1}} = -\frac{\frac{R_c}{2}}{R_{EE} + \frac{1}{2g_{m1}}}$$

66

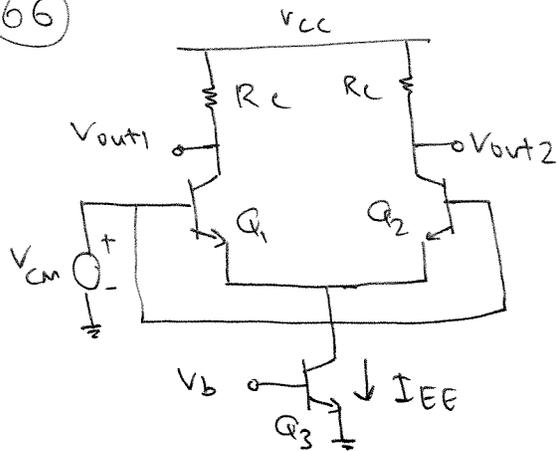


$$A_{cm} = \frac{\Delta V_{out, CM}}{\Delta V_{in, CM}} = \frac{R_c/2}{\frac{1}{2g_m} + r_{o3}} \Rightarrow$$


$$A_{cm} \leq 0.01 \Rightarrow \frac{R_c/2}{\frac{1}{2 \frac{I_{EE}}{2V_T}} + \frac{V_A}{I_{EE}}} < 0.01 \Rightarrow$$

$$\frac{R_c I_{EE}}{2(V_A + V_T)} < 0.01 \Rightarrow R_c I_{EE} < 0.02(V_A + V_T)$$

67

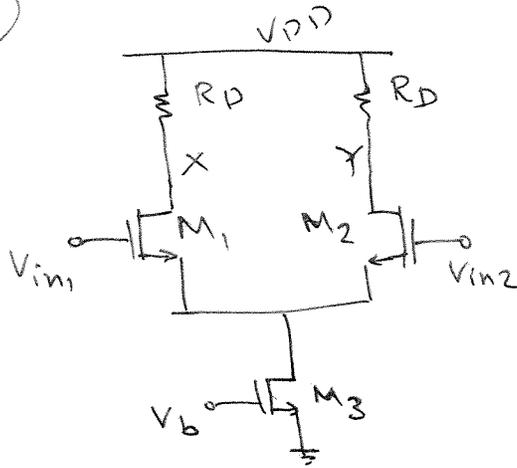

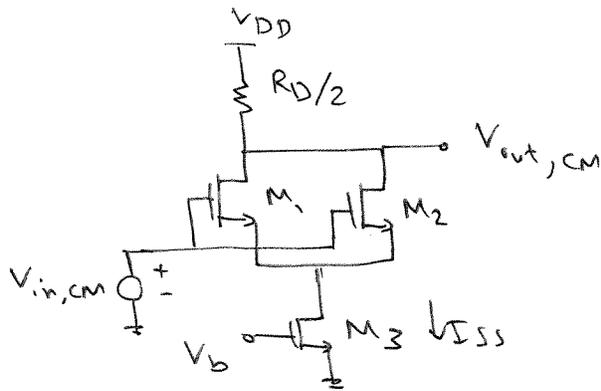The same value for the inputs common-mode leads to the following circuit:



$$g_{m1} = g_{m2} = \frac{2 I_{SS}/2}{(V_{GS} - V_{TH})_{eq}}$$


$$= \frac{I_{SS}}{(V_{GS} - V_{TH})_{eq}}$$

$$\frac{\Delta V_{out, CM}}{\Delta V_{in, CM}} = - \frac{R_D/2}{\frac{1}{2g_{m1}} + r_{o3}}$$

$$= \frac{- R_D}{\frac{1}{g_{m1}} + 2r_{o3}} = \frac{- R_D}{\frac{(V_{GS} - V_{TH})_{eq}}{I_{SS}} + \frac{2}{\lambda I_{SS}}} \Rightarrow$$

$$A_{CM} = - \frac{R_D I_{SS}}{\frac{2}{\lambda} + (V_{GS} - V_{TH})_{eq}}$$

(68)

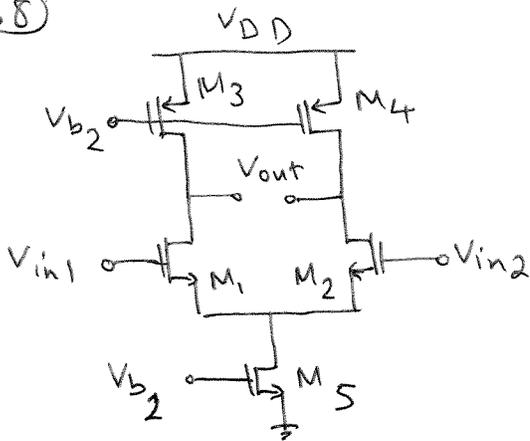


$$\lambda > 0, g_m r_o \gg 1$$

$$r_{o3} = r_{o4}$$

$$r_{o1} = r_{o2}$$

$$g_{m1} = g_{m2}$$

For the common mode input we have:

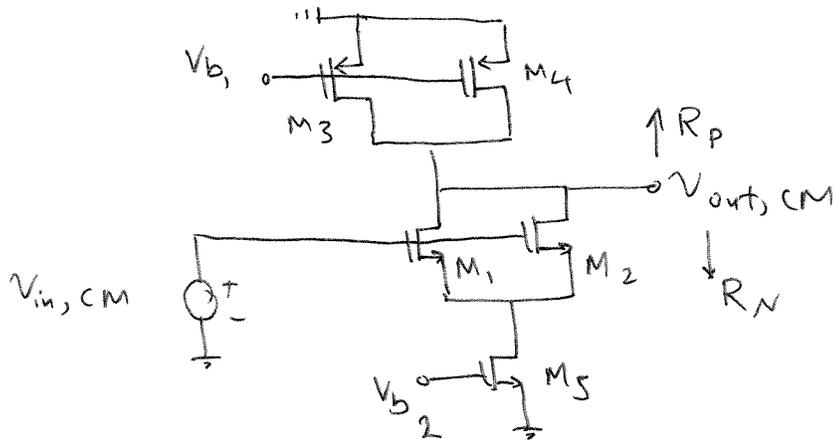


$$R_P = r_{o3} \parallel r_{o4} = \frac{r_{o3}}{2} = \frac{r_{o4}}{2}$$

$$R_N = r_{o5} + \frac{r_{o1}}{2} + 2g_{m1} \frac{r_{o1}}{2} r_{o5} =$$

$$g_{m1} r_{o1} r_{o5} + r_{o5} + \frac{r_{o1}}{2}$$

$$\frac{i_o}{v_{in,CM}} = G_m = \frac{2g_{m1} v_{gs1}}{v_{in,CM}} = 2g_{m1} \frac{\frac{1}{2g_{m1}}}{\frac{1}{2g_{m1}} + r_{o5}}$$
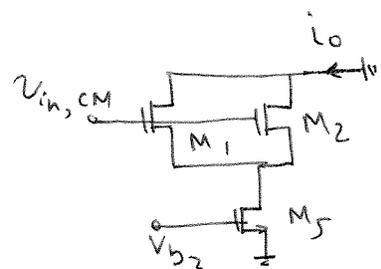
$$\rightarrow G_m = \frac{2g_{m1}}{1 + 2g_{m1} r_{o5}} \approx \frac{1}{r_{o5}}$$



$$\Rightarrow A_{CM} = -G_m R_o$$


$$R_o = R_P \parallel R_N = \frac{r_{o4}}{2} \parallel (g_{m1} r_{o1} r_{o5} + r_{o5} + \frac{r_{o1}}{2})$$

$$\approx \frac{r_{o4}}{2} \parallel g_{m1} r_{o1} r_{o5} \approx \frac{r_{o4}}{2}$$


$$\rightarrow A_{CM} = -\frac{1}{r_{o5}} \frac{r_{o4}}{2} = -\frac{r_{o4}}{2 r_{o5}}$$

(69)

(a)

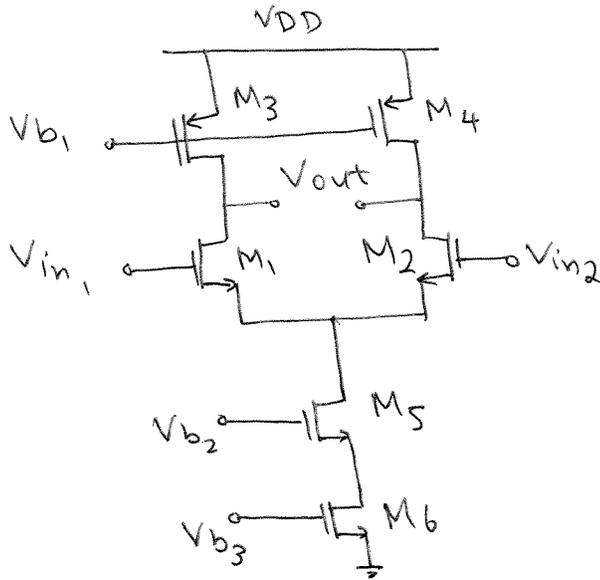

For the common mode input :

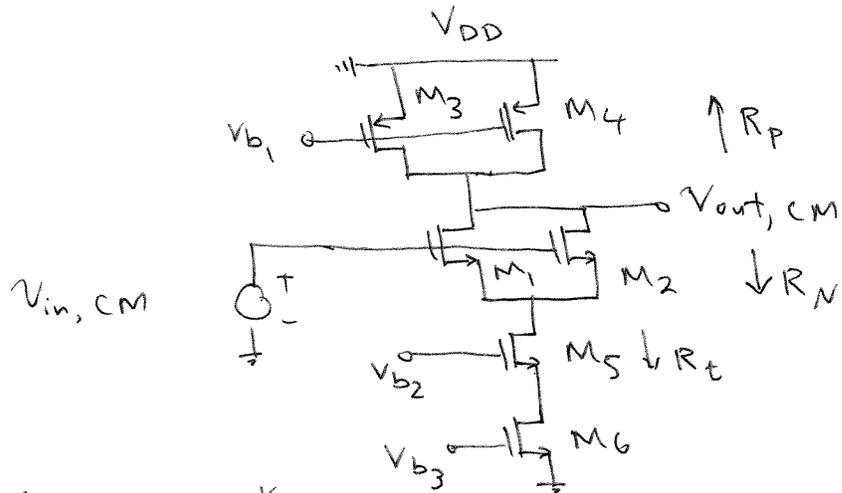

$$R_P = r_{o3} \parallel r_{o4} = \frac{r_{o3}}{2}$$

$$R_N = \frac{r_{o1}}{2} + R_t + 2g_{m1} \frac{r_{o1}}{2} R_t \approx g_{m1} r_{o1} R_t \approx$$


$$g_{m1} r_{o1} g_{m5} r_{o5} r_{o6}$$

$$R_{out} = R_P \parallel R_N = \frac{r_{o3}}{2} \parallel g_{m1} g_{m5} r_{o1} r_{o5} r_{o6} \approx \frac{r_{o3}}{2}$$

To calculate  $G_m$ :

$$G_m = \frac{i_o}{v_{in, CM}} = \frac{2g_{m1} v_{gs1}}{v_{in, CM}}$$
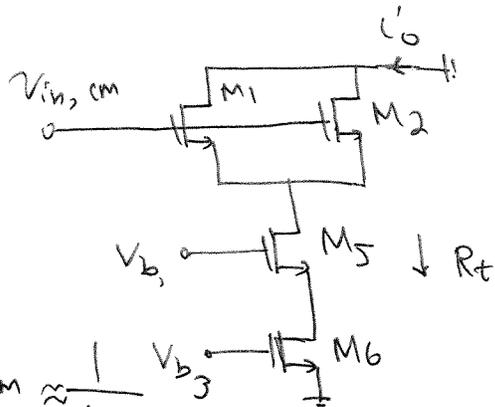
$$= \frac{2g_{m1}}{v_{in, CM}} \frac{\frac{1}{2g_{m1}}}{\frac{1}{2g_{m1}} + R_t} v_{in, CM} \approx \frac{1}{R_t} v_{in, CM}$$




$$\rightarrow A_{CM} = -G_m R_{out} = -\frac{r_{o3}}{2R_t} =$$

$$\frac{r_{o3}}{2g_{m5} r_{o5} r_{o6}}$$

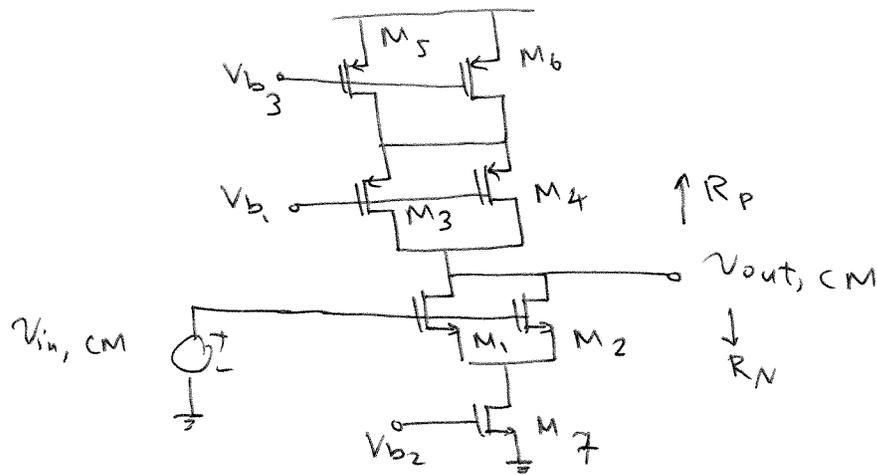(69) (b)

For the common mode input, the circuit is:




$$R_P = 2g_{m3} \frac{r_{o3}}{2} \frac{r_{o5}}{2} + \frac{r_{o3}}{2} + \frac{r_{o5}}{2} \approx \frac{g_{m3} r_{o3} r_{o5}}{2}$$

$$R_N = 2g_{m1} \frac{r_{o1}}{2} r_{o7} + \frac{r_{o1}}{2} + r_{o7} \approx g_{m1} r_{o1} r_{o7}$$

$$R_{out} = R_N \parallel R_P$$

To calculate  $G_m$ :

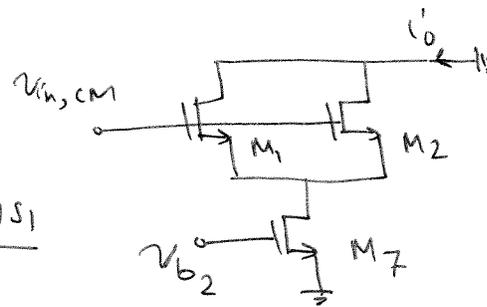


$$G_m = \frac{i'_o}{v_{in,CM}} = \frac{2g_{m1} v_{gs1}}{v_{in,CM}}$$

$$= \frac{2g_{m1}}{v_{in,CM}} \frac{\frac{1}{2g_{m1}} v_{in,CM}}{\frac{1}{2g_{m1}} + r_{o7}} \approx \frac{1}{r_{o7}}$$

$$\rightarrow A_{cm} = -G_m R_{out}$$

(70)


(a)

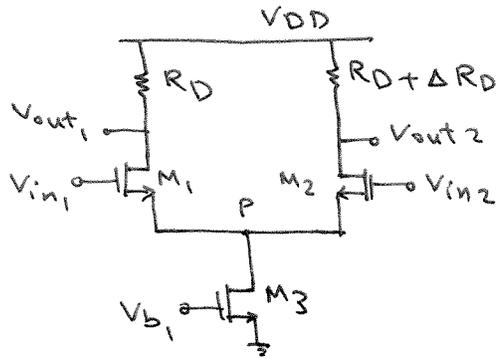

To calculate  $A_{DM}$ , using the half circuit:



To calculate  $A_{CM-DM}$  we have:

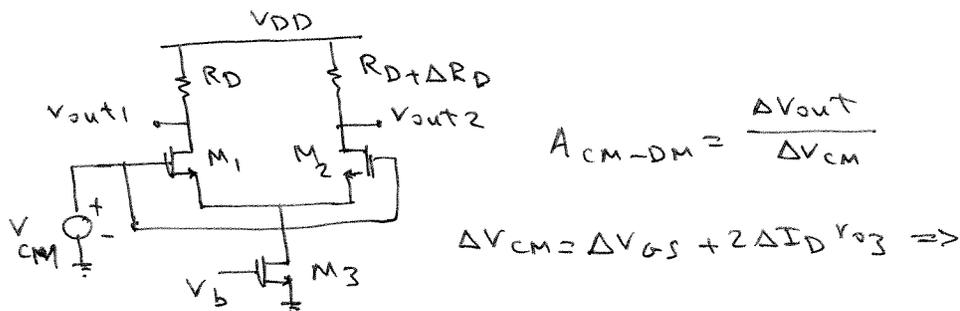


$$\Delta V_{cm} = \Delta I_D \left( \frac{1}{g_{m1}} + 2r_{o3} \right)$$

$$\Delta V_{out} = \Delta V_{out1} - \Delta V_{out2} = -\Delta R_D \Delta I_D \Rightarrow$$

$$A_{CM-DM} = - \frac{\Delta R_D}{\frac{1}{g_{m1}} + 2r_{o3}} \Rightarrow$$

$$CMRR = \frac{A_{DM}}{A_{CM-DM}} = \frac{g_{m1} R_D}{\frac{\Delta R_D}{\frac{1}{g_{m1}} + 2r_{o3}}} = (1 + 2g_{m1} r_{o3}) \frac{R_D}{\Delta R_D}$$

(70) (b)

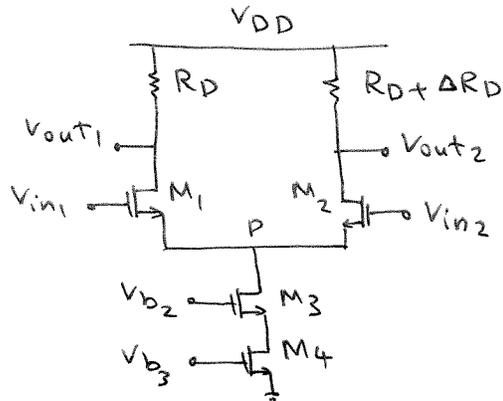

To calculate  $A_{DM}$ , using the half circuit, we have




Similar to part (a) we have:

$$A_{CM-DM} = - \frac{\Delta R_D}{\frac{1}{g_{m1}} + 2 [g_{m3} r_{o3} r_{o4} + r_{o3} + r_{o4}]}$$

$$\Rightarrow CMMR = \frac{A_{DM}}{A_{CM-DM}} = (1 + 2g_{m1} [g_{m3} r_{o3} r_{o4} + r_{o3} + r_{o4}]) \frac{R_D}{\Delta R_D}$$

Notice that CMMR of part (b) is much higher than the one for part (a).

71

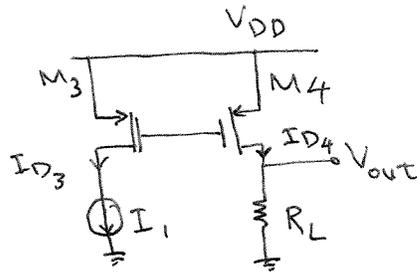


$$\left(\frac{W}{L}\right)_3 = N \left(\frac{W}{L}\right)_4$$

$$\left(\frac{W}{L}\right)_3 = N \left(\frac{W}{L}\right)_4 \Rightarrow I_{D3} = N I_{D4} \Rightarrow \underbrace{i_{d3} = N i_{d4}}_{\text{small signal}}$$

$$\left. \begin{array}{l} i_{d3} = i_1 \\ v_{out} = R_L i_{d4} = \frac{R_L}{N} i_{d3} = \frac{R_L}{N} i_1 \Rightarrow \end{array} \right\}$$

$$\frac{v_{out}}{i_1} = \frac{R_L}{N}$$

72

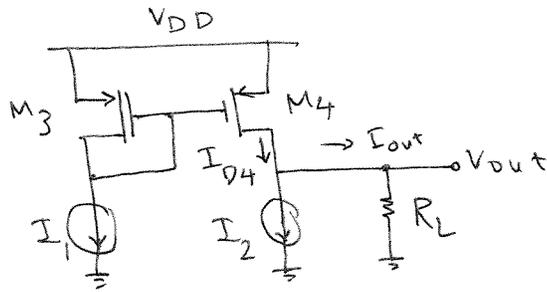

(a)  $\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4$   
 if  $I_1 = I_2 = I_0$   $\Rightarrow \begin{cases} V_{out} = I_{out} \times R_L = 0 & \text{because} \\ I_{out} = I_{D4} - I_2 = I_1 - I_2 = 0 \end{cases}$

if  $I_1 = I_0 + \Delta I \Rightarrow I_{D4} = I_{D3} = I_1 = I_0 + \Delta I$

$I_2 = I_0 - \Delta I \Rightarrow I_{out} = I_{D4} - I_2 = 2\Delta I$

$V_{out} = I_{out} R_L = 2 R_L \Delta I$

(b)  $\left(\frac{W}{L}\right)_3 = 2\left(\frac{W}{L}\right)_4$

$\Rightarrow I_{D3} = 2 I_{D4}$

if  $I_1 = I_2 = I_0$  then  $I_{D3} = I_1 = I_0 \Rightarrow I_{D4} = \frac{I_{D3}}{2}$

$\Rightarrow I_{D4} = \frac{I_0}{2} \Rightarrow I_{out} = I_{D4} - I_2 = -\frac{I_0}{2}$


$\Rightarrow V_{out} = R_L I_{out} = -\frac{R_L I_0}{2}$

if  $I_1 = I_0 + \Delta I \Rightarrow I_{D4} = \frac{I_{D3}}{2} = \frac{I_1}{2} = \frac{I_0 + \Delta I}{2}$

$I_2 = I_0 - \Delta I \Rightarrow I_{out} = I_{D4} - I_2 = -\frac{I_0}{2} + \frac{3\Delta I}{2}$

$\Rightarrow V_{out} = R_L I_{out} = +R_L \left(-\frac{I_0}{2} + \frac{3\Delta I}{2}\right)$

(73)

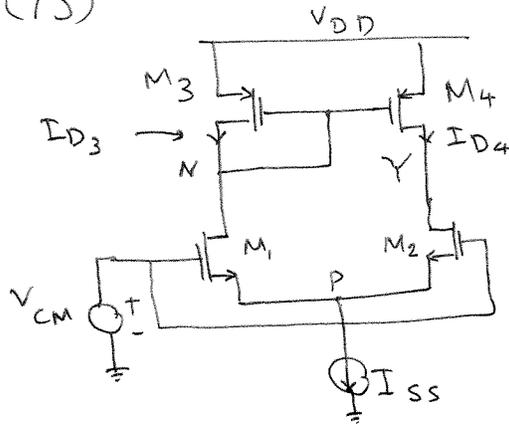

$$V_{TH3} = |V_{TH,P}|$$

$$(a) \quad I_{D3} = \frac{I_{SS}}{2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_3 (V_{SG3} - V_{TH})^2 \Rightarrow$$

$$V_{SG3} = V_{TH3} + \sqrt{\frac{I_{SS}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}}$$


$$V_N = V_{DD} - V_{SG3} = V_{DD} - V_{TH} - \sqrt{\frac{I_{SS}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}}$$

(b) Since the circuit is symmetric:

$$\begin{cases} I_{D3} = I_{D4} \\ V_{SG3} = V_{SG4} \end{cases} \Rightarrow V_{SD3} = V_{SD4} \Rightarrow V_Y = V_N$$

(c) if  $V_{DD}$  changes by a small amount  $\Delta V$ , both  $V_N$  and  $V_Y$  will change by  $\Delta V$ .

74

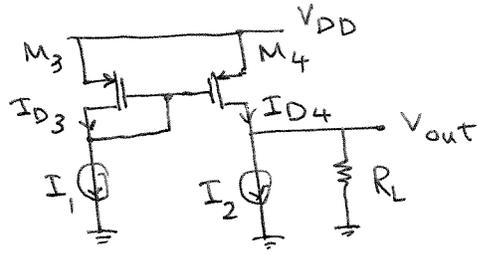


$$I_{D3} = I_{D4} = I_1$$

$$V_{out} = (I_{D4} - I_2) R_L = (I_1 - I_2) R_L$$

$$\begin{array}{l} \text{small} \\ \Rightarrow \\ \text{signal} \end{array} \frac{V_{out}}{i_1} = R_L, \quad \frac{V_{out}}{i_2} = -R_L$$

(75)

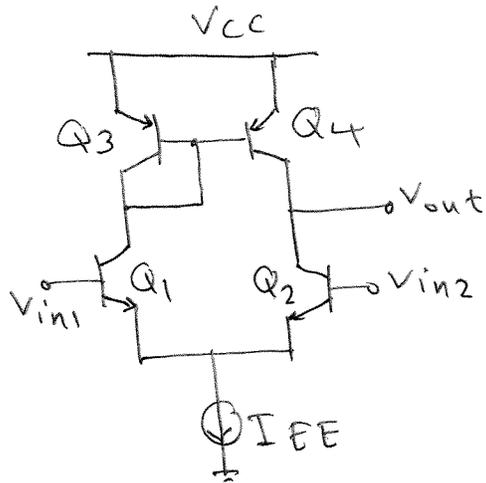

$$V_{A,n} = 5V$$


$$A_v = 100$$

$$\frac{v_{out}}{v_{in1} - v_{in2}} = g_{mN} (r_{oN} \parallel r_{oP}) =$$


$$\frac{I_{EE}/2}{V_T} \left( \frac{V_{A,n}}{I_{EE}/2} \parallel \frac{V_{A,p}}{I_{EE}/2} \right) = \frac{V_{A,n} V_{A,p}}{(V_{A,n} + V_{A,p}) V_T}$$

$$\Rightarrow 100 = \frac{5 V_{A,p}}{(5 + V_{A,p}) 0.026} \Rightarrow V_{A,p} = 5.417V$$

(76)

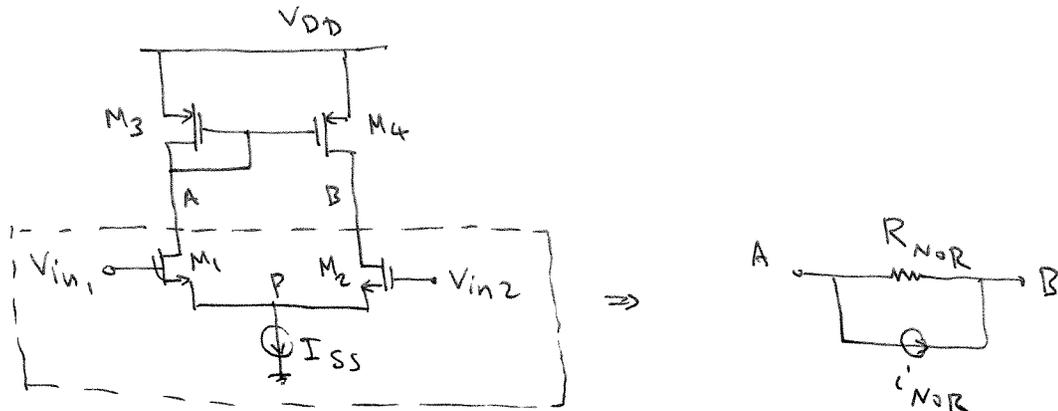

To calculate  $i_{NOR}$  we have:

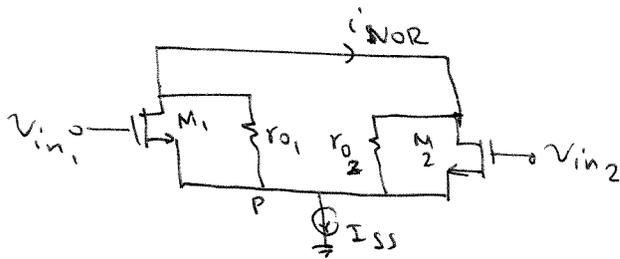


$$r_{o1} (i_{NOR} + g_{m1} v_{in1}) + r_{o2} (i_{NOR} - g_{m2} v_{in2}) = -I_{SS}$$

$$\rightarrow 2 r_{oN} i_{NOR} = -g_{m1} r_{o1} v_{in1} + g_{m2} r_{o2} v_{in2} \Rightarrow$$

$$i_{NOR} = -\frac{g_{mN}}{2} (v_{in1} - v_{in2})$$

To calculate  $R_{NOR}$ :

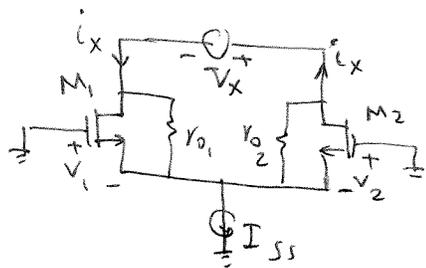


$$v_1 = v_2$$

$$(i_x - g_{m1} v_1) r_{o1} + (i_x + g_{m2} v_2) r_{o2} = v_x$$

$$\Rightarrow R_{NOR} = \frac{v_x}{i_x} = 2 r_{oN}$$

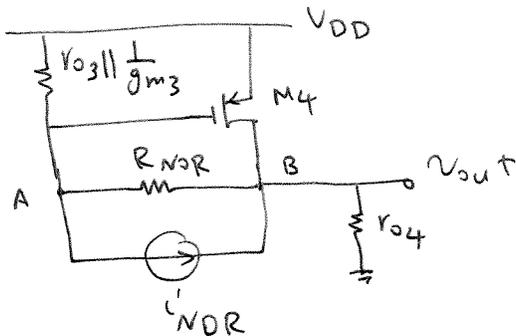Therefore, utilizing the Norton model we have:



$$\begin{cases} \frac{V_A - V_B}{R_{NOR}} + \frac{V_A}{r_{o3} \parallel \frac{1}{g_{m3}}} + i_{NOR} = 0 \Rightarrow V_A = \frac{\frac{V_B}{R_{NOR}} - i_{NOR}}{\frac{1}{R_{NOR}} + \frac{1}{r_{o3} \parallel \frac{1}{g_{m3}}}} \\ \frac{V_B - V_A}{R_{NOR}} + \frac{V_B}{r_{o4}} - i_{NOR} + g_{m4} V_A = 0, V_B = v_{out} \end{cases}$$

$$\Rightarrow v_{out} \left( \frac{1}{R_{NOR}} + \frac{1}{r_{o4}} \right) + \left( g_{m4} - \frac{1}{R_{NOR}} \right) \frac{\frac{v_{out}}{R_{NOR}} - i_{NOR}}{\frac{1}{R_{NOR}} + \frac{1}{r_{o3} \parallel \frac{1}{g_{m3}}}} = i_{NOR}$$

$\frac{1}{g_{m3}} \ll r_{o3}, \frac{1}{g_{m3}} \ll R_{NOR}, g_{m3} = g_{m4} = g_m, r_{o3} = r_{o4} = r_{op}$


$$\Rightarrow v_{out} \left( \frac{1}{R_{NOR}} + \frac{1}{r_{op}} \right) + g_{m4} \frac{\frac{v_{out}}{R_{NOR}} - i_{NOR}}{g_{m3}} = i_{NOR}$$

$$\Rightarrow v_{out} \left( \frac{1}{R_{NOR}} + \frac{1}{r_{op}} \right) + \frac{v_{out}}{R_{NOR}} = 2 i_{NOR} \Rightarrow$$

$$\frac{2 v_{out}}{R_{NOR}} + \frac{v_{out}}{r_{op}} = 2 i_{NOR} \Rightarrow v_{out} \left( \frac{1}{r_{on}} + \frac{1}{r_{op}} \right) = -g_{mN} (v_{in1} - v_{in2})$$

$$\Rightarrow \frac{v_{out}}{v_{in1} - v_{in2}} = -g_{mN} (r_{on} \parallel r_{op})$$


77

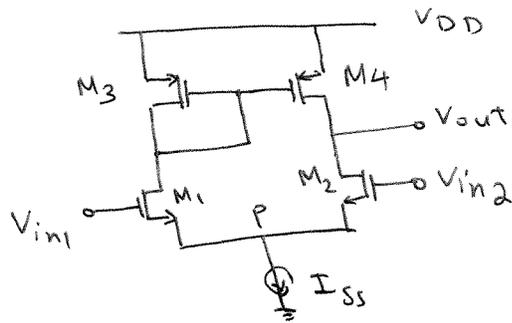

$$g_m r_o \gg 1$$


$$g_{m1} = g_{m2}$$

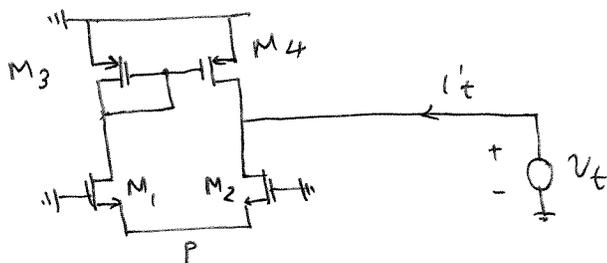To calculate the output impedance we have the following circuit:



$$R_{out} = \frac{v_t}{i_t}$$

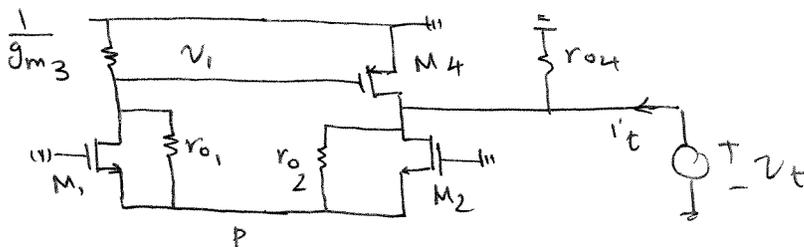↓ neglecting  $r_{o3}$  ( $r_{o3} \gg \frac{1}{g_{m3}}$ )




writing node equations of  $v_i$  and  $v_p$ :

$$\begin{cases} g_{m3} v_i + \frac{v_i - v_p}{r_{o1}} - g_{m1} v_p = 0 \\ 2g_{m1} v_p + \frac{v_p - v_i}{r_{o1}} + \frac{v_p - v_t}{r_{o2}} = 0 \end{cases} \xrightarrow{g_m r_o \gg 1} \begin{cases} g_{m3} v_i \approx g_{m1} v_p \\ 2g_{m1} v_p \approx 0 \end{cases}$$

$$\Rightarrow v_p \approx v_i = 0 \Rightarrow R_{out} = \frac{v_t}{i_t} = r_{o4} \parallel r_{o2} = r_{oN} \parallel r_{oP}$$

78


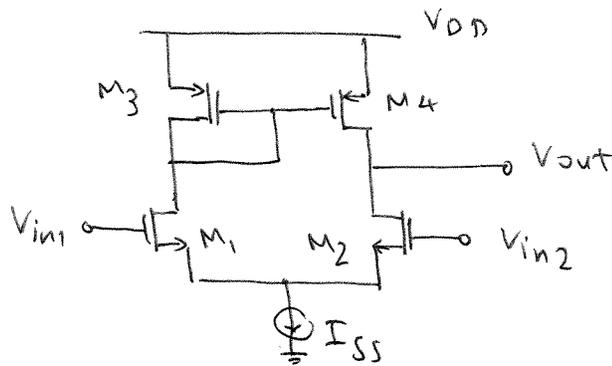


$$g_m r_o \gg 1$$

$$g_{m1} = g_{m2}$$

$$g_{m3} = g_{m4}$$

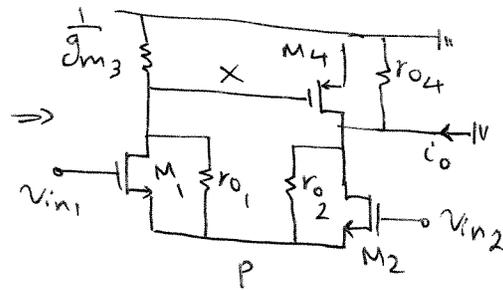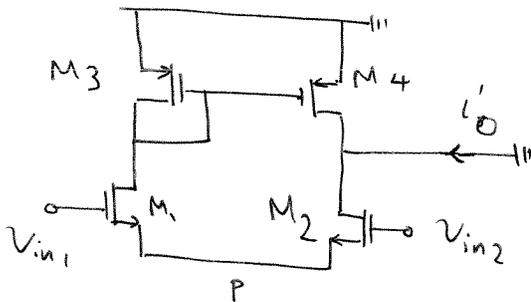To calculate  $G_m$  we have from small signal model:



writing node equations of nodes P and X we have:

$$\begin{cases} g_{m1}(v_p - v_{in1}) + g_{m2}(v_p - v_{in2}) + \frac{v_p - v_x}{r_{o1}} + \frac{v_p}{r_{o2}} = 0 \\ g_{m3} v_x + g_{m1}(v_{in1} - v_p) + \frac{v_x - v_p}{r_{o1}} = 0 \end{cases}$$

Since  $g_m r_o \gg 1$  we have

$$\begin{cases} g_{m1}(v_p - v_{in1}) + g_{m2}(v_p - v_{in2}) = 0 \Rightarrow v_p = \frac{v_{in1} + v_{in2}}{2} \\ v_x = -\frac{g_{m1}}{g_{m3}}(v_{in1} - v_p) = -\frac{g_{m1}}{g_{m3}}\left(\frac{v_{in1} - v_{in2}}{2}\right) \end{cases}$$

$$i_o = -\frac{v_p}{r_{o2}} + g_{m2}(v_{in2} - v_p) - g_{m4}(-v_x)$$

$$\Rightarrow i_o \approx -g_{m4}(-v_x) + g_{m2} \left( v_{in2} - \frac{v_{in1} + v_{in2}}{2} \right)$$


$$= - \left[ g_{m4} \frac{g_{m1}}{g_{m3}} \left( \frac{v_{in1} - v_{in2}}{2} \right) + g_{m2} \left( \frac{v_{in1} - v_{in2}}{2} \right) \right]$$

$$= -g_{m1} (v_{in1} - v_{in2})$$

$$G_m = \frac{i_o}{v_{in1} - v_{in2}} = -g_{m1} = -g_{mN}$$

$$\rightarrow A_v = -G_m R_{out} = g_{mN} (r_{oN} \parallel r_{op})$$

79

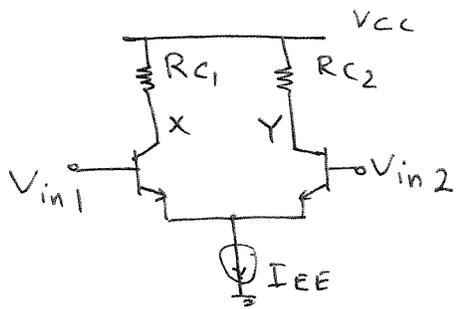


$$\begin{aligned}A_v &= 10, \\ P &= 2 \text{ mW} \\ V_{CC} &= 2.5 \text{ V} \\ V_A &= \infty\end{aligned}$$

$$P = V_{CC} I_{EE} \Rightarrow 2 \times 10^{-3} = 2.5 I_{EE} \Rightarrow I_{EE} = 0.8 \text{ mA}$$

$$A_v = \frac{v_{XY}}{v_{in1} - v_{in2}} = -g_m R_C = -\frac{I_{EE}/2}{V_T} R_C$$

$$\Rightarrow 10 = \frac{0.4 \times 10^{-3}}{0.026} R_C \Rightarrow R_C = 650 \Omega$$

(80)

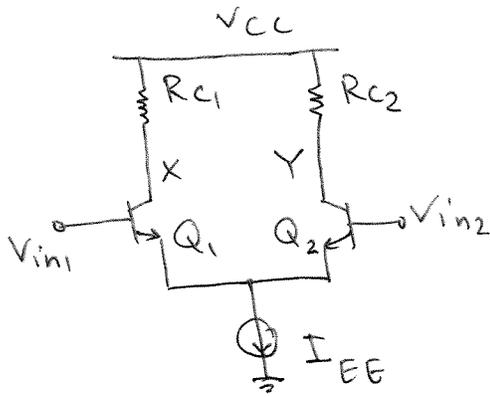

$$V_{in, CM} = 1.2 \text{ V}$$

$$P = 3 \text{ mW}$$

$$V_{CC} = 2.5 \text{ V}$$

$$P = I_{EE} V_{CC} \Rightarrow 3 \times 10^{-3} = 2.5 I_{EE} \Rightarrow I_{EE} = 1.2 \text{ mA}$$

$$A_v = -g_{m1} R_C = -\frac{I_{EE}/2}{V_T} R_C = -\frac{R_C I_{EE}}{2 V_T}$$


To maximize gain,  $R_C I_{EE}$  and therefore  $R_C$  should be maximum. However, the upper bound of  $R_C$  value is limited by the voltage value of  $X$ . because:

$$V_{in, CM} \leq V_X \Rightarrow 1.2 \leq V_{CC} - R_C I_{EE}/2 \Rightarrow$$

$$R_C \leq 2 \frac{V_{CC} - 1.2}{I_{EE}} \Rightarrow R_C \leq 2 \frac{2.5 - 1.2}{1.2 \times 10^{-3}} \Rightarrow$$

$$R_C \leq 2.167 \text{ k}\Omega \Rightarrow R_C = 2.167 \text{ k}\Omega$$

81

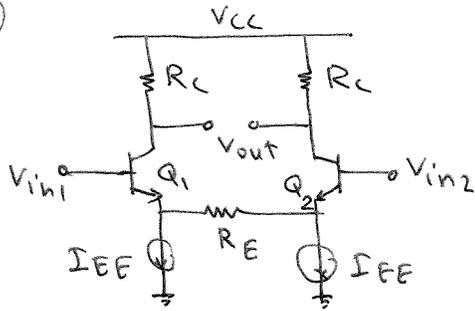


$$A_v = 5$$

$$P = 4 \text{ mW}$$

$$V_{CC} = 2.5 \text{ V}$$

$$V_A = \infty$$

The half circuit is:

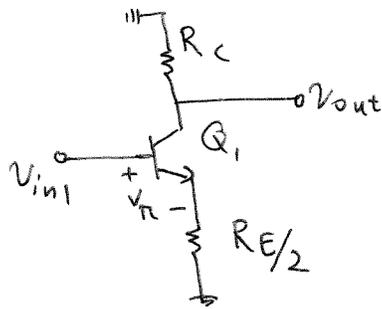

$$A_v = \frac{v_{out}}{v_{in1}} \approx \frac{-g_{m1} v_{\pi} R_C}{v_{in1}} = -\frac{g_{m1} R_C}{\frac{1}{g_{m1}} + \frac{R_E}{2}} v_{in1}$$

$$= -\frac{R_C}{\frac{R_E}{2} + \frac{1}{g_{m1}}}$$

$$P = 4 \text{ mW} = 2 I_{EE} V_{CC} = 5 I_{EE} \Rightarrow I_{EE} = 0.8 \text{ mA}$$

$$g_m = \frac{I_{EE}}{V_T} = 0.03077$$

$$A_v = 5 \Rightarrow \frac{R_C}{\frac{R_E}{2} + 32.5} = 5 \quad (1)$$

if  $I_{EE}$  increases by 10%, the gain will be:

$$A_v = \frac{R_C}{\frac{R_E}{2} + \frac{32.5}{1.1}} \Rightarrow 5 < \frac{R_C}{\frac{R_E}{2} + \frac{32.5}{1.1}} < 5 \times 1.02 \quad (2)$$

if  $I_{EE}$  decreases by 10% then:

$$5 \times 0.98 < \frac{R_C}{\frac{R_E}{2} + \frac{32.5}{0.9}} < 5 \quad (3)$$

The worse case is:

$$\left\{ \begin{array}{l} \frac{R_C}{\frac{R_E}{2} + \frac{32.5}{1.1}} = 5 \times 1.02 \quad (4) \\ \frac{R_C}{\frac{R_E}{2} + \frac{32.5}{0.9}} = 5 \times 0.98 \quad (5) \end{array} \right.$$


dividing (4) and (5) to (1) leads to:

$$\left\{ \begin{array}{l} \frac{\frac{R_E}{2} + 32.5}{\frac{R_E}{2} + \frac{32.5}{1.1}} = 1.02 \Rightarrow R_E = 236.36 \Omega \\ \frac{\frac{R_E}{2} + 32.5}{\frac{R_E}{2} + \frac{32.5}{0.9}} = 0.98 \Rightarrow R_E = 288.89 \Omega \end{array} \right.$$

To ensure less than 2% gain variation for 10% current variation  $R_E = 288.89 \Omega$

$$\text{From (1)} \quad R_C = 5 \left( \frac{R_E}{2} + 32.5 \right) = 884.72 \Omega$$

(82)

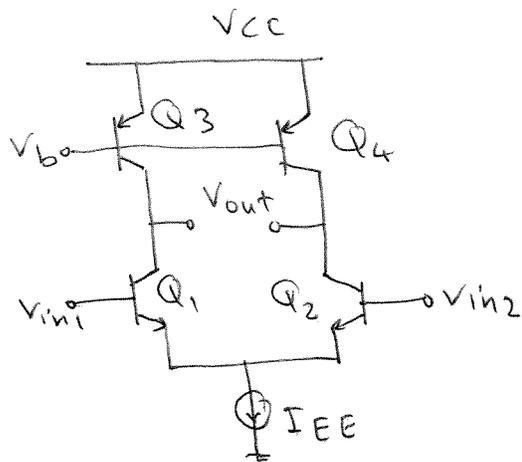

$$A_v = 100$$

$$P = 1 \text{ mW}$$

$$V_{A, n} = 6$$

$$V_{CC} = 2.5 \text{ V}$$

$$P = 1 \text{ mW} = I_{EE} V_{CC} \Rightarrow I_{EE} = \frac{10^{-3}}{2.5} = 0.4 \text{ mA}$$


$$r_{oN} = \frac{V_{A, n}}{I_{EE}/2} = \frac{6}{0.2 \times 10^{-3}} = 30 \text{ k}\Omega, \quad g_{mN} = \frac{I_{EE}/2}{V_T} = \frac{0.2}{26} \text{ S}$$

$$A_v = -g_{mN} (r_{oN} \parallel r_{op}) \Rightarrow$$

$$100 = \frac{0.2}{26} (30 \times 10^3 \parallel r_{op}) \Rightarrow r_{op} = 22.94 \text{ k}\Omega$$


$$\Rightarrow V_{A, P} = r_{op} \frac{I_{EE}}{2} = 4.588 \text{ V}$$

83

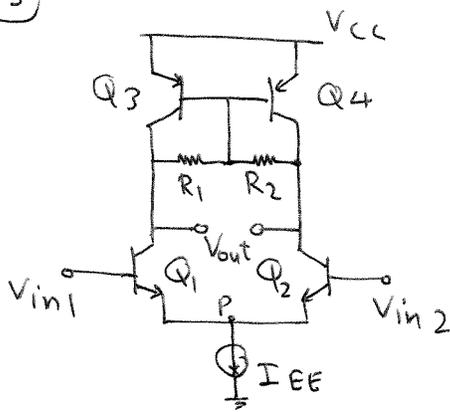

$$\begin{aligned}
 A_v &= 50 \\
 P &= 1 \text{ mW} \\
 V_{A,n} &= 10 \text{ V} \\
 V_{A,p} &= 5 \text{ V} \\
 V_{CC} &= 2.5 \text{ V} \\
 R_1 &= R_2
 \end{aligned}$$

The half circuit is:

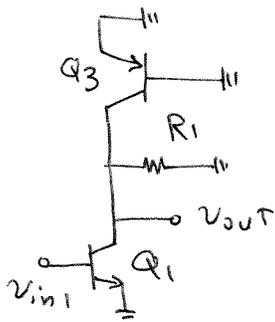

$$A_v = -g_{m_1} (R_1 \parallel r_{o_1} \parallel r_{o_3})$$

$$g_{m_1} = \frac{I_{EE}}{2V_T} \quad r_{o_1} = \frac{2V_{A,n}}{I_{EE}} \quad r_{o_3} = \frac{2V_{A,p}}{I_{EE}}$$

$$\Rightarrow 50 = \frac{1}{2V_T} \left( (R_1 I_{EE}) \parallel \underbrace{(2V_{A,n})}_{20} \parallel \underbrace{(2V_{A,p})}_{10} \right) \Rightarrow$$


$$R_1 I_{EE} = 4.262$$

$$P = 1 \text{ mW} = I_{EE} V_{CC} \Rightarrow I_{EE} = \frac{10^{-3}}{2.5} = 0.4 \text{ mA}$$

$$\rightarrow R_1 = \frac{4.262}{I_{EE}} = 10.655 \text{ k}\Omega$$

Notice that larger value of  $R_1$ , requires smaller  $I_{EE}$  and saves power.

84

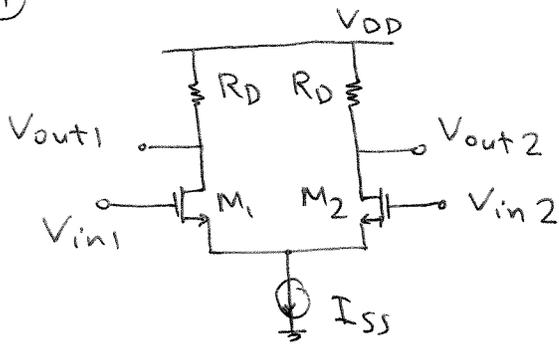

$$\Delta V_{in, \max} = 0.3 \text{ V}$$

$$P = 3 \text{ mW}$$

$$R_D = 500 \Omega$$

$$\lambda = 0, \mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$$

$$V_{DD} = 1.8 \text{ V}$$


$$P = V_{DD} I_{SS} \Rightarrow 3 \times 10^{-3} = 1.8 I_{SS} \Rightarrow$$

$$I_{SS} = 1.67 \text{ mA}$$

$$\Delta V_{in, \max} = \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow$$

$$0.3 = \sqrt{\frac{2 \times 1.67 \times 10^{-3}}{10^{-4} \times \frac{W}{L}}} \Rightarrow \frac{W}{L} = 370.37$$

(85)

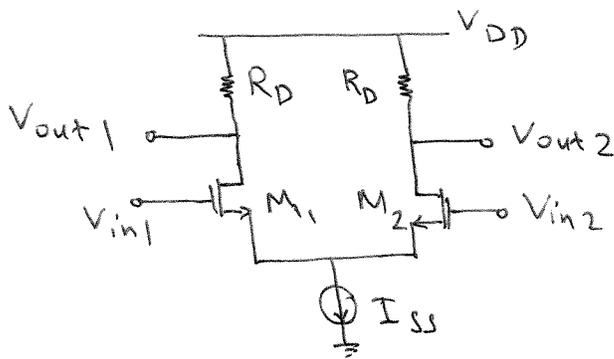

$$\begin{aligned} P &= 2 \text{ mW} \\ \text{overdrive} &= 100 \text{ mV} \\ V_{CM} &= 1 \text{ V} \\ \lambda &= 0, \mu_n C_{ox} = 100 \mu\text{A/V}^2 \\ V_{DD} &= 1.8 \text{ V} \\ V_{TH,n} &= 0.5 \end{aligned}$$

$$P = I_{SS} V_{DD} \Rightarrow 2 \times 10^{-3} = 1.8 I_{SS} \Rightarrow I_{SS} = 1.11 \text{ mA}$$

$$V_{GS1} - V_{TH} = \sqrt{\frac{2 I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow$$

$$0.1^2 = \frac{1.11 \times 10^{-3}}{10^{-4} \times \frac{W}{L}} \Rightarrow \frac{W}{L} = 1111.11$$

$$g_m = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} = \sqrt{10^{-4} \times 1111.11 \times 1.11 \times 10^{-3}} = 0.011$$

To place the transistor at the edge of triode region:


$$V_{in,CM} = V_{out1} + V_{TH,n}$$

$$1 = V_{DD} - R_D \frac{I_{SS}}{2} + 0.5 \Rightarrow$$

$$1 = 1.8 - R_D \frac{1.11 \times 10^{-3}}{2} + 0.5 \Rightarrow R_D = 2.34 \text{ k}\Omega$$

$$A_V = -g_m R_D = -25.74$$

86

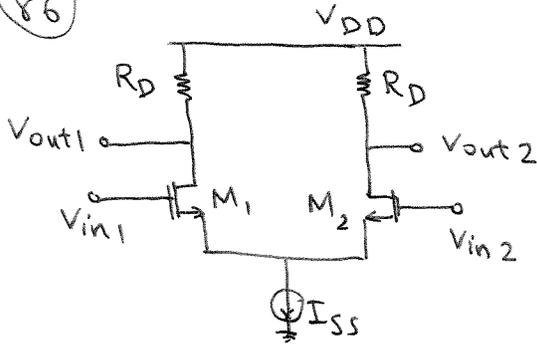

$$A_v = 5$$

$$P = 1 \text{ mW}$$

$$(V_{GS} - V_{TH})_{\text{equil}} = 150 \text{ mV}$$

$$\lambda = 0, \mu_n C_{ox} = 100 \mu\text{A/V}^2$$

$$V_{DD} = 1.8 \text{ V}$$

$$P = 1 \text{ mW} = V_{DD} I_{SS} = 1.8 I_{SS} \Rightarrow I_{SS} = 0.556 \text{ mA}$$

$$g_{m1} = \frac{2 I_{D1}}{(V_{GS} - V_{TH})_{\text{equil}}} = \frac{I_{SS}}{(V_{GS} - V_{TH})_{\text{equil}}} = \frac{0.556 \times 10^{-3}}{0.15}$$


$$= 3.704 \text{ mS}$$

$$A_v = -g_{m1} R_D \Rightarrow 5 = 3.704 \times 10^{-3} \times R_D \Rightarrow R_D = 1.35 \text{ k}\Omega$$

$$(V_{GS} - V_{TH})_{\text{equil}} = \sqrt{\frac{2 I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow$$

$$0.15 = \sqrt{\frac{0.556 \times 10^{-3}}{10^{-4} \times \frac{W}{L}}} \Rightarrow \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 246.91$$

(87)

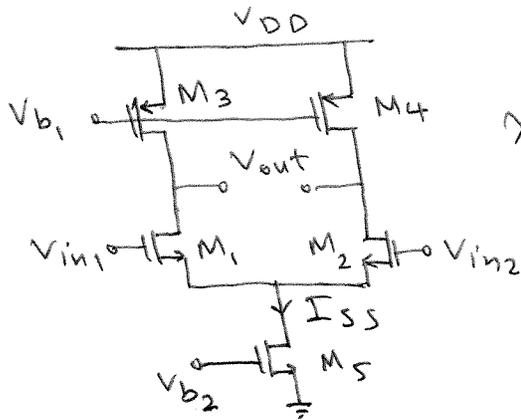

$$A_V = 40$$

$$(V_{GS} - V_{TH})_{equil} = ?$$

$$\lambda_n = 0.1 \text{ V}^{-1} \quad \lambda_p = 0.2 \text{ V}^{-1}$$

$$\mu_n C_{ox} = 100 \text{ MA/V}^2$$

$$\mu_p C_{ox} = 50 \text{ MA/V}^2$$

$$V_{DD} = 1.8$$

$$P = 2 \text{ mW}$$

$$A_V = -g_{m_N} (r_{op} \parallel r_{oN}) = -\frac{I_{SS}}{(V_{GS_1} - V_{TH})_{equil}} \left( \frac{1}{\frac{I_{SS} \lambda_n}{2}} \parallel \frac{1}{\frac{I_{SS} \lambda_p}{2}} \right)$$

$$= -\frac{2}{(V_{GS_1} - V_{TH})_{equil}} \left( \frac{1}{\lambda_n} \parallel \frac{1}{\lambda_p} \right) \Rightarrow$$

$$\frac{2}{(V_{GS_1} - V_{TH})_{equil}} (10 \parallel 5) = 40 \Rightarrow (V_{GS_1} - V_{TH})_{equil} = 166.67 \text{ mV}$$


$$P = 2 \times 10^{-3} = V_{DD} I_{SS} \Rightarrow I_{SS} = \frac{2 \times 10^{-3}}{1.8} = 1.11 \text{ mA}$$

$$\left( \frac{W}{L} \right)_{1,2} = \frac{I_{SS}}{\mu_n C_{ox} (V_{GS_1} - V_{TH})_{equil}^2} = \frac{1.11 \times 10^{-3}}{10^{-4} \times (0.16667)^2} = 400$$

$$\left( \frac{W}{L} \right)_{3,4} = \frac{I_{SS}}{\mu_p C_{ox} (V_{GS} - V_{TH})_{equil}^2} = \frac{1.11 \times 10^{-3}}{0.5 \times 10^{-4} \times (0.16667)^2} = 800$$

$$\left( \frac{W}{L} \right)_5 = \frac{2 I_{SS}}{\mu_n C_{ox} (V_{GS} - V_{TH})_{equil}^2} = \frac{2 \times 1.11 \times 10^{-3}}{10^{-4} \times (0.16667)^2} = 800$$

(88)

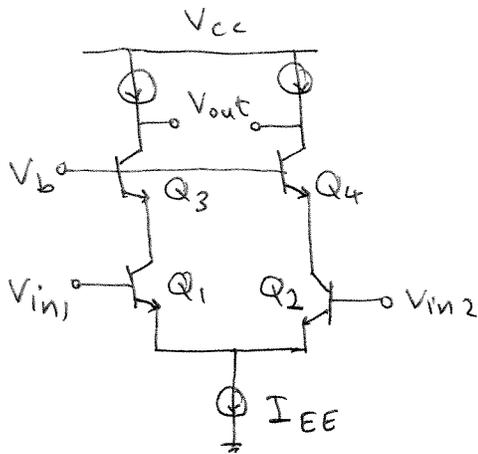

$$A_v = 4000$$

$$\beta = 100$$

$$V_{CC} = 2.5 \text{ V}$$

$$P = 1 \text{ mW}$$

$$P = I_{EE} V_{CC} = 10^{-3} \Rightarrow I_{EE} = \frac{10^{-3}}{2.5} = 0.4 \text{ mA}$$

$$g_{m_{1-4}} = \frac{I_{EE}}{2V_T} = \frac{0.2}{26} = 7.692 \text{ mS}$$

$$r_{\pi_{1-4}} = \frac{\beta}{g_{m_i}} = 13 \text{ k}\Omega$$


$$r_{o_{1-4}} = \frac{V_A}{\frac{I_{EE}}{2}} = 5 \times 10^3 \text{ V}_A$$

$$A_v = -g_{m_1} [g_{m_3} (r_{o_1} \parallel r_{\pi_3}) r_{o_3} + (r_{o_1} \parallel r_{\pi_3}) + r_{o_3}] \Rightarrow$$

$$4000 = \frac{0.2}{26} \left[ \frac{0.2}{26} (5 \times 10^3 \text{ V}_A \parallel 13 \times 10^3) 5 \times 10^3 \text{ V}_A + (5 \times 10^3 \text{ V}_A) \parallel 13 \times 10^3 + 5 \times 10^3 \text{ V}_A \right]$$

$$\Rightarrow V_A = 2.197$$

(89)

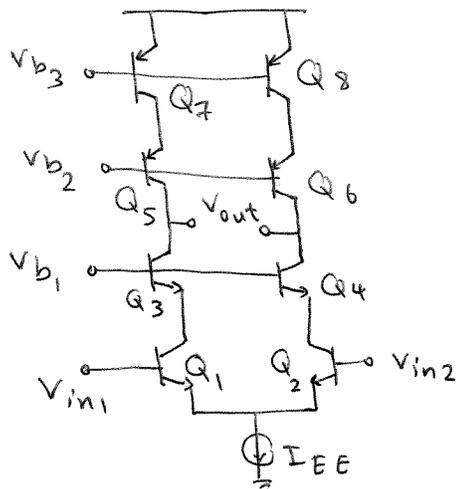

$$A_v = 2000$$

$$\beta_n = 100$$

$$\beta_p = 50$$

$$V_{A,n} = 5V$$

$$V_{CC} = 2.5V$$

$$P = 2mW$$

$$P = I_{EE} V_{CC} = 2 \times 10^{-3} \Rightarrow I_{EE} = \frac{2 \times 10^{-3}}{2.5} = 0.8mA$$

$$g_{m_{1-8}} = \frac{I_{EE}}{2V_T} = \frac{0.4}{26} = 0.0154 \Rightarrow$$

$$r_{\pi_{1-4}} = \frac{\beta_n}{g_{m_1}} = 6.5k\Omega \quad r_{\pi_{5-8}} = \frac{\beta_p}{g_{m_5}} = 3.25k\Omega$$


$$r_{o_{1-4}} = \frac{V_{A,n}}{I_{EE}/2} = 12.5k\Omega \quad r_{o_{5-8}} = \frac{V_{A,p}}{I_{EE}/2}$$

$$A_v \approx -g_{m_1} \left[ g_{m_3} r_{o_3} (r_{o_1} \parallel r_{\pi_3}) \right] \parallel \left[ g_{m_5} r_{o_5} (r_{o_7} \parallel r_{\pi_5}) \right]$$

$$\Rightarrow \frac{0.4}{26} \left[ \frac{0.4}{26} \times 12.5 \times 10^3 (12.5 \times 10^3 \parallel 6.5 \times 10^3) \right] \parallel \left[ \frac{0.4}{26} \frac{V_{A,p}}{I_{EE}/2} \left( \frac{V_{A,p}}{I_{EE}/2} \parallel 3250 \right) \right] = 2000$$

$$\Rightarrow V_{A,p} = 2.027V$$

(90)

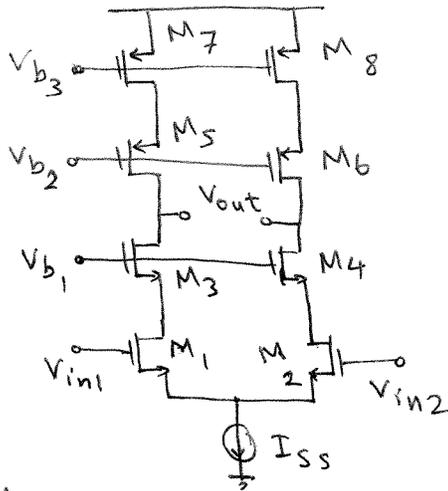

$$A_v = 600$$

$$P = 4 \text{ mW}$$

$$(V_{GS} - V_{TH})_{NMOS} = 100 \text{ mV}$$

$$(V_{GS} - V_{TH})_{PMOS} = 150 \text{ mV}$$

$$\mu_n C_{ox} = 100 \text{ } \mu\text{A/V}^2$$

$$\mu_p C_{ox} = 50 \text{ } \mu\text{A/V}^2$$

$$\lambda_n = 0.1 \text{ V}^{-1}$$

$$A_v \approx -g_{m1} [(g_{m3} r_{o3} r_{o1}) \parallel (g_{m5} r_{o5} r_{o7})] = -600$$

$$P = 4 \text{ mW} = I_{SS} V_{DD} \Rightarrow I_{SS} = \frac{4 \times 10^{-3}}{1.8} = 2.22 \text{ mA}$$

$$g_{m_{1-4}} = \frac{2I_{D1}}{(V_{GS} - V_{TH})_{NMOS}} = \frac{I_{SS}}{(V_{GS} - V_{TH})_{NMOS}} = \frac{2.22 \times 10^{-3}}{0.1} = 22.22 \text{ mS}$$

$$g_{m_{5-8}} = \frac{2I_{D5}}{(V_{GS} - V_{TH})_{PMOS}} = \frac{I_{SS}}{(V_{GS} - V_{TH})_{PMOS}} = \frac{2.22 \times 10^{-3}}{0.15} = 14.815 \text{ mS}$$

$$r_{o_{1-4}} = \frac{1}{\lambda_n \frac{I_{SS}}{2}} = \frac{1}{0.1 \times \frac{2.22}{2} \times 10^{-3}} = 9 \text{ k}\Omega$$

$$r_{o_{5-8}} = \frac{1}{\lambda_p \frac{I_{SS}}{2}} = \frac{1}{\lambda_p \times \frac{2.22 \times 10^{-3}}{2}} = \frac{0.9 \times 10^3}{\lambda_p}$$

in  $A_v$   
 $\Rightarrow$  equation


$$22.22 \times 10^{-3} \left[ (22.22 \times 10^{-3} \times 81 \times 10^6) \parallel (14.815 \times 10^{-3} \times \frac{0.81 \times 10^6}{\lambda_p^2}) \right] = 600 \Rightarrow$$

$$\lambda_p = 0.66 \text{ V}^{-1}$$

$$\left(\frac{W}{L}\right)_{NMOS} = I_{SS} / (\mu_n C_{ox} (V_{GS} - V_{TH})_{NMOS}^2) = 2222.2$$

$$\left(\frac{W}{L}\right)_{PMOS} = I_{SS} / (\mu_p C_{ox} (V_{GS} - V_{TH})_{PMOS}^2) = 1975.31$$

(91)

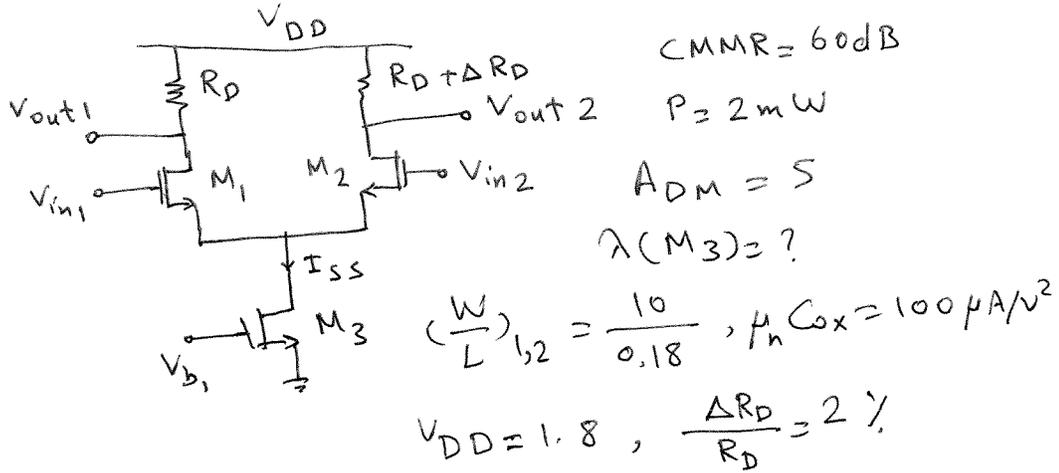


$$P = 2mW = I_{SS} V_{DD} \Rightarrow I_{SS} = \frac{2 \times 10^{-3}}{1.8} = 1.11 mA$$

$$A_{DM} = -g_{m1} R_D$$

$$g_{m1} = \sqrt{\mu_n C_{ox} (\frac{W}{L})_1 I_{SS}} = \sqrt{10^{-4} \times \frac{10}{0.18} \times 1.11 \times 10^{-3}} = 2.4845 mS$$

$$\Rightarrow R_D = \frac{|A_{DM}|}{g_{m1}} = \frac{5}{2.4845 \times 10^{-3}} = 2.012 k\Omega$$

To calculate  $A_{CM,DM}$  we have:

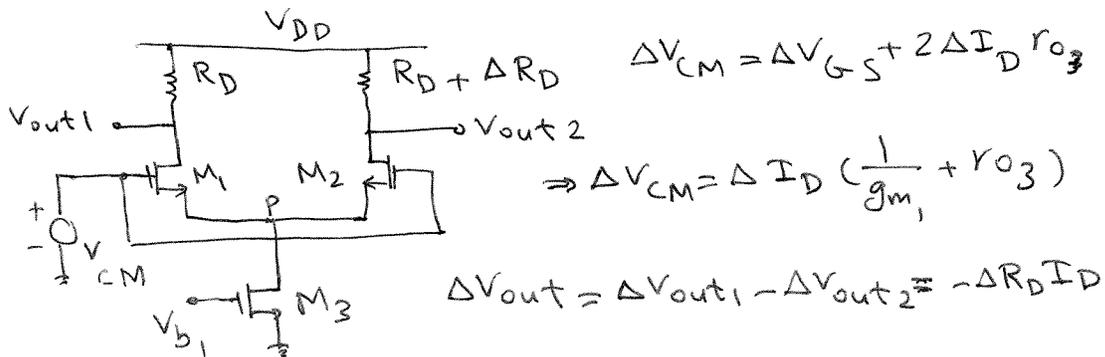


$$\Rightarrow A_{CM,DM} = \frac{\Delta V_{out}}{\Delta V_{CM}} = - \frac{\Delta R_D / 2}{\frac{1}{2g_{m1}} + r_{o3}}$$

$$\Rightarrow CMMR = \frac{A_{DM}}{A_{CM,DM}} = (1 + 2g_{m1} r_{o3}) \frac{R_D}{\Delta R_D}, \quad r_{o3} = \frac{1}{\lambda_3 I_{SS}}$$

$$\Rightarrow \text{CMRR} = 60\text{dB} = 10^3 = \left(1 + 2 \times 2.4845 \times 10^{-3} \frac{1}{\lambda_3 \times 1.11 \times 10^{-3}}\right) 50$$

$$\Rightarrow \lambda_3 = 0.2354$$

92

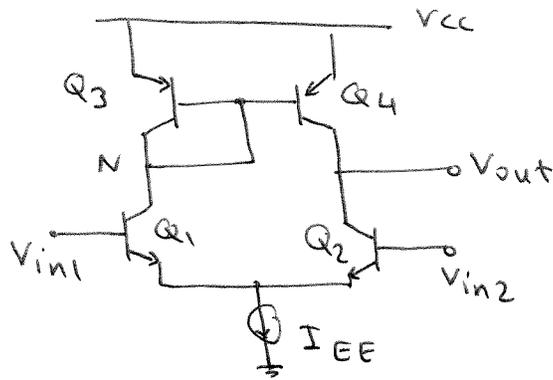

$$A_v = 200$$

$$P = 3 \text{ mW}$$

$$V_{CC} = 2.5 \text{ V}$$

$$V_{A,n} = 2 V_{A,p}$$

$$P = V_{CC} I_{EE} \Rightarrow I_{EE} = \frac{3 \times 10^{-3}}{2.5} = 1.2 \text{ mA}$$

$$g_{m_{1-4}} = \frac{I_{EE}}{2 V_T} = \frac{0.6}{26} = 23.077 \text{ mS}$$


$$r_{o1} = r_{o2} = \frac{V_{A,n}}{\frac{I_{EE}}{2}} = \frac{V_{A,n}}{0.6 \times 10^{-3}}$$

$$r_{o3} = r_{o4} = \frac{V_{A,p}}{\frac{I_{EE}}{2}} = \frac{V_{A,n}}{1.2 \times 10^{-3}}$$

$$A_v = g_{m_i} (r_{o2} \parallel r_{o4}) \Rightarrow \frac{0.6}{26} \left( \frac{V_{A,n}}{0.6 \times 10^{-3}} \parallel \frac{V_{A,n}}{1.2 \times 10^{-3}} \right) = 200$$

$$\Rightarrow V_{A,n} = 15.6 \text{ V}$$

93

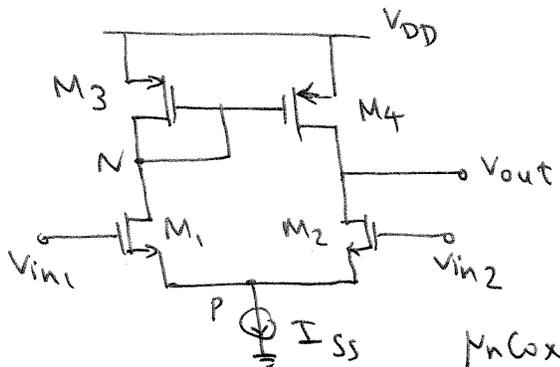

$A_V = 20$   
 $P = 1 \text{ mW}$   
 $V_{DD} = 1.8 \text{ V}$   
 $V_{in,cm} = 1 \text{ V}$

$\mu_n C_{ox} = 2 \mu_p C_{ox} = 100 \mu\text{A/V}^2$   
 $V_{TH,n} = 0.5 \text{ V}, V_{TH,p} = -0.4 \text{ V}$   
 $\lambda_n = \frac{\lambda_p}{2} = 0.1 \text{ V}^{-1}$

$$P = V_{DD} I_{SS} \Rightarrow I_{SS} = \frac{10^{-3}}{1.8} = 0.556 \text{ mA}$$

$$A_V = +g_{m_N} (r_{o_N} \parallel r_{o_P}) = 20$$

$$r_{o_N} = \frac{1}{\lambda_n \frac{I_{SS}}{2}} = \frac{1}{0.1 \frac{0.556 \times 10^{-3}}{2}} = 36 \text{ k}\Omega$$

$$r_{o_P} = \frac{1}{\lambda_p \frac{I_{SS}}{2}} = 18 \text{ k}\Omega$$

$$g_{m_N} (36 \text{ k} \parallel 18 \text{ k}) = 20 \Rightarrow g_{m_N} = 1.667 \text{ mS}$$

$$\Rightarrow g_{m_N} = \frac{2 I_{D_N}}{(V_{GS} - V_{TH})_{NMOS}} = \frac{I_{SS}}{(V_{GS} - V_{TH})_{NMOS}} \Rightarrow$$

$$(V_{GS} - V_{TH})_{NMOS} = 0.333 \text{ V}$$

$$(V_{GS} - V_{TH})_{NMOS} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_{NMOS}}} \Rightarrow \left(\frac{W}{L}\right)_{1/2} = 50$$


$$V_N = V_{in,CM} - V_{TH,n} = 1 - 0.5 = 0.5 \text{ V}$$

$$\rightarrow |V_{G_s} - V_{TH,p}| = 1.3 - 0.4 = 0.9 \text{ V}$$

$$\rightarrow 0.9 = \sqrt{\frac{I_{SS}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_{PMOS}}} \Rightarrow$$

$$\left(\frac{W}{L}\right)_{3,4} = 13.717$$

1)

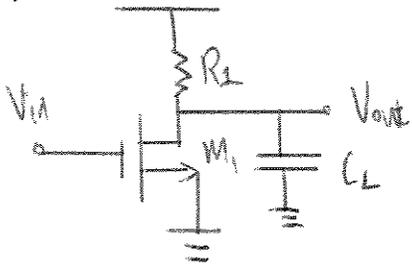

$$R_1 = 1 \text{ k}\Omega$$

$$C_L = 1 \text{ pF}$$


$$V_{out} = -g_{m_1} R_1 \parallel \frac{1}{C_L s} V_{in} \Rightarrow \frac{V_{out}}{V_{in}} = -g_m R_1 \parallel \frac{1}{C_L s}$$

$$\frac{V_{out}}{V_{in}} = -g_{m_1} \left( \frac{R_1}{R_1 C_L s + 1} \right), \quad s \rightarrow j\omega, \quad \frac{V_{out}}{V_{in}}(j\omega) = -g_{m_1} \left( \frac{R_1}{R_1 C_L j\omega + 1} \right)$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{g_m R_1}{\sqrt{1 + (\omega R_1 C_L)^2}}, \quad \text{Fall by } 10\% = \left| \frac{V_{out}}{V_{in}} \right| = g_m R_1 \cdot 0.9$$

$$\Rightarrow \frac{g_m R_1}{\sqrt{1 + (\omega R_1 C_L)^2}} = g_m R_1 \cdot 0.9 \Rightarrow \omega_{-10\%} = 4.84 \times 10^9 \text{ rad/s}$$
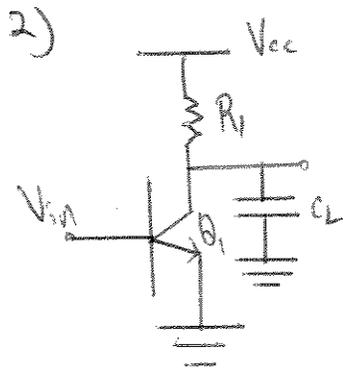
$$2\pi f = 4.84 \times 10^9 \Rightarrow f = 7.708 \times 10^8 \text{ Hz}$$



$$\text{-3dB bandwidth} = 1 \text{ GHz}$$

$$C_L = 2 \text{ pF}$$

$$\text{Power} = 2 \text{ mW}$$

Low freq gain?

$$\text{Power} = 2.5 \text{ V } I_c, \quad I_c = 0.8 \text{ mA}$$


$$\text{Dominant Pole at the output} = \frac{1}{R_L C_L} = 2\pi (1 \text{ GHz})$$

$$R_L = 79.58 \text{ Ohm}$$

$$\text{Low Freq gain: } -g_m R_L = \frac{-I_c R_L}{V_T} = \frac{(79.58)(0.8)}{26}$$


$$A_v \Big|_{\text{low freq}} = -2.45$$

3)

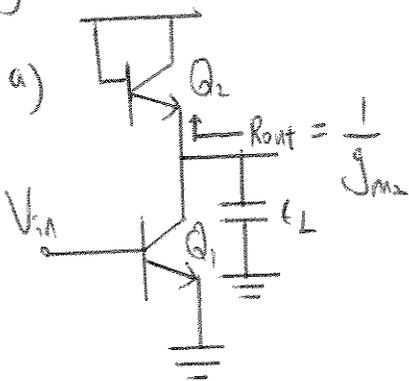


Assume  $\beta \gg 1$

$$-3dB = \frac{g_{m2}}{C_L}$$

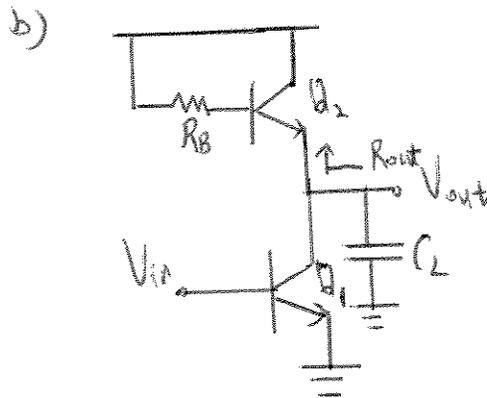


$$R_{out} = \frac{1}{g_{m2}} + \frac{R_B}{\beta + 1}$$
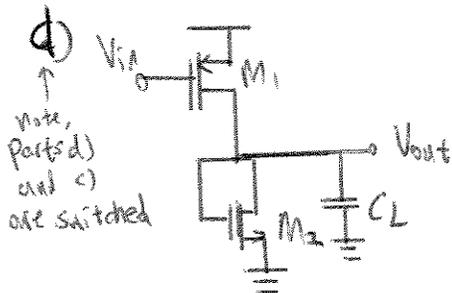
$$-3dB = \frac{(\beta + 1) g_{m2}}{C_L [\beta + R_B g_{m2}]}$$



$$R_{out} = \frac{1}{g_{m2} \parallel Y_{o2} \parallel Y_{o1}} \approx \frac{1}{g_{m2}}$$


$$-3dB = \frac{g_{m2}}{C_L}$$

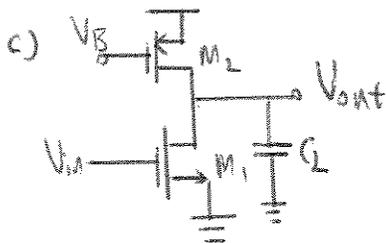


$$R_{out} = Y_{o1} \parallel Y_{o2}$$

$$-3dB = \frac{1}{(Y_{o1} \parallel Y_{o2}) C_L}$$


4)

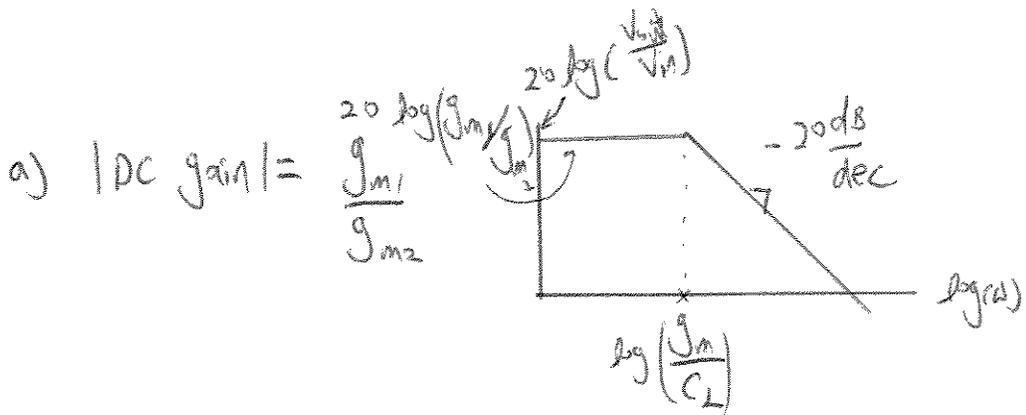


b)  $|DC \text{ gain}| = g_{m1} \left( \frac{1}{g_{m2}} + \frac{R_B}{\beta + 1} \right)$

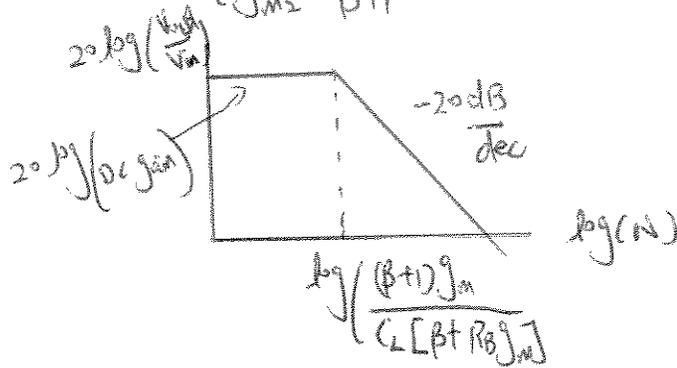


c)  $|DC \text{ gain}| = g_{m1} (R_{o1} / R_{o2})$

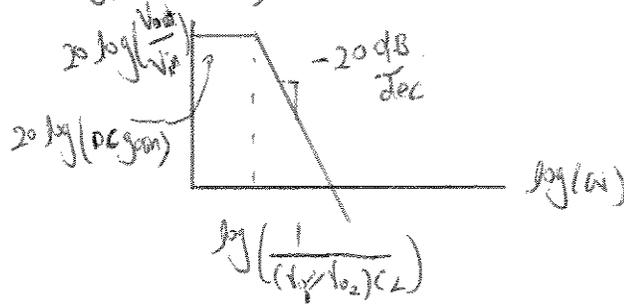

d)  $|DC \text{ gain}| = g_{m1} / g_{m2}$

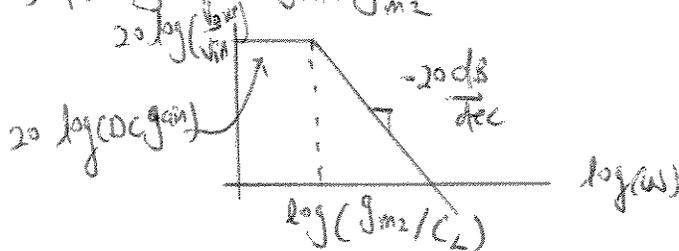

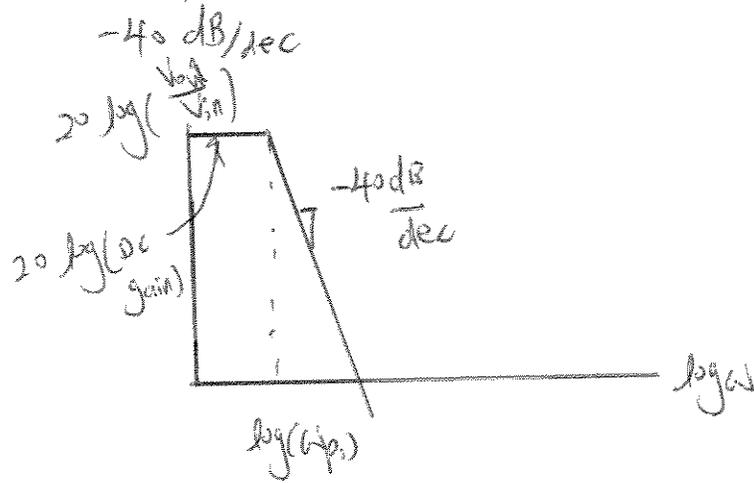5) 2 poles at  $\omega_p$ , means slope is




\* Assuming transfer function is in the form

of

$$\frac{A}{\left(\sqrt{\left(\frac{\omega}{\omega_p}\right)^2 + 1}\right)^2}$$

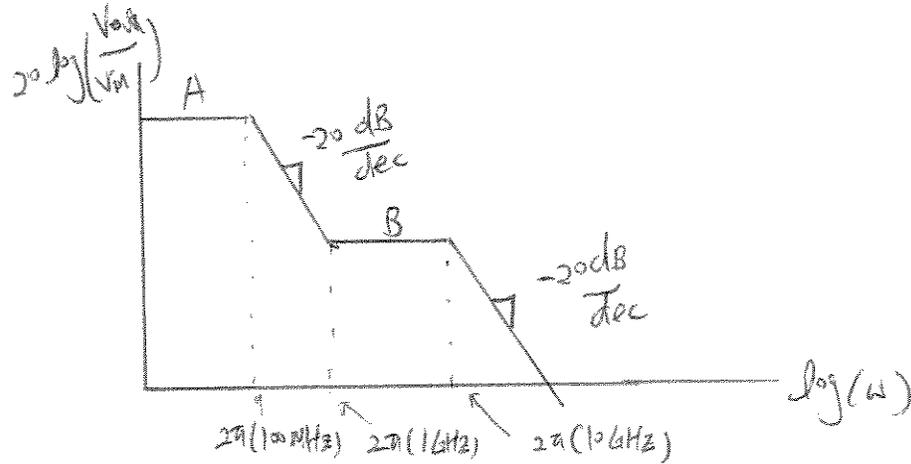6) Poles at 100 MHz, 10 GHz  
Zero at 1 GHz.




$$A(100MHz) = B(1GHz)$$

$$B = 0.1A$$


7) Ideal Integrator:  $\frac{V_{out}(s)}{V_{in}} = \frac{1}{s}$

$$\left| \frac{V_{out}(\omega)}{V_{in}} \right| = \frac{1}{\omega}$$

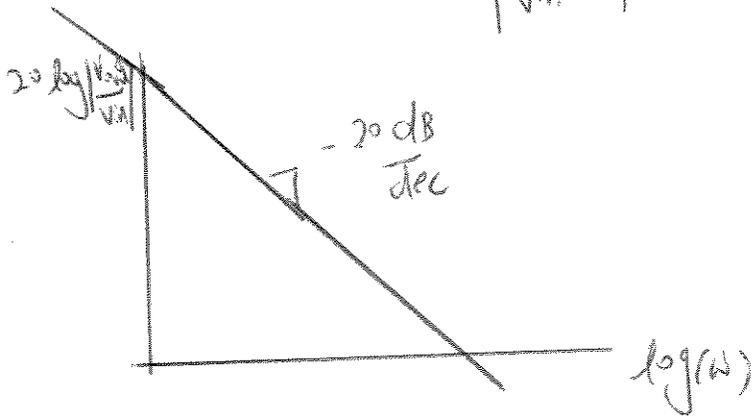


For an integrator, the gain at arbitrary low freq approaches infinity.

8) Ideal differentiator:  $S = \frac{V_{out}}{V_{in}}$ ,  $\left| \frac{V_{out}}{V_{in}}(\omega) \right| = \omega$   
 $20 \log \left| \frac{V_{out}}{V_{in}} \right|$   $\omega_z = 0$

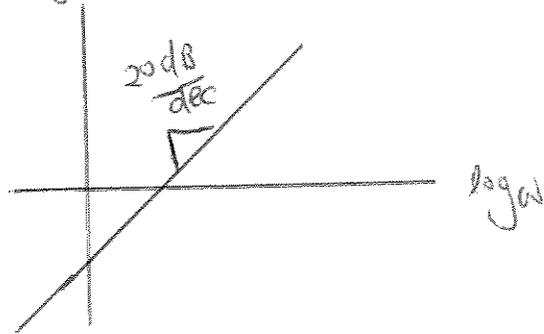

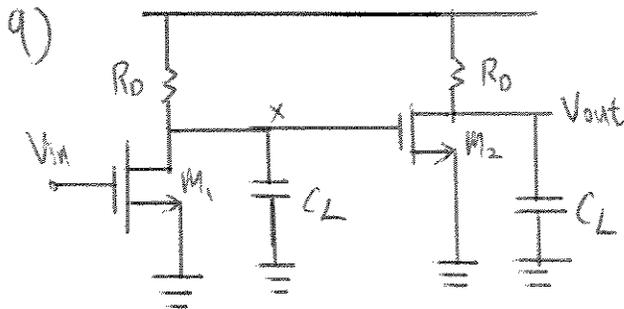For an ideal differentiator, gain at arbitrary high freq approaches infinity.





$\lambda = 0$ ,  $\downarrow$  neglect other caps.

DC gain:  $\frac{V_x}{V_{in}} = -g_m R_o$ ,  $\frac{V_{out}}{V_x} = -g_m R_o$

$$\frac{V_{out}}{V_{in}} = (g_m R_o)^2 \quad (\text{At DC})$$

2 poles at  $\frac{1}{R_o C_L}$

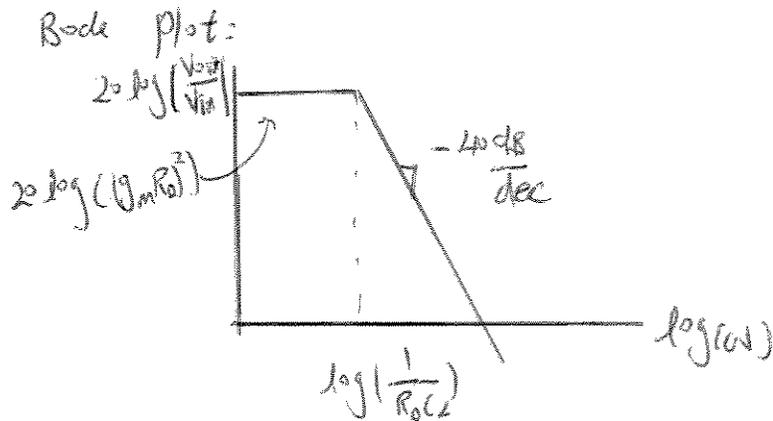

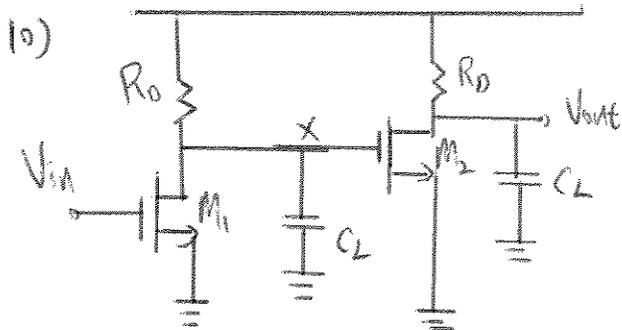

$$\frac{V_x(s)}{V_{in}} = -g_m \left( R_D \parallel \frac{1}{C_L s} \right), \quad \frac{V_{out}(s)}{V_x} = -g_m \left( \frac{R_D}{R_D C_L s + 1} \right)$$

$$= -g_m \left( \frac{R_D}{R_D C_L s + 1} \right)$$

$$H(s) = \frac{V_x(s)}{V_{in}} \frac{V_{out}(s)}{V_x} = \left( \frac{g_m R_D}{R_D C_L s + 1} \right)^2$$

$$s \rightarrow j\omega, \quad H(j\omega) = \left( \frac{g_m R_D}{1 + R_D C_L j\omega} \right)^2$$

$$|H(j\omega)| = \frac{(g_m R_D)^2}{1 + (R_D C_L \omega)^2}$$

-3dB Bandwidth:


$$\frac{(g_m R_D)^2}{1 + (R_D C_L \omega)^2} = \frac{(g_m R_D)^2}{\sqrt{2}}$$

$$\Rightarrow (R_D C_L \omega)^2 + 1 = \sqrt{2}$$

$$\Rightarrow \omega = \frac{\sqrt{\sqrt{2}-1}}{R_D C_L} = \frac{0.6436}{R_D C_L} \text{ (rad/s)}$$

$$2\pi f = \frac{0.6436}{R_D C_L} \Rightarrow f = \frac{0.10243}{R_D C_L} \text{ (Hz)}$$

11)

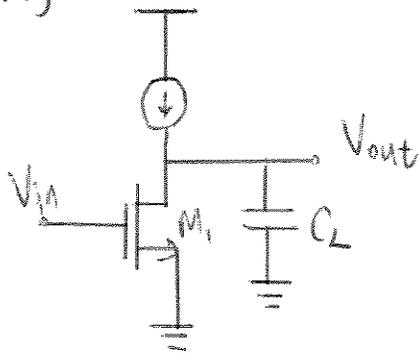

$$\lambda > 0$$

Since  $\lambda > 0$ , and we have an ideal current source, the impedance looking from out to ground is  $r_o \parallel \frac{1}{C_2 s}$


$$\text{So, } V_{out} = -g_m V_{in} \left( r_o \parallel \frac{1}{C_2 s} \right)$$

$$H(s) = -g_m \left( \frac{r_o}{r_o C_2 s + 1} \right), \quad |H(j\omega)| = \frac{g_m r_o}{\sqrt{(r_o C_2 \omega)^2 + 1}}$$

$$\text{For } \lambda \rightarrow 0, r_o \rightarrow \infty \Rightarrow H(s) \rightarrow \frac{-g_m r_o}{r_o C_2 s}$$

$H(s) = \frac{-g_m}{C_2 s}$ , A pole at origin, thus operating as an ideal integrator.

12)

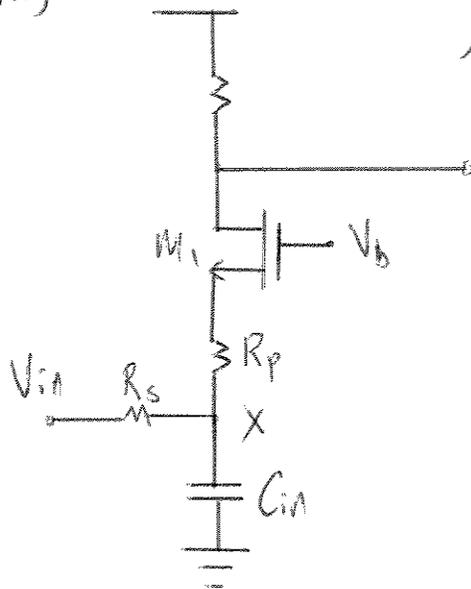

$$\lambda = 0$$


To find input pole,  
let  $V_{in} = 0$  and  
find the equivalent  
resistance and capacitance  
from node X to  
ground.

$$R_x = R_s \parallel \left( R_p + \frac{1}{g_{m_1}} \right), \quad C_x = C_{in}$$

$$\omega_{p.in} = \frac{1}{C_{in} \left[ R_s \parallel \left( R_p + \frac{1}{g_m} \right) \right]}$$

$$\omega_{p.out} = \frac{1}{R_D C_L}$$

13)

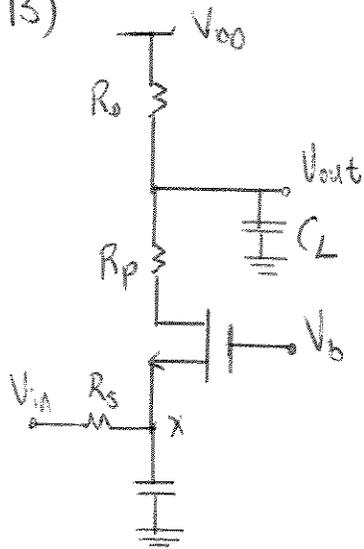

$\lambda=0$ , neglect all other caps.

$$R_x = R_s // \frac{1}{g_m}$$

$$C_x = C_{in}$$


$$R_{out} = R_o \quad (\text{since } V_o = \infty)$$

$$C_{out} = C_L$$

$$\omega_{pin} = \frac{1}{(R_s // \frac{1}{g_m}) C_{in}}$$

$$\omega_{pout} = \frac{1}{R_o C_L}$$


(4)

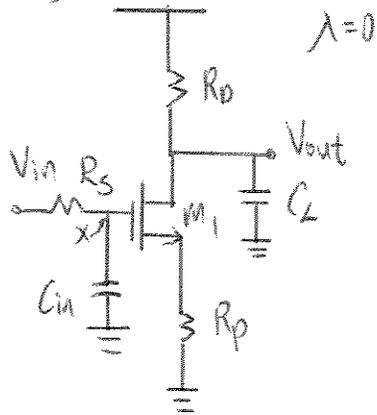

$$R_x = R_S, \quad R_{out} = R_D$$

$$C_x = C_{in}, \quad C_{out} = C_L$$
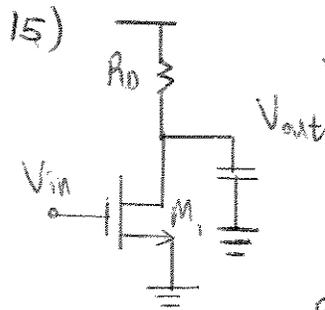
$$\omega_{pin} = \frac{1}{R_S C_{in}}, \quad \omega_{pout} = \frac{1}{R_D C_L}$$



DC Gain:  $g_m R_D = \frac{2I_D R_D}{V_{eff}}$

where  $V_{eff} = V_{GS} - V_{th}$

Band Width:  $\frac{1}{R_D C_L}$

Power Consumption:  $V_{DD} I_D$


F.O.M. (11.5) =  $\frac{\text{Gain} \times \text{Band Width}}{\text{Power Consumption}}$

$$= \frac{\left( \frac{2I_D R_D}{V_{eff}} \right) \left( \frac{1}{R_D C_L} \right)}{V_{DD} I_D}$$

$$= \frac{2}{V_{eff} V_{DD} C_L}$$


For practical design,  $V_{eff} > V_t$ , thus bipolar has a larger F.O.M. than MOS.

16)

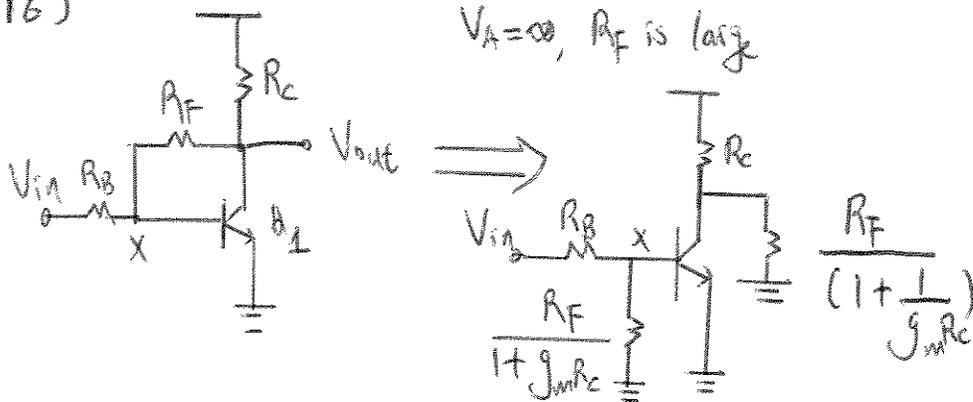

$$R_x = R_B \parallel \left( \frac{R_F}{1 + g_m R_c} \right), \quad R_{out} = R_c \parallel \left( \frac{R_F}{1 + \frac{1}{g_m R_c}} \right)$$

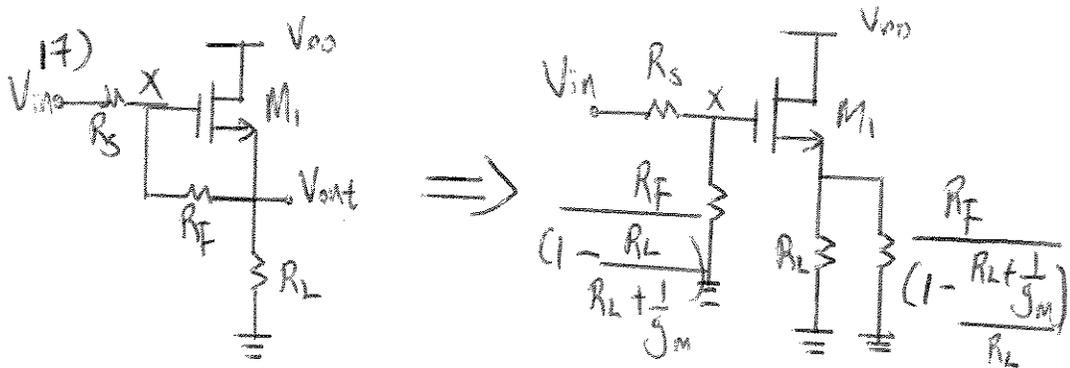
$$\frac{V_{out}}{V_{in}} = \frac{-R_{out}}{\frac{1}{g_m} + \frac{R_x}{\beta + 1}} = \frac{-R_c \parallel \left( \frac{R_F}{1 + 1/g_m R_c} \right)}{\frac{1}{g_m} + \frac{R_B \parallel (R_F / (1 + g_m R_c))}{\beta + 1}}$$



$$R_{out} = R_L \parallel \frac{R_F}{1 - \frac{R_L + \frac{1}{g_m}}{R_L}} = R_L \parallel \frac{R_F}{-\frac{1}{g_m R_L}}$$

$$R_{out} = R_L \parallel -R_F g_m R_L \quad (\text{note that } R_{out} \text{ may be negative})$$

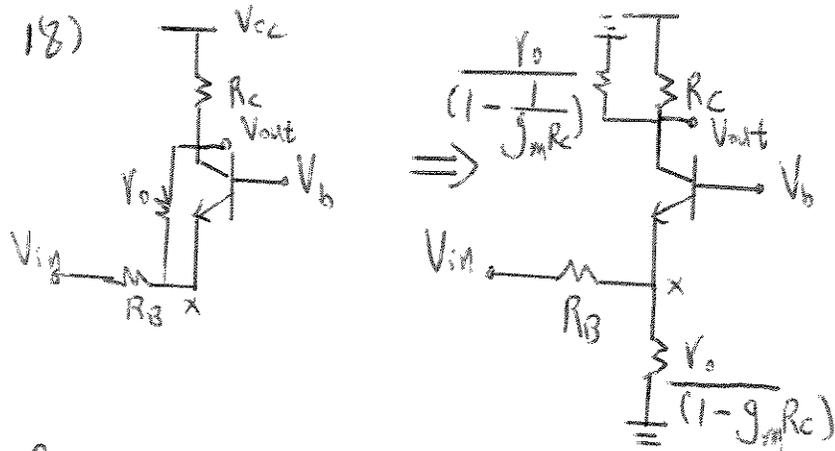
$$\frac{V_{out}}{V_{in}} = \frac{R_L \parallel -R_F g_m R_L}{R_L \parallel (-R_F R_L g_m) + \frac{1}{g_m}}$$



$$R_{out} = R_c \parallel \left( \frac{V_o}{1 - \frac{1}{g_m R_c}} \right)$$

$$R_x = R_B \parallel \left( \frac{V_o}{1 - g_m R_c} \right)$$

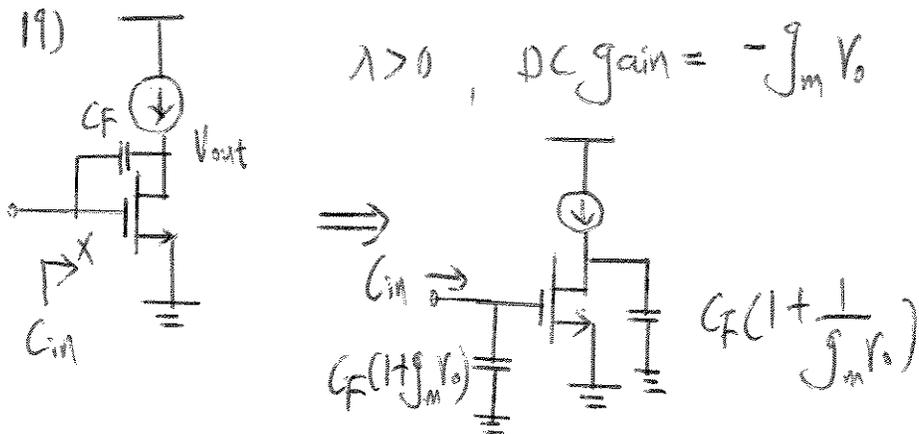
$$\frac{V_{out}}{V_{in}} = \frac{R_{out}}{R_x + \frac{1}{g_m}} = \frac{R_c \parallel \left( \frac{V_o}{1 - \frac{1}{g_m R_c}} \right)}{R_B \parallel \left( \frac{V_o}{1 - g_m R_c} \right) + \frac{1}{g_m}}$$



$$C_{in} = C_F(1 + g_m r_o), \text{ neglecting other caps.}$$

As  $\lambda \rightarrow 0$ ,  $r_o \rightarrow \infty$ , DC gain  $\rightarrow \infty$ ,

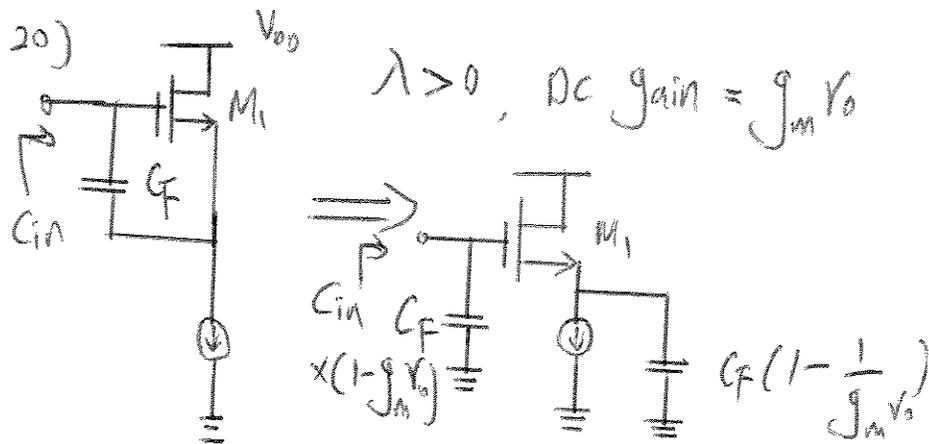$C_{in} \rightarrow \infty$ , this bandwidth will  $\rightarrow 0$ .




$$C_{in} = C_f (1 - g_m V_o)$$


As  $\lambda \rightarrow 0$ ,  $V_o \rightarrow \infty$ ,  $g_m V_o \rightarrow \infty$ ,  $C_{in} = -\infty$

When  $C \rightarrow$  negative in value, we have inductive activity. So right here, we have an effective infinite inductor.

21)

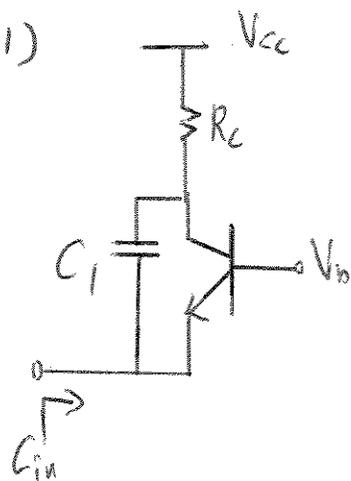


DC gain:  $g_m R_c$

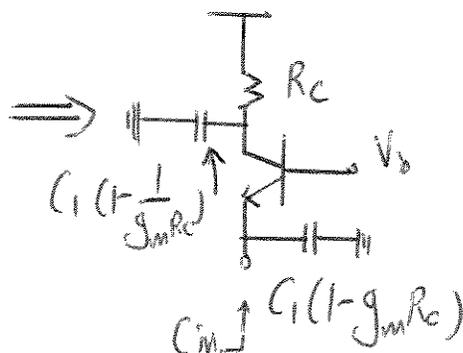


$$C_{in} = C_1 (1 - g_m R_c)$$

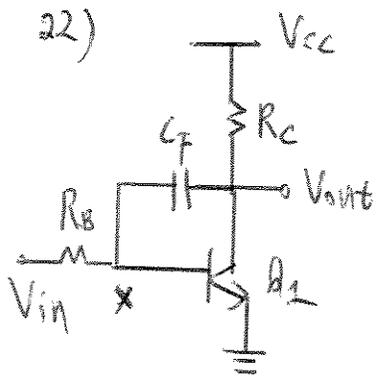If  $g_m R_c$  is designed to be larger than 1, as it normally would, we will have inductive action.



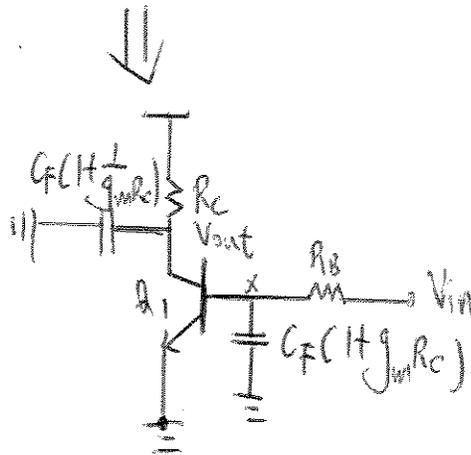DC gain (from  $x$  to out):  
 $-g_m R_c$



$$C_{in} = C_F (1 + g_m R_c)$$

$$R_{in} = R_B \parallel Y_{\pi}$$

$$C_{out} = C_F (1 + \frac{1}{g_m R_c})$$


$$R_{out} = R_c$$

$$\omega_{p1} = \frac{1}{R_B \parallel Y_{\pi} [C_F (1 + g_m R_c)]}$$


$$\omega_{pout} = \frac{1}{R_c C_F (1 + \frac{1}{g_m R_c})} \approx \frac{1}{R_c C_F}$$

(If  $g_m R_c \gg 1$ )

23)

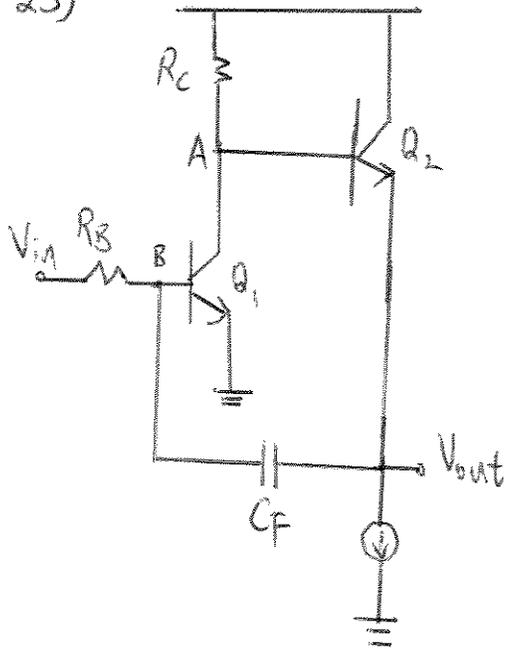

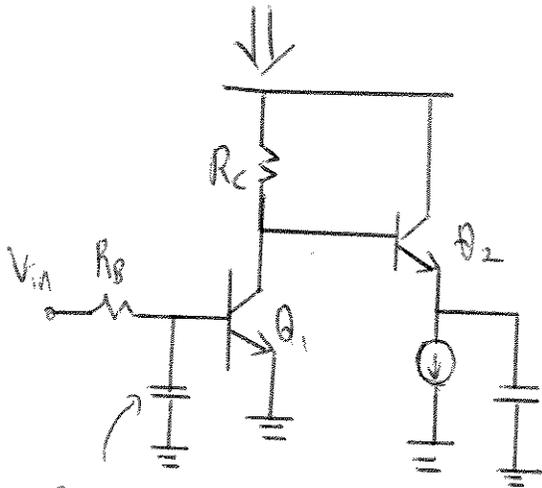The gain from B to A is  $-g_m R_C$ , from A to out is 1 (since we have an ideal current source). So the gain from B to out is  $-g_m R_C$ .



$$R_{in} = R_B \parallel Y_T$$

$$C_{in} = C_F (1 + g_m R_C)$$

$$R_{out} = \frac{1}{g_m} + \frac{R_C}{\beta + 1}$$


$$C_F \left(1 + \frac{1}{g_m R_C}\right)$$

$$C_F (1 + g_m R_C)$$

$$C_{out} = C_F \left(1 + \frac{1}{g_m R_C}\right)$$

$$\omega_{pin} = \frac{1}{R_B \parallel Y_T [C_F (1 + g_m R_C)]}$$

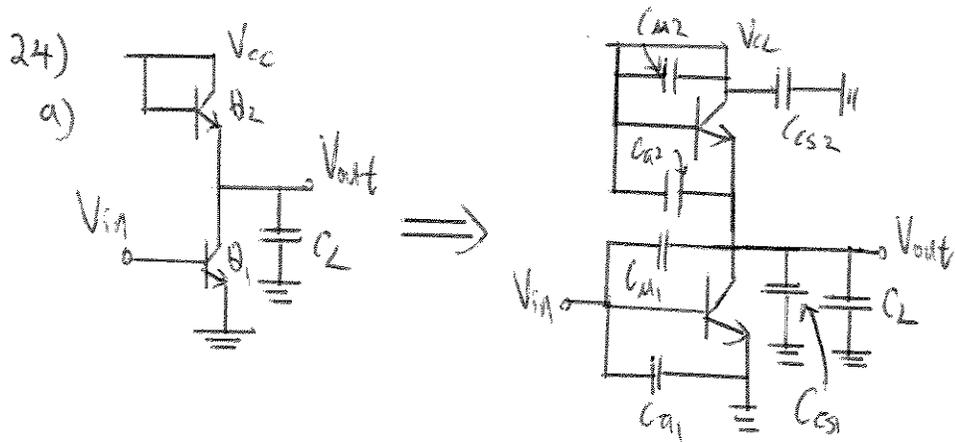
$$\omega_{pout} = \frac{1}{\left(\frac{1}{g_m} + \frac{R_C}{\beta + 1}\right) C_F \left(1 + \frac{1}{g_m R_C}\right)} \approx \frac{1}{\left(\frac{1}{g_m} + \frac{R_C}{\beta + 1}\right) C_F}, \quad (g_m R_C \gg 1)$$



$C_{M2}$ ,  $C_{S1}$ ,  $C_L$  are in parallel

$C_{M1}$ ,  $C_{S2}$  are grounded on both ends.



(and technically in parallel as well)

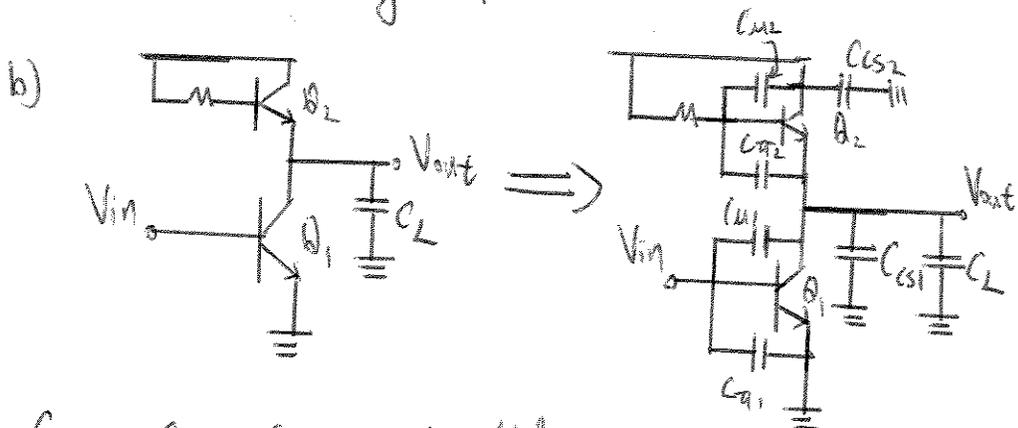


$C_{S1}$ ,  $C_L$  are in parallel

$C_{S2}$  is grounded on both ends


24)

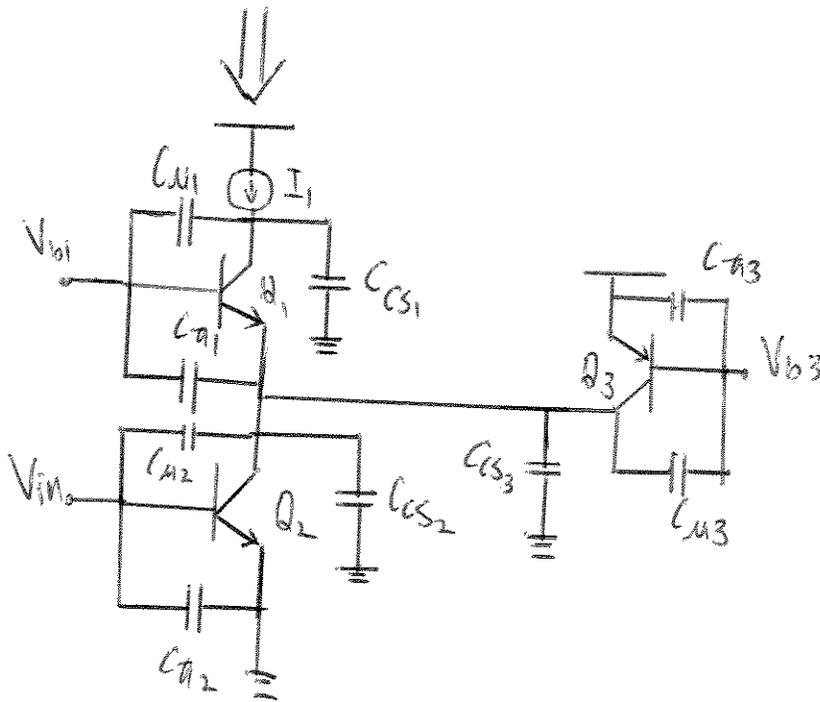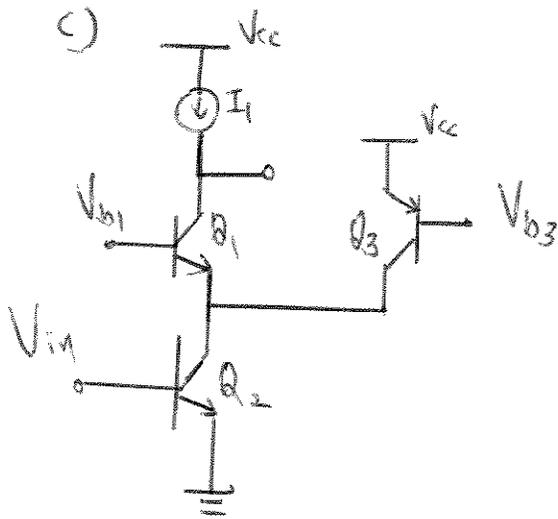

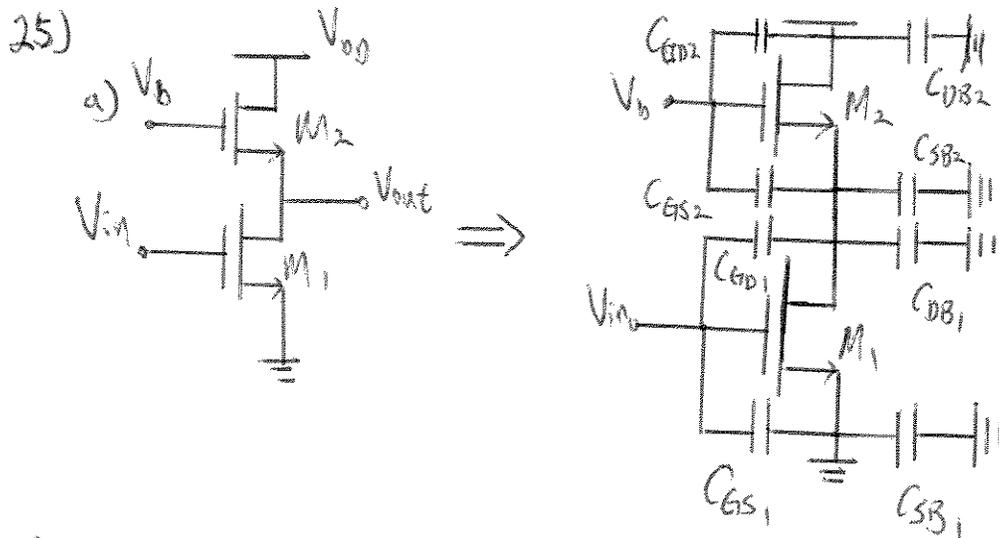$C_{\mu 1}, C_{CS2}, C_{CS3}, C_{\mu 3}$  are in parallel  
 $C_{\mu 1}, C_{CS1}$  are also in parallel  
 $C_{\mu 3}$  is grounded on both ends



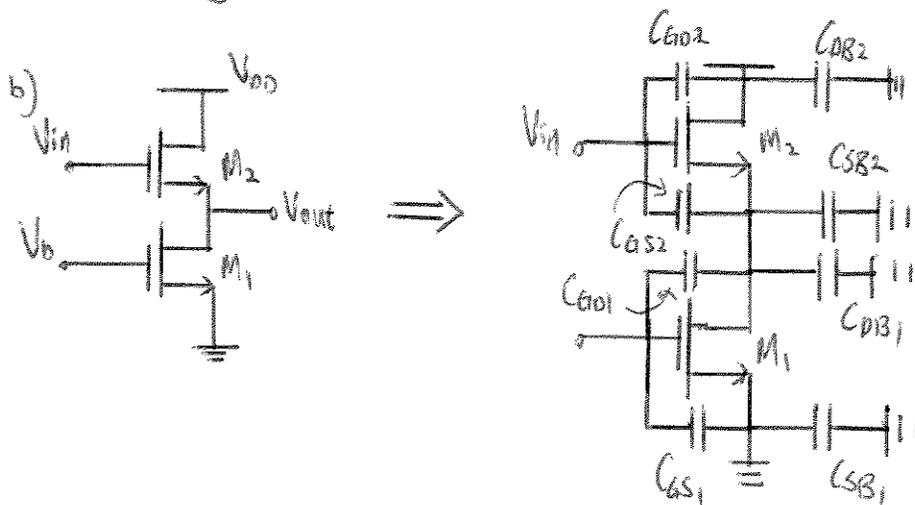$C_{GS2}$ ,  $C_{SB2}$ ,  $C_{DB1}$  are in parallel  
 $C_{GD2}$ ,  $C_{DB2}$  are in parallel and grounded on both ends  
 $C_{SB1}$  is grounded on both ends.




$C_{GD1}$ ,  $C_{DB1}$ ,  $C_{SB2}$  are in parallel

$C_{GS1}$ ,  $C_{SB1}$  are in parallel and grounded on both ends

$C_{DB2}$  is grounded on both ends.

25)

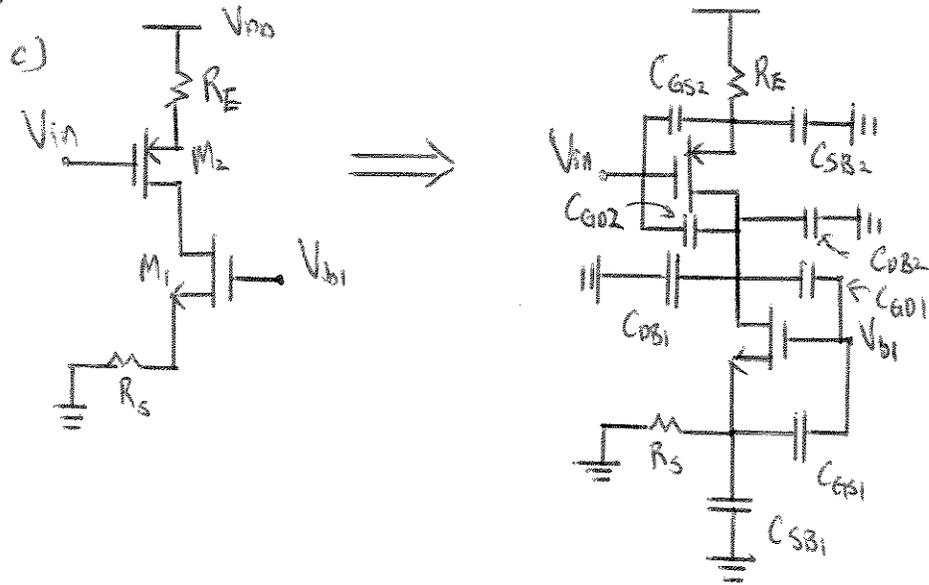


$C_{DB2}$ ,  $C_{GD1}$ ,  $C_{DB1}$ , are in parallel

$C_{SB1}$ ,  $C_{GS1}$  are also in parallel.

26)

Bipolar

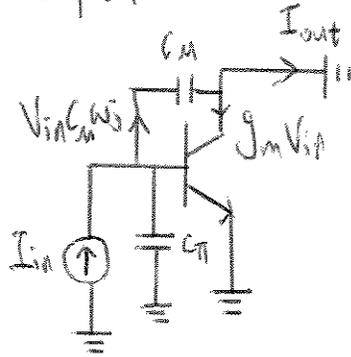


$$V_{in} = (I_{in}) \left( \frac{1}{[C_{\mu} + C_{\pi}] \omega j} \right) \quad (\text{Assuming we are at freq, and } V_A \text{ can be neglected})$$

$$I_{out} = V_{in} C_{\mu} \omega j - g_m I_{in} \left( \frac{1}{[C_{\mu} + C_{\pi}] \omega j} \right)$$

$$\frac{I_{out}}{I_{in}} = \frac{C_{\mu} \omega j - g_m}{[C_{\mu} + C_{\pi}] \omega j} \Rightarrow \left| \frac{I_{out}}{I_{in}} \right| = \frac{\sqrt{(g_m)^2 + (C_{\mu} \omega)^2}}{[C_{\mu} + C_{\pi}] \omega} = 1$$
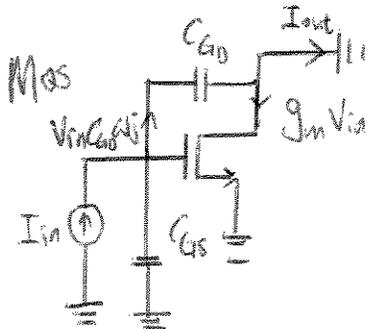
$$\omega_T^2 = \frac{g_m^2}{2C_{\mu}C_{\pi} + C_{\pi}^2} \Rightarrow \omega_T = 2\pi f_T = \frac{g_m}{\sqrt{2C_{\mu}C_{\pi} + C_{\pi}^2}}$$



Similarly for MOS, with  $C_{\mu}$  and  $C_{\pi}$  replaced by  $C_{GD}$  and  $C_{GS}$  respectively.

$$\omega_T = 2\pi f_T = \frac{g_m}{\sqrt{2C_{GD}C_{GS} + C_{GS}^2}}$$


27)

$$C_{\pi} = g_m \tau_F + C_{je}$$

$$2\pi f_T = \frac{g_m}{C_{\pi}} = \frac{g_m}{g_m \tau_F + C_{je}}$$

Assume  $C_{je}$  to be independent  
of  $I_c$ .
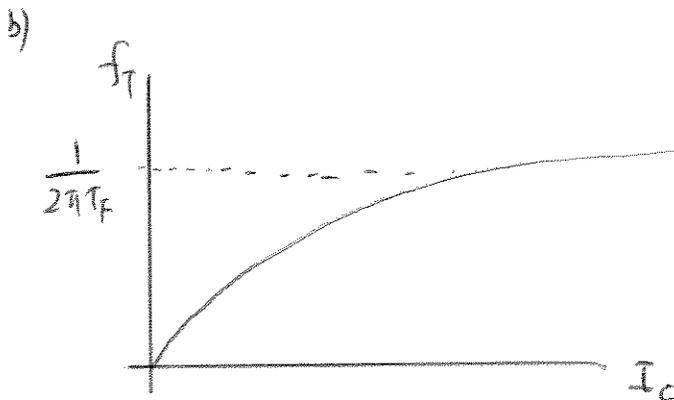
$$a) \quad 2\pi f_T = \frac{\frac{I_c}{V_T}}{\frac{I_c}{V_T} \tau_F + C_{je}} \Rightarrow f_T = \frac{I_c}{2\pi (I_c \tau_F + V_T C_{je})}$$



As  $I_c \rightarrow \infty$ ,  $f_T \rightarrow \frac{1}{2\pi \tau_F}$

28)

$$C_{GS} \approx \left(\frac{2}{3}\right) WL C_{ox}$$

$$2\pi f_T = \frac{g_m}{C_{GS}} = \frac{\frac{W}{L} \mu_n C_{ox} (V_{GS} - V_{TH})}{\frac{2}{3} WL C_{ox}}$$

$$2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$$

29)

$$2\pi f_T = \frac{3}{2} \frac{2I_D}{WLC_{ox}} \frac{1}{(V_{GS} - V_{TH})}$$

Apparently,  $f_T$  decreases with the overdrive.

However, when we look closely,  $I_D$  is

actually proportional to  $(V_{GS} - V_{TH})^2$  (in

saturation), so  $f_T$  is proportional to

$(V_{GS} - V_{TH})$ .


30)

a) As  $W \uparrow$ ,  $(V_{GS} - V_{TH})$  has to  $\downarrow$  by

$\frac{1}{\sqrt{W}}$  in order to maintain  $I_D$  constant

Using equation  $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$


$$2\pi f_T \propto \frac{1}{\sqrt{W}}$$

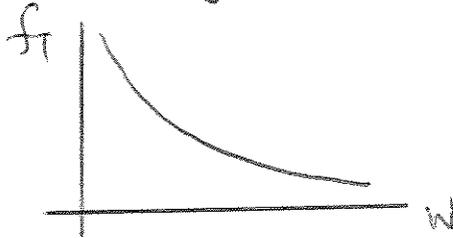

b)  $I_D \uparrow$ ,  $W$  constant it means  $V_{GS} - V_{TH} \uparrow$

With  $\sqrt{I_D}$ . Using equation  $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$


$$2\pi f_T \propto \sqrt{I_D}$$

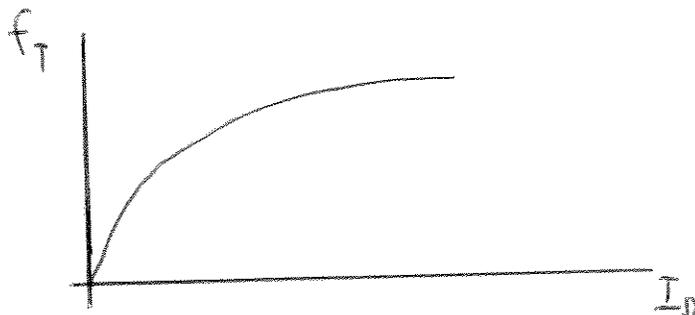

31)


Using equation  $2\pi f_T = \frac{3\mu_n}{2L^2} (V_{GS} - V_{TH})$

a)  $2\pi f_T \propto (V_{GS} - V_{TH})$

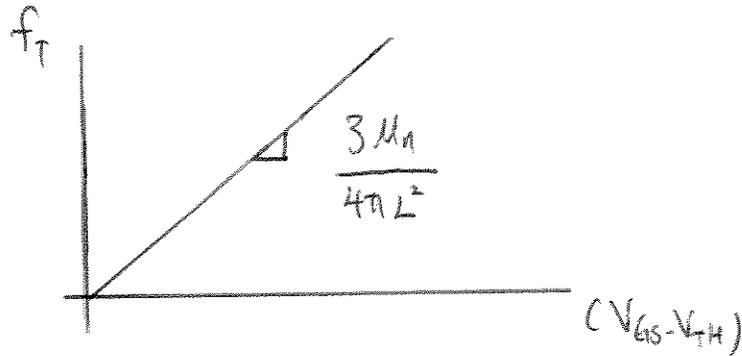

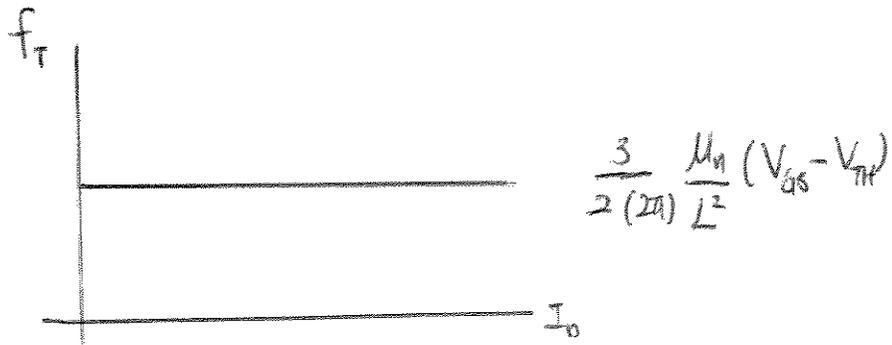b) Using equation  $2\pi f_T = \frac{3\mu_n}{2L^2} (V_{GS} - V_{TH})$


$2\pi f_T = \text{constant for all } I_D$



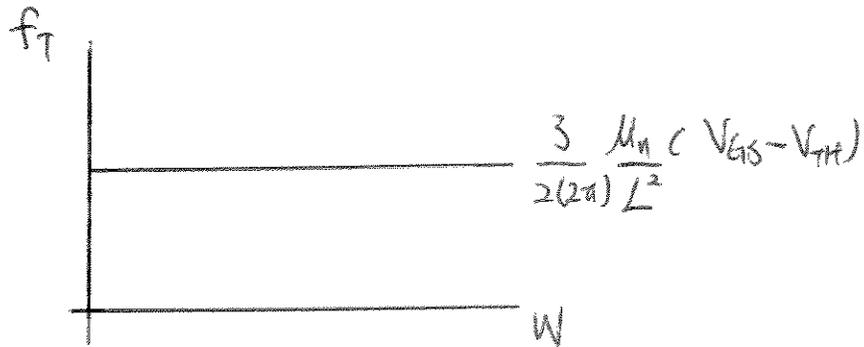32) a)


Using equation  $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$

We know that  $2\pi f_T$  is constant for all  $W$ .



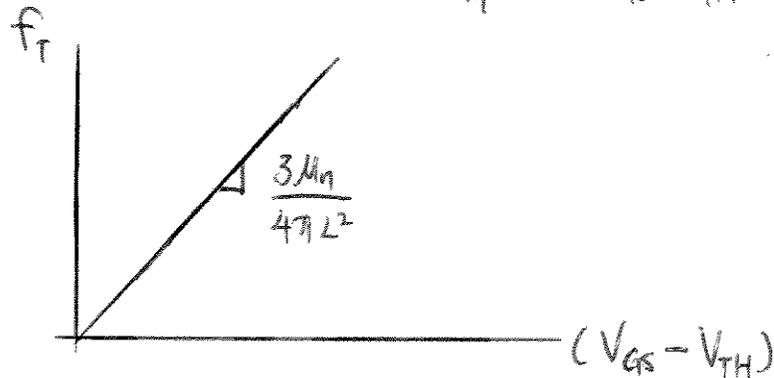b) Using equation  $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$ ,

we know that  $2\pi f_T \propto (V_{GS} - V_{TH})$ .



33)

$$a) I_D = \frac{1}{2} \frac{W}{L} \mu_n C_{ox} (V_{GS} - V_{TH})^2$$

As  $L \uparrow$ , to maintain the same current and overdrive voltage,  $W \uparrow$  as well.

So  $W$  also  $2X$ .

$$b) \text{ Since } 2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH}), \text{ and}$$

$L$   $2X$  while  $(V_{GS} - V_{TH})$  is constant,

$$f_T \downarrow \text{ by } \frac{3}{4} \text{ or } f_{T_{\text{new}}} = \frac{1}{4} f_{T_{\text{old}}}.$$

34)

$$a) V_{GS} - V_{TH} \rightarrow \frac{1}{2} (V_{GS} - V_{TH})$$

constant  $I_D$  and  $W \uparrow$  ( $L$  constant)

$$2\pi f_T = \frac{3}{2} \frac{M_n}{L^2} (V_{GS} - V_{TH})$$

$$f_{T, \text{new}} = \frac{f_{T, \text{old}}}{2}$$

$$b) V_{GS} - V_{TH} \rightarrow \frac{1}{2} (V_{GS} - V_{TH})$$


constant  $W$  and  $I_D \downarrow$  ( $L$  constant)

$$2\pi f_T = \frac{3}{2} \frac{M_n}{L^2} (V_{GS} - V_{TH})$$

$$f_{T, \text{new}} = \frac{f_{T, \text{old}}}{2}$$

35)


### Bipolar CE Stage

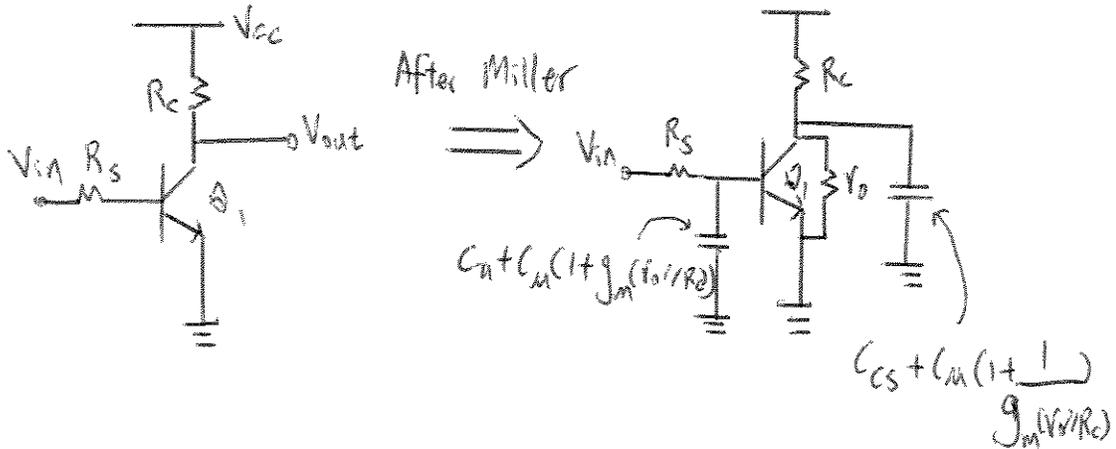

$$\omega_{p_{in}} = \frac{1}{(R_s // R_{in}) [C_c + C_c(1 + g_m(V_o/R_L))]}$$

$$\omega_{p_{out}} = \frac{1}{(R_c // R_o) [C_L + C_c(1 + 1/g_m(V_o/R_L))]}$$


### MOS CS Stage

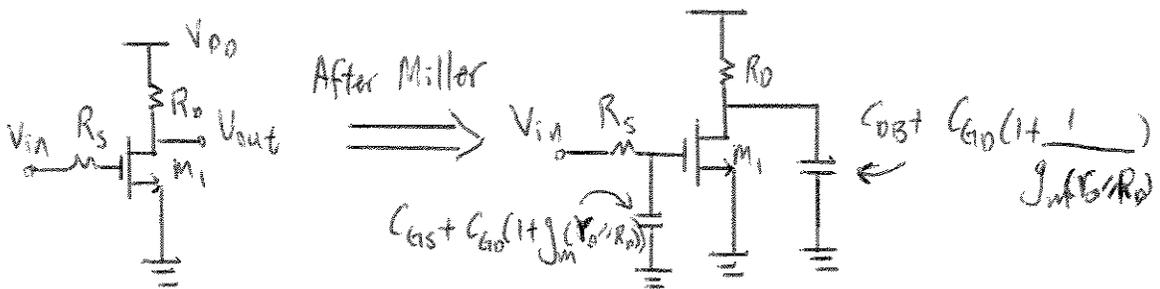

$$\omega_{p_{in}} = \frac{1}{R_s [C_{cs} + C_{cd}(1 + g_m(V_o/R_L))]}$$

$$\omega_{p_{out}} = \frac{1}{(R_d // R_o) [C_L + C_c(1 + 1/g_m(V_o/R_L))]}$$

36)

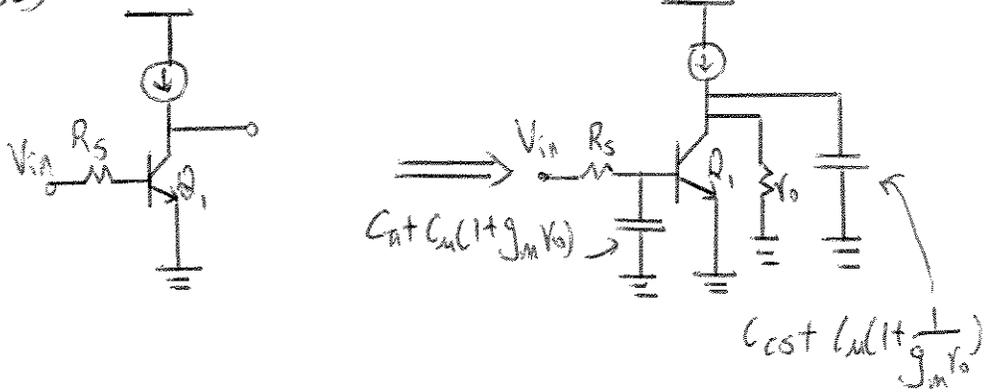


$$\omega_{p1} = \frac{1}{(R_s \parallel r_{\pi}) [C_{\pi} + C_{\mu}(1 + g_m R_o)]}$$

$$\omega_{p2} = \frac{1}{R_o [C_{cs} + C_{\mu}(1 + 1/g_m R_o)]}$$

$$H(s) = \frac{\text{DC gain}}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$
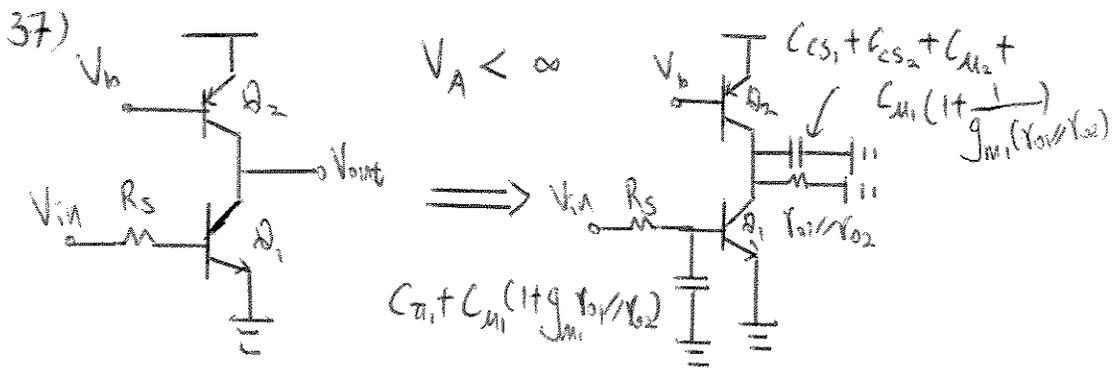
$$H(s) = \frac{g_m R_o (r_{\pi} \parallel (R_s + r_{\pi}))}{\left(1 + \frac{s}{1/(R_s \parallel r_{\pi}) [C_{\pi} + C_{\mu}(1 + g_m R_o)]}\right) \left(1 + \frac{s}{1/(R_o [C_{cs} + C_{\mu}(1 + 1/g_m R_o)])}\right)}$$



$$\omega_{pin} = \frac{1}{(R_s/V_{in}) [C_{\pi 1} + C_{\mu 1} (1 + g_{m1} (V_{o1}/V_{o2}))]}$$



$$\omega_{pout} = \frac{1}{(V_{o1}/V_{o2}) [C_{cs1} + C_{cs2} + C_{\mu 2} + C_{\mu 1} (1 + 1/(g_{m1} (V_{o1}/V_{o2})))]}$$

$$g_m V_o \gg 1$$

$$H(s) = \frac{g_m (V_{o1}/V_{o2}) (V_{in}/V_{in} + R_s)}{(1 + R_s [C_{\pi 1} + C_{\mu 1} (g_m (V_{o1}/V_{o2}))] s) (1 + (V_{o1}/V_{o2}) [C_{cs1} + C_{cs2} + C_{\mu 2} + C_{\mu 1}] s)}$$

3B)

a)

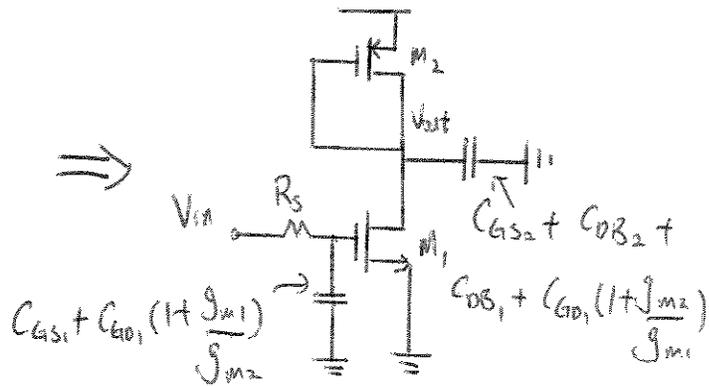
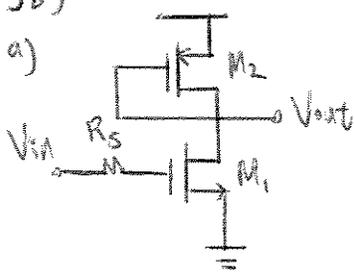


$$\text{DC gain} = -g_{m1} (V_{o1} // V_{o2} // \frac{1}{g_{m2}}) \approx -\frac{g_{m1}}{g_{m2}}$$

$$\omega_{p_{in}} = \frac{1}{R_S (C_{GS1} + C_{GD1} (1 + \frac{g_{m1}}{g_{m2}}))}$$

$$\omega_{p_{out}} = \frac{g_{m2}}{C_{GS2} + C_{DB2} + C_{DB1} + C_{GD1} (1 + \frac{g_{m2}}{g_{m1}})}$$

b)

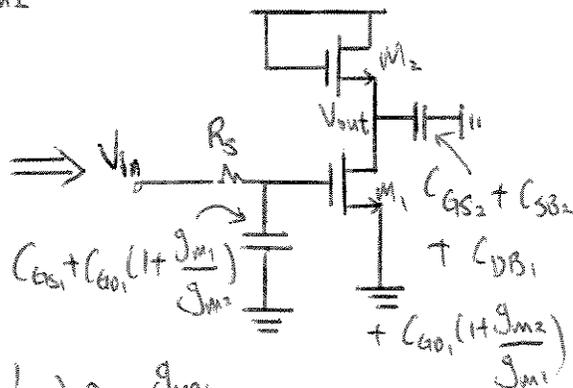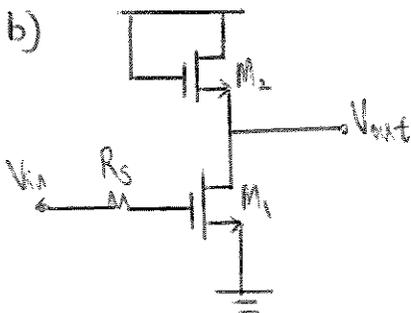


$$\text{DC gain} = -g_{m1} (V_{o1} // V_{o2} // \frac{1}{g_{m2}}) \approx -\frac{g_{m1}}{g_{m2}}$$

$$\omega_{p_{in}} = \frac{1}{R_S (C_{GS1} + C_{GD1} (1 + \frac{g_{m1}}{g_{m2}}))}$$

$$\omega_{p_{out}} = \frac{g_{m2}}{C_{SB2} + C_{GS2} + C_{DB1} + C_{GD1} (1 + \frac{g_{m2}}{g_{m1}})}$$

38)

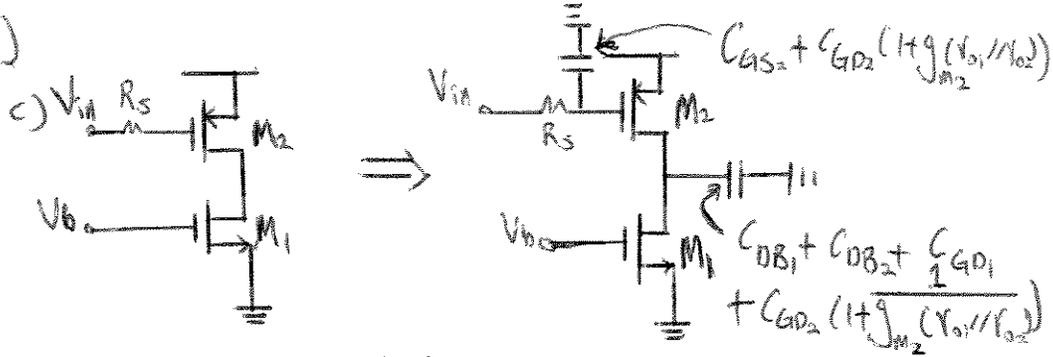

DC gain:  $-g_{m2} (r_{o1} // r_{o2})$


$$\omega_{pin} = \frac{1}{R_S (C_{gs2} + C_{GD2} (1 + g_{m2} (r_{o1} // r_{o2})))}$$

$$\omega_{pout} = \frac{1}{(r_{o1} // r_{o2}) [C_{DB1} + C_{DB2} + C_{GD1} + C_{GD2} (1 + \frac{1}{g_{m2} (r_{o1} // r_{o2})})]}$$

$$\omega_{pout} \approx \frac{1}{(r_{o1} // r_{o2}) [C_{DB1} + C_{DB2} + C_{GD1} + C_{GD2}]}$$

Since  $g_{m2} (r_{o1} // r_{o2}) \gg 1$

39)

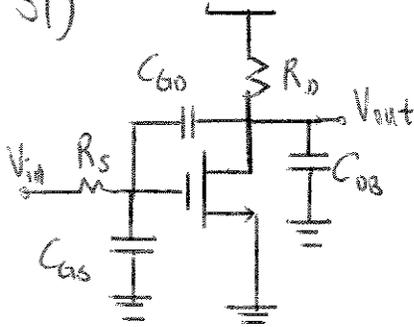


$$R_S = 200\Omega \quad C_{GS} = 5\text{pF}$$

$$R_D = 1\text{k}\Omega \quad C_{GD} = 10\text{pF}$$

$$I_D = 1\text{mA} \quad C_{DB} = 15\text{pF}$$

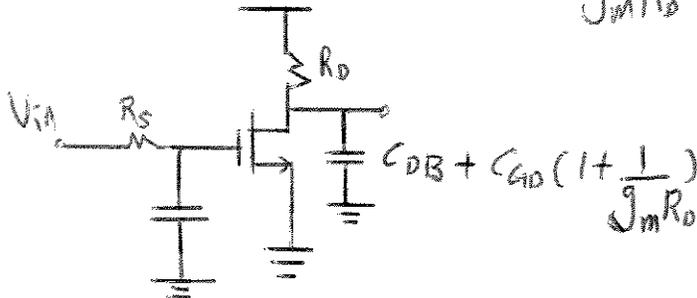a) Miller's approximation:

$$-g_m R_D = \frac{-(1)(2)(1)}{(0.2)} = -10$$



$$C_{GS} + (1 + g_m R_D) C_{GD}$$

$$\omega_{p_{in}} = \frac{1}{R_S (C_{GS} + (1 + g_m R_D) C_{GD})} = \frac{1}{200 (5\text{pF} + (11)(10\text{pF}))} = 31.25\text{GHz}$$

$$\omega_{p_{out}} = \frac{1}{R_D (C_{DB} + (1 + \frac{1}{10}) C_{GD})} = \frac{1}{1000 (15\text{pF} + (1 + 0.1) 10\text{pF})} = 38.46\text{GHz}$$

39)

$$b) \text{ Equation } \frac{V_{out}(s)}{V_{Thev}} = \frac{(C_{xy}s - g_m)R_L}{as^2 + bs + 1}$$

$$a = R_{Thev}R_L(C_{in}C_{xy} + C_{out}C_{xy} + C_{in}C_{out})$$

$$R_{Thev} = R_S, C_{in} = C_{GS}, C_{out} = C_{OB}, R_L = R_O, C_{xy} = C_{GD}$$

$$a = (200 \times 1000) [(50 \times 10^{-15})(10 \times 10^{-15}) + (15 \times 10^{-15})(10 \times 10^{-15}) + (50 \times 10^{-15})(15 \times 10^{-15})] = 2.8 \times 10^{-22}$$

$$b = (1 + g_m R_L)C_{xy}R_{Thev} + R_{Thev}C_{in} + R_L(C_{xy} + C_{out})$$

$$b = (1 + 10)(10 \times 10^{-15})(200) + (200)(50 \times 10^{-15}) + (1000)(10 \times 10^{-15}) + 1000(15 \times 10^{-15})$$

$$b = 5.7 \times 10^{-11}$$

$$\text{So denominator} = (2.8 \times 10^{-22} s^2 + 5.7 \times 10^{-11} s + 1)$$

$$s = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$s = -1.93909 \times 10^{10}, -1.84181 \times 10^{11}$$

$$\omega_{p1} = 19.39 \text{ GHz}, \omega_{p2} = 184.2 \text{ GHz}$$

Which one is  $\omega_{pin}$ , and which one is  $\omega_{pout}$ ?

This can be seen from inspection, at output and high frequency  $C_{GD}$  starts to become a short and thus the output resistance collapses to  $1/g_m$ , and pushes the output pole out. Whereas at the input the pole location does not change too much because  $R_S$  is small and  $C_{GS}$  is large.

Therefore, we conclude that when solving the transfer function directly, the  $\omega_{pin}$  is 19.39 GHz (on the same order as

39)

b). that obtained from Miller's approximation), while  $\omega_{\text{pout}}$  is pushed out significantly, 184.2 GHz (when compared to that obtained from Miller's approximation).

Miller Approximation

$$\omega_{\text{pin}} = 31.25 \text{ GHz}$$


$$\omega_{\text{pout}} = 38.46 \text{ GHz}$$

Transfer Function


$$\omega_{\text{pin}} = 19.39 \text{ GHz}$$

$$\omega_{\text{pout}} = 184.2 \text{ GHz}$$

40)

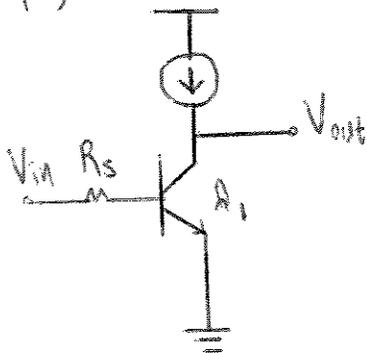

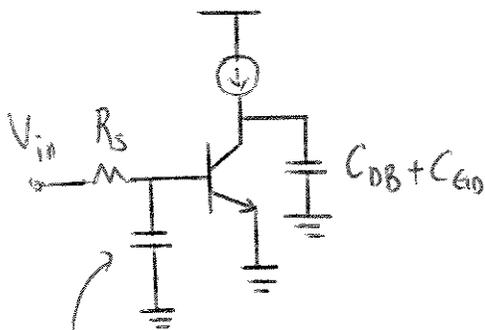a) Miller's Approximation: DC gain:  $-\infty$



$C_{GS} + \infty$

$$\omega_{pin} = \frac{1}{R_s(\infty)} = 0, \quad \omega_{part} = \frac{1}{\infty(C_{OB} + C_{GD})} = 0$$

b) Transfer Function:

$$\frac{V_{out}(s)}{V_{thv}} = \frac{(C_{xy}s - g_m)R_L}{as^2 + bs + 1}$$

$$a = R_{Thev}R_L(C_{in}C_{xy} + C_{out}C_{xy} + C_{in}C_{out})$$

$$b = (1 + g_mR_L)C_{xy}R_{Thev} + R_{Thev}C_{in} + R_L(C_{xy} + C_{out})$$

40)

b)  $R_L \rightarrow \infty$

$$\frac{V_{out}}{V_{thv}} = \frac{C_{xy} S - g_m}{S [R_{thv} (C_{in} C_{xy} + C_{out} C_{xy} + C_{in} C_{out}) S + g_m C_{xy} R_{thv} + (C_{xy} + C_{out})]}$$

So  $\omega_{p1} = 0$

$$\omega_{p2} = \frac{(g_m C_{xy} R_{thv} + (C_{xy} + C_{out}))}{R_{thv} [C_{in} C_{xy} + C_{out} C_{xy} + C_{in} C_{out}]}$$

$$\omega_{p2} = \frac{g_m C_u R_S / R_{th} + C_u + C_{cs}}{R_S / R_{th} [C_{in} C_u + C_{cs} C_u + C_{in} C_{cs}]}$$

$\omega_{p1} = \omega_{pin}, \quad \omega_{p2} = \omega_{pout}.$

Miller:

$\omega_{pin} = 0, \quad \omega_{pout} = 0$

Again, the output pole predicted by the transfer function is pushed out, and the input poles are similar. (In fact, they are the same this time.)

This shows one of the short-comings of Miller's approximation.

4) Dominant-pole approximation:

$$\omega_{p1} = \frac{1}{(1 + g_m R_L) C_{xy} R_{Thev} + R_{Thev} C_{in} + R_L (C_{xy} + C_{out})}$$

$$\omega_{p1} = 0 \quad (\text{Since } R_L = \infty)$$

$$\omega_{p2} = \frac{(1 + g_m R_L) C_{xy} R_{Thev} + R_{Thev} C_{in} + R_L (C_{xy} + C_{out})}{R_{Thev} R_L (C_{in} C_{xy} + C_{out} C_{xy} + C_{in} C_{out})}$$


Since  $R_L = \infty$

$$\omega_{p2} = \frac{g_m C_{xy} R_{Thev} + C_{xy} + C_{out}}{R_{Thev} (C_{in} C_{xy} + C_{out} C_{xy} + C_{in} C_{out})}$$

$$\omega_{p2} = \frac{g_m C_M R_S' R_{\pi} + C_M + C_{CS}}{R_S (C_{\pi} C_M + C_{CS} C_M + C_{\pi} C_{CS})}$$

Dominant-pole approximation gives the same result as the transfer function method.

42)

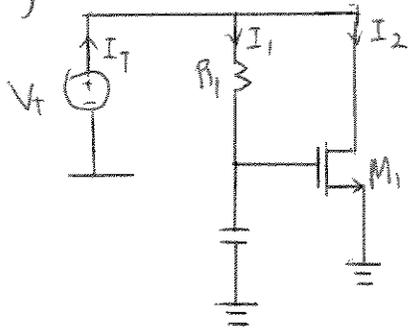

$\lambda=0$ , and neglect other capacitances.

$$I_T = I_1 + I_2$$

$$I_1 = \frac{V_T}{(R_1 + \frac{1}{C_1 s})}, \quad I_2 = \frac{g_m V_T}{C_1 R_1 s + 1}$$


$$I_T = \frac{C_1 s V_T}{C_1 R_1 s + 1} + \frac{g_m V_T}{C_1 R_1 s + 1} \Rightarrow \frac{V_T}{I_T} = \frac{C_1 R_1 s + 1}{C_1 s + g_m}$$

$$s \rightarrow j\omega \Rightarrow \frac{C_1 R_1 (j\omega) + 1}{C_1 j\omega + g_m} = Z_T(j\omega)$$

$$|Z_T| = |Z_{in}| = \frac{\sqrt{(C_1 R_1 \omega)^2 + 1}}{\sqrt{C_1^2 \omega^2 + g_m^2}} = \frac{\sqrt{C_1 R_1 \omega^2 + 1}}{g_m \sqrt{\left(\frac{C_1 \omega}{g_m}\right)^2 + 1}}$$



At  $\omega = \frac{1}{C_1 R_1}$ , we have a zero, at  $\omega = \frac{g_m}{C_1}$ , we have a pole. If  $R_1 > \frac{1}{g_m}$ , the zero  $C_1$  is at a lower frequency than the pole, and the bode-plot for magnitude would look like the following.

$20 \log(Z_{in})$

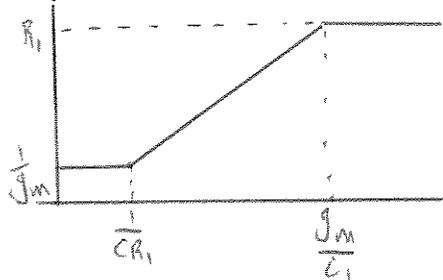

The bode-plot shows an impedance that increases with frequency, an inductive behavior.

43)

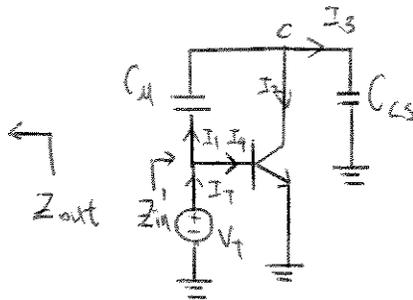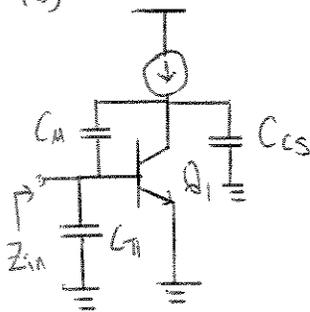

$$Z_{in} = Z_{in}' \parallel \frac{1}{C_{\pi} s}, \quad I_T = I_1 + I_4 = C_{\mu} s V_{bc} + \frac{g_m V_T}{\beta}$$

$$V_{bc} = V_T - V_c, \quad V_c = (I_1 - g_m V_T) \frac{1}{C_{cs} s}$$

$$I_1 = \left[ V_T - (I_1 - g_m V_T) \frac{1}{C_{cs} s} \right] C_{\mu} s$$

$$I_1 = V_T \left[ C_{\mu} s + \frac{g_m C_{\mu}}{C_{cs}} \right] / \left( 1 + \frac{C_{\mu}}{C_{cs}} \right)$$


$$I_T = V_T \left[ C_{\mu} s + \frac{g_m C_{\mu}}{C_{cs}} \right] / \left( 1 + \frac{C_{\mu}}{C_{cs}} \right) + \frac{g_m V_T}{\beta}$$

$$Z_{in}' = \frac{V_T}{I_T} = \frac{1}{\frac{g_m}{\beta} + \frac{C_{\mu} s}{\left( 1 + \frac{C_{\mu}}{C_{cs}} \right)} + \frac{g_m \frac{C_{\mu}}{C_{cs}}}{\left( 1 + \frac{C_{\mu}}{C_{cs}} \right)}}$$

$$Z_{in} = Z_{in}' \parallel \frac{1}{C_{\pi} s} = r_{\pi} \parallel \frac{1}{\frac{C_{cs} C_{\mu} s}{C_{cs} + C_{\mu}}} \parallel \frac{1}{C_{\pi} s} \parallel \frac{C_{cs} + C_{\mu}}{g_m C_{\mu}}$$

$$Z_{out} = \frac{1}{(C_{\mu} + C_{cs}) s}$$

44)

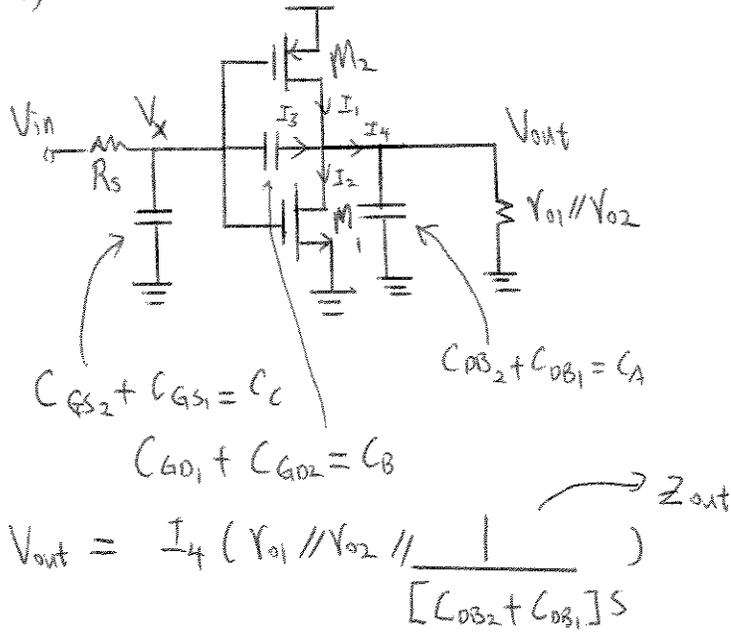 $\lambda > 0$ 

$$I_4 = I_1 + I_3 - I_2$$

$$I_1 = (0 - V_x) g_{m2}$$

$$I_2 = V_x g_{m1}$$

$$I_3 = (V_x - V_{out}) (C_{GO1} + C_{GO2}) s$$

$$I_4 = -V_x g_{m2} + (V_x - V_{out}) C_B s - V_x g_{m1}$$

$$V_{out} = Z_{out} [-V_x (g_{m2} + g_{m1}) + (V_x - V_{out}) C_B s]$$

Writing a node equation at X.

$$\frac{V_x - V_{in}}{R_s} + V_x C_C s + (V_x - V_{out}) C_B s = 0$$

$$V_x = \frac{V_{out} C_B s + V_{in}/R_s}{(1/R_s + C_C s + C_B s)}$$

$$(1/R_s + C_C s + C_B s)$$

44)

Substitute everything and we get

$$V_{out} = Z_{out} \left[ -(g_{m1} + g_{m2}) \left( \frac{V_{out} C_B s + V_{in}/R_s}{1/R_s + C_c s + C_B s} \right) + \left( \frac{V_{out} C_B s + V_{in}/R_s}{1/R_s + C_c s + C_B s} - V_{out} \right) C_B s \right]$$

Collect all the  $V_{out}$ 's on one-side and likewise for  $V_{in}$ 's,  
we will get

$$\frac{V_{out}}{V_{in}} = \frac{Z_{out} (C_B s - (g_{m1} + g_{m2}))}{R_s}$$


$$\frac{1}{R_s + (C_c + C_B) s} + Z_{out} C_B s (g_{m1} + g_{m2}) + Z_{out} C_B s \left( \frac{1}{R_s} + (C_c + C_B) s \right) - Z_{out} C_B^2 s^2$$

$$\text{where } Z_{out} = Y_{o1} // Y_{o2} // \frac{1}{[C_{DB1} + C_{DB2}] s}$$

$$C_B = C_{GD1} + C_{GD2}$$

$$C_c = C_{GS1} + C_{GS2}$$

45)

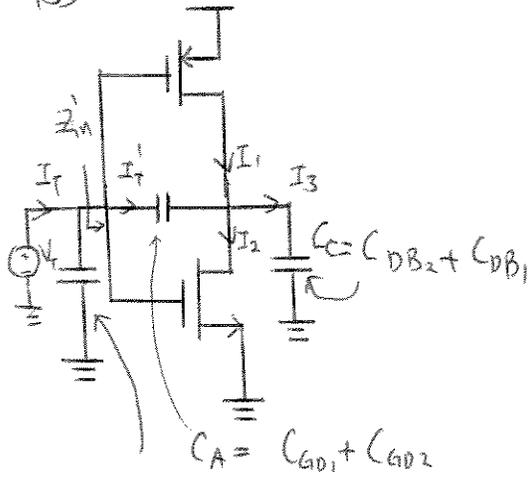

$$Z_{in} = \frac{V_T}{I_T} = \frac{1}{C_B} \parallel Z_{in}'$$

$$Z_{in}' = \frac{V_T}{I_T'}$$

$$C_B = C_{GS1} + C_{GS2}$$

$$I_T' = \left[ V_T - \left( I_3 \frac{1}{C_{CS}} \right) \right] C_{AS}$$

$$I_3 = I_T' - V_T g_{m2} - g_{m1} V_T$$


$$\text{We get } \Rightarrow I_T' \left( 1 + \frac{C_A}{C_C} \right) = V_T \left[ C_{AS} + (g_{m1} + g_{m2}) \frac{C_A}{C_C} \right]$$

$$Z_{in}' = \frac{V_T}{I_T'} = \frac{\left( 1 + \frac{C_A}{C_C} \right)}{\left[ C_{AS} + (g_{m1} + g_{m2}) \frac{C_A}{C_C} \right]}$$

$$Z_{in} = \frac{1}{[C_{GS1} + C_{GS2}]s} \parallel \frac{\left( 1 + \frac{C_{GD1} + C_{GD2}}{C_{DB1} + C_{DB2}} \right)}{\left[ (C_{GD1} + C_{GD2})s + (g_{m1} + g_{m2}) \frac{C_{GD1} + C_{GD2}}{C_{DB2} + C_{DB1}} \right]}$$

46)

a)

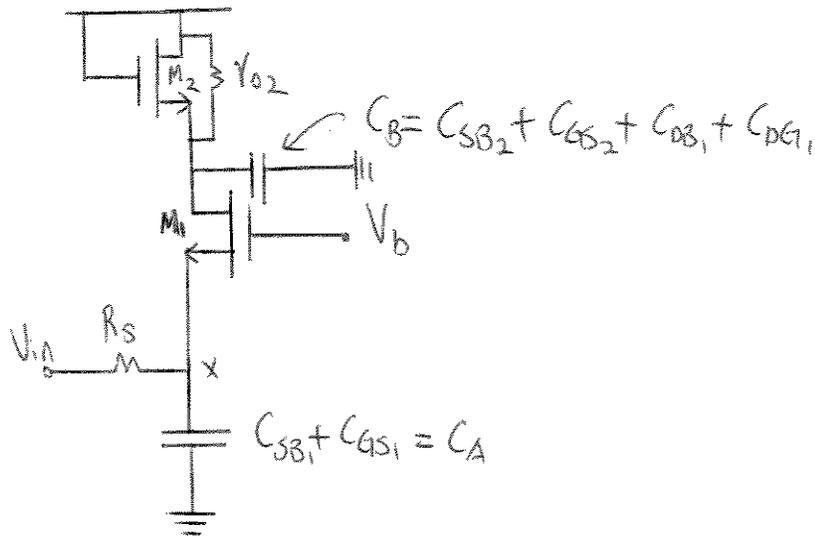

$$V_{out} = -(0 - V_x) g_{m1} \left[ \frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right] = V_x g_{m1} \left[ \frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right]$$

Node equation at X,  $\frac{V_x - V_{in}}{R_s} + V_x C_A s - g_m (0 - V_x) = 0$

$$V_x \left( \frac{1}{R_s} + C_A s + g_m \right) = \frac{V_{in}}{R_s} \Rightarrow V_x = \frac{V_{in}}{(1 + R_s C_A s + R_s g_m)}$$

substitute in  $V_x$  and solving for  $V_{out}/V_{in} \Rightarrow$


$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} \left[ \frac{1}{g_{m2}} \parallel \frac{1}{C_B s} \right]}{(1 + R_s C_A s + R_s g_m)}$$

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} (1/g_{m2})}{(C_B (1/g_{m2}) s + 1) (1 + R_s C_A s + R_s g_m)}$$

Where  $C_B = C_{SB2} + C_{CS2} + C_{DB1} + C_{DB2}$

$C_A = C_{SB1} + C_{CS1}$

46)

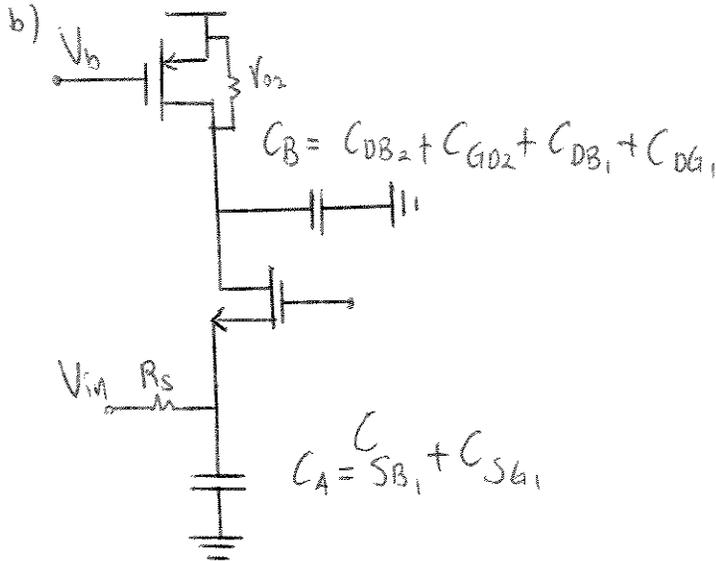

Similar to part a), with  $\frac{1}{g_{m2}}$  replaced by  $V_{o2}$ ,  
and different  $C_B$


$$\text{So } \frac{V_{out}}{V_{in}} = \frac{g_{m1} V_{o2}}{(C_B V_{o2} s + 1)(1 + R_S C_A s + R_S g_{m1})}$$

Where  $C_B = C_{DB2} + C_{GO2} + C_{DB1} + C_{DG1}$

$$C_A = C_{SB1} + C_{SE1}$$

46)

c)

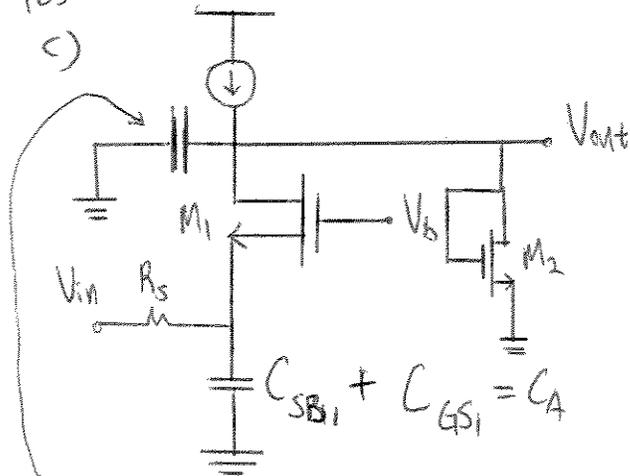

$$C_B = C_{DB1} + C_{GD1} + C_{DB2} + C_{GS2}$$


AC-wise, this circuit is very similar to part a), Its transfer function is the same as part a), except for  $C_B$ .

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} (1/g_{m2})}{(C_B (V_{g_{m2}})^2 s + 1) (1 + R_S C_A s + R_S g_{m1})}$$

Where  $C_B = C_{DB1} + C_{GD1} + C_{DB2} + C_{GS2}$

$$C_A = C_{SB1} + C_{GS1}$$

47)

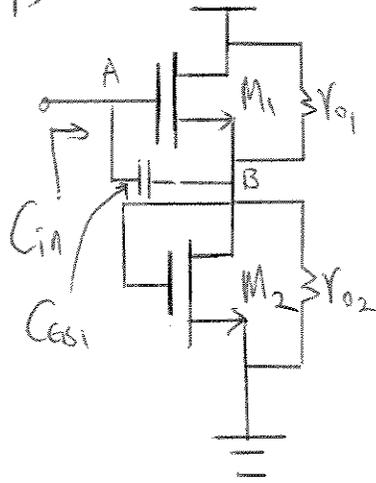

DC gain from A to B:

$$A_V = \frac{\frac{1}{g_{m2}} \parallel r_{O1} \parallel r_{O2}}{\frac{1}{g_{m2}} \parallel r_{O1} \parallel r_{O2} + \frac{1}{g_{m1}}}$$

$$A_V \approx \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m2}} + \frac{1}{g_{m1}}} = \frac{g_{m1}}{g_{m1} + g_{m2}}$$


since  $g_{m1} r_{O1} \gg 1$

Using Miller's Capacitance:

$$C_{in} = C_{GS1} (1 - A_V) = C_{GS1} \left( 1 - \frac{g_{m1}}{g_{m1} + g_{m2}} \right)$$

$$C_{in} = C_{GS1} \left( \frac{g_{m2}}{g_{m2} + g_{m1}} \right)$$

48)

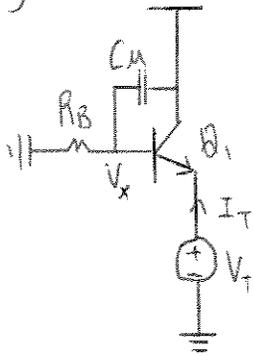

$V_A = \infty$ ,

$\frac{\beta}{\beta+1} \approx 1$ , if  $\beta \gg 1$

$$I_T = -(V_x - V_T) g_m \approx -(V_x - V_T) g_m$$

$$V_x = \frac{I_T}{\beta} \left( R_B \parallel \frac{1}{C_u s} \right)$$

$$I_T = \left( V_T - \frac{I_T}{\beta} \left( R_B \parallel \frac{1}{C_u s} \right) \right) g_m$$

$$I_T = g_m V_T - \frac{g_m}{\beta} \left( R_B \parallel \frac{1}{C_u s} \right) I_T$$


$$I_T \left( 1 + \frac{g_m}{\beta} \left( R_B \parallel \frac{1}{C_u s} \right) \right) = g_m V_T$$


$$\frac{V_T}{I_T} = \frac{1}{g_m} + \frac{R_B \parallel \frac{1}{C_u s}}{\beta} = \frac{\beta C_u R_B (s + \frac{\beta + R_B g_m}{\beta C_u R_B})}{g_m \beta (1 + C_u R_B s)}$$

Zero:  $\frac{\beta + R_B g_m}{\beta C_u R_B}$ , Pole:  $\frac{1}{C_u R_B}$

At DC,  $|Z_{out}| = \frac{1}{g_m} + \frac{R_B}{\beta}$

At very high freq:  $|Z_{out}| = \frac{1}{g_m}$

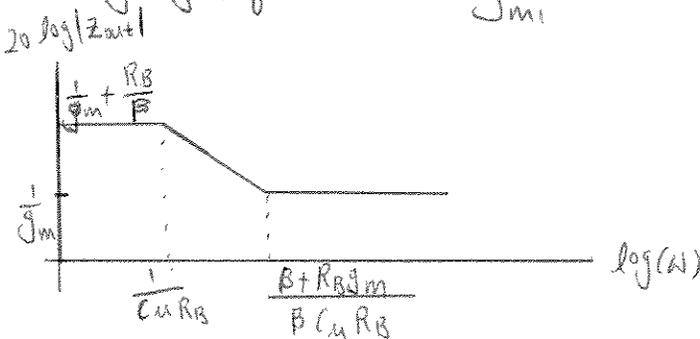

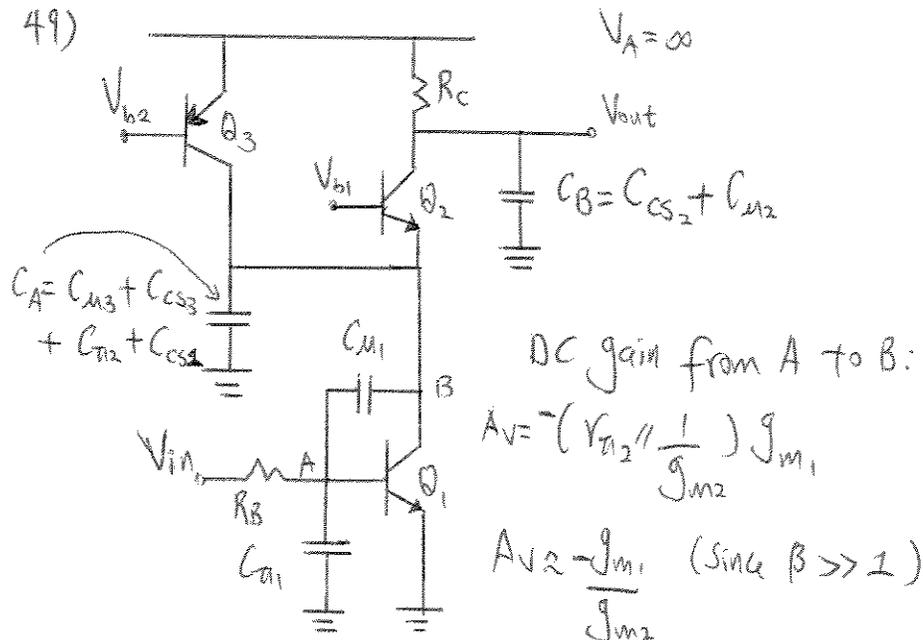

We have  $I_{C2} = 0.25 I_{C1}$ ,  $g_m = \frac{I_C}{V_T} \Rightarrow g_{m2} = 0.25 g_{m1}$

$A_v = -\frac{g_{m1}}{g_{m2}} = -4$ . (If  $I_{C2} = I_{C1}$ ,  $A_v = -1$ )

Applying Miller's Theorem:  $C_{in} = C_{A1} + C_{M1}(1+4) = C_{A1} + 5C_{M1}$   
 $C_B = C_A + C_M(1+\frac{1}{4}) = C_A + C_M(\frac{5}{4})$


$\omega_{p1} (\omega_{pA}) = \frac{1}{(R_B \parallel r_{\pi 1}) [C_{A1} + 5C_{M1}]}$ ,  $\omega_{pB} = \frac{0.25 g_{m1}}{[C_A + \frac{5}{4} C_{M1}]}$

$\omega_{pB} = \frac{g_{m2}}{[C_A + \frac{5}{4} C_{M1}]}$ ,  $\omega_{pout} = \frac{1}{R_C [C_{CS2} + C_{M2}]}$

Where  $C_A = C_{M3} + C_{CS3} + C_{M2} + C_{CS1}$ .

Since the DC gain is increased, Miller effect is more significant.  
 (In magnitude)

50)

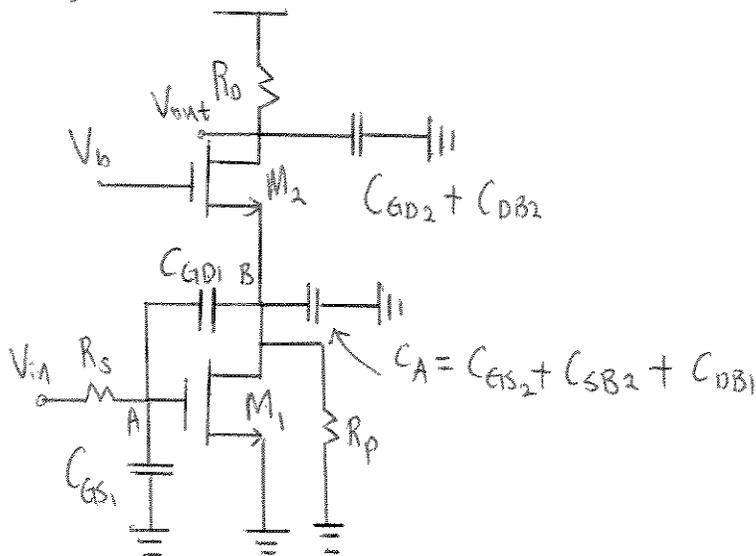

DC gain from A to B is  $-g_{m1} (R_p \parallel \frac{1}{g_{m2}})$


Applying Miller's Theorem:

$$\omega_{pin} (\omega_{pA}) = \frac{1}{R_s (C_{GS1} + C_{GD1} (1 + g_{m1} (R_p \parallel \frac{1}{g_{m2}})))}$$

$$\omega_{pB} = \frac{1}{R_p \parallel \frac{1}{g_{m2}} [C_{GS2} + C_{SB2} + C_{DB1} + C_{GD1} (1 + 1/g_{m1} (R_p \parallel \frac{1}{g_{m2}}))]}$$

$$\omega_{pout} = \frac{1}{R_o (C_{GD2} + C_{DB2})}$$

51)

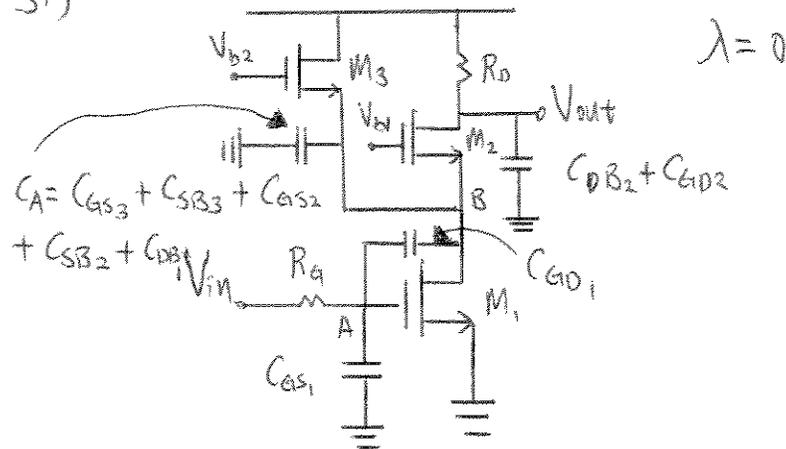

$$\text{DC gain from A to B: } -g_{m1} \left( \frac{1}{g_{m3}} \parallel \frac{1}{g_{m2}} \right) = -g_{m1} \left( \frac{1}{g_{m2} + g_{m3}} \right)$$

Applying Miller's Theorem:


$$\omega_{p1} (\omega_{pa}) = \frac{1}{R_A \left( C_{as1} + C_{D1} \left( \frac{g_{m1} + g_{m2} + g_{m3}}{g_{m2} + g_{m3}} \right) \right)}$$

$$\omega_{pB} = \frac{g_{m3} + g_{m2}}{\left( C_A + C_{D1} \left( \frac{g_{m1} + g_{m2} + g_{m3}}{g_{m1}} \right) \right)}$$

$$\omega_{pout} = \frac{1}{R_D (C_{DB2} + C_{D2})}$$

Where  $C_A = C_{as3} + C_{sB3} + C_{as2} + C_{sB2} + C_{DB1}$

52)

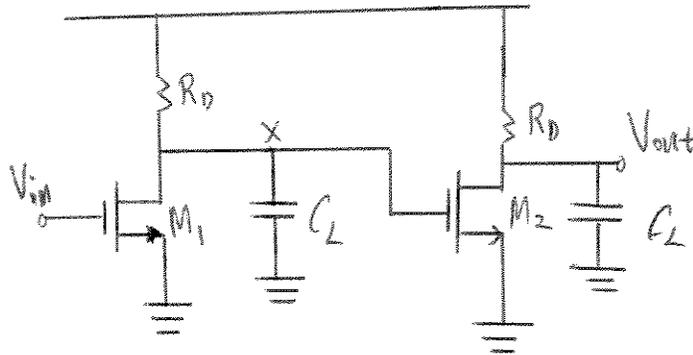

Bias Current = 1mA (each stage)

$$C_L = 50 \text{ fF}$$

$\mu_n C_{ox} = 100 \mu\text{A/V}^2$ ,  $A_V = 20$ , -3dB: 1GHz

DC gain:  $(g_m R_D)^2 = 20$

-3dB bandwidth:  $0.10243 / (R_D C_L) = 1 \text{ GHz}$

Since  $C_L = 50 \text{ fF}$ ,  $R_D = 2048.6 \Omega$

$$(g_m R_D)^2 = 20 \Rightarrow g_m = 0.002183 = \frac{2I_D}{V_{eff}} \Rightarrow V_{eff} = 0.916 \text{ V}$$


$$V_{eff} = V_{GS} - V_{th} = 0.916 \text{ V}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{eff}) \Rightarrow \frac{W}{L} = \frac{g_m}{\mu_n C_{ox} (V_{eff})} = 23.83$$

So  $R_D = 2.05 \text{ K}$ ,  $C_L = 50 \text{ fF}$

$V_{GS} - V_{th} = 0.916 \text{ V}$ ,  $W/L = 23.83$

53)

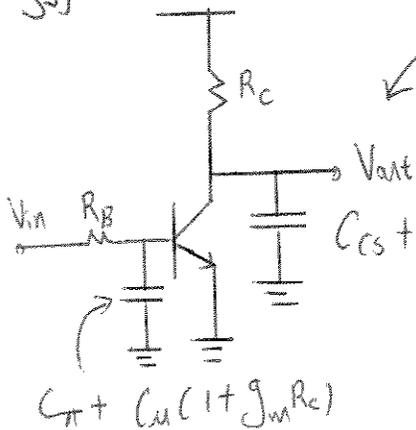

After apply Miller's theorem

$$\omega_{pin} = (2\pi)(500\text{MHz})$$

$$\omega_{pout} = (2\pi)(2\text{G})$$

$$I_c = 1\text{mA}, C_{\pi} = 2\text{pF},$$

$$C_u = 5\text{fF}, C_{cs} = 1\text{pF}$$

$$V_A = \infty$$

Low frequency Voltage gain: 
$$\frac{V_{out}}{V_{in}} = \frac{-R_c}{\frac{1}{g_m} + \frac{R_B}{\beta + 1}}$$

$$\omega_{pin} = \frac{1}{(R_B // r_{\pi})(C_{\pi} + C_u(1 + g_m R_c))} = (2\pi)(500\text{MHz})$$

$$\omega_{pout} = \frac{1}{R_c [C_{cs} + (1 + 1/(g_m R_c))C_u]} = (2\pi)(2\text{G})$$

$$\Rightarrow g_m = 2\pi(2\text{G}) [g_m R_c C_{cs} + g_m R_c C_u + C_u]$$

$$\Rightarrow R_c = \left( \frac{g_m}{(2\pi)(2\text{G})} - C_u \right) / (g_m (C_{cs} + C_u))$$

$$g_m = \frac{I_c}{V_T} = 0.0386 \frac{1}{\Omega}, R_c = 5296.53 \Omega$$

53)

In order to maximize low frequency gain  $V_{out}/V_{in}$ ,  $R_B$  should be as small as possible (restricted by the input pole location). So  $R_B \approx R_{in} \approx R_B$ .

$$\omega_{pin} \approx \frac{1}{R_B (C_{in} + C_u (1 + g_m R_c))} = (2\pi \times 500 \times 10^6)$$

$$g_m R_c = 204.446$$


$$R_B = \frac{1}{\omega_{pin} (C_{in} + C_u (1 + g_m R_c))} \approx 303.95 \Omega$$

So

$$R_B = 303.95 \Omega$$

$$R_c = 5296.53 \Omega$$

54)

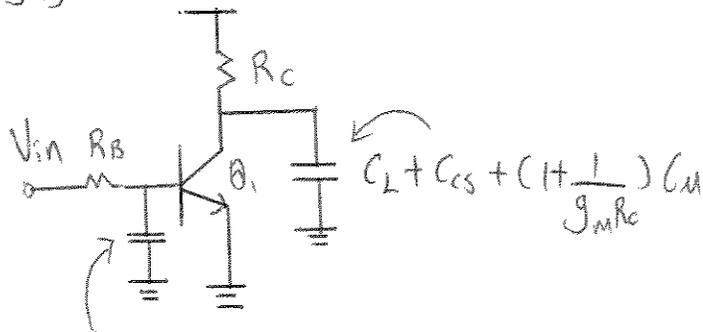

$$C_{\pi} + (1 + g_m R_c) C_M$$

Low freq Voltage gain: 
$$\frac{V_{out}}{V_{in}} = \frac{-R_c}{\frac{1}{g_m} + \frac{R_B}{\beta + 1}}$$

$$\omega_{pout} = \frac{1}{R_c [C_L + C_{CS} + (1 + \frac{1}{g_m R_c}) C_M]} = (2\pi)(2 \text{ GHz})$$

$$g_m = \frac{I_c}{V_T} = 0.0386 \frac{1}{\Omega}$$

$$g_m = (2\pi)(2 \text{ GHz}) [g_m R_c [C_L + C_{CS}] + g_m R_c (C_M + C_{\pi})]$$

$$R_c = \left[ \frac{g_m}{(2\pi)(2 \text{ GHz})} - C_M \right] / (g_m [C_L + C_{CS} + C_{\pi}])$$

$$R_c = 2269.94 \Omega \approx 2.27 \text{ K}\Omega$$


Again, to maximize low freq gain,  $R_B$  should be as small as possible, so  $R_B / (\beta + 1) \approx R_B$

$$\omega_{pin} \approx \frac{1}{R_B (C_{\pi} + C_M (1 + g_m R_c))} = (2\pi)(500 \times 10^6), g_m R_c = 87.62$$

$$R_B = 687.35 \Omega$$

So,  $R_c = 2.27 \text{ K}\Omega, R_B = 687.35 \Omega$

55)

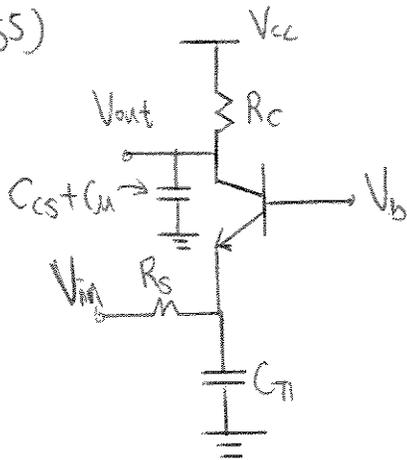

$$V_A = \infty, I_C = 1 \text{ mA}, R_S = 50 \Omega,$$

$$C_{\pi} = 20 \text{ fF}, C_{cs} = 20 \text{ fF}, C_u = 5 \text{ fF}$$

$$-3 \text{ dB bandwidth} = 10 \text{ GHz}$$

Since the output node sees a larger capacitance and resistance than the input, ( $R_C$  usually large for large gain), dominant pole and thus  $-3 \text{ dB}$  bandwidth occurs at the output.


$$\omega_{\text{pout}} = \frac{1}{R_C [C_u + C_{cs}]} = (2\pi)(10 \text{ GHz})$$

$$R_C = 636.62 \Omega, \quad \frac{1}{g_m} = \frac{25.9 \text{ mV}}{1 \text{ mA}}$$

$$\text{Maximum achievable gain} = \frac{R_C}{R_S + \frac{1}{g_m}} = 8.4$$

Here we have a tradeoff between gain and bandwidth.

36)

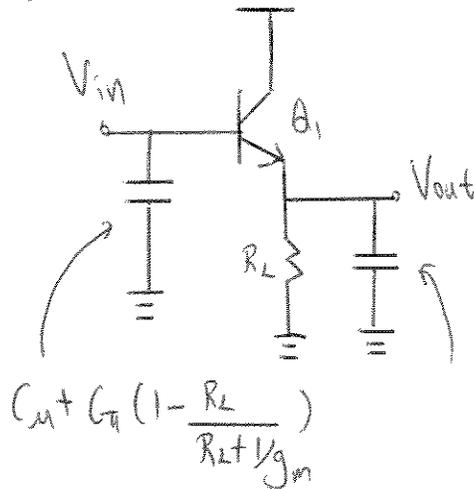

$$\text{DC gain: } \frac{R_L}{R_L + 1/g_m}$$

$$V_A = \infty$$

$$C_u = 10 \text{ fF}, C_{\pi} = 100 \text{ fF}$$

$$C_{\pi} \left( 1 - \frac{R_L + 1/g_m}{R_L} \right)$$

$$C_u + C_{\pi} \left( 1 - \frac{R_L}{R_L + 1/g_m} \right)$$

$$C_{in} < 50 \text{ fF} \Rightarrow C_u + C_{\pi} \left( 1 - \frac{R_L}{R_L + 1/g_m} \right) < 50 \text{ fF}$$


$$10 \text{ fF} + 100 \text{ fF} \left( 1 - \frac{R_L}{R_L + 1/g_m} \right) < 50 \text{ fF}$$

$$100 \text{ fF} \left( 1 - \frac{R_L}{R_L + 1/g_m} \right) < 40 \text{ fF}$$

$$\left( \frac{1/g_m}{R_L + 1/g_m} \right) < 0.4$$

$$R_L > \frac{3}{2g_m} = 38.85 \Omega$$

57)

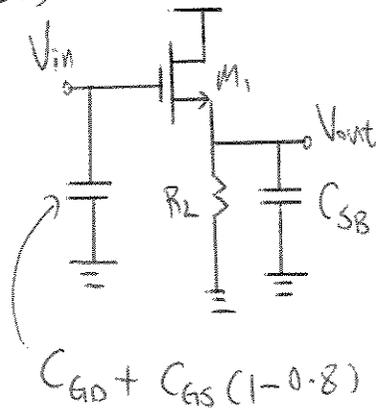

$$R_L = 100\Omega, \quad I_D = 1\text{mA}$$

$$A_V = \frac{V_{out}}{V_{in}} = 0.8 \quad \mu_n C_{ox} = 100 \mu\text{A/V}^2$$

$$L = 0.18 \mu\text{m}, \quad \lambda = 0, \quad C_{GD} \approx 0,$$

$$C_{SB} \approx 0, \quad C_{GS} = \left(\frac{2}{3}\right) WL C_{ox}$$

$$C_{ox} = 12 \text{ fF}/\mu\text{m}^2$$

$$C_{in} = C_{GD} + C_{GS}(0.2), \quad C_{in} = C_{GS}(0.2) = C_{in, \min}$$


$$A_V = \frac{R_L}{R_L + 1/g_m} = 0.8, \quad \frac{1}{g_m} = 25 = \frac{V_{eff}}{2I_D}$$

$$V_{eff} = 50 \text{ mV}, \quad I_D = \frac{1}{2} \frac{W}{L} \mu_n C_{ox} (V_{eff})^2 \Rightarrow W = 1440$$

$$C_{in, \min} = 0.2 C_{GS} = 0.2 \left(\frac{2}{3}\right) WL C_{ox} = 414.72 \text{ fF}$$

$$\text{or } C_{in, \min} = 0.415 \text{ pF}$$

58)

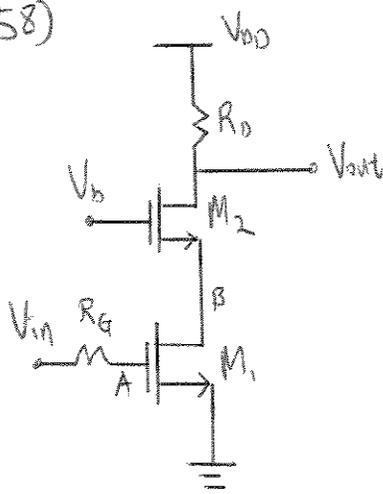

$$\begin{aligned} \omega_{pin} &= 5 \text{ GHz}, \quad \omega_{pout} = 10 \text{ GHz} \\ V_{eff} &= 200 \text{ mV} (V_{GS} - V_{th}), \quad I_D = 0.5 \text{ mA} \\ \lambda &= 0, \quad C_{GS} = (2/3) W L C_{ox}, \\ L &= 0.18 \mu\text{m}, \quad \mu_n C_{ox} = 100 \mu\text{A/V}^2 \\ C_{GD} &= W C_o, \quad C_o = 0.2 \text{ fF}/\mu\text{m} \\ C_{ox} &= 12 \text{ fF}/\mu\text{m}^2 \end{aligned}$$

$$\text{DC gain from A to B: } -\frac{g_{m1}}{g_{m2}} = 1$$

$$C_{in} = C_{GS} + C_{GD} (1 + g_{m1}/g_{m2}) = C_{GS} + 2 C_{GD}$$

$$I_D = \frac{1}{2} \frac{W}{L} \mu_n C_{ox} (V_{eff})^2 = 0.5 \text{ mA} \Rightarrow \frac{W}{L} = 250$$

$$L = 0.18 \mu\text{m}, \quad W = 45 \mu\text{m}$$

$$\omega_{pin} = (2\pi)(5 \times 10^9) = \frac{1}{R_D \left[ \frac{2}{3} (45)(0.18)(12 \text{ fF}/\mu\text{m}^2) + (0.2)(45)(2) \right]}$$

$$R_D = 384.43 \Omega$$

$$\omega_{pout} = \frac{1}{R_D [0.2 W]} = (10 \times 10^9)(2\pi), \quad W = 45 \mu\text{m}$$

$$\Rightarrow R_D = 1.8 \text{ k}\Omega \quad (1768.4 \Omega) \text{ exact value}$$

$$\text{Gain} = |g_m R_D| = \frac{2 I_D R_D}{V_{eff}} = 8.842$$

59)

$$W_2 = 4W_1, \quad V_{eff2} = \frac{V_{eff1}}{2} \quad (\text{To maintain the current constant})$$

$$V_{eff1} = 200 \text{ mV}, \quad V_{eff2} = 100 \text{ mV} \quad (\text{Assume } V_{eff1} \text{ is not changed})$$

$$\text{DC gain: } -\frac{g_{m1}}{g_{m2}} = -\frac{g_{m1}}{2g_{m1}} = -\frac{1}{2}$$

$$\omega_{pin} = \frac{1}{R_G \left[ \frac{2}{3} W L (C_x + (0.2) W \left( \frac{1}{2} \right) \right]} = (5 \times 10^9) (2\pi)$$


$$W = 45 \mu\text{m}$$

$$\Rightarrow R_G = 459.32 \Omega$$

$$R_0 = \frac{1}{(10 \times 10^9) (2\pi) (0.2) (4) (45)} = 442.097 \Omega$$

$$\text{DC gain: } |g_{m1} R_0| = \frac{2I_D R_0}{V_{eff1}} = 2.2105$$

1. (a)

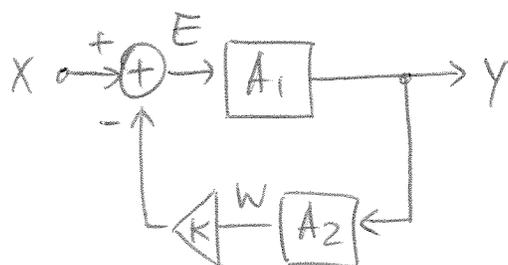


$$Y = A_1 E_1$$

$$= A_1 [X - Y A_2 k]$$

$$\Rightarrow \frac{Y}{X} = \frac{A_1}{1 + k A_1 A_2}$$

(b)

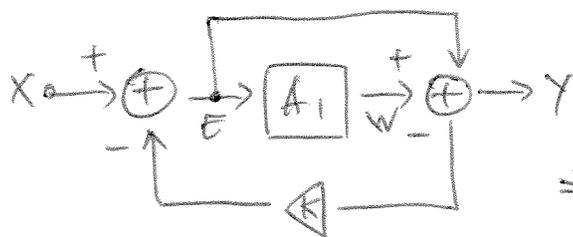


$$Y = E - A_1 W$$

$$= (X - kY) - A_1 (X - kY)$$

$$\Rightarrow \frac{Y}{X} = \frac{1 - A_1}{1 + (1 - A_1)k}$$

(c)

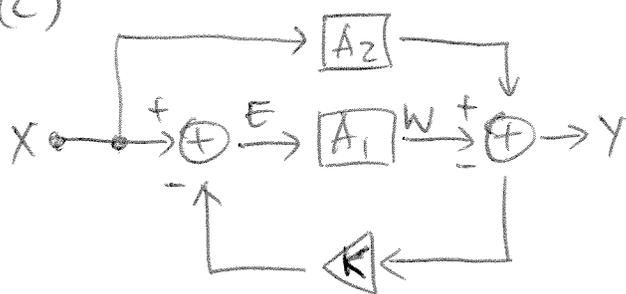


$$Y = X A_2 - W$$

$$= X A_2 - A_1 (X - Y k)$$

$$\Rightarrow \frac{Y}{X} = \frac{A_2 - A_1}{1 - A_1 k}$$

(d)

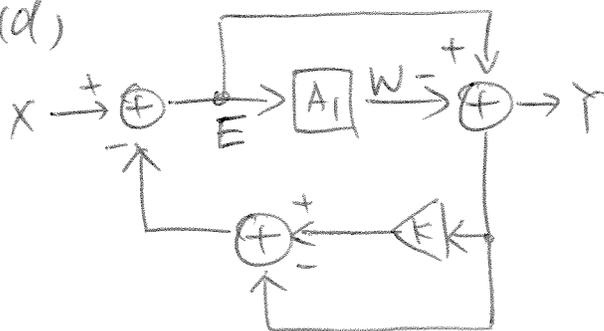

$$Y = E - W$$

$$= (X - (kY - Y)) - A_1 [X - (kY - Y)]$$

$$\Rightarrow \frac{Y}{X} = \frac{(1 - A_1)}{1 + (k - 1)(1 - A_1)}$$

$$2. \quad (a) \quad W = A_2 Y = A_2 [(X - kW)A_1]$$

$$\Rightarrow \frac{W}{X} = \frac{A_1 A_2}{1 + A_1 A_2 k}$$

$$(b) \quad W = A_1 X E = A_1 [X - k(\frac{W}{A_1} - W)]$$

$$\Rightarrow \frac{W}{X} = \frac{A_1}{1 + k(1 - A_1)}$$

$$(c) \quad W = A_1 E = A_1 [X - (A_2 X - W)k]$$

$$\Rightarrow \frac{W}{X} = \frac{A_1 (1 - A_2 k)}{(1 - A_1 k)}$$

$$(d) \quad W = A_1 E = A_1 [X - \left\{ \left( \frac{W}{A_1} - W \right) k - \left( \frac{W}{A_1} - W \right) \right\}]$$

$$\Rightarrow \frac{W}{X} = \frac{A_1}{1 + (k-1)(1-A_1)}$$

$$3. (a) E = X - KA_2A_1E$$
$$\Rightarrow \frac{E}{X} = \frac{1}{1 + KA_2A_1}$$

$$(b) E = X - K[E - A_1E]$$

$$\Rightarrow \frac{E}{X} = \frac{1}{1 + K(1 - A_1)}$$

$$(c) E = X - K[A_2X - A_1E]$$


$$\Rightarrow \frac{E}{X} = \frac{1 - A_2K}{1 - A_1K}$$

$$(d) E = X - \{K[E - A_1E] - [E - A_1E]\}$$

$$\Rightarrow \frac{E}{X} = \frac{1}{1 + (K-1)(1-A_1)}$$

4.

(a)

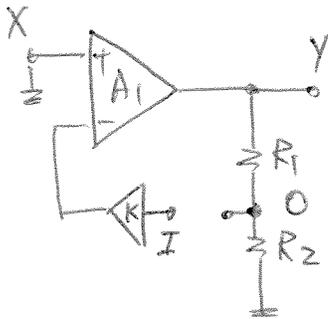


(X is grounded  
in loop-gain calculation)

$$0 = Y \frac{R_2}{R_1 + R_2} = (-IK)A_1 \left( \frac{R_2}{R_1 + R_2} \right)$$

$$\Rightarrow -\frac{0}{I} = \text{Loop Gain} = +KA_1 \left( \frac{R_2}{R_1 + R_2} \right)$$

(b)

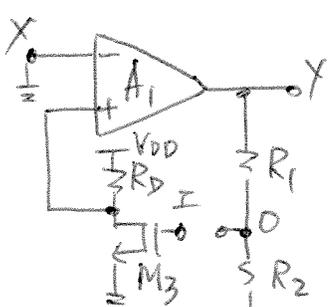


(X is grounded)

$$0 = Y \left( \frac{R_2}{R_1 + R_2} \right) = -I g_{m3} R_D A_1 \left( \frac{R_2}{R_1 + R_2} \right)$$

$$\Rightarrow -\frac{0}{I} = \text{Loop Gain} = +g_{m3} R_D A_1 \left( \frac{R_2}{R_1 + R_2} \right)$$

(c)

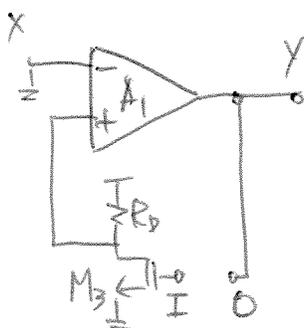


(X is grounded)

$$0 = Y = -I g_{m3} R_D A_1$$

$$\Rightarrow -\frac{0}{I} = \text{Loop Gain} = +g_{m3} R_D A_1$$

(d)

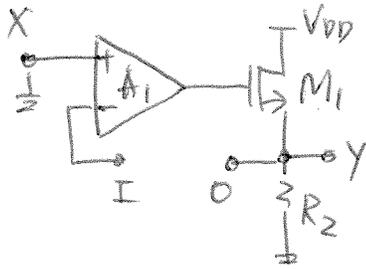

(X is grounded)

$$0 = Y = -I \times \frac{g_{m1} R_2}{1 + g_{m1} R_2} \times A_1$$

$$\Rightarrow -\frac{0}{I} = \text{Loop Gain}$$
$$= + A_1 \frac{g_{m1} R_2}{1 + g_{m1} R_2}$$

5. (a)  $\frac{Y}{X} = \frac{A_{o.l.}}{1 + \text{Loop Gain}} = \frac{A_1}{1 + A_1 K \left( \frac{R_2}{R_1 + R_2} \right)}$

(b)  $\frac{Y}{X} = \frac{A_1}{1 + g_{m3} R_D A_1 \left( \frac{R_2}{R_1 + R_2} \right)}$

(c)  $\frac{Y}{X} = \frac{A_1}{1 + g_{m3} R_D A_1}$

(d)  $\frac{Y}{X} = \frac{A_1}{1 + A_1 \left( \frac{g_{m1} R_2}{1 + g_{m1} R_2} \right)}$

b.  $A_1 = 500$   
 $R_1/R_2 = 7$


$$\frac{Y}{X} \approx 1 + \frac{R_1}{R_2} = 8$$

$$\Rightarrow \frac{R_2}{R_1 + R_2} = \frac{1}{8} = K$$

$$E = \frac{X}{1 + KA_1} = \frac{2 \text{ mV}}{1 + 500/8} \approx 0.031 \text{ mV}$$

$\therefore$  Amplitude of feedback waveform  
 $= X - E \approx 1.969 \text{ mV}$

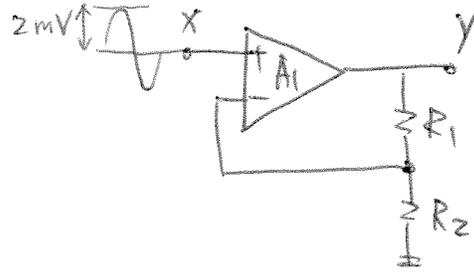Amplitude of output waveform  
 $= X \frac{A_1}{1 + KA_1} \approx 15.75 \text{ mV}$



$$1. \quad A_{CL} = \frac{A_1}{1+A_1K}$$

$$\frac{dA_{CL}}{dA_1} = \frac{1}{(1+A_1K)^2} \Rightarrow dA_{CL} = \frac{dA_1}{(1+A_1K)^2}$$

$$\begin{aligned} \Rightarrow \frac{dA_{CL}}{A_{CL}} &= \frac{dA_{CL}}{\left(\frac{A_1}{1+A_1K}\right)} = dA_1 \left(\frac{1+A_1K}{A_1}\right) \left(\frac{1}{(1+A_1K)^2}\right) \\ &= \frac{(dA_1/A_1)}{(1+A_1K)} \end{aligned}$$

This equation implies that for a fractional change in  $A_{CL}$ , it is reduced by  $(1+A_1K)$  compared to a fractional change in  $A_1$ .

$$\Rightarrow 0.01 > \frac{0.2}{1+A_1K} \Rightarrow A_1K > 19$$

$$8. A_{OL} = -g_m r_{o1} \quad (\text{max gain})$$

$$= -\frac{2}{\lambda V_{eff}}$$

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL}K}$$

$$\frac{dA_{CL}}{d\lambda} = \frac{d}{d\lambda} \left( \frac{A_{OL}}{1 + A_{OL}K} \right) = \frac{\frac{2}{\lambda^2 V_{eff}}}{(1 + A_{OL}K)^2} = \frac{-A_{OL} \times \frac{1}{\lambda}}{(1 + A_{OL}K)^2}$$

$$\Rightarrow \frac{dA_{CL}}{A_{CL}} = \frac{-A_{OL} \times \frac{d\lambda}{\lambda}}{(1 + A_{OL}K)^2} \times \frac{(1 + A_{OL}K)}{A_{OL}} = \frac{-\frac{d\lambda}{\lambda}}{(1 + A_{OL}K)}$$

⇒ This implies a change in  $\lambda$  ( $\frac{d\lambda}{\lambda}$ ) leads to a change in  $A_{CL}$  ( $\frac{dA_{CL}}{A_{CL}} = \frac{d\lambda}{\lambda} \cdot \frac{1}{(1 + \text{Loop Gain})}$ ) in the opposite direction (i.e. the sign)

$$590 > \frac{20\%}{1 + A_{OL}K} \Rightarrow \text{Loop Gain} = A_{OL}K > 3$$

9. From the question,

$$(1-10\%)A_0 = |A(j\omega')| \quad \text{where } \omega' = \text{-1-dB bandwidth frequency}$$

$$0.9A_0 = \frac{A_0}{|1+j\frac{\omega'}{\omega_0}|} = \frac{A_0}{\sqrt{1+(\frac{\omega'}{\omega_0})^2}}$$

$$\Rightarrow \omega' \cong 0.48\omega_0$$

$\Rightarrow$  This is the open-loop -1dB bandwidth.

Similarly,

$$0.9 \frac{A_0}{1+L.G.} = \left| \frac{Y}{X}(j\omega'') \right| \quad \text{where } \omega'' = \text{-1dB bandwidth frequency}$$



$$0.9 \frac{A_0}{1+L.G.} = \frac{\frac{A_0}{1+L.G.}}{\left| 1 + j \frac{\omega''}{\omega_0(1+L.G.)} \right|} = \frac{\frac{A_0}{1+L.G.}}{\sqrt{1 + \left[ \frac{\omega''}{\omega_0(1+L.G.)} \right]^2}}$$

L.G. = Loop Gain

$$\Rightarrow \omega'' \cong 0.48\omega_0(1+L.G.)$$

$\therefore$  -1dB bandwidth is boosted (expected) by  $(1+L.G.)$  in closed-loop measurement.

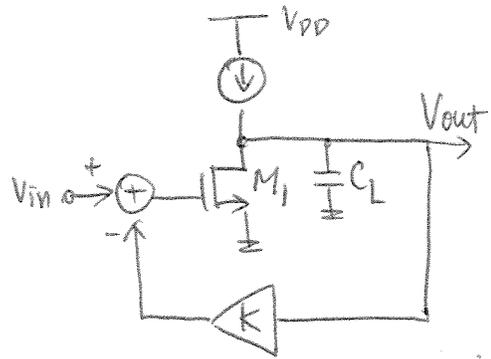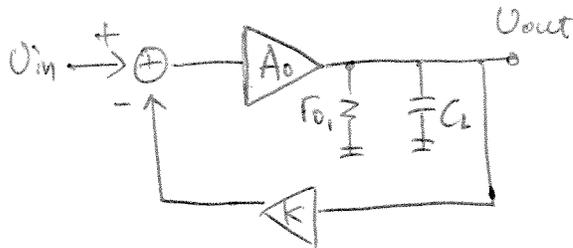10. An equivalent circuit is shown below:



Open-loop transfer function (without feedback):

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_p}} = \frac{-g_{m1} r_{o1}}{1 + \frac{s}{r_{o1} C_L}}$$

$$\text{Loop Gain} = A_0 k = g_{m1} r_{o1} k$$

⇒ Closed-loop -3dB bandwidth


$$= B = (r_{o1} C_L)(1 + A_0 k) = r_{o1} C_L (1 + g_{m1} r_{o1} k)$$

$$\therefore k = \left( \frac{B}{r_{o1} C_L} - 1 \right) \times \frac{1}{g_{m1} r_{o1}}$$

11.

## Feedforward System

$M_1$  &  $R_D$  (common-gate stage)

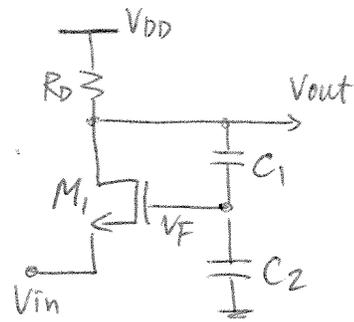

## Sense Mechanism (Feedback):

$C_1 + C_2$  (capacitive divider)

$$\Rightarrow V_F = \frac{C_1}{C_2 + C_1} \times V_{out}$$

Comparison Mechanism:  $M_1$  itself.

$$\text{Open-loop gain} = A_o = g_m R_D$$

$$\begin{aligned} \text{Closed-loop gain} &= \frac{V_{out}}{V_{in}} = \frac{A_o}{1 + K A_o} \\ &= \frac{g_m R_D}{1 + \frac{C_1}{C_1 + C_2} g_m R_D} \end{aligned}$$

$$\text{Open-loop } r_{in} = \frac{1}{g_m}$$


$$r_{out} = R_D$$

$$\begin{aligned} \text{Closed-loop } r_{in} &= r_{in,ol} \times (1 + K A_o) \\ &= \frac{1}{g_m} \left( 1 + \frac{C_1}{C_1 + C_2} g_m R_D \right) \end{aligned}$$

$$r_{out} = \frac{r_{out,ol}}{(1 + K A_o)} = \frac{R_D}{1 + \frac{C_1}{C_1 + C_2} g_m R_D}$$

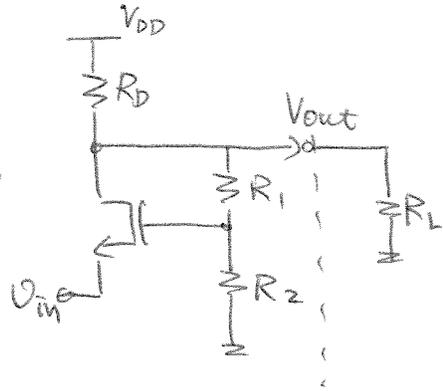12.

Given:  $\frac{\text{Gain}_{\text{loaded}} - \text{Gain}_{\text{loaded}}}{\text{Gain}_{\text{unloaded}}} = 10\%$   
 $= 0.1$



$$\text{Gain}_{\text{unloaded}} \cong \frac{g_m R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D} \quad (\text{assume } R_1 + R_2 \gg R_D)$$

$$\text{Gain}_{\text{loaded}} = \frac{g_m (R_D \parallel R_L)}{1 + \frac{R_2}{R_1 + R_2} g_m (R_D \parallel R_L)}$$

$$\therefore 0.1 = \frac{\frac{g_m R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D} - \frac{g_m (R_D \parallel R_L)}{1 + \frac{R_2}{R_1 + R_2} g_m (R_D \parallel R_L)}}{\frac{g_m R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D}}$$

After solving for  $R_L$ :

$$R_L = \frac{g_m R_D}{1 + \left(\frac{R_2}{R_1 + R_2}\right) g_m R_D}$$

$$13. \text{ Gain at } x_1 = \frac{500}{1+500K}$$

$$\text{Gain at } x_2 = \frac{420}{1+420K}$$

$$\Rightarrow \frac{\frac{500}{1+500K} - \frac{420}{1+420K}}{\frac{500}{1+500K}} < 0.05$$

$$\Rightarrow K > \frac{11}{2100}$$

$$A_{x_1} = \frac{500}{1+500(K)} = \frac{2625}{19} \approx 138.16$$

$$A_{x_2} = \frac{420}{1+420(K)} = \frac{525}{4} \approx 131.25$$

$$14. \quad y = \alpha_1 x - \alpha_3 x^3$$

$$(a) \quad \frac{\partial y}{\partial x} = \alpha_1 - 3\alpha_3 x^2$$

$$\left. \frac{\partial y}{\partial x} \right|_{x=0} = \alpha_1$$




$$\left. \frac{\partial y}{\partial x} \right|_{x=\Delta x} = \alpha_1 \quad (\text{around } x=0)$$

$$(b) \quad \text{Closed-loop } \left. \right|_{x=0} = \frac{\alpha_1}{1 + \alpha_1 k}$$




$$\text{Closed-loop } \left. \right|_{x=\Delta x} = \frac{\alpha_1}{1 + \alpha_1 k} \quad (\text{around } x=0)$$

15.




(a)

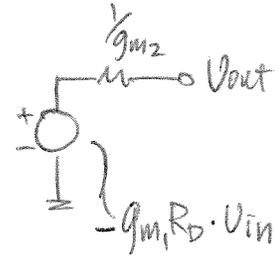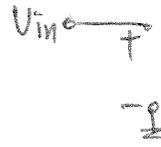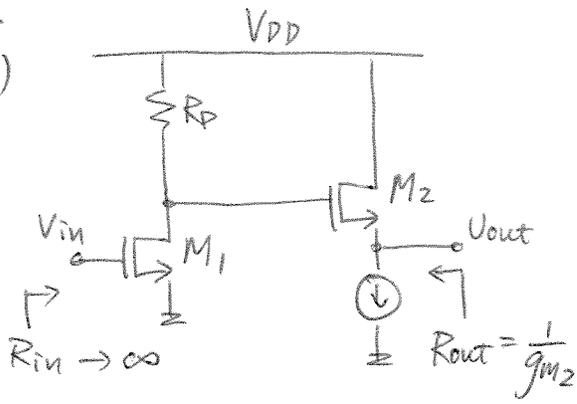




(b)

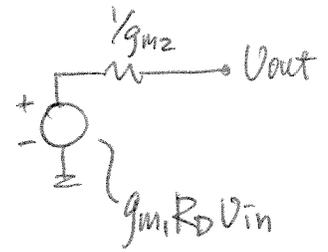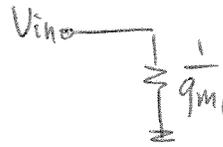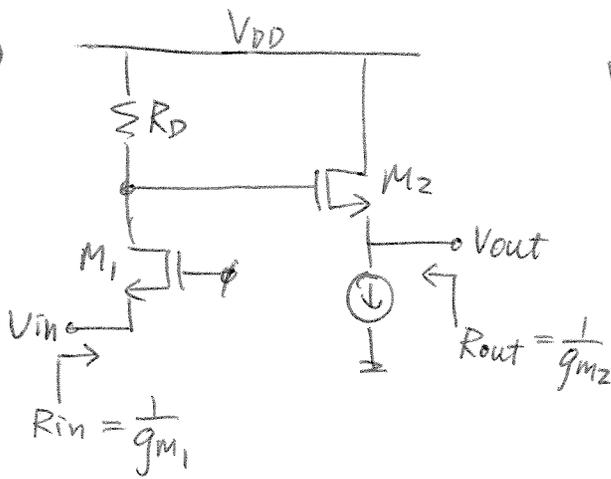

(c)

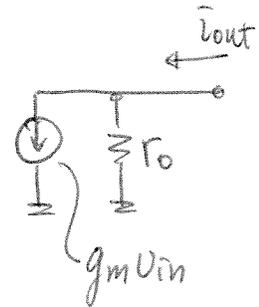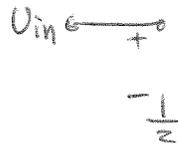
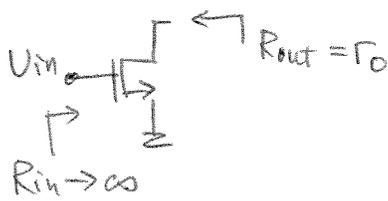


(d)

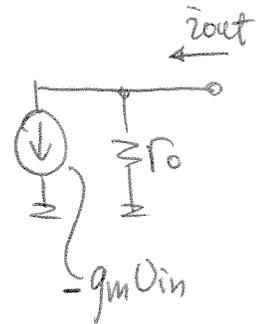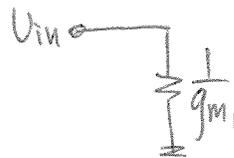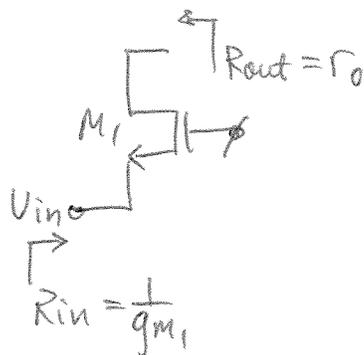


16.

$\lambda > 0$

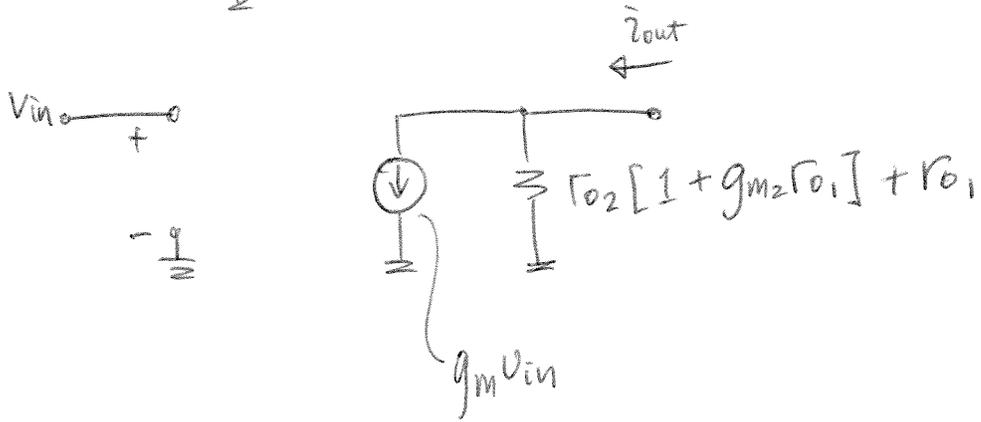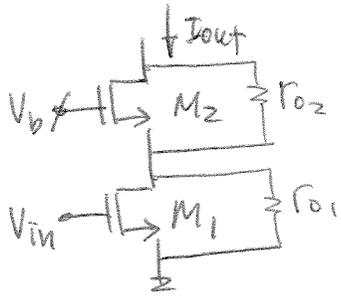

17.

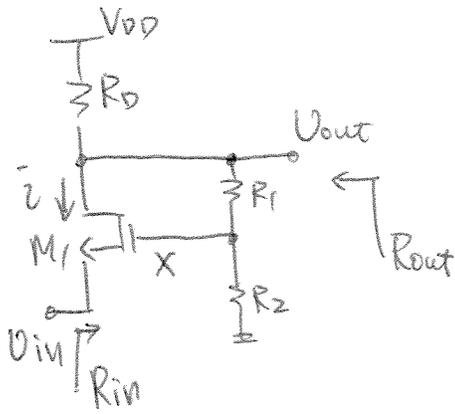


$$-V_{out} = \bar{i} [R_D \parallel (R_1 + R_2)]$$

$$\bar{i} = g_{m1}(V_x - V_{in}) = g_{m1} \left( V_{out} \times \frac{R_2}{R_1 + R_2} - V_{in} \right)$$

Combining the equations above yields:

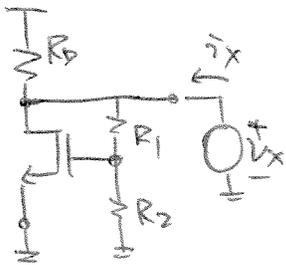
$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} [R_D \parallel (R_1 + R_2)]}{1 + \frac{R_2}{R_1 + R_2} g_{m1} [R_D \parallel (R_1 + R_2)]} \triangleq A_v$$



By KCL,

$$\bar{i}_x = \frac{V_x}{R_1 + R_2} + \frac{V_x}{R_D} + g_{m1} \left( V_x \frac{R_2}{R_1 + R_2} \right)$$
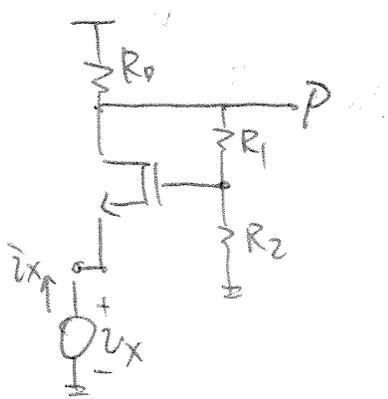
$$\Rightarrow \frac{V_x}{\bar{i}_x} = R_{out} = [(R_1 + R_2) \parallel R_D] \left[ 1 + g_{m1} \frac{R_2}{R_1 + R_2} (R_D \parallel (R_1 + R_2)) \right]$$



By KCL,

$$\bar{i}_x = g_{m1} \left( v_x - v_p \frac{R_2}{R_1 + R_2} \right)$$



$$\Rightarrow v_p = \left( v_x - \frac{\bar{i}_x}{g_{m1}} \right) \left( \frac{R_1 + R_2}{R_2} \right) \quad \text{--- (1)}$$

$$\bar{i}_x = \frac{v_p}{R_0 \parallel (R_1 + R_2)} \quad \text{--- (2)}$$

Substitute (1) into (2) & solve for  $\frac{v_x}{\bar{i}_x}$ :


$$\frac{v_x}{\bar{i}_x} = R_{in} = \frac{1}{g_{m1}} \left[ 1 + g_{m1} \left\{ R_0 \parallel (R_1 + R_2) \right\} \frac{R_2}{R_1 + R_2} \right]$$

Model:

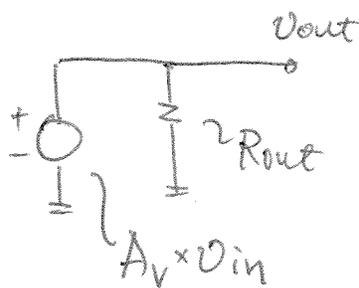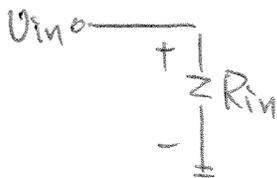

18. (a) Sense Mechanism : Current from  $M_3$   
Return Mechanism : Voltage to Gate of  $M_2$ .
- (b) Sense Mechanism : Voltage output ( $M_3$ )  
Return Mechanism : Voltage to Gate of  $M_2$ .
- (c) Sense Mechanism : Current from  $M_3$   
Return Mechanism : Voltage to Gate of  $M_2$ .
- (d) Sense Mechanism : Current from  $M_3$   
Return Mechanism : Voltage to Gate of  $M_2$ .
- (e) Sense Mechanism : Voltage Divider ( $\frac{R_2}{R_1+R_2}$ )  
Return Mechanism : Voltage to Gate of  $M_2$ .
- (f) Sense Mechanism : From Common Source of  $M_3$   
Return Mechanism : Voltage to Gate of  $M_2$ .

19. (a)

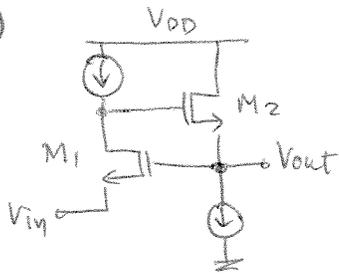


Sense Mechanism:

Voltage sensing at  $V_{out}$ .

Return Mechanism:

Voltage to Gate of  $M_1$ .

(b)

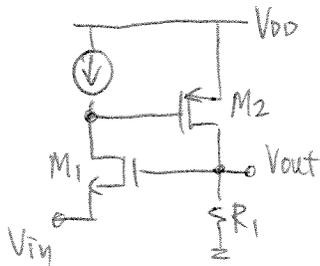


Sense Mechanism:

Voltage output from  $M_2$ .

Return Mechanism:

Voltage to Gate of  $M_1$ .

(c)

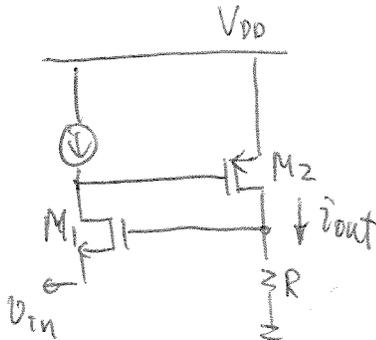


Sense Mechanism:

$R_1$

Return Mechanism:

Voltage to Gate of  $M_1$ .

(d)

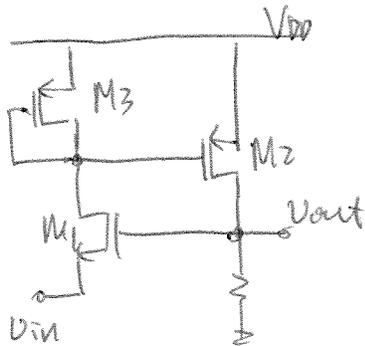

Sense Mechanism:


Voltage output of  $M_2$

Return Mechanism:

Voltage to Gate of  $M_1$

20.

(a)

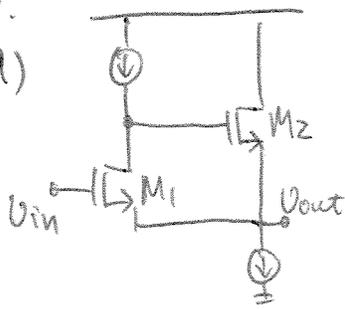


Sense Mechanism:

Voltage output of  $M_2$

Return Mechanism:

Voltage to Source of  $M_1$

(b)

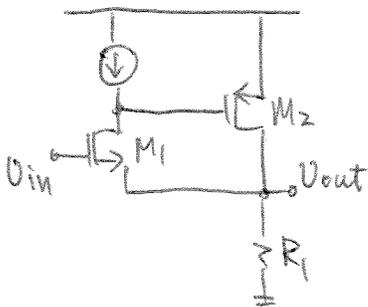


Sense Mechanism:

Voltage output of  $M_2$

Return Mechanism:

Voltage to Source of  $M_1$

(c)

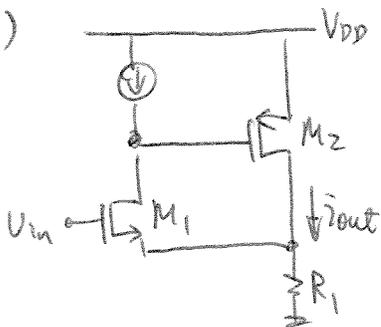


Sense Mechanism:

Current through  $R_1$ .

Return Mechanism:

$i_{out} \times R_1$  to Source of  $M_1$ .

(d)

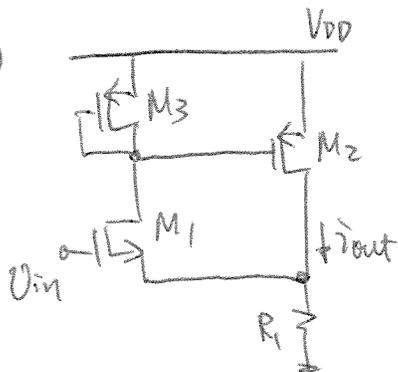

Sense Mechanism:

Current through  $R_1$ .

Return Mechanism:

$i_{out} \times R_1$  to Source of  $M_1$


21. (a)

Sense Mechanism:

Gate of  $M_2$  (Voltage)

Return Mechanism:

Current output of  $M_2$ .

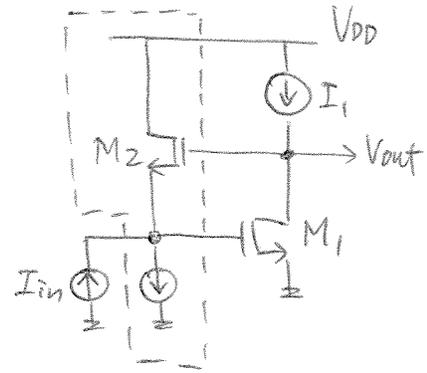


(b)

Sense Mechanism:

Gate of  $M_2$  (Voltage)

Return Mechanism:

Current output of  $M_2$ .

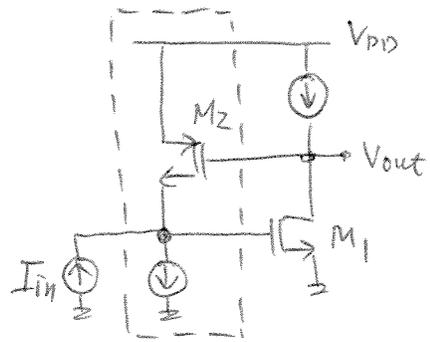


(c)

Sense Mechanism:

Source of  $M_2$  (Voltage)

Return Mechanism:

Current output of  $M_2$

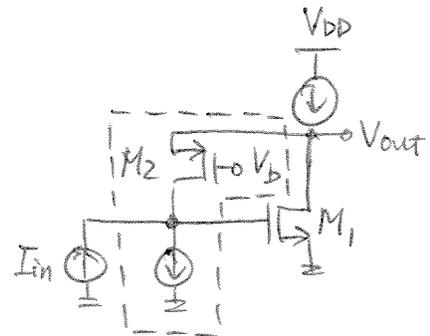


(d) Sense Mechanism:

Gate of  $M_2$  (Voltage)

Return Mechanism:

Current output of  $M_2$

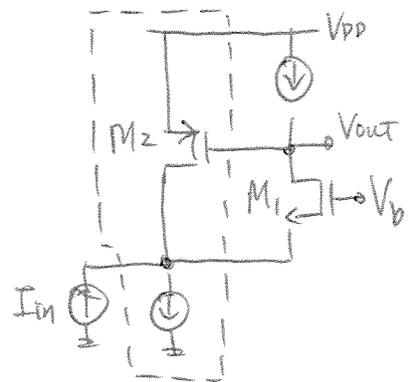


22.

(a) Sense Mechanism:


Resistor ( $R_F$ ) - Voltage

Return Mechanism:

Current through  $R_F$ .

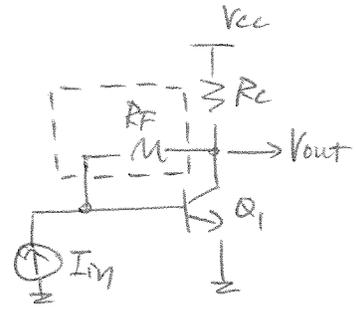

(b)

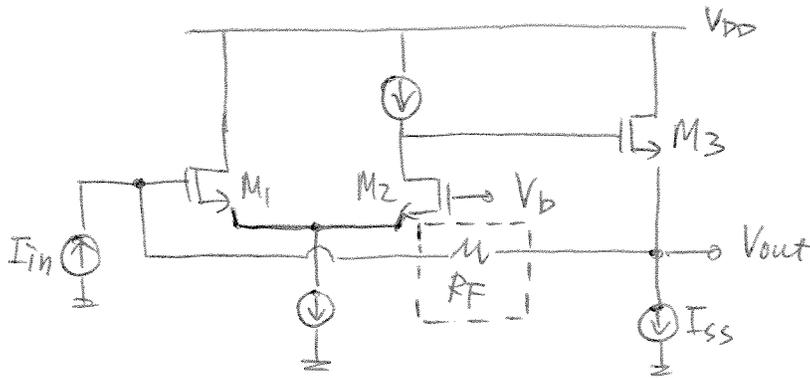


Sense Mechanism:

Resistor ( $R_F$ ) - Voltage

Return Mechanism:

Current through  $R_F$

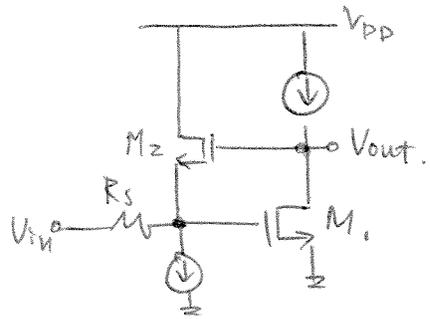23. First, recognize that  
 (a) both input & output  
 are voltages.



\*  $V_{in}$  primarily drives the  
 Gate of  $M_1$ .

Sequence: Suppose  $V_{in}$  increases by  $\Delta V_{in}$

$\Rightarrow V_{out}$  drops by  $+g_{m1} \Delta V_{in} \times r_{o1}$  (Common-  
 Source)

$\Rightarrow$  Source of  $M_2$  decreases by same  
 amount (Source follower)

$\therefore V_{in} \uparrow \Rightarrow V_{M_2, D} \downarrow \Rightarrow V_{M_1, G} \downarrow$   
 $\Rightarrow$  effective  $V_{in}$  driving  $M_{1, G} \downarrow$

$\Rightarrow$  negative feedback

(b)  $V_{in} \uparrow \Rightarrow V_{out} \downarrow \Rightarrow V_{M_2, G} \uparrow$

$\Rightarrow$  effective  $V_{in}$  driving  $M_{1, G} \uparrow$

$\Rightarrow$  positive feedback.

(c)  $v_{in} \uparrow \Rightarrow v_{out} \downarrow \Rightarrow v_{M1, G} \downarrow$

$\Rightarrow$  effective  $v_{in}$  driving  $M1, G \downarrow$

$\Rightarrow$  negative feedback.


(d)  $v_{in} \uparrow \Rightarrow v_{out} \uparrow$  (common-base,  $M1$ )

$\Rightarrow v_{M1, S} \downarrow$

$\Rightarrow$  effective  $v_{in}$  driving  $M1, S \downarrow$

$\Rightarrow$  negative feedback.

24.

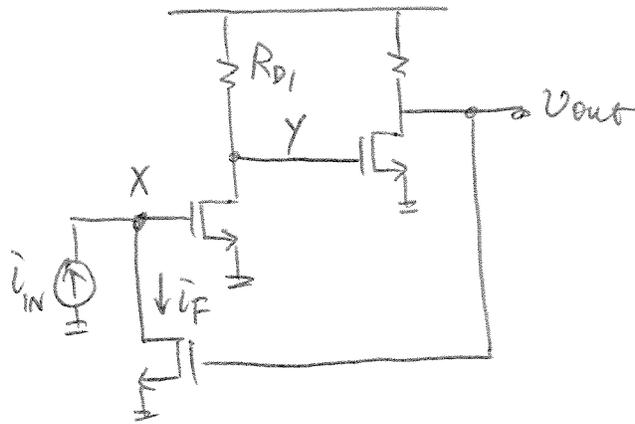

$i_{IN} \uparrow \Rightarrow v_X \uparrow \Rightarrow v_Y \downarrow \Rightarrow v_{out} \uparrow \Rightarrow i_F \uparrow$   
 $\Rightarrow$  effective  $v_X \downarrow$   
 $\Rightarrow$  negative feedback.

25.

Figure 12.79

↑ = increases by  
↓ = decreases by

(a)  $V_{in} \uparrow \Rightarrow V_{G,M3} \uparrow$

$\Rightarrow V_{out} \uparrow$  same amount (Emitter Follower)

$\Rightarrow$  effective  $V_{in} (V_{G,M1} - V_{G,M2}) \downarrow$

$\Rightarrow$  Negative feedback.

(b)  $V_{in} \uparrow \Rightarrow V_{G,M3} \uparrow$

$\Rightarrow V_{out} \uparrow$  by  $\Delta V_{G,M3} \times g_{m3} (\tau_{o3} \parallel R_1)$

$\Rightarrow$  effective  $V_{in} (V_{G,M1} - V_{G,M2}) \downarrow$

$\Rightarrow$  Negative feedback.

(c) Same as (b)

(d) Same as (a)

(e)  $V_{in} \uparrow \Rightarrow V_{out} \uparrow$

$\Rightarrow V_{G,M2} \uparrow$  by  $\Delta V_{out} \times \frac{R_2}{R_1 + R_2}$

$\Rightarrow$  effective  $V_{in} (V_{G,M1} - V_{G,M2}) \downarrow$

$\Rightarrow$  Negative feedback.

- (f)  $V_{in} \uparrow \Rightarrow V_{G,M_3} \uparrow$   
 $\Rightarrow V_{out} \uparrow$  (Common-Source Stage)  
 $\Rightarrow$  effective  $V_{in}$  ( $V_{G,M_1} - V_{G,M_2}$ )  $\downarrow$   
 $\Rightarrow$  Negative feedback.

Figure 12.80

- (a)  $V_{in} \uparrow \Rightarrow V_{G,M_2} \uparrow$  (Common-Gate)  
 $\Rightarrow V_{out} \uparrow$  (Source Follower)  
 $\Rightarrow$  effective  $V_{eff}$  ( $V_{in} - V_{out}$ )  $\downarrow$   
 $\Rightarrow$  Negative feedback.

- (b)  $V_{in} \uparrow \Rightarrow V_{G,M_2} \uparrow$  (Common-Gate)  
 $\Rightarrow V_{out} \uparrow$  (Common Source)  
 $\Rightarrow$  effective  $V_{eff}$  ( $V_{in} - V_{out}$ )  $\downarrow$   
 $\Rightarrow$  Negative feedback.

(c) Same as (b)

- (d)  $V_{in} \uparrow \Rightarrow V_{G,M_2} \uparrow$  (Common-Gate)  
 $\Rightarrow V_{out} \uparrow$  (Common Source)  
 $\Rightarrow$  effective  $V_{eff}$  ( $V_{in} - V_{out}$ )  $\downarrow$   
 $\Rightarrow$  Negative feedback.

Figure 12.81

(a)  $V_{in} \uparrow \Rightarrow V_{G, M_2} \downarrow$  (Common Source)

$\Rightarrow V_{out} \uparrow$  (Source Follower)

$\Rightarrow$  effective  $V_{in}$  ( $V_{in} - V_{out}$ )  $\uparrow$

$\Rightarrow$  Positive feedback.

(b)  $V_{in} \uparrow \Rightarrow V_{G, M_2} \downarrow$  (Common Source)

$\Rightarrow V_{out} \uparrow$  (Common Source)

$\Rightarrow$  effective  $V_{in}$  ( $V_{in} - V_{out}$ )  $\downarrow$

$\Rightarrow$  Negative feedback.

(c) Same as (b) ( $V_{out} = I_{out} \times R_1$ )

(d)  $V_{in} \uparrow \Rightarrow V_{G, M_2}$  (Common Source)

$\Rightarrow V_{out} \uparrow$  (Common Source)

$\Rightarrow$  effective  $V_{in}$  ( $V_{in} - V_{out}$ )  $\downarrow$

$\Rightarrow$  Negative feedback.

Figure 12.82

- (a)  $\bar{i}_{in} \uparrow \Delta \Rightarrow V_{out} \downarrow$  (Common Source,  
through current gain of  $M_1$ )  
 $\Rightarrow \bar{i}_{D,M_2} \downarrow$  (Source Follower,  $M_2$ )  
 $\Rightarrow$  Counteracts the effect of  $\bar{i}_{in}$   
 $\Rightarrow$  Negative feedback.
- (b)  $\bar{i}_{in} \uparrow \Delta \Rightarrow V_{out} \downarrow$  (Common Source,  
through current gain of  $M_1$ )  
 $\Rightarrow \bar{i}_{D,M_2} \uparrow$  (Common Source,  $M_2$ )  
 $\Rightarrow$  Enhances  $V_{out}$  through  $M_1$   
 $\Rightarrow$  Positive feedback.
- (c)  $\bar{i}_{in} \uparrow \Delta \Rightarrow V_{out} \downarrow$  (Common Source,  
through current gain of  $M_1$ )  
 $\Rightarrow \bar{i}_{D,M_2} \downarrow$  (Common Gate)  
 $\Rightarrow$  Counteracts the effect of  $\bar{i}_{in}$   
 $\Rightarrow$  Negative feedback.
- (d)  $\bar{i}_{in} \uparrow \Delta \Rightarrow V_{out} \uparrow$  (Common Gate)  
 $\Rightarrow \bar{i}_{D,M_2} \downarrow$  (Common Source)  
 $\Rightarrow$  Counteracts the effect of  $\bar{i}_{in}$   
 $\Rightarrow$  Negative feedback.

Figure 12.83

(a)  $\bar{i}_{IN} \uparrow \Delta \Rightarrow V_{out} \downarrow$  (Common Emitter)

$\Rightarrow R_F$  demands more current momentarily

$\Rightarrow$  effective  $\bar{i}_{IN}$  into  $Q_1 \downarrow$

$\Rightarrow V_{out} \uparrow$

$\Rightarrow$  Negative feedback.

(b)  $\bar{i}_{IN} \uparrow \Delta \Rightarrow V_{G_1, M_3} \uparrow$  (Diff Pair Action)

$\Rightarrow V_{out} \uparrow$  (Source Follower)

$\Rightarrow V_{out}$  "tracks" behavior of  $\bar{i}_{IN}$

(Current demanded by  $R_F$  from  $\bar{i}_{IN} \uparrow$ )

$\Rightarrow$  Positive feedback.

2b.

(Without feedback)

$$\frac{V_{out}}{V_{in}} = A_{o.L.} = g_m R_D$$


Feedback factor,  $k$ :

$$k = \frac{R_2}{R_1 + R_2}$$

$$\Rightarrow A_{c.L.} = \left. \frac{V_{out}}{V_{in}} \right|_{c.L.} = \frac{A_{o.L.}}{1 + A_{o.L.} \cdot k} = \frac{g_m R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D}$$

$$R_{in, closed} = \frac{1}{g_{m1}} \left( 1 + \frac{R_2}{R_1 + R_2} g_m R_D \right)$$
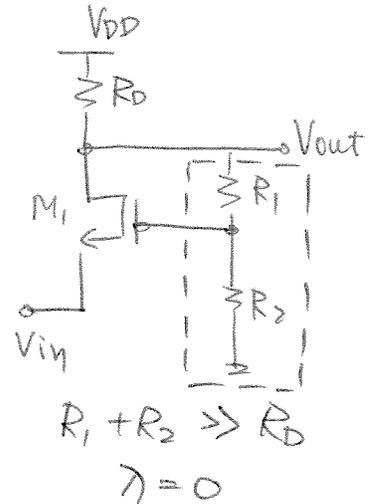
$$R_{out, closed} = \frac{R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D}$$




27.

(Without feedback)

$$A_{o.L.} = g_m R_D$$

Feedback factor,  $k$  :

$$k = \frac{C_1}{C_1 + C_2}$$

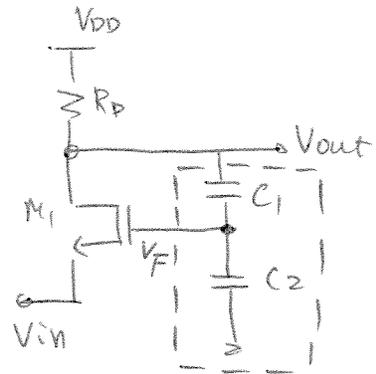


$\lambda = 0$   
 $C_1, C_2$  small.

$$\Rightarrow A_{c.L.} = \left. \frac{V_{out}}{V_{in}} \right|_{c.L.} = \frac{A_{o.L.}}{1 + A_{o.L.} k} = \frac{g_m R_D}{1 + \frac{C_1}{C_1 + C_2} g_m R_D}$$

$$R_{in, closed} = \frac{1}{g_m} \left[ 1 + \frac{C_1}{C_1 + C_2} g_m R_D \right]$$


$$R_{out, closed} = \frac{R_D}{1 + \frac{C_1}{C_1 + C_2} g_m R_D}$$

28.

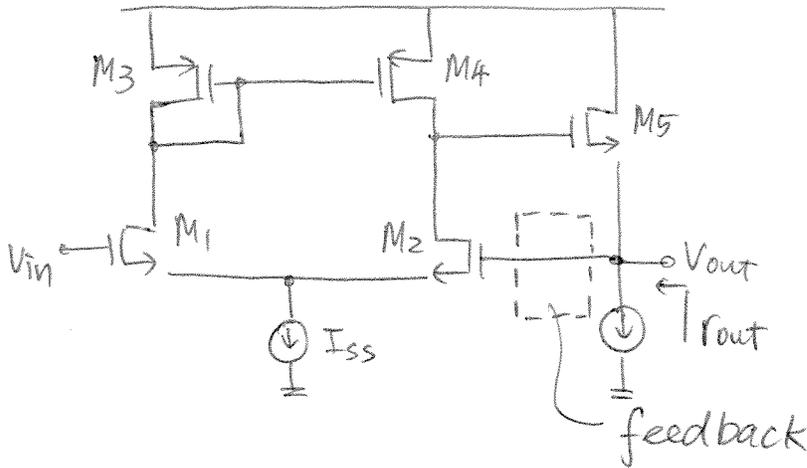

$\lambda > 0$   
 $r_{out}$  low.

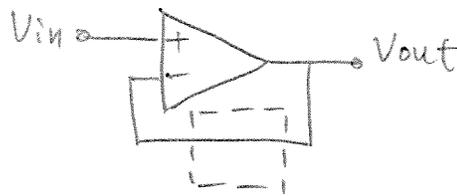Note that  $V_{out}$  is directly fed back to input:



$\therefore$  gain  $\approx 1$   
 (a buffer)  
 $\Rightarrow k = 1.$

$A_{OL}$  (i.e. without feedback)


$$= g_{m1} (r_{o2} \parallel r_{o4}) \times \frac{g_{m5} r_{o5}}{g_{m5} r_{o5} + 1} \left( \approx g_{m1} (r_{o2} \parallel r_{o4}) \right)$$

$$\Rightarrow A_{CL} = \frac{A_{OL}}{1 + A_{OL} \cdot k} = \frac{g_{m1} (r_{o2} \parallel r_{o4}) \left( \frac{g_{m5} r_{o5}}{g_{m5} r_{o5} + 1} \right)}{1 + g_{m1} (r_{o2} \parallel r_{o4}) \left( \frac{g_{m5} r_{o5}}{g_{m5} r_{o5} + 1} \right)}$$

$$r_{out} = \frac{r_{out}(\text{no feedback})}{1 + A_{OL} \cdot k} = \frac{\left( \frac{1}{g_{m5}} \parallel r_{o5} \right)}{1 + g_{m1} (r_{o2} \parallel r_{o4}) \left( \frac{g_{m5} r_{o5}}{g_{m5} r_{o5} + 1} \right)}$$

$$\text{Gain} = A = \frac{g_m r_o}{g_m r_o + 1}$$

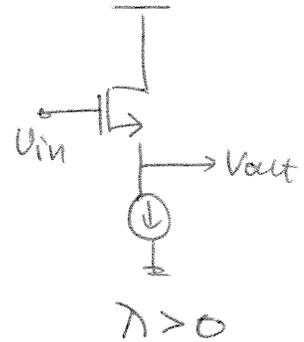
$$r_{out} = \frac{1}{g_m} \parallel r_o$$



In comparison, the amplifier's gain is reduced by  $\frac{g_{m1}(r_{o2} \parallel r_{o4})}{1 + g_{m1}(r_{o2} \parallel r_{o4}) \left( \frac{g_{m5} r_{o5}}{g_{m5} r_{o5} + 1} \right)}$  times.

(=  $\frac{A_{c.L.}}{A}$ ). Output resistance of the amplifier is reduced by  $\left[ 1 + g_{m1}(r_{o2} \parallel r_{o4}) \left( \frac{g_{m5} r_{o5}}{g_{m5} r_{o5} + 1} \right) \right]$  times.

29.

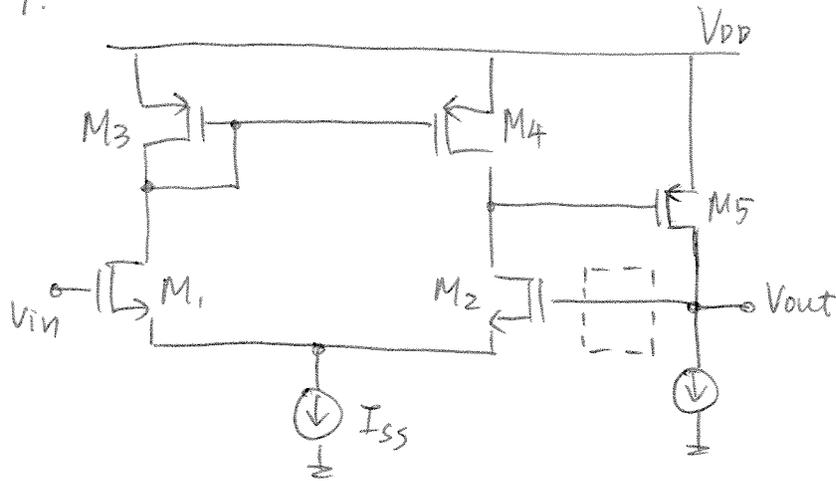

(a) By inspection,

$V_{in} \uparrow \Rightarrow V_{G, M5} \uparrow$

$\Rightarrow \underline{V_{out} \downarrow}$  (Common Source)

$\Rightarrow$  effective  $V_{in}$  ( $V_{in} - V_{out}$ )  $\uparrow \Rightarrow V_{G, M5} \uparrow$

$\Rightarrow$  Positive feedback.

(b)  $A_{o.l.}$  (without feedback)


$$= g_{m1} (r_{o2} \parallel r_{o4}) \times (-g_{m5} r_{o5})$$

$$k \text{ (feedback factor)} = 1$$

$$\Rightarrow \text{loop gain} = A_{o.l.} \times k = -g_{m5} r_{o5} \times g_{m1} (r_{o2} \parallel r_{o4})$$

$\Rightarrow$   $A_{c.l.}$  becomes negative  $\Rightarrow$  Positive feedback.

30.

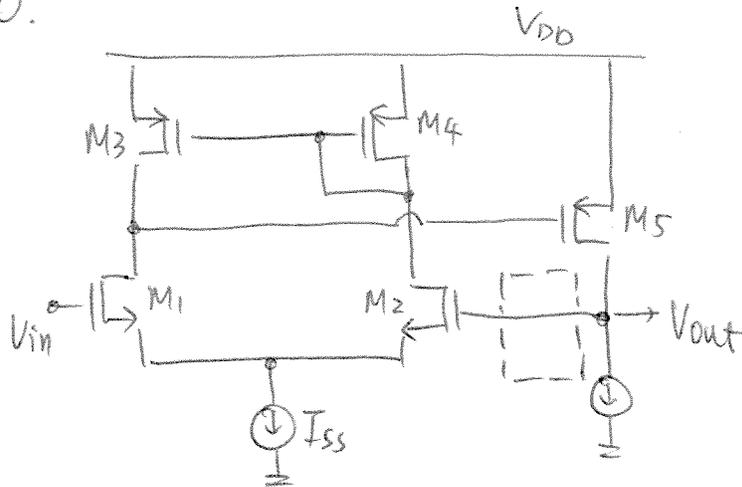

$$k = 1.$$

$$\lambda > 0$$

Ao.L. (without feedback)


$$= -g_{m1}(r_{o1} \parallel r_{o3}) \times (-g_{m5}r_{o5}) = g_{m1}g_{m5}(r_{o1} \parallel r_{o3})r_{o5}$$

$$\Rightarrow A_{c.L.} = \frac{V_{out}}{V_{in}} = \frac{g_{m1}g_{m5}(r_{o1} \parallel r_{o3})r_{o5}}{1 + g_{m1}g_{m5}(r_{o1} \parallel r_{o3})r_{o5}}$$

$$r_{in} \rightarrow \infty$$


$$r_{out} = \frac{r_{out}(\text{no feedback})}{1 + A_{o.L.} \times k} = \frac{r_{o5}}{1 + g_{m1}g_{m5}(r_{o1} \parallel r_{o3})r_{o5}}$$

31.

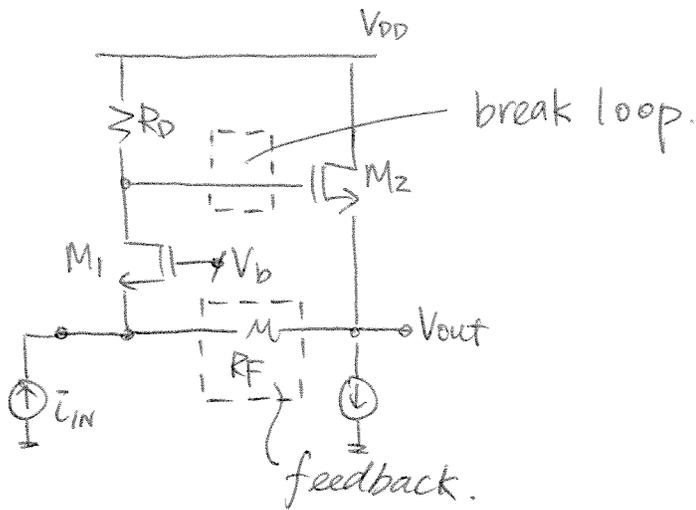

- (a)  $i_{IN} \uparrow \Rightarrow V_{G, M2} \uparrow$  (Common Gate;  $i_{IN}$  mostly flows to  $M_1$   $\because$  resistance  $= \frac{1}{g_{m1}}$ )  
 $\Rightarrow V_{out} \uparrow$  (Source Follower)  
 $\Rightarrow R_F$  momentarily provides more current to source of  $M_1$ )  
 $\Rightarrow V_{G, M2} \uparrow$   
 $\Rightarrow$  Positive feedback.

(b)

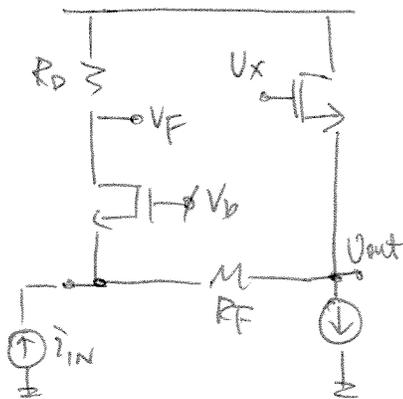

$$V_F = V_x \frac{g_{m1} R_D}{1 + g_{m2} (R_F + \frac{1}{g_{m1}})}$$

$$\Rightarrow -\frac{V_F}{V_x} = \text{Loop Gain} = -\frac{g_{m1} R_D}{1 + g_{m2} (R_F + \frac{1}{g_{m1}})}$$

$\therefore$  feedback is positive.


32.

(a)  $\bar{v}_{in} \uparrow \Delta \Rightarrow \Delta \bar{v}_{in}$  mostly  
flows in  $\frac{1}{g_{m1}} \Rightarrow V_{G,M2} \uparrow$   
(Common Gate)

$\Rightarrow V_{out} \downarrow$  (Common Source)

$\Rightarrow R_F$  momentarily demands  
more current from  $\bar{v}_{in}$

$\Rightarrow$  Negative feedback.

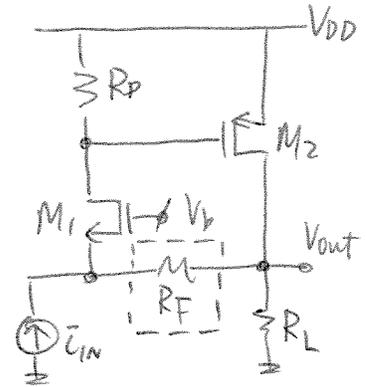

$$\lambda = 0$$

$$R_F \gg 1.$$

$$(b) R_{o.L.} = \left. \frac{V_{out}}{\bar{v}_{in}} \right|_{o.L.} = -R_D \times g_{m2} R_L$$

$$(c) \kappa \text{ (feedback factor)} = \frac{-1}{R_F}$$

$$\Rightarrow R_{c.L.} = \frac{R_{o.L.}}{1 + R_{o.L.} \times \kappa} = \frac{-R_D \times g_{m2} R_L}{1 + \frac{R_D}{R_F} g_{m2} R_L}$$


33.

$$R_{e.l.} = \frac{-g_{m2} R_D R_L}{1 + \frac{g_{m2} R_D R_L}{R_F}}$$

$$\text{loop gain} = \frac{g_{m2} R_D R_L}{R_F}$$

$$r_{in} \approx \frac{1}{g_{m1}}$$

$$\Rightarrow r_{in|c.l.} = \frac{1/g_{m1}}{1 + \frac{g_{m2} R_D R_L}{R_F}}$$

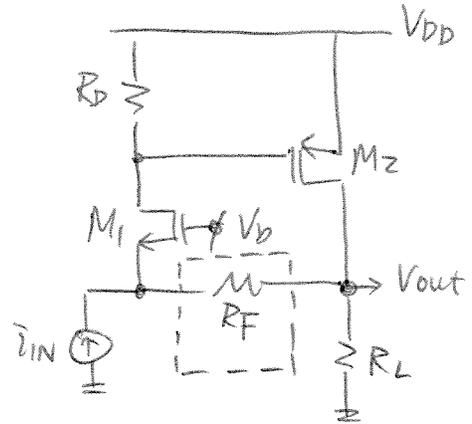

$$r_{out} \approx R_L \quad (R_F \text{ large})$$

$$r_{out|c.l.} = \frac{R_L}{1 + \frac{g_{m2} R_D R_L}{R_F}}$$


34.

$$R_{oL} = \frac{V_{out}}{\bar{v}_{IN}} \quad (\text{no feedback})$$

$$= R_D$$

$K$  (feedback factor)
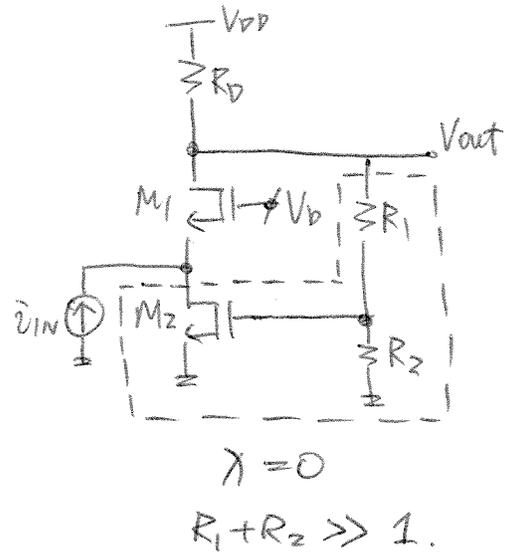
$$= g_{m2} \times \frac{R_2}{R_1 + R_2}$$



$$\Rightarrow R_{c.L.} = \frac{V_{out}}{\bar{v}_{IN}} = \frac{R_D}{1 + R_D \times g_{m2} \frac{R_2}{R_1 + R_2}}$$

$$r_{in|c.L.} = \frac{1/g_{m1}}{1 + R_D \times g_{m2} \frac{R_2}{R_1 + R_2}}$$

$$\Gamma_{out|c.L.} = \frac{R_D}{1 + R_D \times g_{m2} \frac{R_2}{R_1 + R_2}}$$

35.

$$R_{o.l.} = \frac{V_{out}}{\bar{v}_{in}} \text{ (no feedback)}$$

$$= R_D$$


$K$  (feedback factor)

$$= g_{m2} \times \frac{C_1}{C_1 + C_2}$$

$$\Rightarrow R_{c.l.} = \frac{V_{out}}{\bar{v}_{in}} = \frac{R_D}{1 + R_D \times g_{m2} \frac{C_1}{C_1 + C_2}}$$

$$\Gamma_{in|c.l.} = \frac{g_{m1}}{1 + R_D \times g_{m2} \frac{C_1}{C_1 + C_2}}$$


$$\Gamma_{out|c.l.} = \frac{R_D}{1 + R_D \times g_{m2} \frac{C_1}{C_1 + C_2}}$$

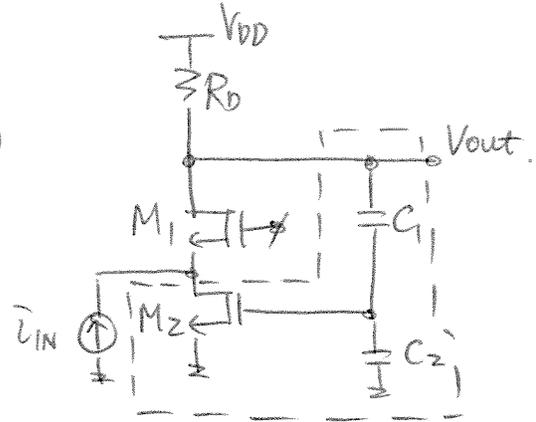

36.

$$(a) G_{OL} = \frac{i_{out}}{v_{in}} = g_m A_1$$

(common emitter)

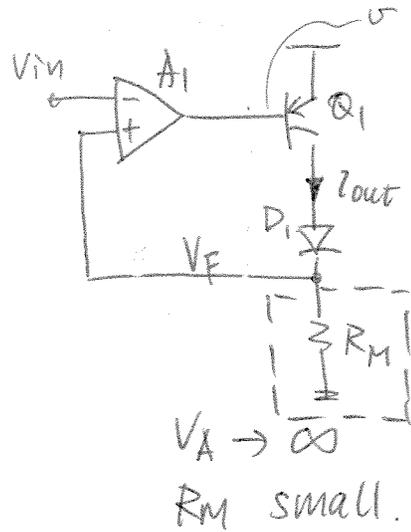

(b)  $K$  (feedback factor)


$$\Rightarrow V_F = i_{out} \times R_M$$

$$\Rightarrow K = \frac{V_F}{i_{out}} = R_M$$


$$\therefore \text{Loop Gain} = G_{OL} K = g_m A_1 R_M$$

$$G_{CL} = \frac{G_{OL}}{1 + G_{OL} K} = \frac{g_m A_1}{1 + g_m A_1 R_M}$$

37.

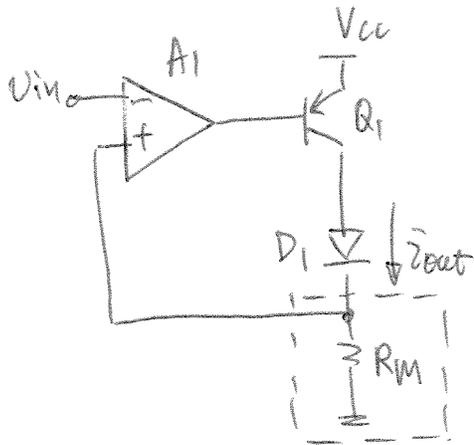

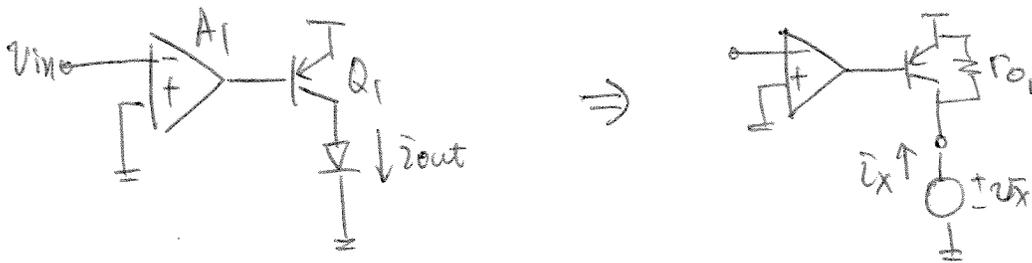Since  $R_M$  is small, the following circuit results:




$$\therefore R_{out, OPEN} = \frac{V_x}{i_x} = r_{o1}$$


$$G_{OL} = \frac{i_{out}}{v_{in}} = A_1 g_{m1} \quad k = R_M$$

$$\begin{aligned} \therefore R_{out, CLOSED} &= R_{out, OPEN} (1 + G_{OL} k) \\ &= r_{o1} (1 + A_1 g_{m1} R_M) \end{aligned}$$

38.

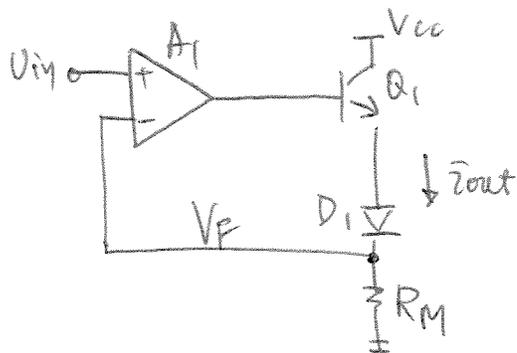

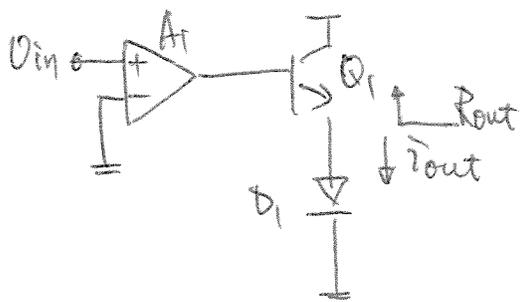Since  $R_M$  is small, the open-loop equivalent becomes the following:



$$G_{OL} = \frac{i_{out}}{i_{in}} \approx A_T g_{m_1}$$

$$R_{out} = \frac{r_o}{\beta + 1} \approx \frac{1}{g_{m_1}}$$

$$K = \frac{V_F}{i_{out}} = R_M$$

$$\Rightarrow G_{CL} = \frac{G_{OL}}{1 + G_{OL}K} = \frac{A_T g_{m_1}}{1 + g_{m_1} A_T R_M}$$

$$\text{Loop Gain} = G_{OL}K = g_{m_1} A_T R_M$$

$$R_{out, \text{closed}} = \frac{1}{g_{m_1}} (1 + g_{m_1} A_T R_M)$$

This circuit provides a much lower output resistance which in general is non-desirable (ideally any current source should have high impedance.)

39.

Using procedure in Ex 12.21


$$G_{o.l.} = \frac{\bar{i}_{out}}{v_{in}} = g_{m2} R_C \times g_{m1}$$

$K$  (feedback factor)

$$= \frac{v_F}{\bar{i}_{out}} = R_M$$

$$\Rightarrow \text{loop gain} = G_{o.l.} \times K = g_{m1} g_{m2} R_C R_M$$
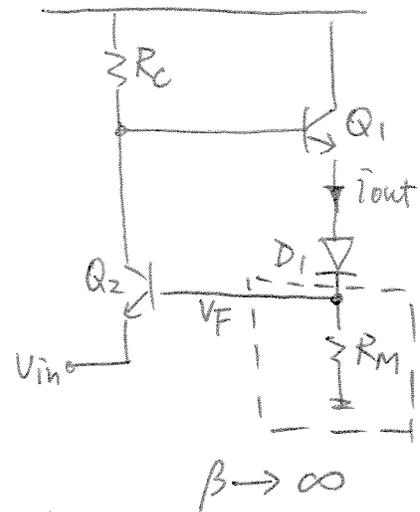
$$\Rightarrow \text{closed-loop gain } G_{c.l.} = \frac{g_{m1} g_{m2} R_C}{1 + g_{m1} g_{m2} R_C R_M}$$



Using procedure in Ex. 12.22

$$G_{o.l.} = g_{m1} g_{m2} R_C$$

$$K = R_M$$

$$r_{in|o.l.} = \frac{1}{g_{m1}}$$

$$r_{out|o.l.} \cong \frac{1}{g_{m2}}$$

$$r_{in|c.l.} = \frac{1}{g_{m1}} (1 + g_{m1} g_{m2} R_C R_M)$$

$$r_{out|c.l.} = \frac{1}{g_{m2}} (1 + g_{m1} g_{m2} R_C R_M)$$

40.


(a)  $\bar{i}_{IN} \uparrow \Delta \Rightarrow$  Most of  $\bar{i}_{IN}$  flows into  $1/g_{m1}$

$\Rightarrow V_{G,M2} \uparrow$  (Common Gate)

$\Rightarrow V_x \uparrow$  (Source Follower)

$\Rightarrow R_F$  momentarily provides more current to Source of  $M_1$

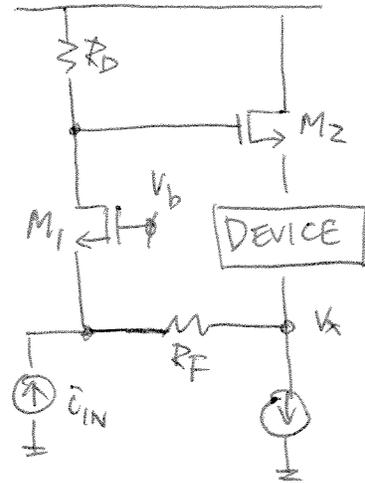$\Rightarrow V_{G,M2} \uparrow \Rightarrow$  Positive feedback.




(b)

$$V_a \times g_{m2} \times R_D = V_b$$



$$\Rightarrow \text{loop gain} = -\frac{V_b}{V_a} = -g_{m2} R_D.$$

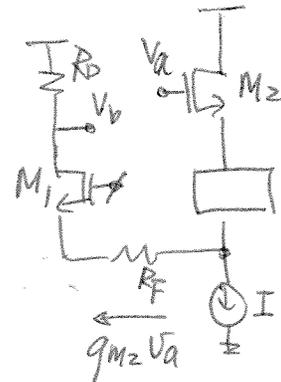Since loop gain is negative, feedback is positive.



41.

(a) The open-loop equivalent becomes:

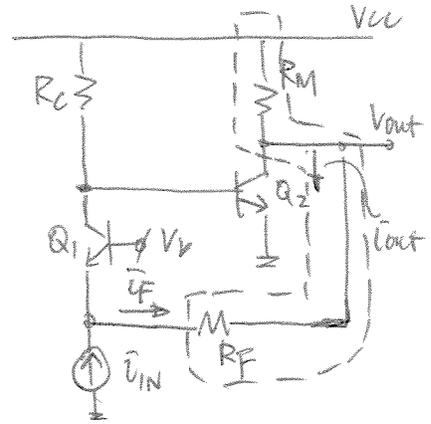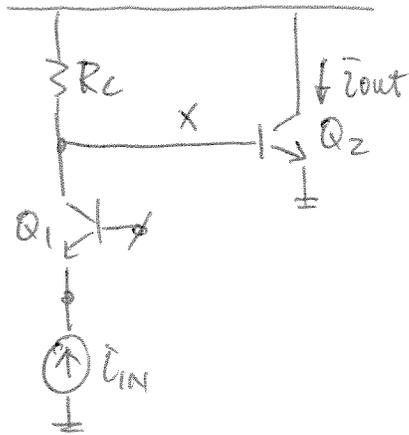


$V_A \rightarrow \infty$   
 $R_M$  small  
 $R_F$  large

$$A_I = \frac{\hat{i}_{out}}{\hat{i}_{IN}} = \frac{\hat{i}_{out}}{v_x} \times \frac{v_x}{\hat{i}_{IN}} \approx g_{m2} \times R_C$$

$$R_{in, OPEN} \approx \frac{1}{g_{m1}}$$

$$R_{out, OPEN} \rightarrow \infty \quad (\because V_{A2} \rightarrow \infty)$$
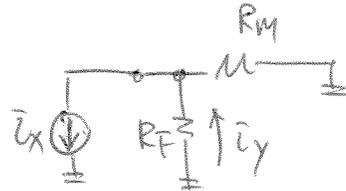
$$K = \frac{\hat{i}_y}{\hat{i}_x} = + \frac{(R_F \parallel R_M)}{R_F}$$





$$A_{CL} = \frac{A_I}{1 + A_I K} = \frac{g_{m2} R_C}{1 + g_{m2} R_C \frac{(R_F \parallel R_M)}{R_F}}$$

$$R_{in, CLOSED} = \frac{\frac{1}{g_{m1}}}{1 + g_{m2} R_C \frac{(R_F \parallel R_M)}{R_F}}$$

$$R_{out, CLOSED} \rightarrow \infty$$

(b) The open-loop equivalent becomes:

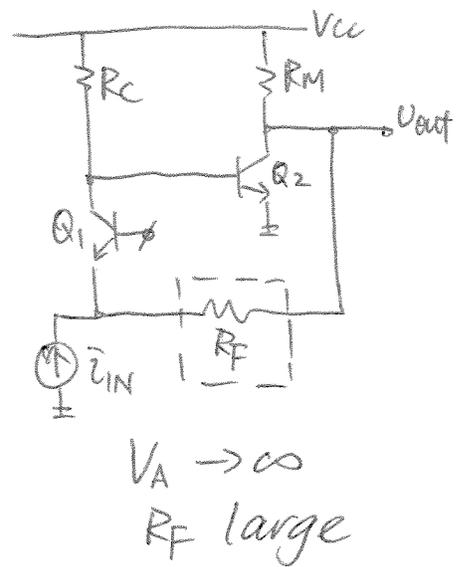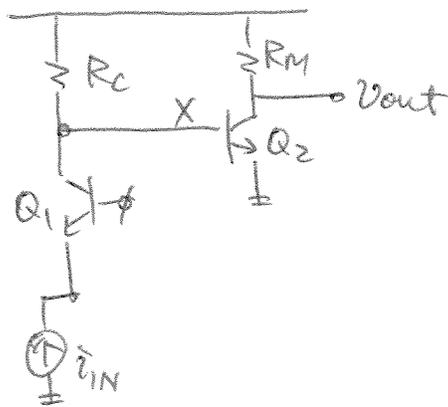

$$R_{OL} = \frac{v_{out}}{i_{IN}} = \frac{v_{out}}{v_X} \times \frac{v_X}{i_{IN}} \cong -g_{m2} R_M \times R_C$$

$$R_{in, OPEN} = \frac{1}{g_{m1}} \quad R_{out, OPEN} = R_M$$



$$K = -\frac{1}{R_M}$$

$$R_{CL} = \frac{R_{OL}}{1 + R_{OL}K} = \frac{-g_{m2} R_M R_C}{1 + g_{m2} R_C}$$


$$R_{in, CLOSED} = \frac{1/g_{m1}}{1 + g_{m2} R_C}$$

$$R_{out, CLOSED} = \frac{R_M}{1 + g_{m2} R_C}$$

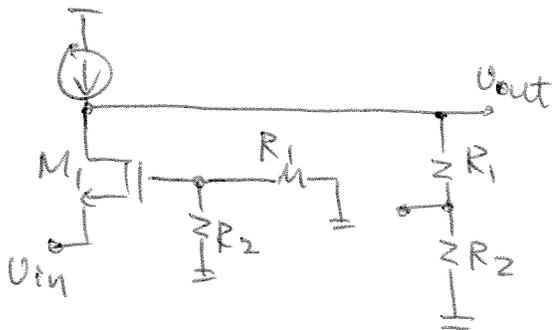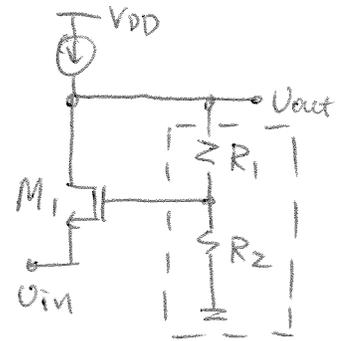42. Breaking the feedback network results in the following circuit:



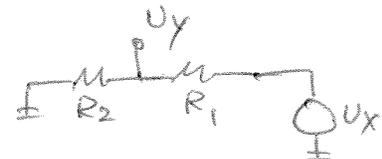Feedback factor  
 $= K = \frac{V_y}{V_x} = \frac{R_2}{R_1 + R_2}$



$$A_{o.L.} = +g_{m1} (R_1 + R_2)$$


$$\text{Loop Gain} = A_{o.L.} K = g_{m1} R_2$$

$$\therefore A_{c.L.} = \frac{A_{o.L.}}{1 + A_{o.L.} K} = \frac{g_{m1} (R_1 + R_2)}{1 + g_{m1} R_2}$$

$$R_{in, \text{closed}} = \frac{1}{g_{m1}} (1 + g_{m1} R_2)$$


$$R_{out, \text{closed}} = \frac{R_1 + R_2}{1 + g_{m1} R_2}$$

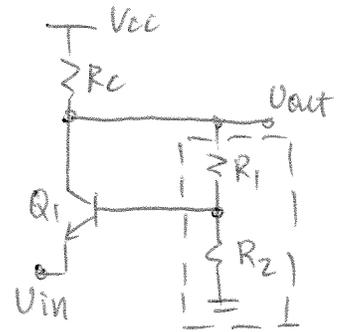43. Breaking the feedback network results in the following circuit:



$$V_A \rightarrow \infty$$


$$1 \ll \beta < \infty$$

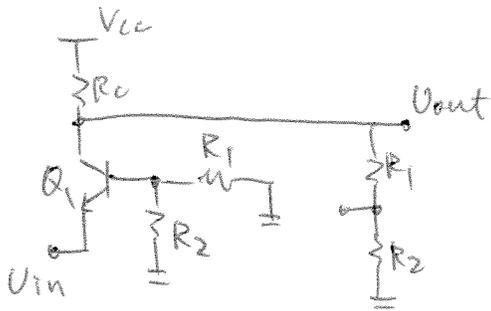

$$A_{OL} \approx g_{m1} [R_c \parallel (R_1 \parallel R_2)] \quad \text{since } \bar{v}_b \rightarrow 0 \quad (\beta \gg 1)$$

Feedback factor
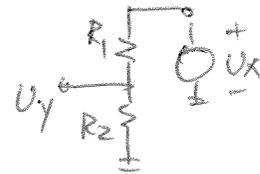
$$= k = \frac{U_Y}{U_X} = \frac{R_2}{R_1 + R_2}$$



$$R_{in, OPEN} = \frac{r_{\pi 1} + (R_1 \parallel R_2)}{\beta_1 + 1} \approx \frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{\beta_1 + 1}$$


$$R_{out, OPEN} = R_c \parallel (R_1 + R_2)$$

$$\Rightarrow A_{CL} = \frac{A_{OL}}{1 + A_{OL}k} = \frac{g_{m1} [R_c \parallel (R_1 + R_2)]}{1 + g_{m1} [R_c \parallel (R_1 + R_2)] \times \frac{R_2}{R_1 + R_2}}$$

$$R_{in, CLOSED} = \left( \frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{\beta_1 + 1} \right) (1 + A_{OL}k)$$


$$R_{out, CLOSED} = \frac{R_c \parallel (R_1 + R_2)}{1 + A_{OL}k}$$

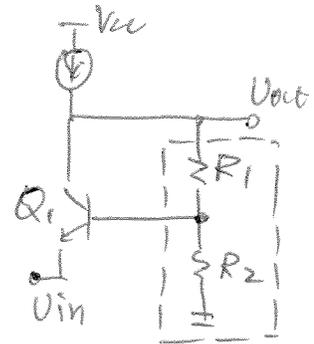44. Breaking the feedback network results in the following circuit:



$$V_A \rightarrow \infty$$


$$1 \ll \beta \ll \infty$$

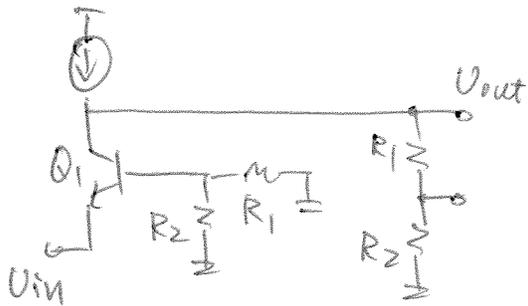

$$A_{OL} \cong g_{m1} (R_1 + R_2) \quad \text{since } i_b \rightarrow 0 (\beta \gg 1)$$

Feedback factor
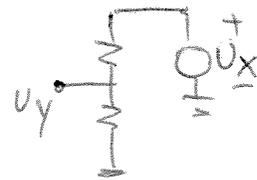
$$= K = \frac{U_Y}{U_X} = \frac{R_2}{R_1 + R_2}$$



$$R_{in, OPEN} \cong \frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{\beta_1 + 1}$$



$$R_{out, OPEN} = R_1 + R_2$$

$$\Rightarrow A_{CL} = \frac{A_{OL}}{1 + A_{OL}K} = \frac{g_{m1} (R_1 + R_2)}{1 + g_{m1} R_2}$$

$$R_{in, CLOSED} = \left( \frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{\beta_1 + 1} \right) (1 + g_{m1} R_2)$$

$$R_{out, CLOSED} = \frac{R_1 + R_2}{1 + g_{m1} R_2}$$

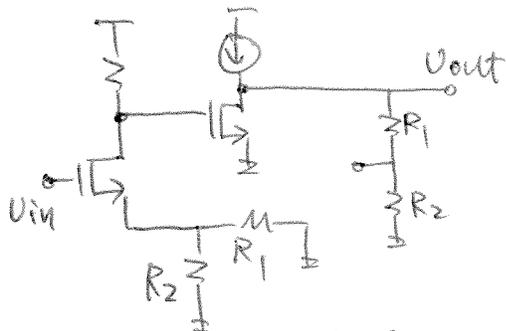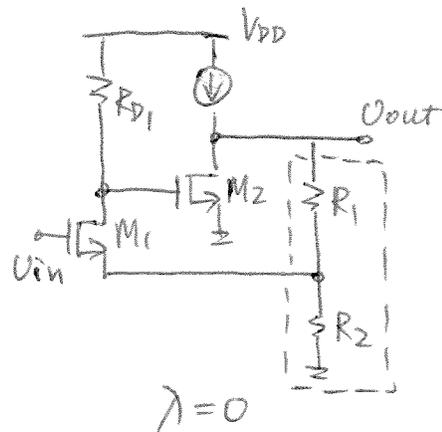45. Breaking the feedback network results in the following circuit:




$$A_{OL} = \frac{-g_{m1} R_{D1}}{1 + g_{m1}(R_1 \parallel R_2)} \times -g_{m2}(R_1 + R_2)$$

$$K = \frac{V_y}{V_x} = \frac{R_2}{R_1 + R_2}$$

$$R_{in, OPEN} \rightarrow \infty$$

$$R_{out, OPEN} = R_1 + R_2$$


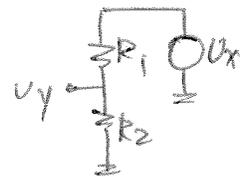


$$\therefore A_{CL} = \frac{A_{OL}}{1 + A_{OL}K} = \frac{\left[ \frac{g_{m1} g_{m2} R_{D1} (R_1 + R_2)}{1 + g_{m1} (R_1 \parallel R_2)} \right]}{1 + \frac{g_{m1} g_{m2} R_{D1}}{1 + g_{m1} (R_1 \parallel R_2)}}$$

$$R_{in, CLOSED} \rightarrow \infty$$

$$R_{out, CLOSED} = \frac{R_1 + R_2}{1 + A_{OL}K}$$

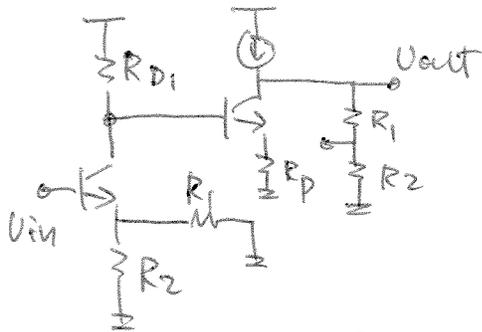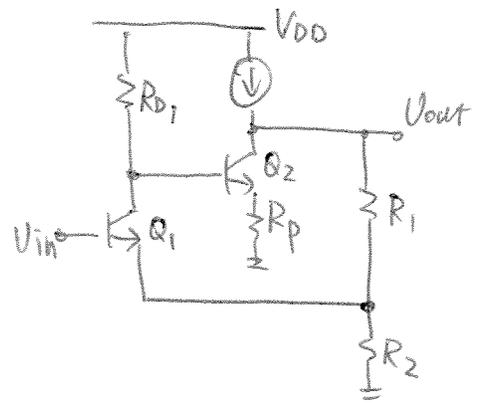4b. Breaking the feedback network results in the following circuit:




$$A_{OL} \cong \frac{-g_{m1} \times \{R_{D1} \parallel [\Gamma_{\pi 2} + (\beta_2 + 1)R_p]\}}{1 + g_{m1}(R_1 \parallel R_2)} \times \frac{-g_{m2}(R_1 + R_2)}{1 + g_{m2}R_p}$$

$$R_{in, OPEN} = \Gamma_{\pi 1} + (R_1 \parallel R_2)$$

$$R_{out, OPEN} = R_1 + R_2$$
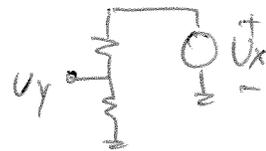
$$K = \frac{V_Y}{V_X} = \frac{R_2}{R_1 + R_2}$$




$$\Rightarrow A_{CL} = \frac{A_{OL}}{1 + A_{OL}K}$$

$$R_{in, CLOSED} = [\Gamma_{\pi 1} + (R_1 \parallel R_2)] (1 + A_{OL}K)$$


$$R_{out, CLOSED} = \frac{R_1 + R_2}{1 + A_{OL}K}$$

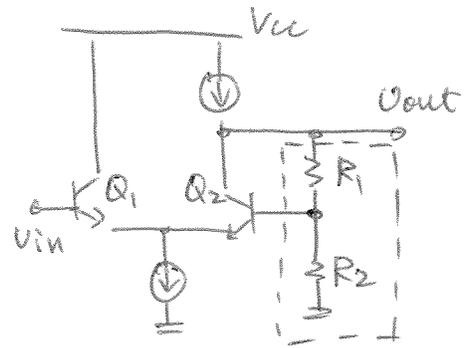47. Breaking the feedback network results in the following circuit:



$(V_A \rightarrow \infty)$

$$K = \frac{R_2}{R_1 + R_2}$$

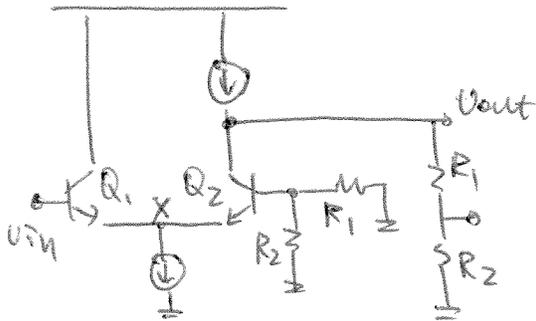

$$A_{OL} \cong \underbrace{\frac{g_{m1} \left( \frac{1}{g_{m2}} + \frac{R_1 || R_2}{\beta_2 + 1} \right)}{1 + g_{m1} \left( \frac{1}{g_{m2}} + \frac{R_1 || R_2}{\beta_2 + 1} \right)}}_{\text{emitter follower (Q}_1\text{)} = \frac{V_x}{V_{in}}} \times \underbrace{g_{m2} (R_1 + R_2)}_{\text{common-base stage (Q}_2\text{)} = \frac{V_{out}}{V_x}}$$

$$R_{in, OPEN} = r_{\pi 1} + (\beta_1 + 1) \left( \frac{1}{g_{m2}} + \frac{R_1 || R_2}{\beta_2 + 1} \right)$$



$$R_{out, OPEN} = R_1 + R_2$$

$$\therefore A_{CL} = \frac{A_{OL}}{1 + A_{OL} K}$$


$$R_{in, CLOSED} = \left[ r_{\pi 1} + (\beta_1 + 1) \left( \frac{1}{g_{m2}} + \frac{R_1 || R_2}{\beta_2 + 1} \right) \right] \times (1 + A_{OL} K)$$

$$R_{out, CLOSED} = \frac{R_1 + R_2}{1 + A_{OL} K}$$

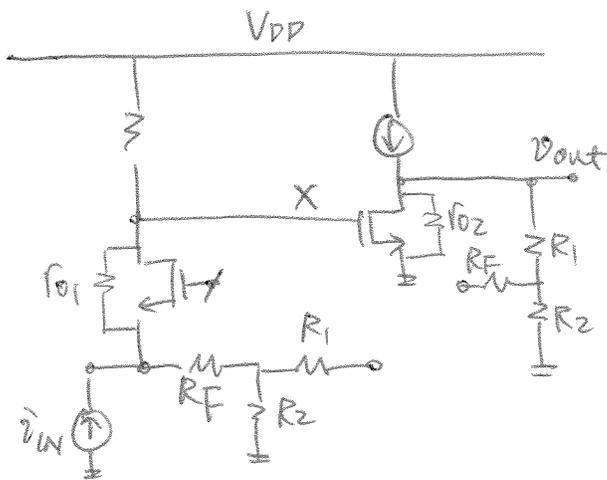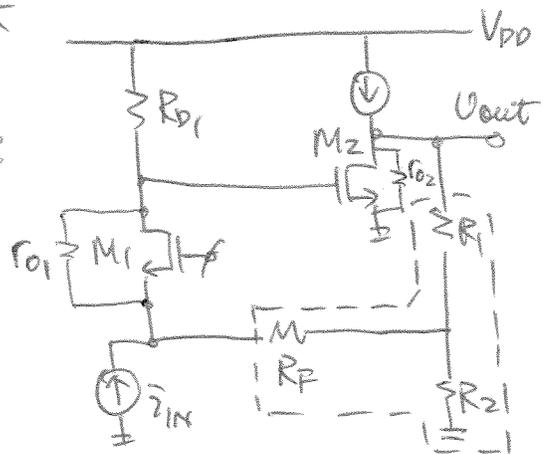48. Breaking the feedback network results in the following circuit:


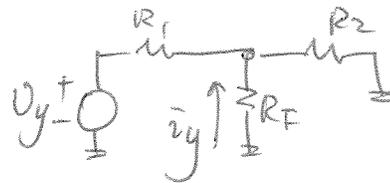
$$K = -\frac{(R_F \parallel R_2) / R_F}{R_F \parallel R_2 + R_1}$$



$$R_{OL} = \frac{v_{out}}{i_{IN}} = \frac{v_{out}}{v_x} \times \frac{v_x}{i_{IN}}$$

$$= -g_{m2} [r_{o2} \parallel (R_1 + R_2)] \times \left\{ \frac{\frac{1}{r_{o1}} + \frac{1}{R_{D1}}}{\frac{1}{r_{o1}} + g_{m1}} \times \left[ \frac{1}{(R_F + R_2) \parallel \frac{1}{g_{m1}}} + \frac{1}{r_{o1}} \right] - \frac{1}{r_{o1}} \right\}$$

$$R_{in, OPEN} \cong \frac{1}{g_{m1}} \parallel (R_F + R_2) \parallel \frac{r_{o1}}{1 - g_{m1} R_{D1}}$$



$$R_{out, OPEN} = r_{o2} \parallel (R_1 + R_2)$$

$$R_{CL} = \frac{R_{OL}}{1 + R_{OL} K}$$

$$R_{in, CLOSED} = \frac{R_{in, OPEN}}{1 + R_{OL} K}$$

$$R_{out, CLOSED} = \frac{R_{out, OPEN}}{1 + R_{OL} K}$$

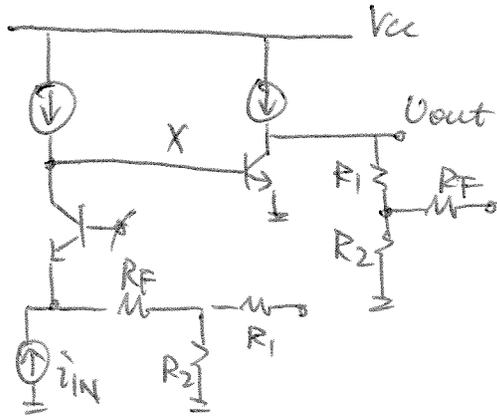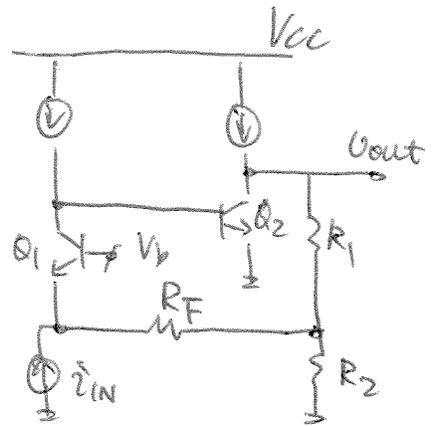49. Breaking the feedback network results in the following circuit:




$$R_{OL} = \frac{U_{out}}{i_{IN}} = \frac{U_{out}}{U_X} \times \frac{U_X}{i_{IN}} = [-g_{m2}(R_1 + R_2)] \times [g_{m1}, r_{\pi 2} \left\{ \frac{1}{g_{m1}} \parallel (R_F + R_2) \right\}]$$

$$R_{in, OPEN} = \frac{1}{g_{m1}} \parallel (R_F + R_2)$$

$$R_{out, OPEN} = R_1 + R_2$$
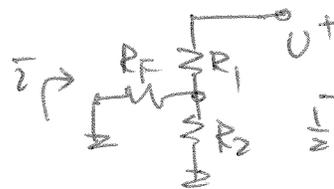
$$K = \frac{\dot{U}}{U} = - \frac{(R_2 \parallel R_F) / R_F}{R_1 + (R_2 \parallel R_F)}$$





$$\therefore R_{CL} = \frac{R_{OL}}{1 + R_{OL}K}$$

$$R_{in, CLOSED} = \frac{\frac{1}{g_{m1}} \parallel (R_F + R_2)}{1 + R_{OL}K}$$

$$R_{out, CLOSED} = \frac{R_1 + R_2}{1 + R_{OL}K}$$

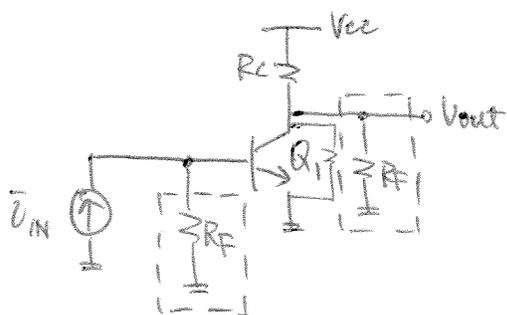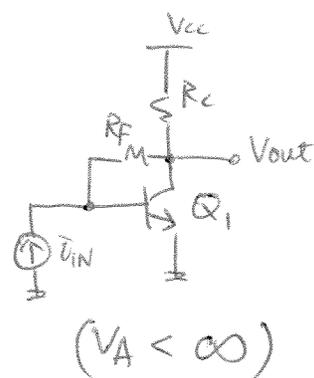50. The feedback network consists of  $R_F$ .

Using the method discussed in lecture, break the circuit as follows:



This is the open-loop circuit with consideration of I/O loading.

- By inspection,

$$v_{out} = i_c \times (R_C \parallel R_F \parallel r_o)$$

$$= -g_m (i_{in} \times (R_F \parallel r_{\pi})) \times (R_C \parallel R_F \parallel r_o)$$

$$\Rightarrow R_{o.l.} = \frac{v_{out}}{i_{in}} = -g_m (R_F \parallel r_{\pi}) (R_C \parallel R_F \parallel r_o) \quad \text{--- (1)}$$

$$R_{in, open} = (R_F \parallel r_{\pi}) \quad R_{out, open} = (R_C \parallel R_F \parallel r_o)$$

- Feedback factor  $k$ :

$$k = \frac{v_x}{i_x} = -\frac{1}{R_F}$$



$$\therefore R_{o.L.} = \frac{R_{o.L.}}{1 + R_{o.L.} \times K} = \frac{-g_m(R_F \parallel r_{\pi})(R_C \parallel R_F \parallel r_o)}{1 + \frac{g_m(R_F \parallel r_{\pi})(R_C \parallel R_F \parallel r_o)}{R_F}}$$



$$R_{in,CLOSED} = \frac{(R_F \parallel r_{\pi})}{1 - \frac{R_{o.L.}}{R_F}}$$

$$R_{out,CLOSED} = \frac{(R_C \parallel R_F \parallel r_o)}{1 - \frac{R_{o.L.}}{R_F}}$$

where  $R_{o.L.}$  is given by (1).

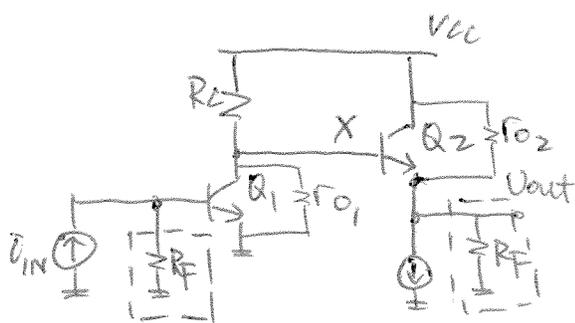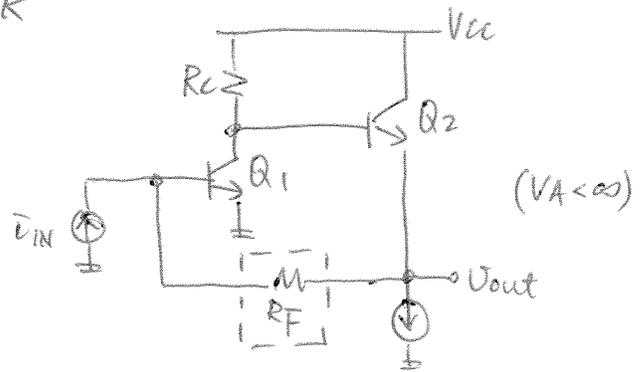51. The feedback network consists of  $R_F$ .

Using the method discussed in lecture, break the circuit as follows:



This is the open-loop circuit with consideration of I/O loading.

- Gain of common-emitter stage:

$$\frac{v_x}{v_{in}} = -g_{m1}(R_F \parallel r_{\pi 1}) \times \left\{ R_c \parallel r_{o1} \parallel \left[ r_{\pi 2} + (\beta_2 + 1)(R_F \parallel r_{o2}) \right] \right\}$$

- Gain of emitter-follower stage:

$$\frac{v_{out}}{v_x} = \frac{g_{m2}(R_F \parallel r_{o2})}{1 + g_{m2}(R_F \parallel r_{o2})}$$


$$\Rightarrow R_{o.l.} = \frac{v_x}{i_{in}} \cdot \frac{v_{out}}{v_x} \quad \text{--- (1)}$$

$$R_{in, OPEN} = R_F \parallel r_{\pi 1}$$

$$R_{out, OPEN} \cong R_F \parallel r_{o2} \parallel \frac{1}{g_{m2}}$$

- Feedback factor  $k$ :
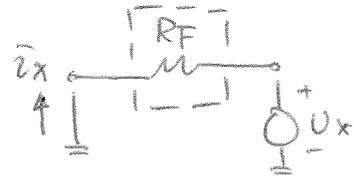
$$k = \frac{v_x}{\bar{v}_x} = -\frac{1}{R_F}$$





$$\therefore R_{o,L} = \frac{R_{o,L}}{1 + R_{o,L} \times k} = \frac{R_{o,L}}{1 - R_{o,L}/R_F}$$

$$R_{in,CLOSED} = \frac{(R_F \parallel \Gamma_{\pi_1})}{1 - \frac{R_{o,L}}{R_F}} \quad R_{out,CLOSED} = \frac{R_F \parallel r_{o2} \parallel \frac{1}{g_{m2}}}{1 - \frac{R_{o,L}}{R_F}}$$

where  $R_{o,L}$  is given by (1).

52.

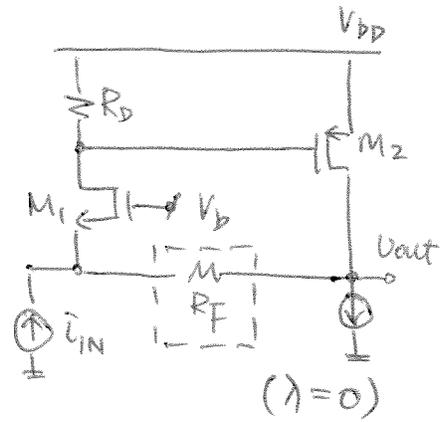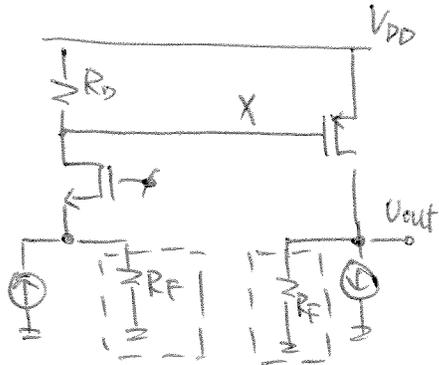(a) Breaking the feedback loop results in the following circuit:



$$R_{o.l.} = \frac{v_x}{i_{in}} \cdot \frac{v_{out}}{v_x}$$

$$= g_{m1} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right) \times (-g_{m2} R_F)$$

$$R_{in, OPEN} = \frac{1}{g_{m1}} \parallel R_F$$

$$R_{out, OPEN} = R_F$$

- Feedback factor  $k$ :

$$k = \frac{v_x}{v_x} = -\frac{1}{R_F}$$





$$\Rightarrow R_{c.l.} = \frac{R_{o.l.}}{1 + R_{o.l.} \times k} = \frac{-g_{m1} g_{m2} R_D R_F \left( \frac{1}{g_{m1}} \parallel R_F \right)}{1 + g_{m1} g_{m2} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right)}$$

$$R_{in, CLOSED} = \frac{\left( \frac{1}{g_{m1}} \parallel R_F \right)}{1 + g_{m1} g_{m2} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right)}$$

$$R_{out, CLOSED} = \frac{R_F}{1 + g_{m1} g_{m2} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right)}$$

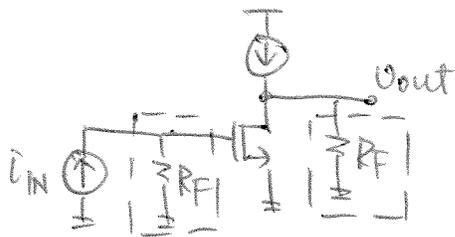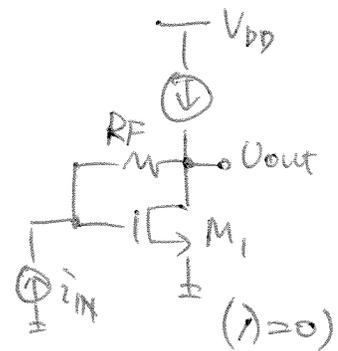(b) Breaking the feedback loop results in the following circuit:




$$R_{o.L.} = \frac{V_{out}}{i_{IN}} = -g_m R_F R_F = -g_m R_F^2$$

$$R_{in, OPEN} = R_F \quad R_{out, OPEN} = R_F$$

- Feedback factor  $K$ :

$$K = \frac{V_x}{i_x} = -\frac{1}{R_F}$$

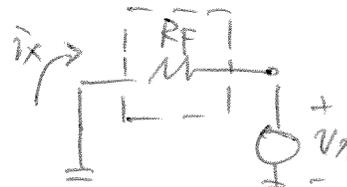


$$\Rightarrow R_{c.L.} = \frac{-g_m R_F^2}{1 + g_m R_F}$$

$$R_{in, CLOSED} = \frac{R_F}{1 + g_m R_F}$$

$$R_{out, CLOSED} = \frac{R_F}{1 + g_m R_F}$$

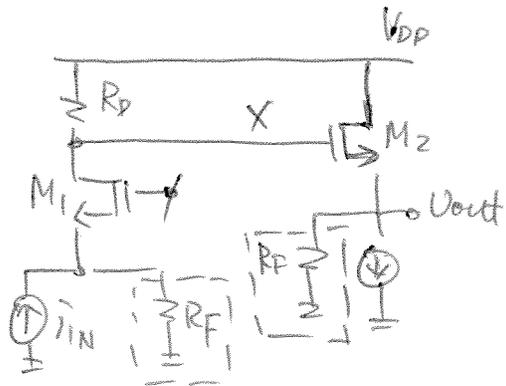(c) Breaking the feedback loop results in the following circuit:



$$R_{in, OPEN} = \left( \frac{1}{g_{m1}} \parallel R_F \right)$$

$$R_{o.L.} = \frac{v_{out}}{i_{IN}} = \frac{v_x}{i_{IN}} \cdot \frac{v_{out}}{v_x}$$

$$= g_{m1} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right) \times g_{m2} \left( R_F \parallel \frac{1}{g_{m2}} \right)$$

$$R_{out, OPEN} = \left( R_F \parallel \frac{1}{g_{m2}} \right)$$

- Feedback factor  $K$ :

$$K = \frac{v_x}{i_x} = -\frac{1}{R_F}$$



(Note: Feedback is positive.)



$$\Rightarrow R_{c.L.} = \frac{R_{o.L.}}{1 + R_{o.L.} \times K}$$

$$= \frac{g_{m1} g_{m2} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right) \left( \frac{1}{g_{m2}} \parallel R_F \right)}{1 - g_{m1} g_{m2} \left( \frac{R_D}{R_F} \right) \left( \frac{1}{g_{m1}} \parallel R_F \right) \left( \frac{1}{g_{m2}} \parallel R_F \right)}$$

$$R_{in, CLOSED} = \frac{\left( \frac{1}{g_{m1}} \parallel R_F \right)}{1 - \frac{R_{o.L.}}{R_F}}$$

$$R_{out, CLOSED} = \frac{\left( \frac{1}{g_{m2}} \parallel R_F \right)}{1 - \frac{R_{o.L.}}{R_F}}$$

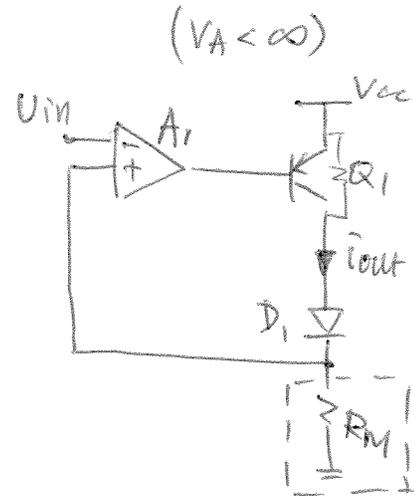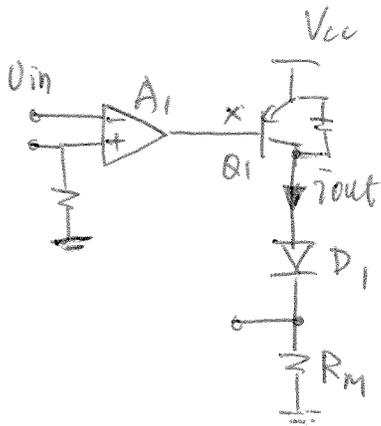
53. Breaking the feedback network (i.e.  $R_M$ ) results in the following circuit:



$$G_{OL} = \frac{\bar{i}_{out}}{U_{in}} = \frac{\bar{i}_{out}}{U_x} \times \frac{U_x}{U_{in}} \quad (1)$$

$$= \underbrace{g_{m1} \times \frac{[(R_L + R_M) \parallel r_{o1}]}{(R_L + R_M)}}_{\text{(current division)}} \times (-A_1)$$

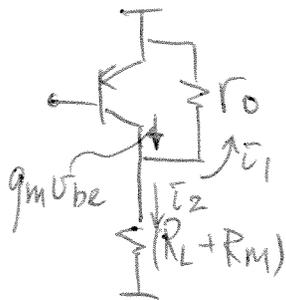Note: current ( $g_m V_{be}$ ) splits between  $r_o$  &  $[R_L$  (impedance of  $D_1$ ) +  $R_M$ ]




$$g_m V_{be} = \bar{i}_1 + \bar{i}_2$$

$$R_{in, OPEN} \rightarrow \infty$$

$$R_{out, OPEN} = r_{o1} + R_M$$

- Feedback factor  $K$ :

$$K = \frac{U_x}{\bar{i}_x} = R_M$$

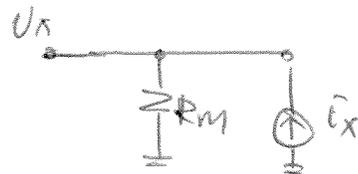

$$\therefore G_{o.l.} = \frac{G_{o.l.}}{1 + G_{o.l.} \times K} = \frac{G_{o.l.}}{1 + G_{o.l.} \times R_M}$$



$$R_{in, CLOSED} \rightarrow \infty$$

$$R_{out, CLOSED} = (T_{o1} + R_M)(1 + G_{o.l.} \times R_M)$$

where  $G_{o.l.}$  is given by (1)

54.

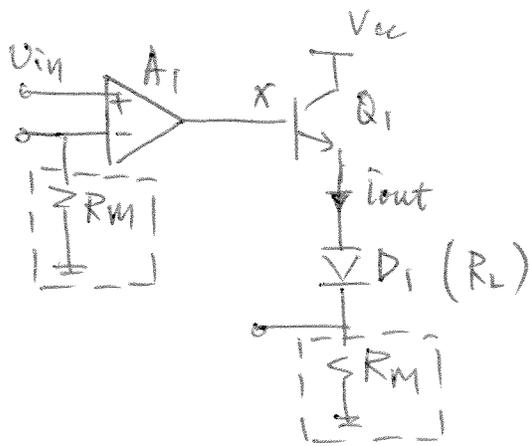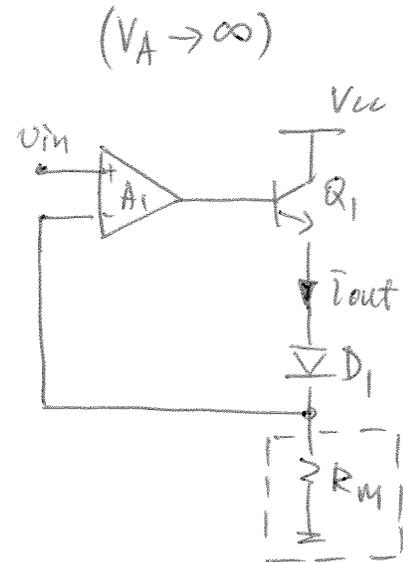(a) Breaking the feedback loop results in the following circuit:



$$G_{o.l.} = \frac{i_{out}}{v_{in}} = \frac{i_{out}}{v_x} \cdot \frac{v_x}{v_{in}} = \frac{g_{m1} (R_L + R_M)}{1 + g_{m1} (R_L + R_M)} \times A_1$$

$$R_{in, OPEN} \rightarrow \infty$$

$$R_{out, OPEN} \approx R_M + \frac{1}{g_{m1}}$$

- Feedback factor  $k$ :

$$k = \frac{v_x}{v_x} = R_M$$





$$G_{c.l.} = \frac{G_{o.l.}}{1 + G_{o.l.} k} = \frac{G_{o.l.}}{1 + G_{o.l.} R_M}$$

$$R_{in, CLOSED} \rightarrow \infty$$

$$R_{out, CLOSED} = \left( R_M + \frac{1}{g_{m1}} \right) \times (1 + G_{o.l.} R_M)$$

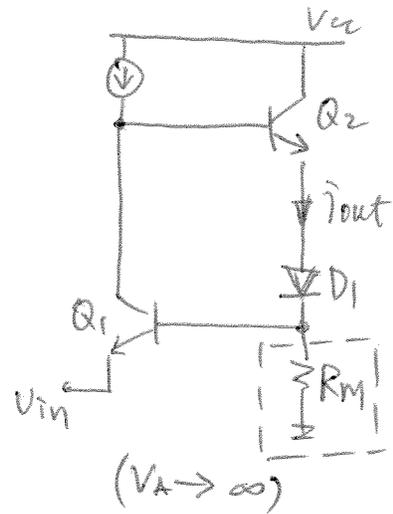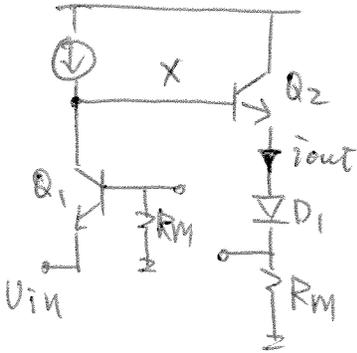(b) Breaking the feedback loop results in the following circuit:




$$G_{o.L.} = \frac{i_{out}}{v_{in}} = \frac{i_{out}}{v_x} \times \frac{v_x}{v_{in}} \approx \frac{g_{m2}(R_L + R_M)}{1 + g_{m2}(R_L + R_M)} \times g_{m1} [\tau_{\pi 2} + (\beta_2 + 1)(R_L + R_M)]$$

$$R_{in, open} = \frac{\tau_{\pi 1} + R_M}{\beta_1 + 1} \approx \frac{1}{g_{m1}} + \frac{R_M}{\beta_1 + 1}$$

$$R_{out, open} = \frac{1}{g_{m2}} + R_M$$

- Feedback Factor \$k\$:

$$k = \frac{v_x}{i_x} = R_M$$

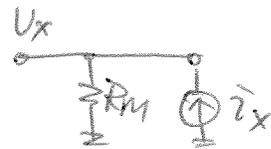

$$\Rightarrow G_{c.L.} = \frac{G_{o.L.}}{1 + G_{o.L.} \times k} = \frac{G_{o.L.}}{1 + G_{o.L.} R_M}$$

$$R_{in, closed} = \left( \frac{1}{g_{m1}} + \frac{R_M}{\beta_1 + 1} \right) (1 + G_{o.L.} R_M)$$

$$R_{out, closed} = \left( \frac{1}{g_{m2}} + R_M \right) (1 + G_{o.L.} R_M)$$

55.

$$V_{out} = [-g_{m1}(V_{in} - V_x)R_D] \cdot [-g_{m2} \{r_{o2} \parallel (\frac{1}{g_{m1}} + R_L)\}]$$

(ignore  $r_{o1}$  for now) — ①

$$\frac{V_{out} - V_x}{R_L} = \bar{i}_{out}$$

$$\Rightarrow V_{out} = \bar{i}_{out} R_L + V_x \quad \text{--- ②}$$

$$\bar{i}_{out} = -g_{m1}(V_{in} - V_x) \Rightarrow V_{in} + \frac{\bar{i}_{out}}{g_{m1}} = V_x \quad \text{--- ③}$$

- Substitute ② & ③ into ① and solve for



$$\frac{\bar{i}_{out}}{V_{in}} :$$

$$\frac{\bar{i}_{out}}{V_{in}} \cong - \frac{1}{R_L + \frac{1}{g_{m1}} + g_{m2}R_D \{r_{o2} \parallel (\frac{1}{g_{m1}} + R_L)\}} = G_{c.L.}$$



$$R_{in, closed} \rightarrow \infty$$

$$R_{out, closed}$$
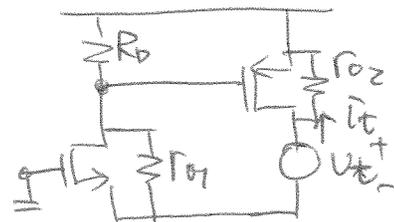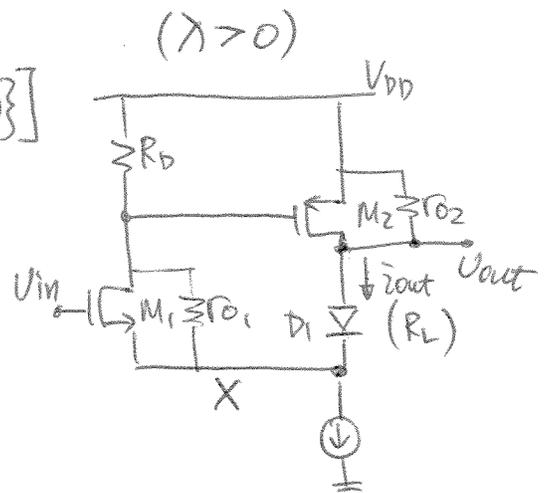
$$= r_{o2} + \left( \frac{r_{o1} + R_D}{1 + g_{m1}r_{o1}} \right)$$



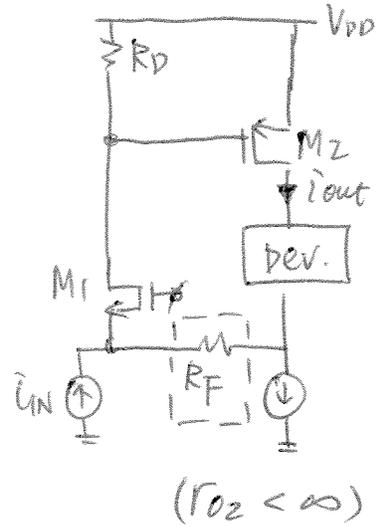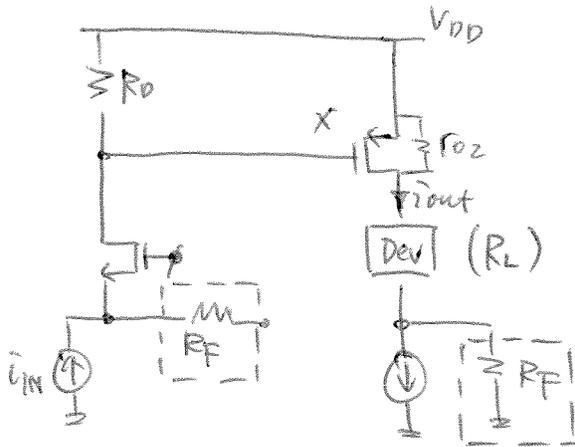5b. Breaking the feedback loop results in the following circuit :



$$A_{I, o.l.} = \frac{\bar{i}_{out}}{\bar{i}_{in}} = \frac{\bar{i}_{out}}{V_x} \times \frac{V_x}{\bar{i}_{in}}$$

$$= -g_{m2} \times \frac{(R_L + R_F) \parallel r_{o2}}{(R_L + R_F)} \times R_D$$

$$R_{in, open} = \frac{1}{g_{m1}}$$

$$R_{out, open} = r_{o2} + R_F$$

- Feedback factor  $K$  :

$$K = \frac{\bar{i}_y}{\bar{i}_x} = -1$$





$$\Rightarrow A_{I, c.l.} = \frac{A_{I, o.l.}}{1 + A_{I, o.l.} \times K} = \frac{A_{I, o.l.}}{1 - A_{I, o.l.}}$$

$$R_{in, closed} = \frac{1/g_{m1}}{1 - A_{I, o.l.}}$$

$$R_{out, closed} = (r_{o2} + R_F)(1 - A_{I, o.l.})$$

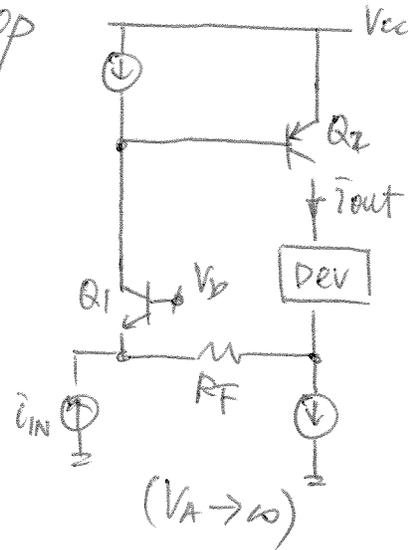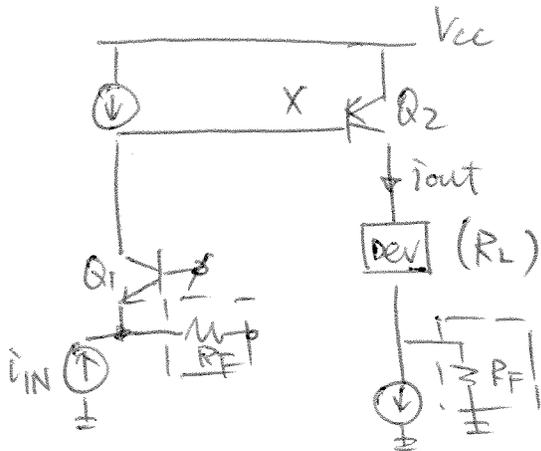57. Breaking the feedback loop results in the following circuit:





$$A_{I, o.l.} = \frac{i_{out}}{i_{in}} = \frac{i_{out}}{v_x} \times \frac{v_x}{i_{in}}$$

$$\cong -g_{m2} \times r_{\pi2} = \beta_2$$

$$R_{in, OPEN} = \frac{r_{\pi1}}{\beta_1 + 1} \approx \frac{1}{g_{m1}} \quad R_{out, OPEN} \rightarrow \infty$$

(Note:  $R_{out} \rightarrow \infty$  because there is no current path:)

- Feedback factor  $k$ :

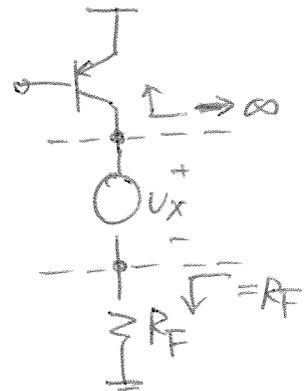
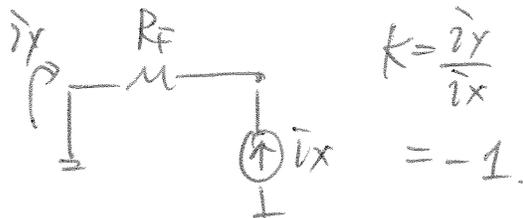


$$\Rightarrow A_{I, \text{C.L.}} = \frac{A_{I, \text{O.L.}}}{1 + A_{I, \text{O.L.}} \times K} = \frac{\beta_2}{1 - \beta_2}$$

$$R_{\text{in, CLOSED}} = \frac{1/g_{m_1}}{1 - \beta_2}$$

$$R_{\text{out, CLOSED}} \rightarrow \infty$$

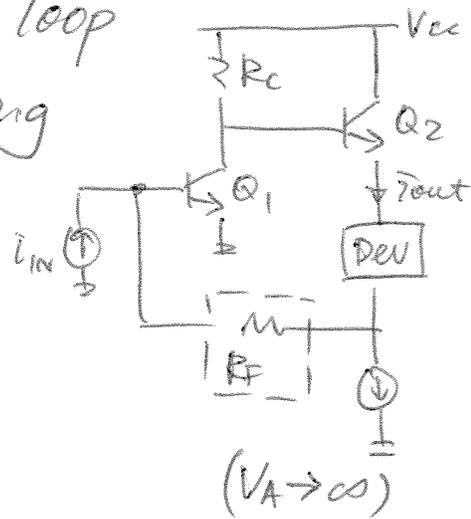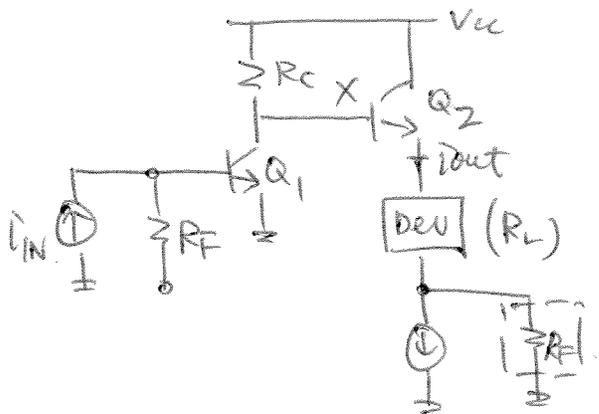58. Breaking the feedback loop results in the following circuit:



$$A_{I,OL} = \frac{i_{out}}{i_{in}} = \frac{i_{out}}{u_x} \times \frac{u_x}{i_{in}}$$


$$= \frac{g_{m2}(R_L + R_F)}{1 + g_{m2}(R_L + R_F)} \times \left[ \beta_1 \times \left[ R_C \parallel \left\{ r_{\pi 2} + (\beta_2 + 1)(R_L + R_F) \right\} \right] \right]$$

$$R_{in,open} = r_{\pi 1}$$

$$R_{out,open} \approx \frac{1}{g_{m2}} + R_F$$

- Feedback factor  $K$ :

$$K = \frac{i_y}{i_x} = -1$$

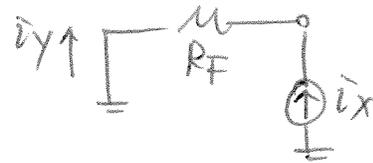


$$\Rightarrow A_{I,CL} = \frac{A_{I,OL}}{1 + A_{I,OL} \times K} = \frac{A_{I,OL}}{1 - A_{I,OL}}$$

$$R_{in,closed} = \frac{r_{\pi 1}}{1 - A_{I,OL}}$$


$$R_{out,closed} = \left( \frac{1}{g_{m2}} + R_F \right) (1 - A_{I,OL})$$

59.

(a)

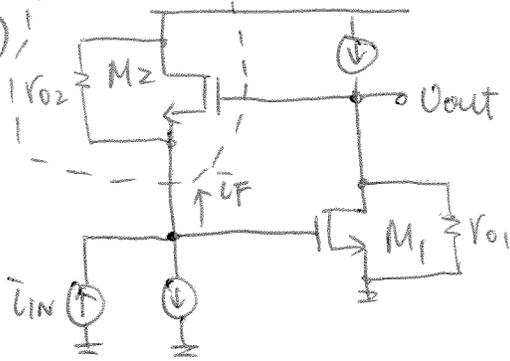

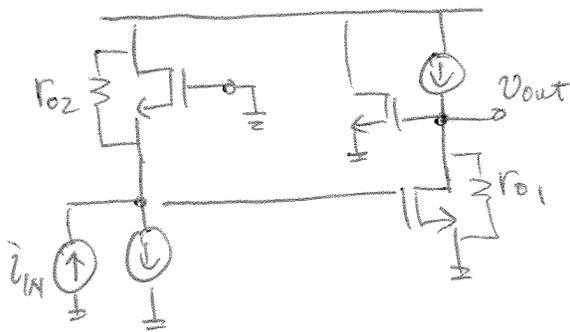Breaking the feedback network results in the following:




$$R_{OL} = \frac{v_{out}}{i_{IN}}$$

$$= -(r_{O2} \parallel \frac{1}{g_{m2}}) g_{m1} r_{O1}$$

$$R_{in, OPEN} = r_{O2} \parallel \frac{1}{g_{m2}}$$

$$R_{out, OPEN} = r_{O1}$$

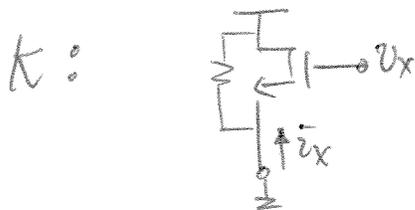



$$k = \frac{i_x}{v_x} = g_{m2}$$

$$\therefore R_{CL} = \frac{R_{OL}}{1 + R_{OL}k} = \frac{(r_{O2} \parallel \frac{1}{g_{m2}}) g_{m1} r_{O1}}{1 + g_{m1} g_{m2} r_{O1} (r_{O2} \parallel \frac{1}{g_{m2}})}$$

$$R_{IN, CLOSED} = \frac{(r_{O2} \parallel \frac{1}{g_{m2}})}{1 + g_{m1} g_{m2} r_{O1} (r_{O2} \parallel \frac{1}{g_{m2}})}$$

$$R_{out, CLOSED} = \frac{r_{O1}}{1 + g_{m1} g_{m2} r_{O1} (r_{O2} \parallel \frac{1}{g_{m2}})}$$

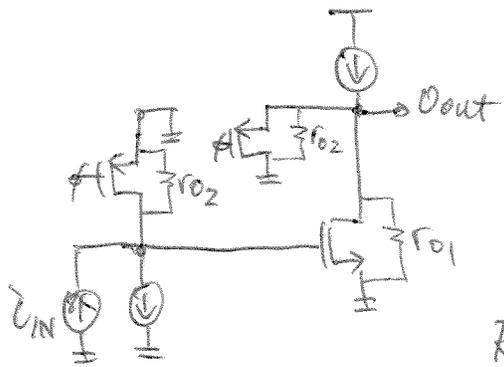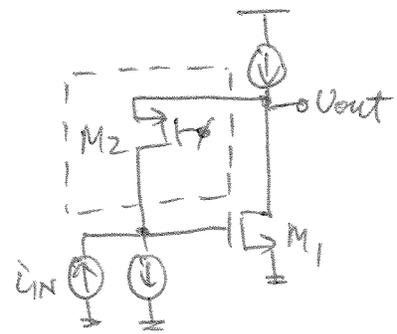(b) Breaking the feedback network results in the following:




$$R_{OL} = \frac{v_{out}}{v_{in}}$$

$$= -r_{O2} \times g_{m1} [r_{O1} \parallel r_{O2} \parallel \frac{1}{g_{m2}}]$$

$$R_{in, OPEN} = r_{O2}$$
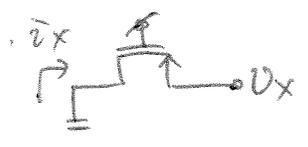
$$R_{out, OPEN} = r_{O1} \parallel r_{O2} \parallel \frac{1}{g_{m2}}$$





$$K = \frac{v_x}{v_x} = -g_{m2}$$

$$\therefore R_{CL} = \frac{R_{OL}}{1 + R_{OL}K} = \frac{-g_{m1}r_{O2} [r_{O1} \parallel r_{O2} \parallel \frac{1}{g_{m2}}]}{1 + g_{m1}g_{m2}r_{O2} [r_{O1} \parallel r_{O2} \parallel \frac{1}{g_{m2}}]}$$

$$R_{in, CLOSED} = \frac{r_{O2}}{1 + R_{OL}K}$$

$$R_{out, CLOSED} = \frac{r_{O1} \parallel r_{O2} \parallel \frac{1}{g_{m2}}}{1 + R_{OL}K}$$

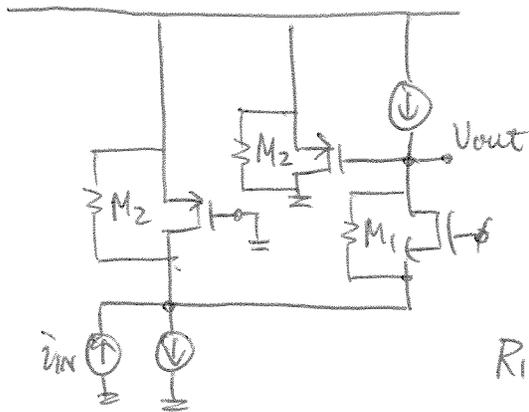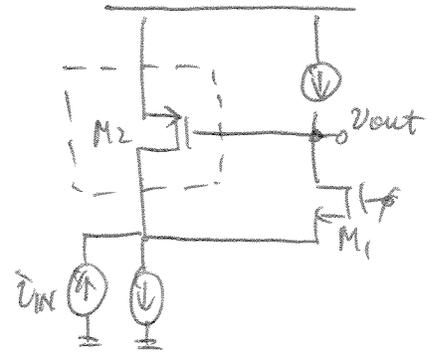(c) Breaking the feedback network results in the following:




$$R_{OL} = \frac{v_{out}}{i_{IN}}$$

$$\approx \left( \frac{1}{g_{m1}} \parallel r_{o2} \right) (1 + g_{m1} r_{o1})$$

$$R_{in, OPEN} \approx \frac{1}{g_{m1}} \parallel r_{o2}$$

$$R_{out, OPEN} = r_{o2} + r_{o1} (1 + g_{m1} r_{o2})$$

K:

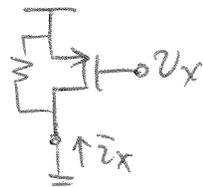

$$K = \frac{i_X}{v_X} = g_{m2}$$


$$\therefore R_{CL} = \frac{R_{OL}}{1 + R_{OL} K} = \frac{\left( \frac{1}{g_{m2}} \parallel r_{o2} \right) (1 + g_{m1} r_{o1})}{1 + g_{m2} \left( \frac{1}{g_{m1}} \parallel r_{o2} \right) (1 + g_{m1} r_{o1})}$$

$$R_{in, CLOSED} = \frac{\frac{1}{g_{m1}} \parallel r_{o2}}{1 + R_{OL} \cdot K}$$


$$R_{out, CLOSED} = \frac{r_{o2} + r_{o1} (1 + g_{m1} r_{o2})}{1 + R_{OL} \cdot K}$$

60.


(a)

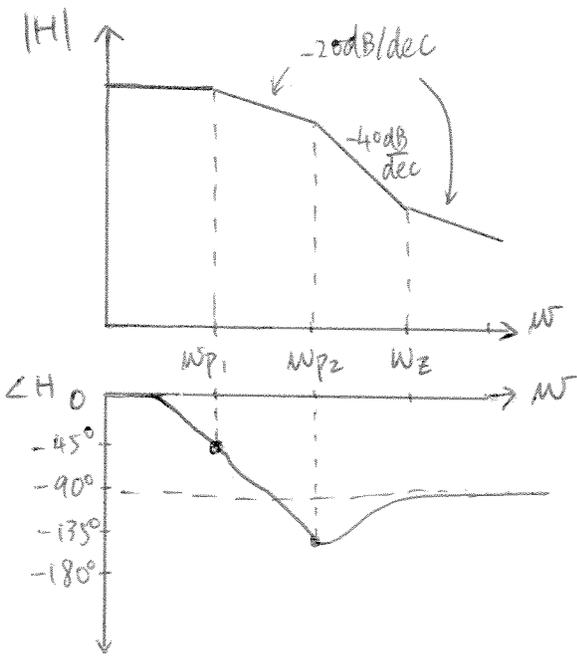


(b)

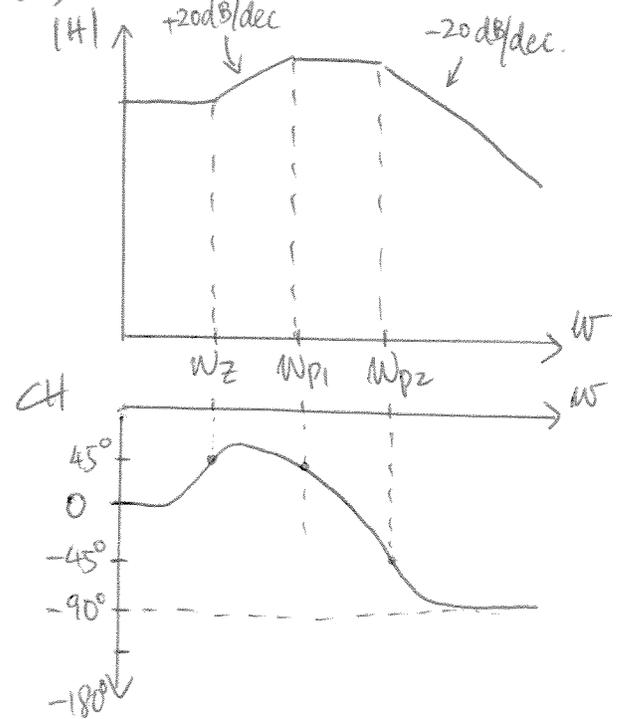

(c)

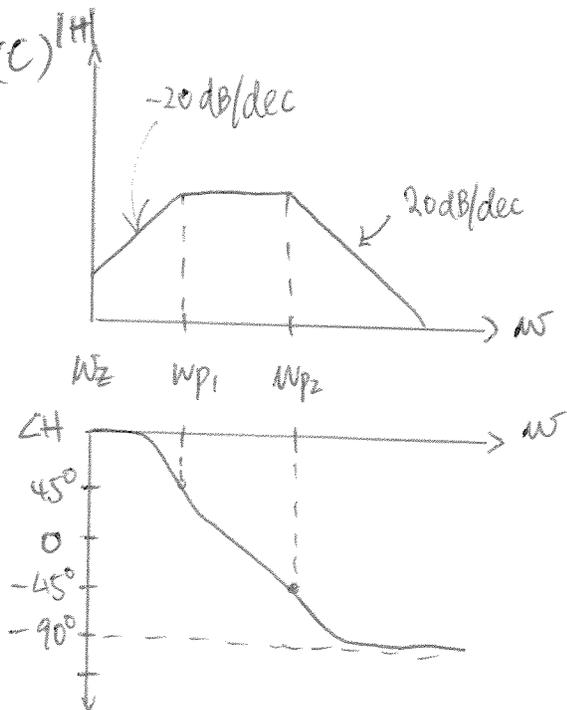



(d)

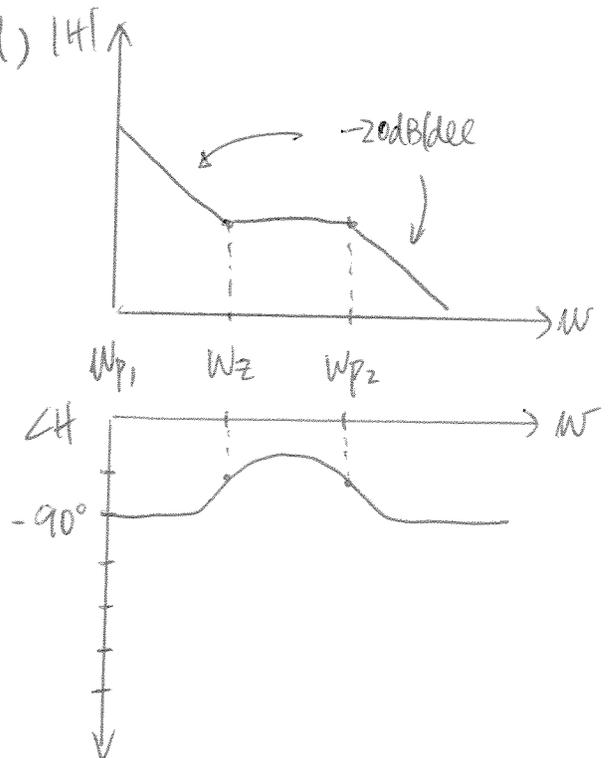

61. As  $\omega_z$  comes closer to  $\omega_{p1}$  or  $\omega_{p2}$ , it cancels out the effect (i.e.  $-20\text{dB/dec}$  decrease) — pole-zero cancellation. It would appear as if nothing occurred at that overlapping frequency.


62.

Calculate  $G_m(s)$  of circuit:

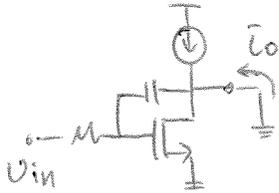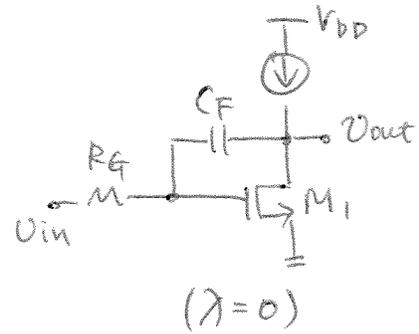



$$G_m = \frac{\bar{i}_o}{V_{in}}$$
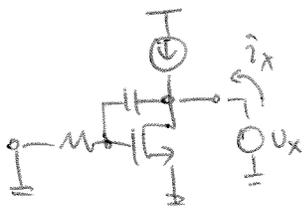
$$= g_{m1} \times \frac{1}{1 + sC_F R_G}$$




$$Z_{out} = \frac{V_x}{\bar{i}_x} = \frac{1 + sC_F R_G}{sC_F (1 + g_{m1} R_G)}$$
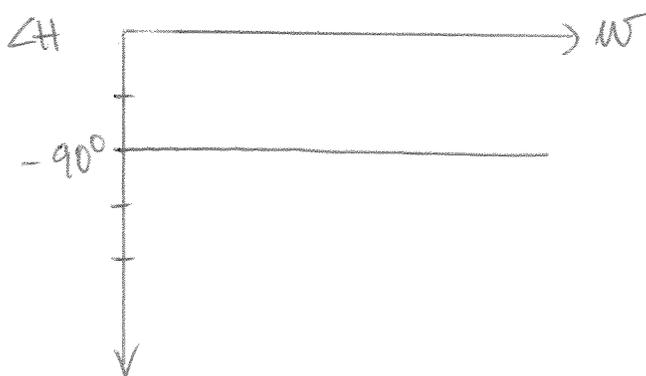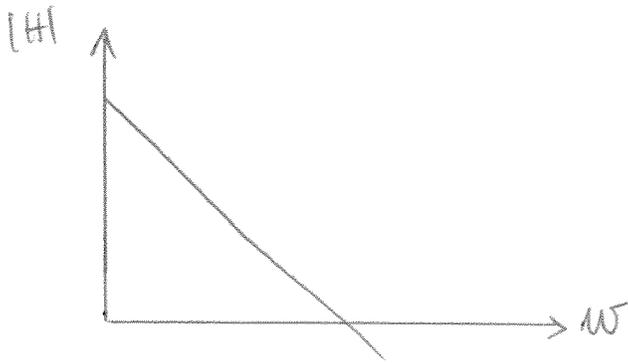
$$\Rightarrow H(s) = G_m \times Z_{out} = \frac{g_{m1}}{g_{m1} R_G + 1} \times \frac{1}{sC_F} = \frac{1}{(g_{m1} R_G + 1) s \left( \frac{C_F}{g_{m1}} \right)}$$



63. By Nyquist Criterion, decreasing  $K$  ( $K \rightarrow 0$ ) eventually leads to  $|KH| < 1$  at  $\angle H = -180^\circ$ , which implies stability.

6A.

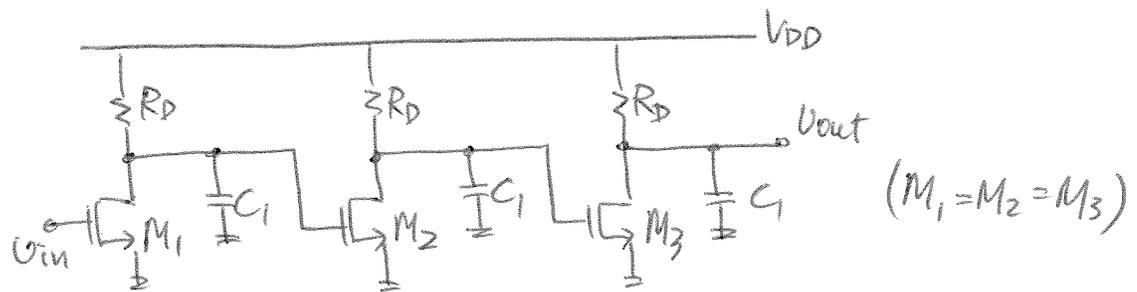

$$H(s) = \frac{V_{out}}{V_{in}}(s) = \frac{(-g_m R_D)^3}{\left(1 + \frac{s}{\omega_p}\right)^3} \quad \text{where } \omega_p = \frac{1}{R_D C_1}$$

$$\begin{aligned} \Rightarrow \angle H(j\omega) &= \angle (-g_m R_D)^3 - \angle \left(1 + j\frac{\omega}{\omega_p}\right)^3 \\ &= 0 - 3 \text{TAN}^{-1}\left(\frac{\omega}{\omega_p}\right) \end{aligned}$$

$$\therefore \angle H \Big|_{\omega=0.1\omega_p} = -3 \text{TAN}^{-1}\left(\frac{0.1\omega_p}{\omega_p}\right) \cong -17.1^\circ$$


$$65. \quad H(s) = \frac{(-g_m R_D)^3}{\left(1 + \frac{s}{\omega_p}\right)^3} \quad (M_1 = M_2 = M_3)$$

$$\Rightarrow |H| \Big|_{\omega=\omega_p} = \frac{|g_m R_D|^3}{\left|(1 + j \frac{\omega_p}{\omega_p})^3\right|} = \frac{(g_m R_D)^3}{(\sqrt{1+1})^3} = \frac{(g_m R_D)^3}{\sqrt{8}}$$

$$\begin{aligned} \Rightarrow 20 \log |H| \Big|_{\omega=\omega_p} &= 20 \log (g_m R_D)^3 - 20 \log \sqrt{8} \\ &\cong 20 \log (g_m R_D)^3 - (9 \text{ dB}) \end{aligned}$$

$\therefore |H|$  falls by 9 dB due to the three coincident poles.

6b.

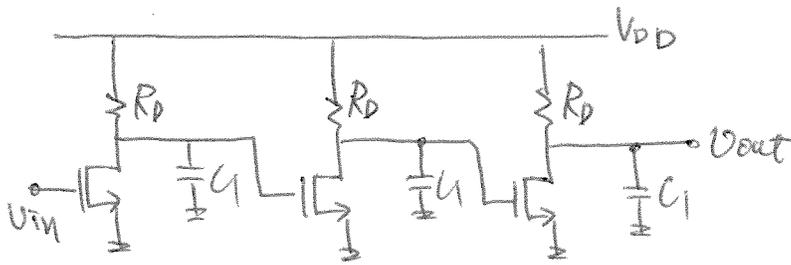


$$\omega_p = \frac{1}{R_D C_1}$$

$$k = 0.1$$

$$H(j\omega) = \frac{(-g_m R_D)^3}{(1 + j\frac{\omega}{\omega_p})^3}$$
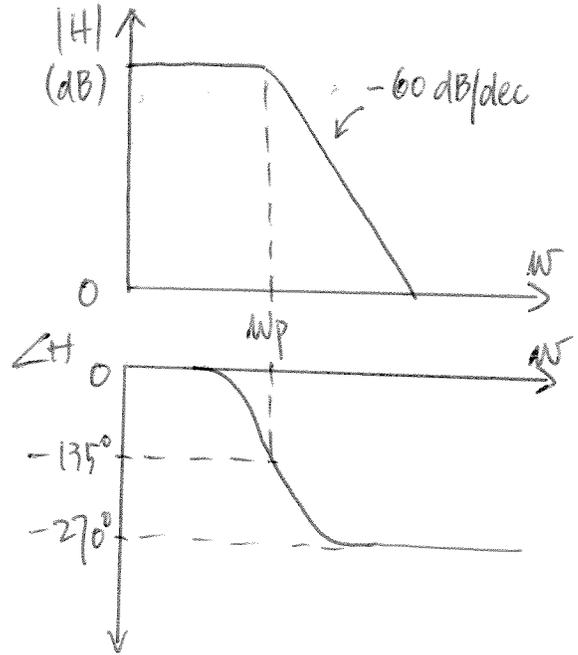
$$\angle H = -3 \tan^{-1}\left(\frac{\omega}{\omega_p}\right)$$




- Need to guarantee that  $|KH| < 1$  when  $\angle H = -180^\circ$ :

$$\angle H = -180^\circ = -3 \tan^{-1}\left(\frac{\omega}{\omega_p}\right) \Rightarrow \omega = \sqrt{3} \omega_p$$

$$|KH(j\omega)|_{\omega=\omega_p\sqrt{3}} = \frac{(g_m R_D)^3}{(\sqrt{1+3})^3} \times 0.1 < 1$$



$$\Rightarrow g_m R_D < \sqrt[3]{80} \approx 8.94$$

67.

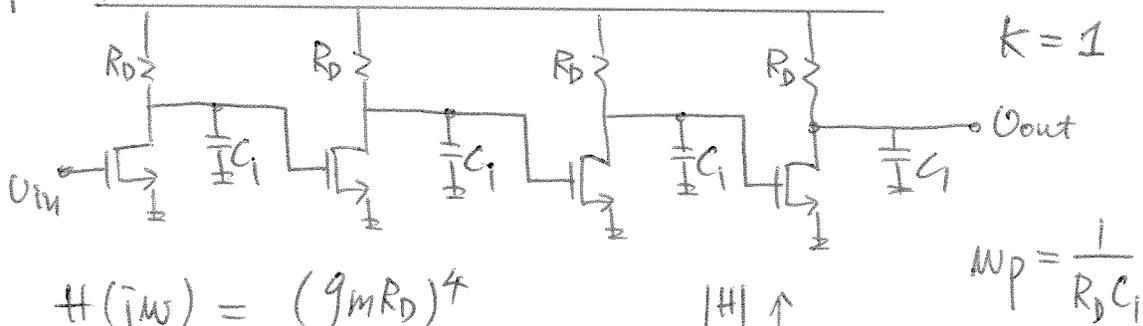

$$H(j\omega) = \frac{(g_m R_D)^4}{(1 + j\frac{\omega}{\omega_p})^4}$$
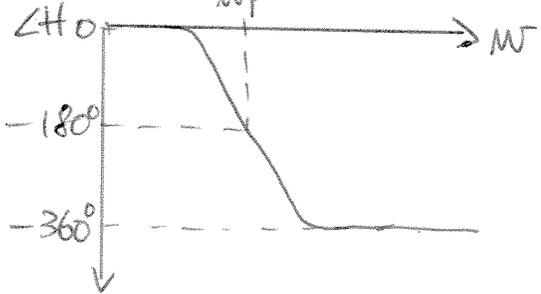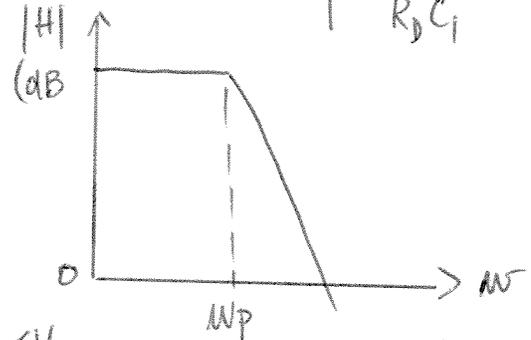
$$\angle H = -4 \tan^{-1}\left(\frac{\omega}{\omega_p}\right)$$



- To guarantee stability,

$$|KH| < 1 \text{ when } \angle H = -180^\circ$$

$$\angle H = -180^\circ = -4 \tan^{-1}\left(\frac{\omega}{\omega_p}\right) \Rightarrow \omega = \omega_p$$


$$|KH| \Big|_{\omega=\omega_p} = \frac{(g_m R_D)^4}{(\sqrt{1+1})^4} < 1$$

$$\Rightarrow g_m R_D < \sqrt{2}$$

This four-pole system implies a lower upper-limit ( $=\sqrt{2}$ ) on  $g_m R_D$ , which makes sense since  $|H|$  drops faster here.

68.  $H(s) = \frac{A_0}{1 + \frac{s}{\omega_p}}$

$k = 1.$

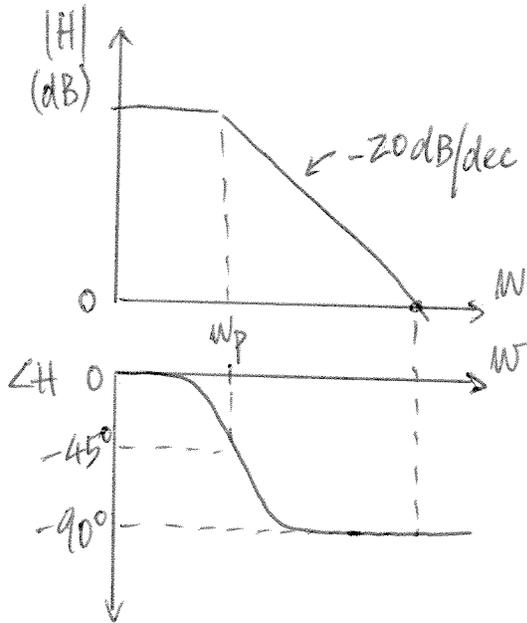


$\therefore$  Phase margin  
 $= 180^\circ - 90^\circ = 90^\circ$

(i.e. system is stable.)

69.  $H(s) = \frac{A_0}{1 + \frac{s}{\omega_p}}$

$K = 0.5$

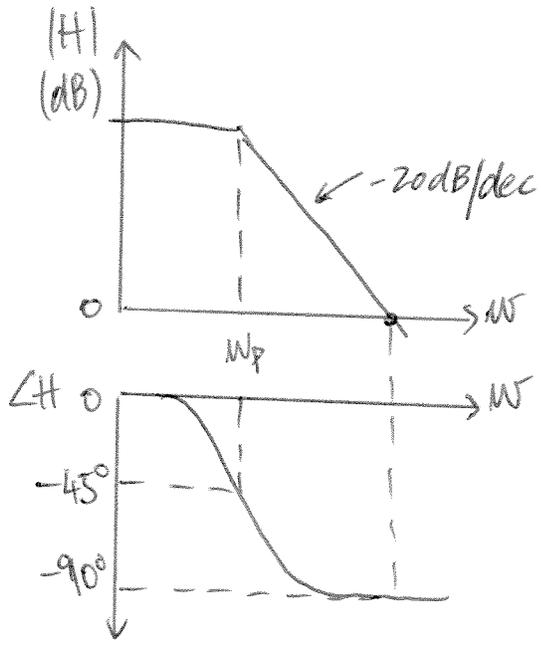

Phase margin =  $90^\circ$   
 (independent of  $K$  for one-pole systems.)

70. All three scenarios will become stable eventually (depending on how far  $w_{ax}$  is from  $w_{px}$ , &  $w_{ax} < w_{px}$ .)

71. In the  $20 \cdot \log |kH|$  vs.  $\log |w|$  plot, the magnitude plot decreases at a rate of  $20 \text{ dB/dec}$ . between  $w_{p1}$  &  $w_{p2}$ .

$$k=1 \Rightarrow 20 \log |H|$$


$$k=0.5 \Rightarrow 20 \log \left| \frac{H}{2} \right| = 20 \log |H| - 6 \text{ dB}$$

$\therefore k=0.5$  induces a  $6 \text{ dB}$  decrease on the magnitude plot at all frequencies.

$$\Rightarrow \Delta W_{ax} [\log] = \frac{6 \text{ dB}}{20 \text{ dB}} \approx -0.3$$

$$\frac{W_{ax}}{W_{ax}'} = 10^{\frac{6 \text{ dB}}{20 \text{ dB}}} \approx 0.5$$
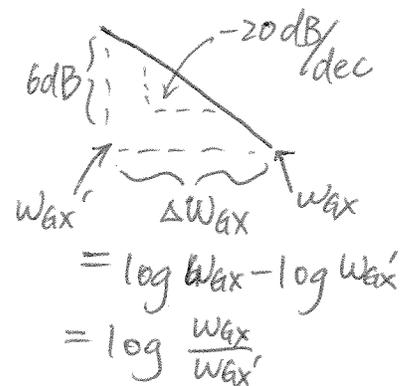
$$\Rightarrow W_{ax}' = \frac{W_{ax}}{0.5} = 2W_{ax}$$



$$\angle H = -\text{TAN}^{-1} \left[ w \left( \frac{1}{w_{p1}} + \frac{1}{w_{p2}} \right) \right] \approx -\text{TAN}^{-1} \left( \frac{w}{w_{p1}} \right) \quad (w_{p2} \gg w_{p1})$$

$\Rightarrow$  Phase plot stays the same with  $k=0.5$ .


$$\text{In original example } \angle H(w_{p2}) \approx -\text{TAN}^{-1} \left( \frac{w_{ax}}{w_{p1}} \right) = -135^\circ$$

$$\angle H(w_{ax}') = \angle H(2w_{ax}) \approx -\text{TAN}^{-1} \left( \frac{2w_{ax}}{w_{p1}} \right)$$


$$\Rightarrow \angle H(w_{ax}') = -\text{TAN}^{-1} [2 \text{TAN } 135^\circ] \approx -116^\circ$$

$$\Rightarrow \text{Phase Margin} = 180^\circ + \angle H(w_{ax}') \approx 63^\circ$$

(72) When  $k$  drops by a factor of 2, the phase margin improves. This is because a lower  $k$  corresponds to shifting the amplitude part of  $kH$  down by 6 dB. (The phase  $\angle kH$  remains unchanged, since phase is only dependent on pole location and is independent of amplitude of  $kH$ .)  
 Thus, the gain  $|kH|$  drops to 0 dB at a lower frequency. This results in a larger phase margin.

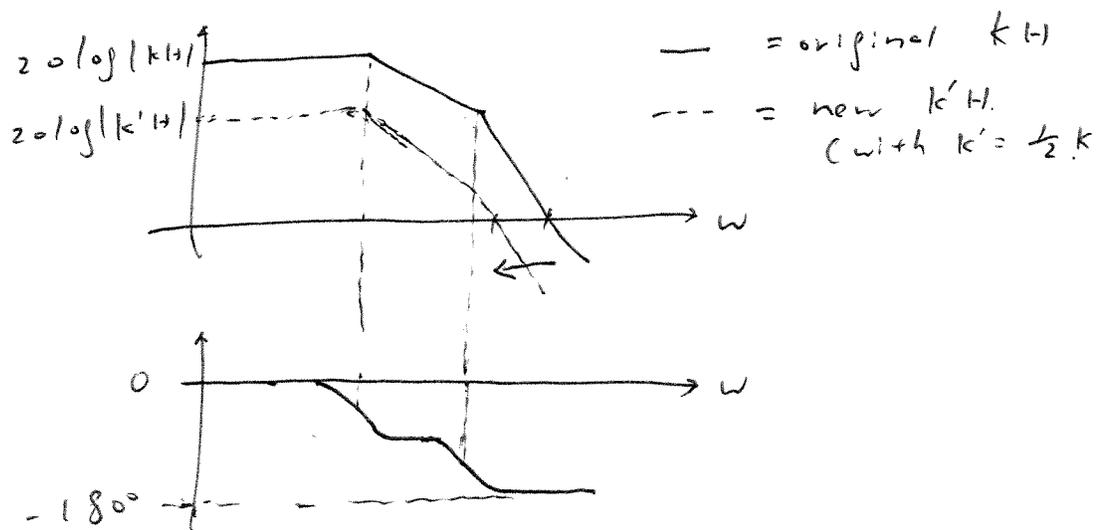

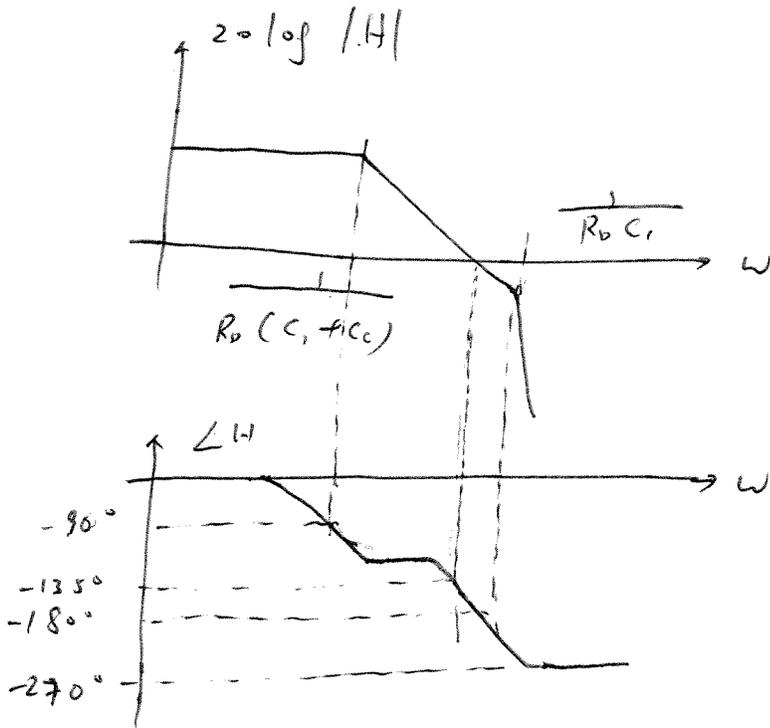73) With the compensation capacitor  $C_c$  in place, the pole associated with  $C_c$  becomes dominant (i.e. at a lower frequency than the other 2 poles at  $\frac{1}{R_D C_1}$ ).



74

Open-loop gain,  $A_o = f_{mN} (R_{oN} // R_{op})$

$$= 50$$

Closed-loop gain,  $\frac{V_{out}}{V_{in}} = \frac{f_{mN} (R_{oN} // R_{op})}{1 + \frac{R_2}{R_1 + R_2} f_{mN} (R_{oN} // R_{op})}$

$$= \frac{50}{1 + \frac{R_2}{R_1 + R_2} \times 50}$$

$$= 4$$

$$\therefore 4 = \frac{50}{1 + \frac{R_2}{R_1 + R_2} \times 50}$$

$$1 + \frac{50 R_2}{R_1 + R_2} = 12.5$$

$$\frac{R_2}{R_1 + R_2} = 0.23$$

Choosing  $R_{o2} // R_{o4} = 5 \text{ k}\Omega$ ,

i.e.  $f_{mN} = 10 \text{ mS} //$

and  $R_1 + R_2 \approx 50 \text{ k}\Omega$ ,

$$\therefore R_2 = 0.23 \times 50 \text{ k}\Omega$$

$$= 11.5 \text{ k}\Omega //$$

$$\text{and } R_1 = 38.5 \text{ k}\Omega //$$

75

Open loop gain,  $A_0 = \beta_m R_D$

(assuming  $R_1 + R_2$  is very large.)

$$\text{i.e. } \beta_m R_D = 10$$

$$\begin{aligned} \text{Closed-loop gain} &= \frac{\beta_m R_D}{1 + \left(\frac{R_2}{R_1 + R_2}\right) \beta_m R_D} \\ &= 2 \end{aligned}$$

$$\therefore \frac{10}{1 + \left(\frac{R_2}{R_1 + R_2}\right) \times 10} = 2$$

$$\frac{R_2}{R_1 + R_2} = 0.4$$

$$\begin{aligned} \text{Closed-loop input impedance} &= \frac{1}{\beta_m} \left[ 1 + \frac{R_2}{R_1 + R_2} \times 10 \right] \\ &= 50 \Omega. \end{aligned}$$

$$\therefore \frac{1}{\beta_m} \times 5 = 50$$

$$\beta_m = 0.15 //$$

$$\therefore R_D = 100 \Omega //$$

$$\begin{aligned} \therefore R_1 + R_2 &= 10 \times 100 \Omega \\ &= 1 \text{ k}\Omega. \end{aligned}$$

$$\therefore R_2 = 400 \Omega //$$

$$R_1 = 600 \Omega //$$

$$\textcircled{76} \quad \text{Open-loop gain} = R_{D1} (g_{m2} R_{D2})$$

$$= 10 \text{ k}\Omega$$

$$\text{closed-loop gain} = \frac{10 \text{ k}\Omega}{1 + \frac{10 \text{ k}\Omega}{R_F}}$$

$$= 1 \text{ k}\Omega.$$

$$\frac{10}{1 + \frac{10 \text{ k}\Omega}{R_F}} = 1 \text{ k}\Omega$$

$$\therefore R_F = 1.11 \text{ k}\Omega //$$

$$\text{closed-loop input impedance} = \frac{1}{g_{m1}} (1 + g) ^{-1}$$

$$= 50 \Omega.$$

$$\therefore g_{m1} = 2 \text{ mS} //$$

$$\text{closed-loop output impedance} = \frac{R_{D2}}{10}$$

$$= 200 \Omega.$$

$$\therefore R_{D2} = 2000 \Omega //$$

$$\therefore R_{D1} = 1 \text{ k}\Omega.$$

$$\therefore g_{m2} = 5 \text{ mS} //$$

(77) Assuming  $R_F$  is very large,

$$\text{open-loop gain} = R_D (f_{m2} R_C)$$

$$= 10 \text{ k}\Omega$$

$$\text{closed-loop gain} = \frac{10 \text{ k}\Omega}{1 + \frac{10 \text{ k}\Omega}{R_F}}$$

$$= 1 \text{ k}\Omega.$$

$$\therefore R_F = 1.11 \text{ k}\Omega //$$

$$\text{closed-loop input impedance} = \frac{1}{f_{m1}} (1 + \beta)^{-1} = 50 \Omega.$$

$$f_{m1} = 2 \text{ mS} //$$

$$\text{closed-loop output impedance} = \frac{R_C}{10}$$

$$\therefore R_C = 2000 \Omega //$$

$$R_D = 1 \text{ k}\Omega.$$

$$\therefore f_{m2} = 5 \text{ mS} //$$

$$\textcircled{78} \text{ a) open-loop gain} = R_c (f_m R_m)$$

$$\approx 20 \text{ k}\Omega$$

$$f_m = \frac{I}{V_T}$$

$$\therefore f_m = \frac{1 \text{ mA}}{26 \text{ mV}} = 38.5 \text{ ms}$$

$$\therefore R_c R_m = \frac{20 \text{ k}\Omega}{38.5 \text{ ms}}$$

$$\text{open-loop output impedance} = R_m \quad (-: V_o = \infty)$$

$$\therefore R_m = 500 \Omega //$$

$$R_c = 1040 \Omega //$$

---

$$\text{b) closed-loop gain} = \frac{20 \text{ k}\Omega}{1 + \frac{20 \text{ k}\Omega}{R_F}}$$

$$= 1 \text{ k}\Omega$$

$$\therefore R_F = 1053 \Omega //$$

$$\text{c) closed-loop input impedance} = \frac{\frac{1}{38.5 \text{ ms}}}{1 + \frac{20 \text{ k}}{1053}}$$

$$= 1.30 \Omega //$$

$$\text{closed-loop output impedance} \approx (500) \left( \frac{1}{20} \right)$$

$$= 25 \Omega //$$

79

Open-loop voltage gain

$$= \frac{R_{D1}}{\frac{1}{g_{m1}} + R_1 // R_2} \cdot [g_{m2} (R_1 // R_2)]$$

$$= 20 \quad \text{--- (1)}$$

$$\text{closed-loop gain} = \frac{20}{1 + 20 \left( \frac{R_2}{R_1 + R_2} \right)} = 4$$

$$\therefore \frac{R_2}{R_1 + R_2} = 0.2 \quad \text{--- (2)}$$

Open-loop output impedance =  $R_1 + R_2$

$$= 2 \text{ k}\Omega$$

$$\therefore R_2 = 0.4 \text{ k}\Omega //$$

$$R_1 = 1.6 \text{ k}\Omega //$$

From (1),

$$\frac{R_{D1}}{\frac{1}{g_{m1}} + 2 \text{ k}\Omega} [g_{m2} \times 320 \Omega] = 20$$

$$\frac{g_{m1} R_{D1}}{1 + 2 \text{ k} g_{m1}} \times g_{m2} = 0.0625$$

$$\text{Setting } g_{m1} = g_{m2} = 20 \text{ mS} //$$

$$R_{D1} = 6400 \Omega //$$

To minimize power consumption,  $g_{m1}$  and  $g_{m2}$  should be minimized. (and  $R_D$  maximized)

80

$$\text{Since } A_{OL} = \frac{f_{m1} \left( \frac{1}{f_{m2}} + \frac{R_1 // R_2}{\beta_2 + 1} \right)}{1 + f_{m1} \left( \frac{1}{f_{m2}} + \frac{R_1 // R_2}{\beta_2 + 1} \right)} \times f_{m2} (R_1 + R_2)$$

$$R_{out, closed} = \frac{R_1 + R_2}{1 + A_{OL} k}$$

$$\therefore A_{OL} = 2$$

$$\therefore 2 = \frac{A_{OL}}{1 + A_{OL} k}$$

$$\text{set } f_{m1} = f_{m2} = 50 \text{ mV}, \quad (R_1 + R_2) = 1 \text{ k}$$

$$A_{OL} = \frac{50 \text{ mV} \left( \frac{1}{50 \text{ mV}} + \frac{R_1 // R_2}{101} \right)}{1 + 50 \text{ mV} \left( \frac{1}{50 \text{ mV}} + \frac{R_1 // R_2}{101} \right)} \times 50 \text{ mV} (1 \text{ k})$$

$$\approx \frac{1 + 10^{-5} (R_1 // R_2)}{2 + 10^{-5} (R_1 // R_2)} \times 50$$

$$\approx 25$$

$$\therefore 2 = \frac{25}{1 + .25 \text{ k}}$$

$$\therefore k = 0.46 \quad [\therefore R_1 = 460 \Omega, \quad R_2 = 540 \Omega]$$

$$R_{out, closed} = \frac{1 \text{ k}\Omega}{1 + 25 \times 0.46}$$

$$= 80 \Omega //$$

$$\textcircled{81} \text{ open-loop gain } (A_{OL}) = -\beta m_1 (R_F // r_{\pi 1}) / x \\ [R_C // [r_{\pi 2} + (\beta_2 + 1) R_F]]$$

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL} \frac{1}{R_F}}$$

$$\therefore A_{CL} = 1000 \Omega$$

$$1000 = \frac{A_{OL}}{1 + \frac{A_{OL}}{R_F}}$$

$$R_{in, \text{closed}} = \frac{R_F // r_{\pi 1}}{1 + \frac{A_{OL}}{R_F}} = 50 \Omega$$

$$R_{out, \text{closed}} = \frac{R_C}{1 + \frac{A_{OL}}{R_F}} = 50 \Omega$$

setting  $R_F = 1200 \Omega$ .

$$\therefore A_{OL} = 6000 \Omega //$$

$$\therefore r_{\pi 1} = 400 //$$

$$\beta m_2 = 2.5 \text{ mV} //$$

Assume  $\beta_2 = 100$ , and  $\beta m_1 = \beta m_2$ ,

$$R_C = 8570 \Omega //$$