

# CMOS Analog Integrated Circuit Design

## Lecture 9: Bandgap Voltage References & SC Circuits

Reading: Razavi, Chs. 11, 12, Johns, Chs. 7, 14


Mohammad Yavari  
Amirkabir University of Technology

E-mail: [myavari@aut.ac.ir](mailto:myavari@aut.ac.ir)

Copyright © 2013 by M. Yavari
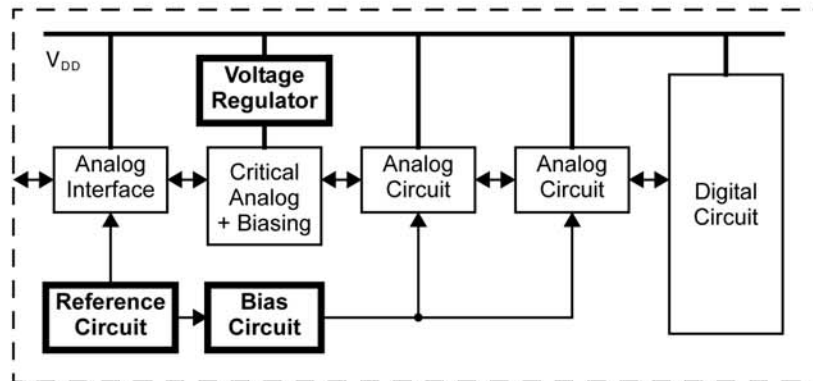
## Applications

- Bias currents and voltages in analog circuits: mirrors, diff pairs, common-mode levels, etc.
- Reference voltage or current in A/D and D/A converters.




## Basic Idea

- The main goal is to establish a dc voltage that is independent of the supply voltage, process parameters, and the temperature variations.
- Use a Zener diode breakdown voltage: it is beyond the supply voltage.
- Difference between threshold voltages of an enhancement and a depletion MOSFETs => depletion devices are not available.
- Combine two phenomena that vary with T in opposite directions, e.g., add two voltages with positive and negative TCs, such that the sum has zero TC.
- The dependence on temperature assumes one of two forms:
  - Proportioned to absolute temperature (PTAT)
  - Contrary to absolute temperature (CTAT)

$$V_{Ref} = \alpha_1 V_1 + \alpha_2 V_2 \quad \rightarrow \quad \frac{\partial V_{Ref}}{\partial T} = \alpha_1 \frac{\partial V_1}{\partial T} + \alpha_2 \frac{\partial V_2}{\partial T} = 0$$

**Zero temp coefficient**

## CTAT Voltage Generation

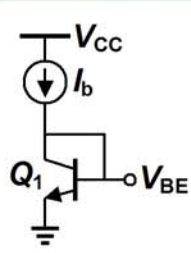

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$V_T = kT/q$$

$$I_S \propto \mu kT n_i^2, \quad \mu \propto \mu_0 T^{m=-3/2}$$

$$n_i^2 \propto T^3 \exp\left(-\frac{E_g}{kT}\right)$$

→

$$I_S \propto T^{4+m} \exp\left(-\frac{E_g}{kT}\right)$$

→

$$V_{BE} = V_T \ln \frac{I_C}{I_S} \quad \rightarrow \quad \frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln \frac{I_C}{I_S} - \frac{V_T}{I_S} \frac{\partial I_S}{\partial T}$$

→


$$\frac{\partial V_{BE}}{\partial T} = \frac{V_T}{T} \ln \frac{I_C}{I_S} - (4+m) \frac{V_T}{T} - \frac{E_g}{kT^2} V_T = \frac{V_{BE} - (4+m)V_T - E_g/q}{T}$$

→

$$V_{BE} \approx 750 mV \Rightarrow \frac{\partial V_{BE}}{\partial T} @ T = 300^\circ K \approx -1.5 mV / ^\circ K \quad \text{An example}$$


- The base-emitter voltage of a forward biased diode-connected BJT with a fixed collector current has a negative TC. => **CTAT generator**
- TC of  $V_{BE}$  is temperature dependent => needing a variable PTAT generator.

## PTAT Voltage Generation

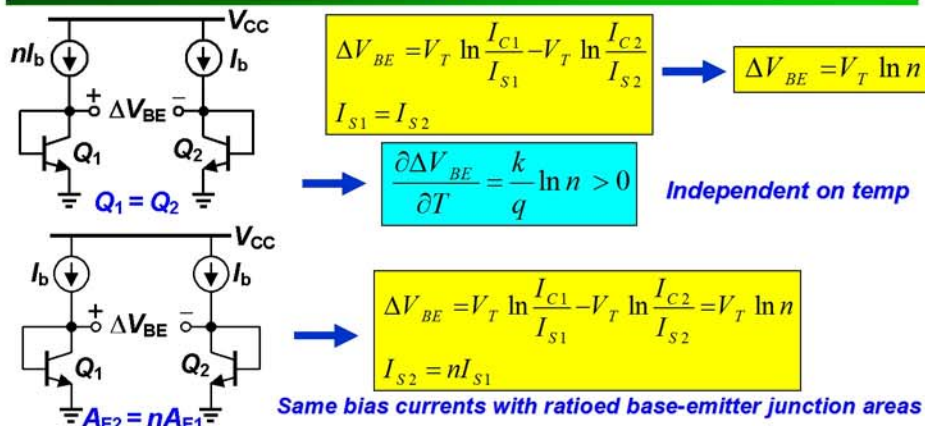


- Two identical transistors biased with different currents.
- The difference between the base-emitter voltage of two BJT transistors with different collector currents has a positive TC. => **PTAT generator**
- Base currents are neglected => in practice, a beta correction circuit is needed.

## General Block Diagram

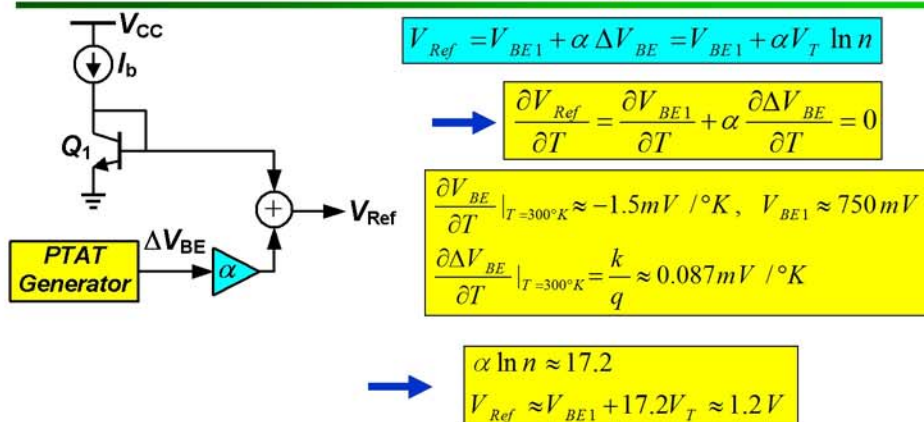


- Add PTAT and CTAT voltages with proper weights to achieve a zero TC.
- A temperature independent voltage reference is only realized at  $T = 300^{\circ}K$ .

## Conceptual Scheme

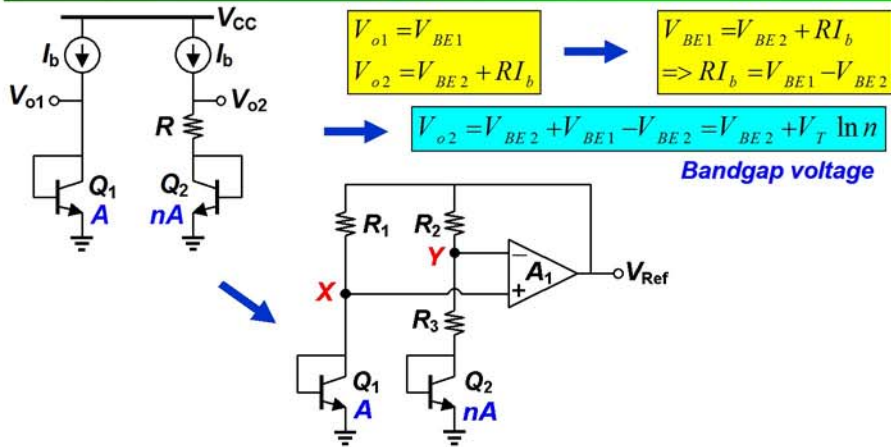

- Suppose  $V_{O1}$  and  $V_{O2}$  are somehow made equal.
- How do we make the  $V_{O1}$  and  $V_{O2}$  equal?
- How do we avoid  $\ln n = 17.2$ ?
- Use an op-amp in negative feedback and a passive voltage divider.

## Bandgap Voltage Reference Circuit

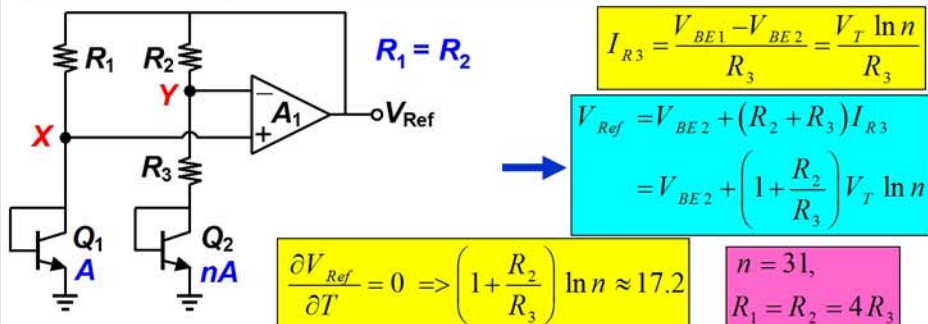

$$n = 31,$$

$$R_1 = R_2 = 4R_3$$

**An example**

$$I_{C1} = I_{C2} \approx \frac{V_T \ln n}{R_3}$$

**PTAT**

→


$$\frac{\partial V_{BE}}{\partial T} = \frac{V_{BE} - (3+m)V_T - E_g/q}{T}$$

- But, the collector current of both transistors is not temperature independent => changing TC of  $V_{BE}$ .
- In practice, accurate simulations are needed to estimate the TC of  $V_{BE}$ .


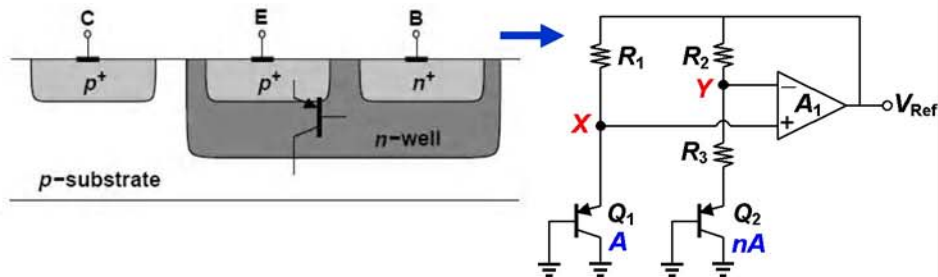
## Compatibility with CMOS Technology

- Bipolar characteristics are essential here. Attempts at building purely CMOS precision references have not been very successful.
- How do we build this in CMOS?
- Called the lateral BJT has a small beta respected to the conventional vertical BJT transistors.
- Substrate is connected to the ground => collector is also connected to the GND.




M. Yavari

CMOS Analog IC Design

Lecture 9: Bandgap References & SC Circuits
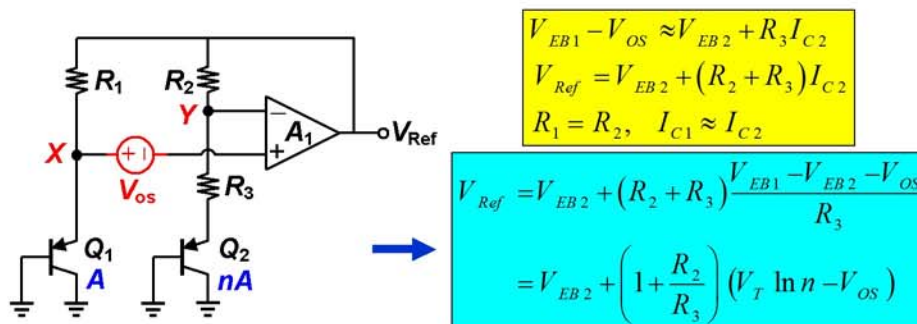
## Effect of Circuit Non-Idealities

- The op-amp non-idealities introduce various errors here. Let's consider the effect of offset.
- The op-amp offset voltage is multiplied by  $(1+R_2/R_3)$ .
- $V_{OS}$  changes with temperature => increasing the overall TC.
- Note, the TC of resistors is not important!




M. Yavari

CMOS Analog IC Design

Lecture 9: Bandgap References & SC Circuits
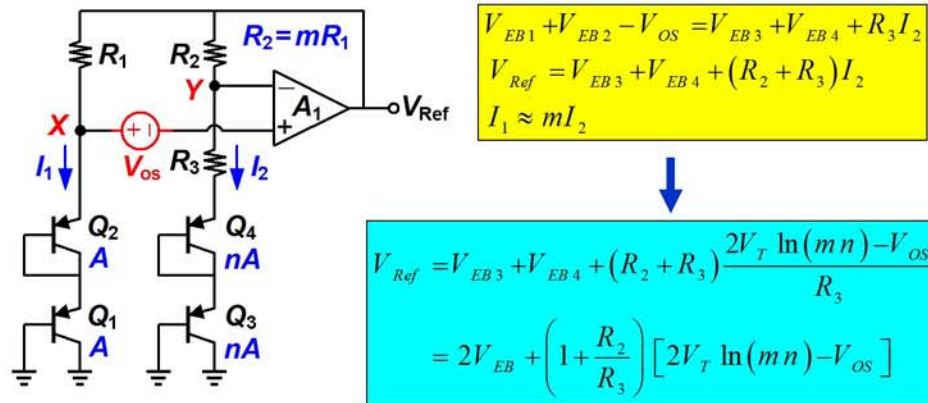
## Reducing the Effect of Op-Amp Offset Voltage

- Use of different currents and series connection of two diodes.
- But, the resulted reference voltage is about 2.5 V => its implementation is impossible in low supply voltages!
- This circuit cannot also be implemented in standard CMOS process.




M. Yavari

CMOS Analog IC Design

Lecture 9: Bandgap References & SC Circuits

## Modified Circuit

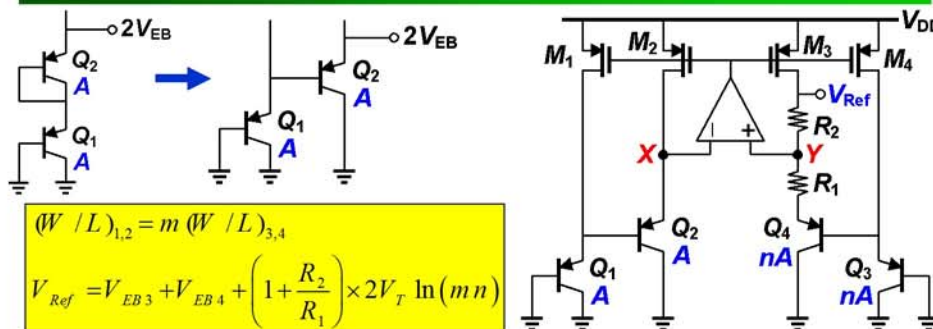


- Op-amp adjusts the gate voltage of PMOS current source transistors so as to equalize  $V_X$  and  $V_Y$ .
- Op-amp is not loaded by the resistors.
- Mismatch between PMOS transistors makes an error in  $V_{Ref}$ .
- Channel length modulation in PMOS transistors increases the power supply sensitivity. => Use cascode current sources with long channel lengths.
- The limited beta of BJT transistors makes also an error in  $V_{Ref}$ . => needing a beta correction circuit.

M. Yavari

CMOS Analog IC Design

Lecture 9: Bandgap References & SC Circuits

## Feedback Polarity

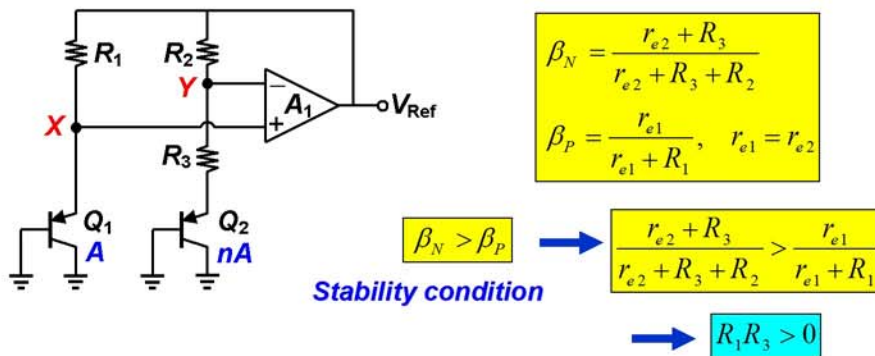

- There are two feedback networks here: one positive and one negative feedbacks!
- In practice,  $\beta_N > 2\beta_P$  is considered to have a well behavior transient response with large capacitive loads!

## Why It Is Called Bandgap?

$$V_{Ref} = V_{BE} + V_T \ln n$$

**General form of a bandgap voltage**

$$\frac{\partial V_{Ref}}{\partial T} = \frac{\partial V_{BE}}{\partial T} + \frac{V_T}{T} \ln n = 0$$

$$\frac{\partial V_{BE}}{\partial T} = \frac{V_{BE} - (4+m)V_T - E_g / q}{T}$$


$$\rightarrow V_{BE} + V_T \ln n = (4+m)V_T + E_g / q$$

$$\rightarrow V_{Ref} = (4+m)V_T + E_g / q$$

$$T \rightarrow 0 \Rightarrow V_{Ref} \rightarrow E_g / q \approx 1.12V$$

- So,  $V_{Ref}$  is called the bandgap reference voltage.

## Supply Dependence and Start-Up

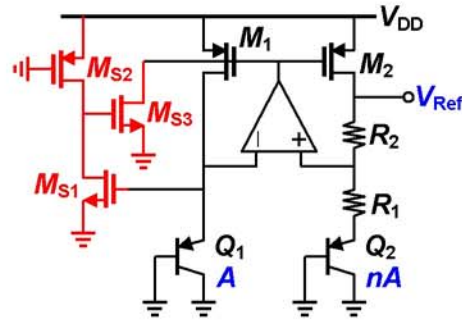


$$(W/L)_1 = m (W/L)_2$$

$$V_{Ref} = V_{EB2} + \left(1 + \frac{R_2}{R_1}\right) \times V_T \ln(mn)$$

- A high dc gain amplifier is needed to achieve low sensitivity to  $V_{DD}$  variations => large PSRR.
- A start-up circuit is necessary to ensure non-zero current operating point during the circuit power on.

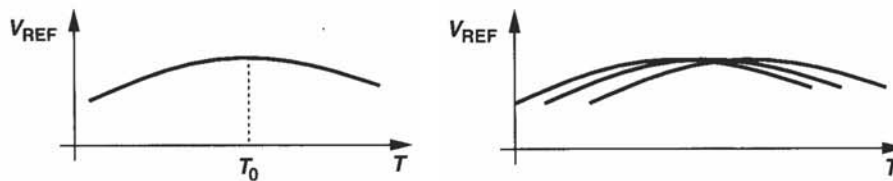
## Curvature Correction

- TC of  $V_{Ref}$  is only zero at room temperature. In other temps, it is not zero due to second-order effects such as the amplifier offset voltage,  $V_{BE}$  TC changes, etc. => needs a curvature correction technique to achieve less than 20 ppm/°C TC.
- Samples of a bandgap reference displays substantially different zero-TC temperatures making it to correct the curvature reliably.
- A useful reference on curvature correction:
  - P. Malcovati et al., JSSC, July 2001.
  - This is the topic of ongoing active research.






## PTAT Current Generation

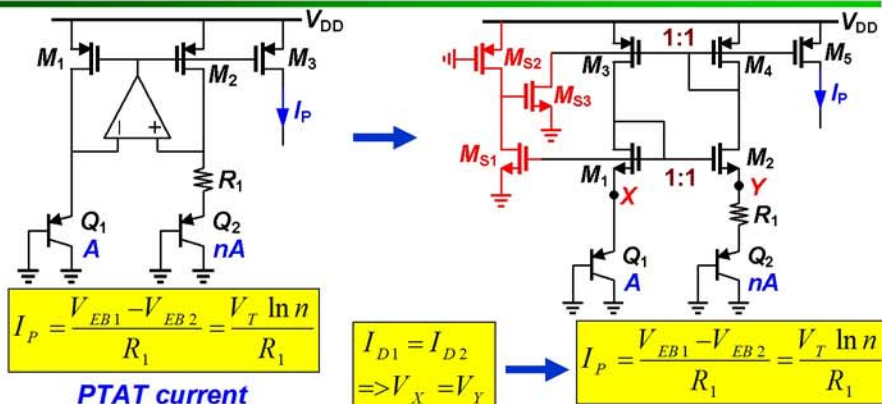


- Assume identical PMOS transistors.
- It can also be used as a temperature sensor.
- We can use the constant- $g_m$  biasing circuit to equalize  $V_X$  and  $V_Y$  without using an amplifier.  $\Rightarrow$  positive feedback
- In practice, the TC of resistor and mismatch between transistors changes the TC of  $I_P$ .
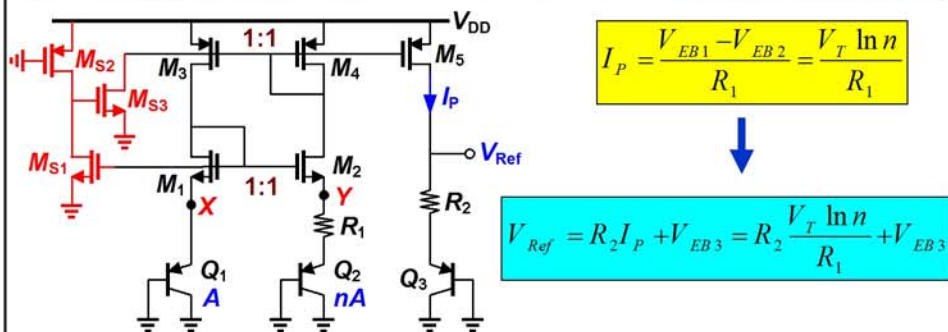
## Bandgap Circuit with Constant- $g_m$ Biasing



- Assume identical PMOS transistors.
- Low PSRR respected to when an op-amp is utilized.
- Use long channel length in current-mirror transistors or wide-swing cascode current mirrors to enhance the PSRR.

## Low-Voltage Bandgap Circuit

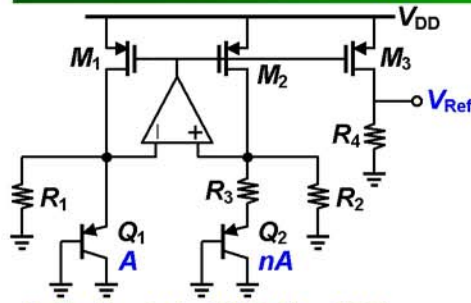

H. Banba et al., JSSC, May 1999.

$$I_{R3} = \frac{V_{EB1} - V_{EB2}}{R_3} = \frac{V_T \ln n}{R_3}$$

PTAT current

$$R_1 = R_2 \Rightarrow I_{R2} = \frac{V_{EB1}}{R_2}$$

CTAT current

$$I_{D3} = \frac{V_T \ln n}{R_3} + \frac{V_{EB1}}{R_2}$$

$$V_{Ref} = R_4 I_{D3} = \frac{R_4 V_T}{R_3} \ln n + \frac{R_4 V_{EB1}}{R_2}$$

$$\frac{\partial V_{Ref}}{\partial T} = 0 \Rightarrow \frac{R_4 V_T}{R_3 T} \ln n + \frac{R_4}{R_2} \frac{\partial V_{EB1}}{\partial T} = 0$$


$$\left. \frac{\partial V_{BE}}{\partial T} \right|_{T=300K} \approx -1.5mV / ^\circ K, V_{BE1} \approx 750mV$$

$$R_1 = R_2 = 10k\Omega, R_3 = 2k\Omega = 2k\Omega, n = 31$$

$$V_{Ref} = 239mV$$

- How do generate a bandgap voltage less than 1.25 V?
- Assume identical PMOS transistors for simplicity.

## Banba Bandgap Circuit Implementation

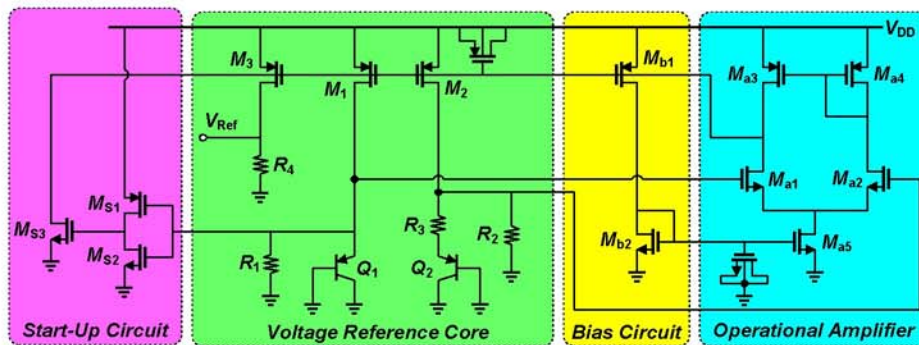

- A simple diff pair was used to realize the amplifier.
- The bias current generated by the bandgap core is used to bias the amplifier.
- It needs a start-up circuit.

